

Supply Impedance and Voltage Conversion Requirements for CMOS Digital ICs


Elad Alon



Dept. of EECS and BWRC
UC Berkeley

Scaling and Supply Impedance

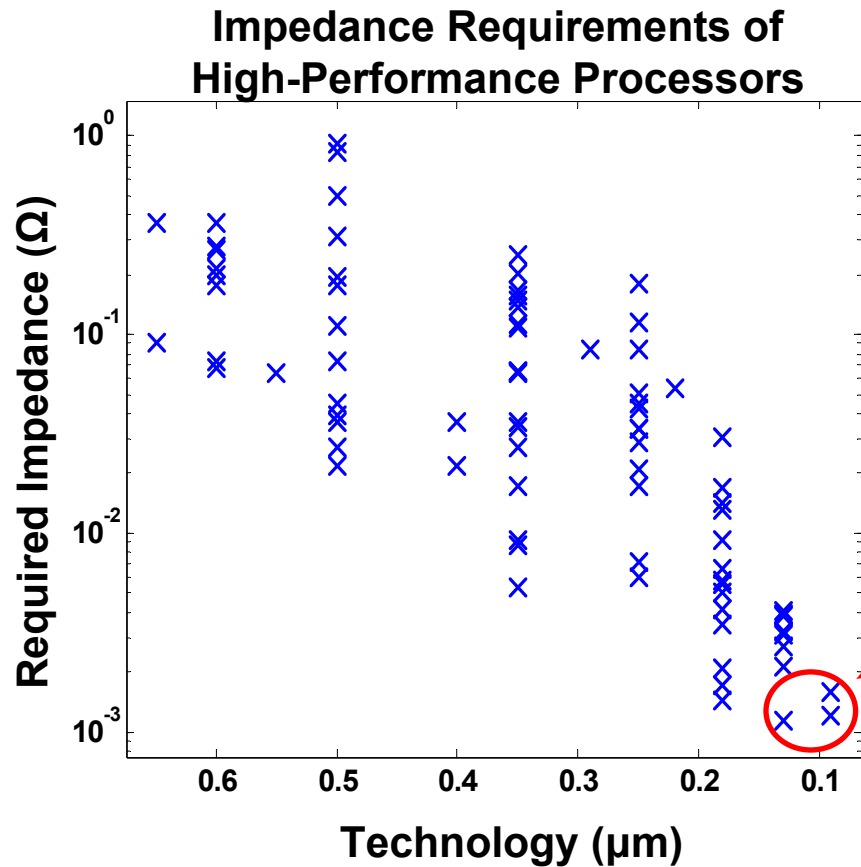
- CMOS scaling led to lower supply voltages and constant (or increasing) power consumption



- This forces drastic drop in supply impedance
 - Even at constant power:
 - $V_{\text{dd}} \downarrow, I_{\text{dd}} \uparrow \rightarrow |Z_{\text{required}}| \downarrow\downarrow$
- Today's chips:
 - $|Z_{\text{required}}| \approx 1 \text{ m}\Omega!$

Power Distribution and Regulation


- **Significant resources spent to meet impedance requirement**
- **Initial motivation for integrated DC-DC:**
 - **Relaxed package/PCB $|Z|$**
 - **Active linear regulation can be used to reduce on-chip $|Z|$ too**
- **But, so far these regulators increased total power**
 - **Prevents adoption in today's power-limited chips**

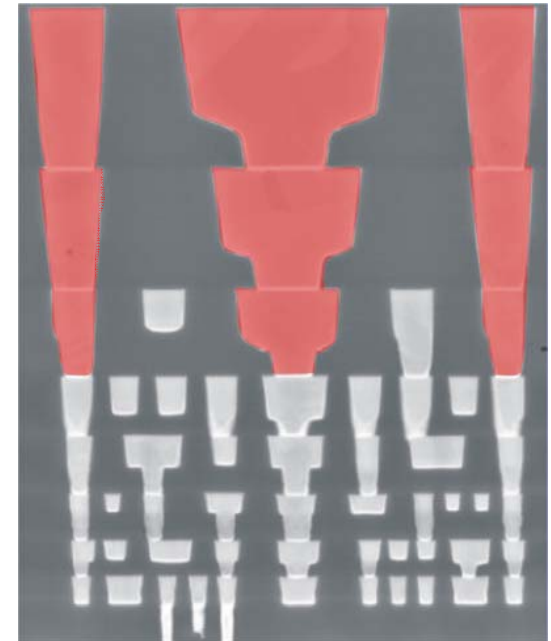

Power-Neutral Regulation

- Gate delay depends on V_{dd} :
 - So V_{dd} needs to be greater than some V_{min}

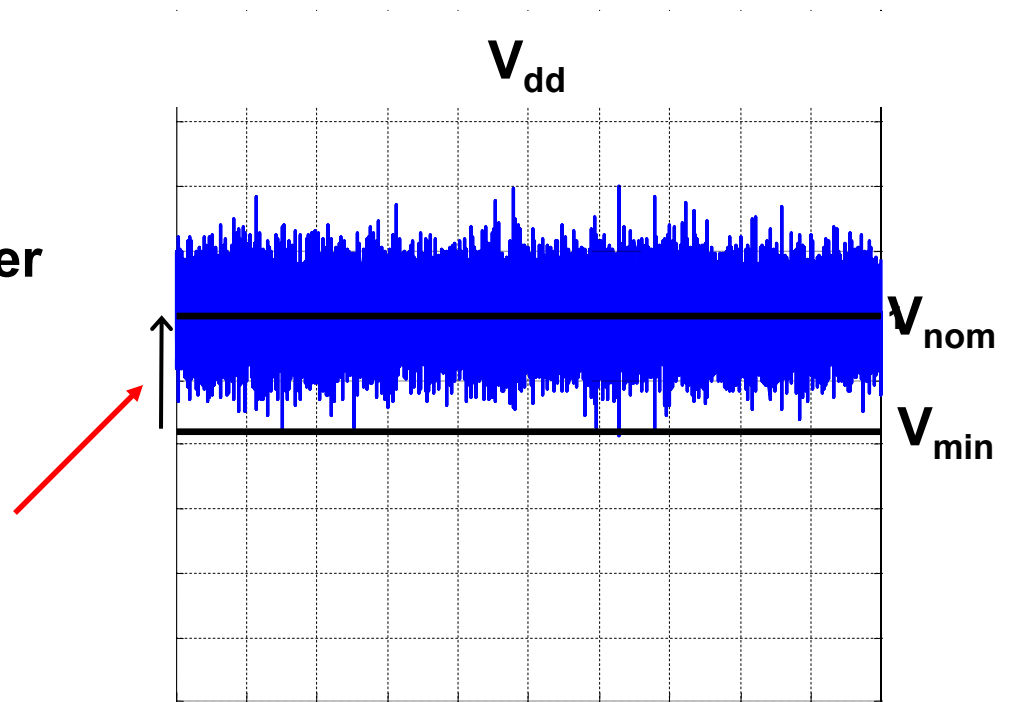- Supply variations force higher nominal voltage
 - Causes extra power dissipation




- Goal: Build regulator without negatively impacting chip power
 - Regulator power needs to be less than recovered power

Outline


- Motivation
- **Linear Regulation and Power Efficiency**
- **Implications on Integrated Converters**
- **Conclusions**

Linear Regulators


Series Regulator

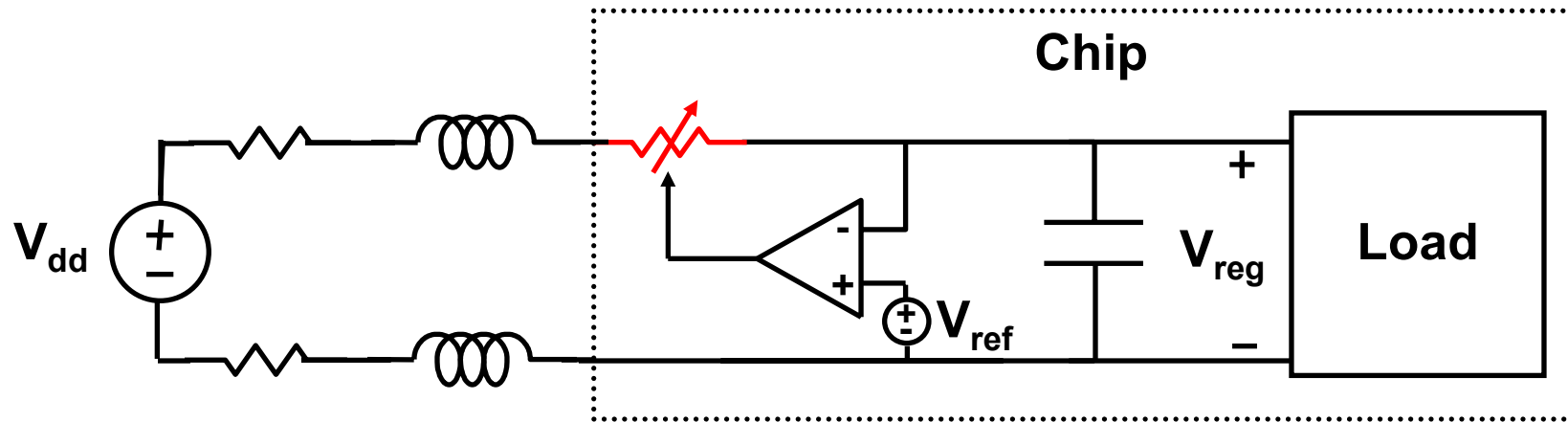

Shunt (Parallel) Regulator


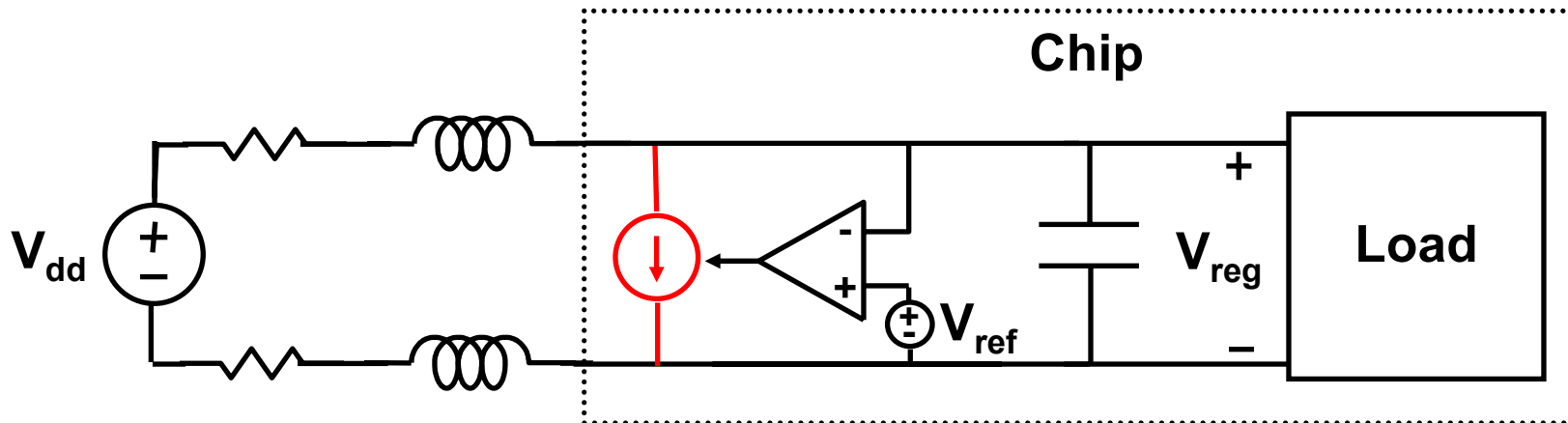


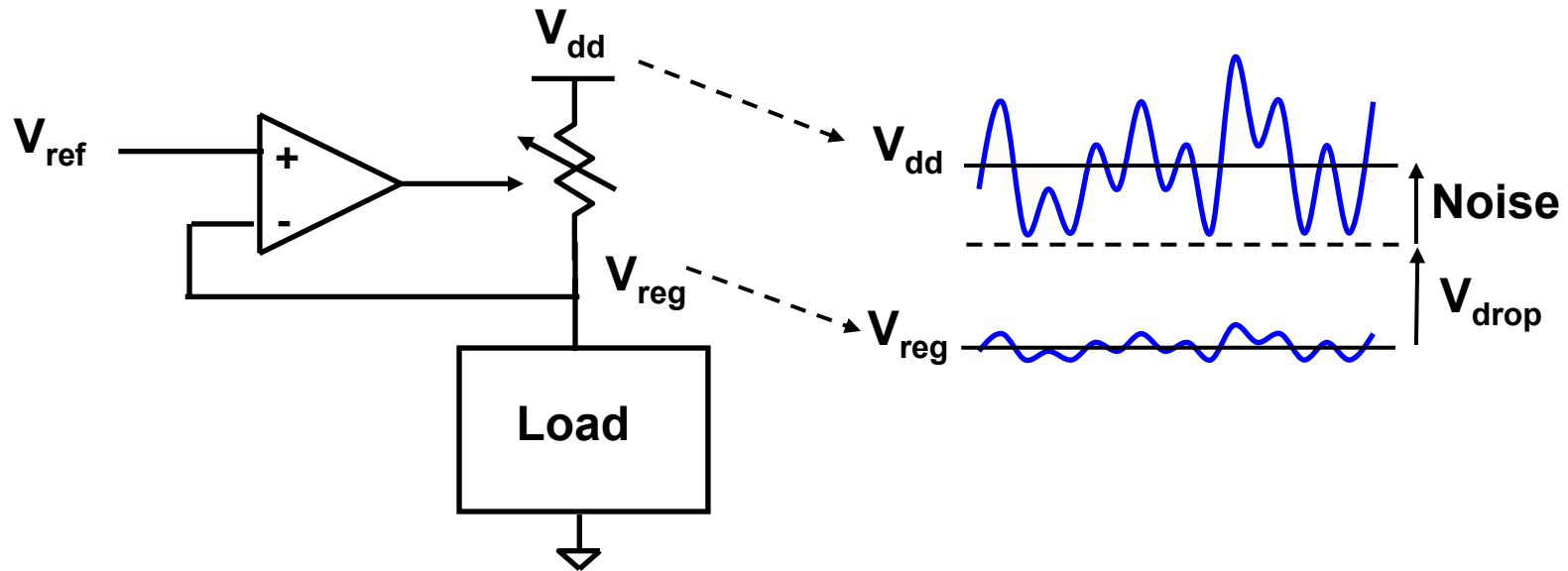Improved Efficiency with Series Regulator?




- **Clearly won't meet efficiency goal:**
 - Regulator doesn't really change noise on V_{dd}
 - So still need same margin
 - But added an extra V_{drop} from variable resistor...

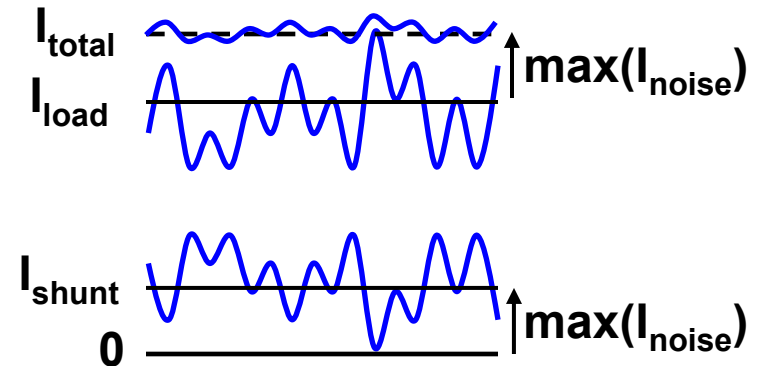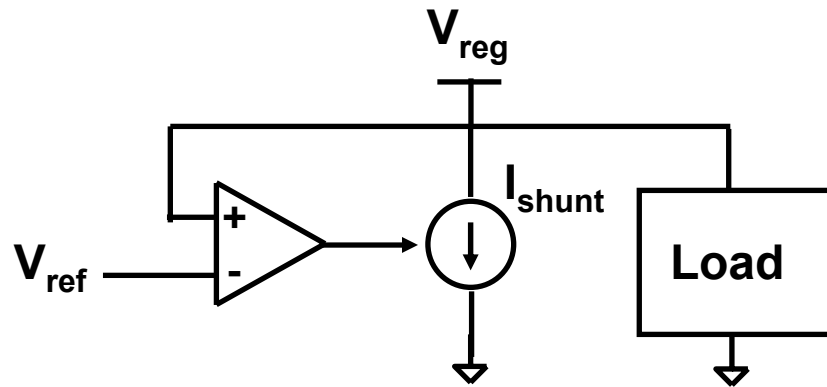Improved Efficiency with Shunt Regulator?



- **Regulator can only pull current out of supply**
 - To counter noise in both directions, need to burn significant static current
 - Again, clearly inefficient
- **Need to allow shunt to deliver energy to the load**
 - Not just dissipate it

Push-Pull Shunt Regulator

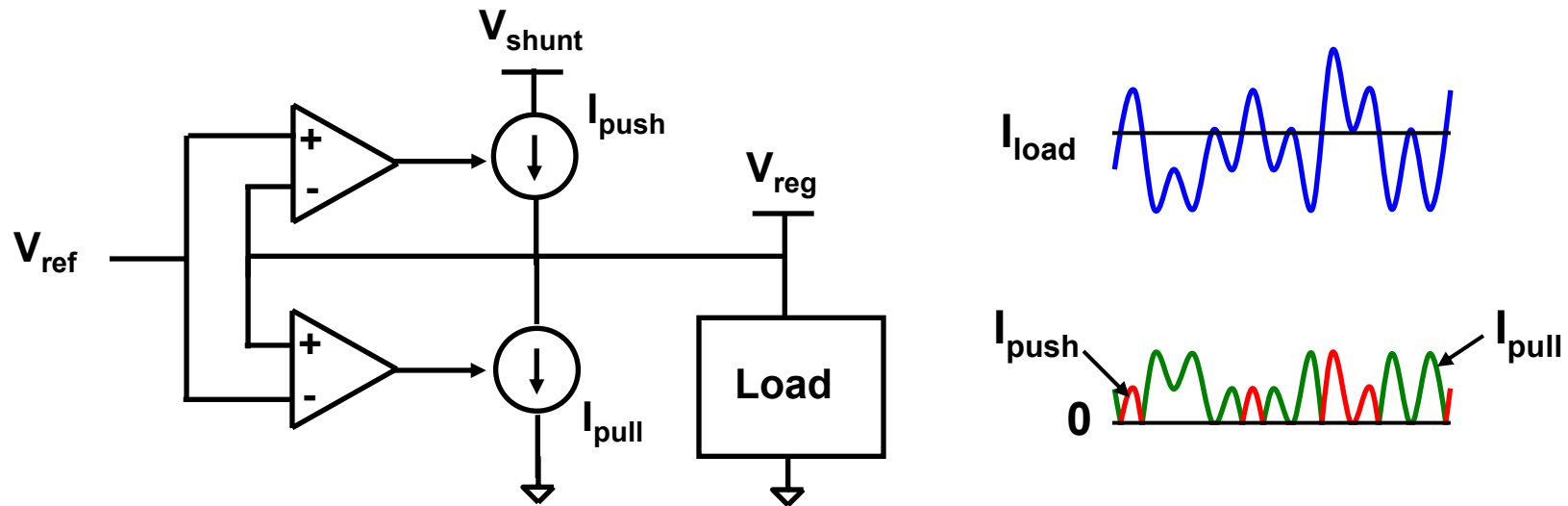


- Use extra “shunt” supply to push current into V_{reg}
 - Regulator capable of countering large variations
 - But regulator loss set mostly by (significantly smaller) average variation
- Similar to Active Clamp* for board VRMs
 - Build on previous work to improve on-die impedance

*A.M. Wu and S.R. Sanders, “An Active Clamp Circuit for Voltage Regulation Module (VRM) Applications,” *Transactions on Power Electronics*. Sept. 2001.


Regulator Design Challenges

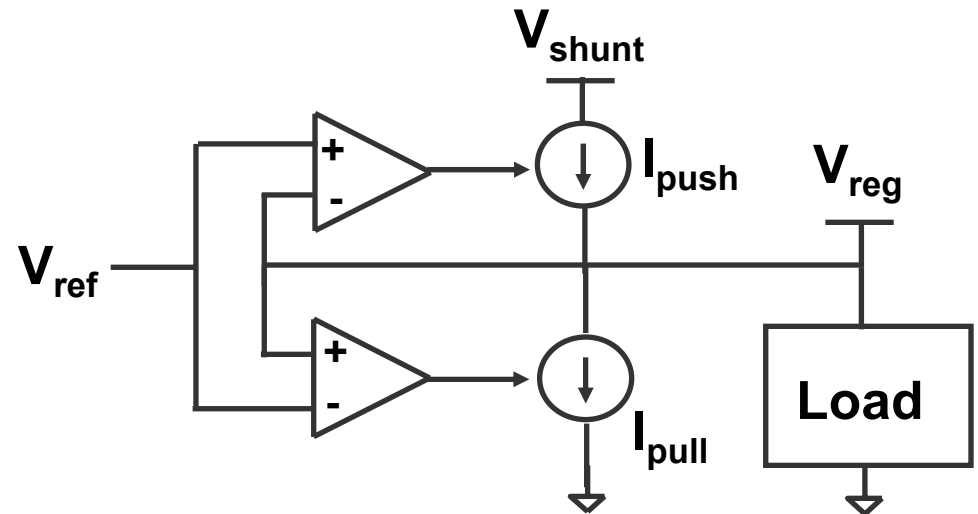- V_{shunt} isn't free
 - Takes resources away from main supply
 - Increases loss



- Need to minimize quiescent output current
 - Otherwise regulator too inefficient
- Need GHz bandwidth feedback path
 - With minimum feedback circuit power

Allocating Resources for Shunt Supply

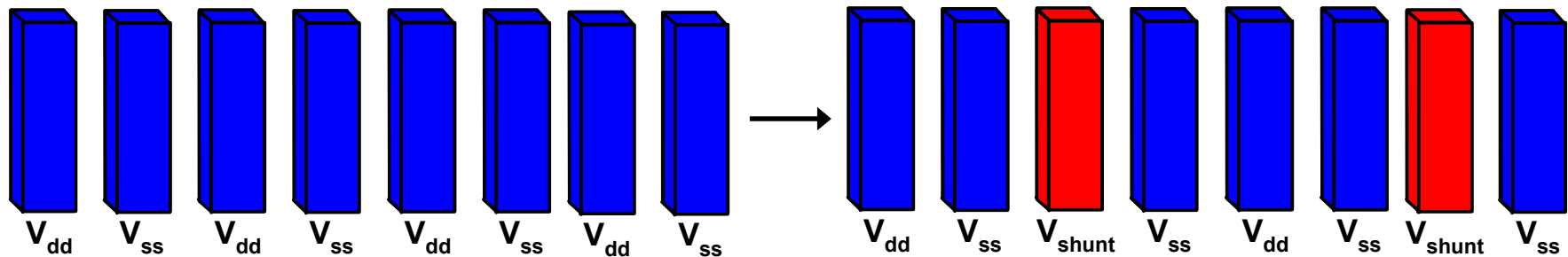


- Limited number of pins, metal lines for power
 - Need to allocate resources between main and shunt supplies
- For resistive losses:

$$P_{shunt} = \frac{\overline{I_{shunt}}}{\overline{I_{load} + I_{shunt}}}, \quad P_{main} = \frac{\overline{I_{load}}}{\overline{I_{load} + I_{shunt}}}$$

- If guarantee that V_{shunt} only handles transients
 - Resistive losses of main supply not really affected

Quiescent Output Current

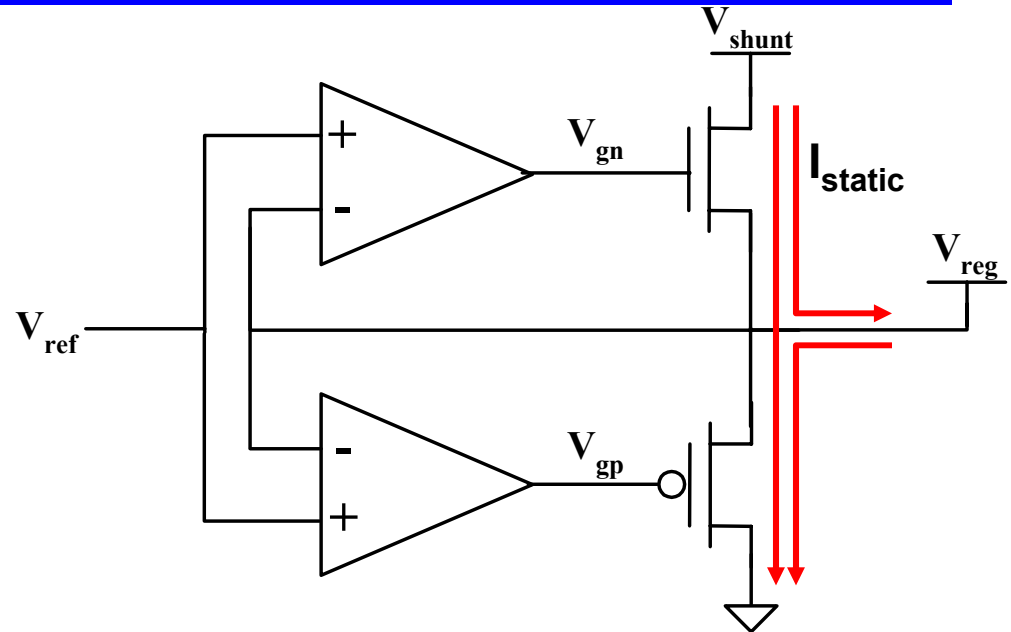
- Went to push-pull to minimize regulator power overhead
- But many designs have significant I_{static}



- Similar issues in RF and audio power amplifiers
 - In all cases, need to efficiently deliver energy based on a (small) input signal
- Build on PA knowledge to achieve high efficiency:
 - Non-linearly switch the output power devices


Switched-Output Regulator: Comparator Feedback with Dead-Band

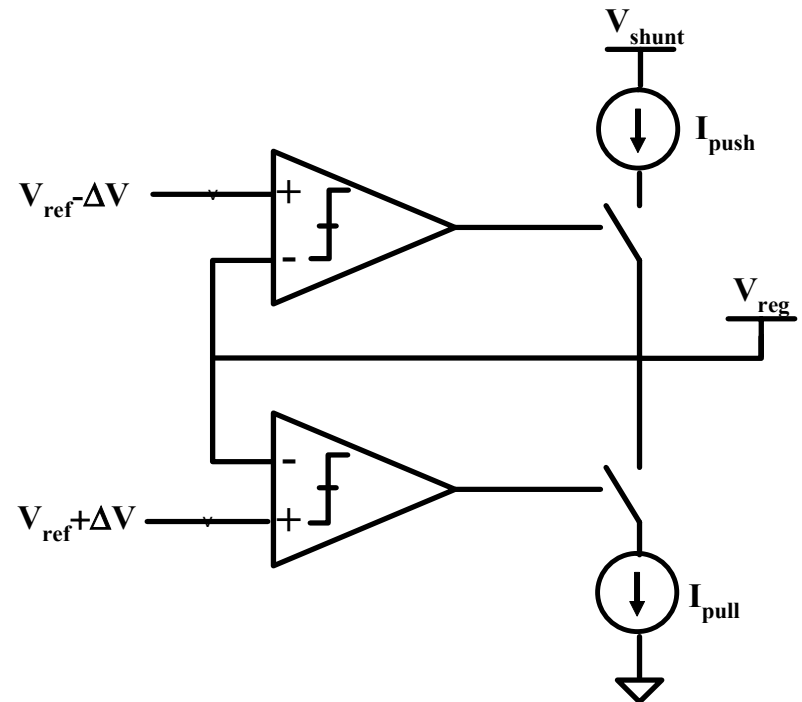- Convert small signal on V_{reg} into full-swing to drive switch
 - Use comparators in feedback path
- To avoid limit cycle:
 - Offset thresholds to create dead-band




Feedback Delay

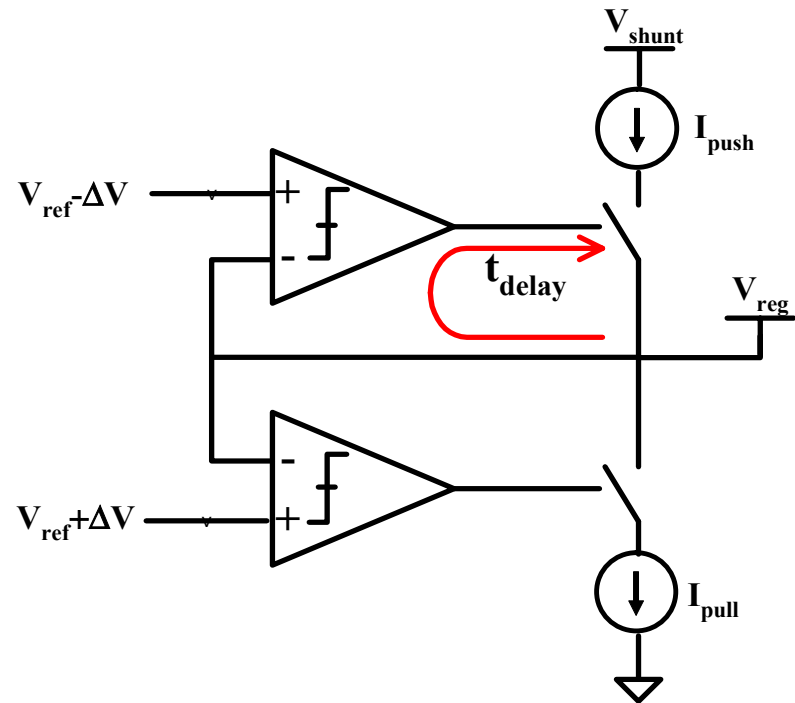- For optimal response to noise at output, feedback bandwidth is critical
- For non-linear loop, this translates into low t_{delay}
- Can we exploit comparator's properties to improve effective delay?



Linear Loop with Derivative Control

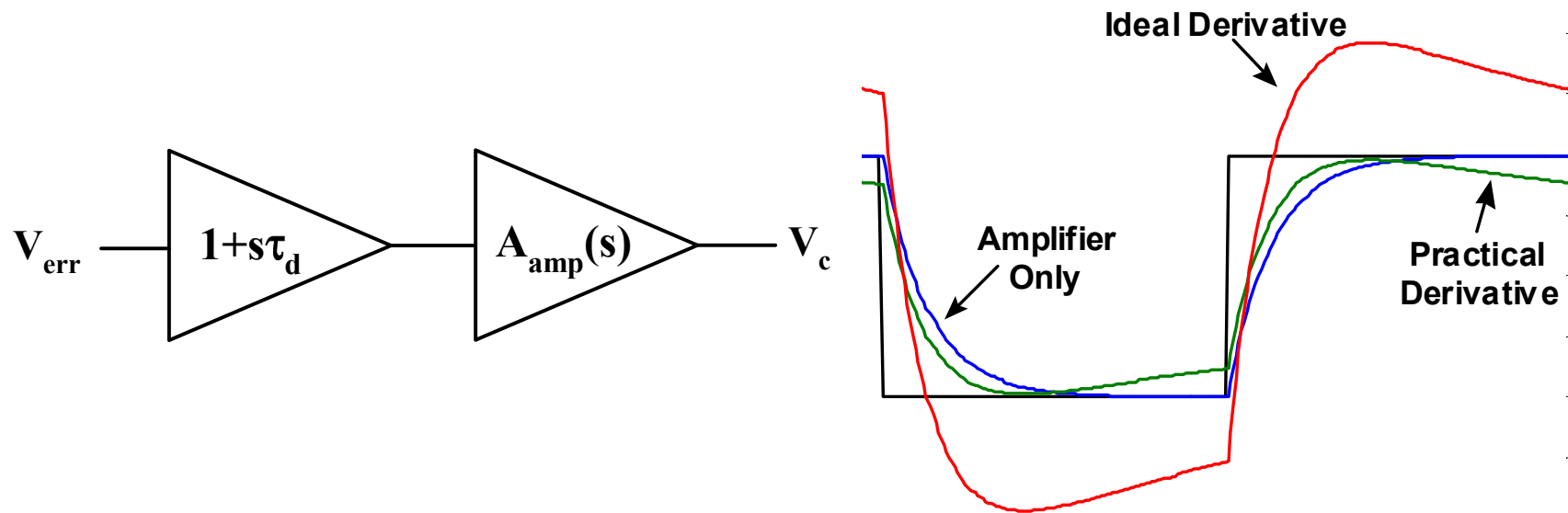

- Addition of $s\tau_d$ to input cancels some of the phase shift from limited amplifier bandwidth
- But, implementing derivative behavior (without inductors) requires reduction of DC gain
 - Limits usefulness in a linear loop

Derivative Feedback with Comparators


- As long as comparators swing full-rail

- Only shape of TF in front of comparators matters
- “Gain” is restored by the comparators

- Net effect of derivative: reduces impact of t_{delay}

- Similar to sliding mode control

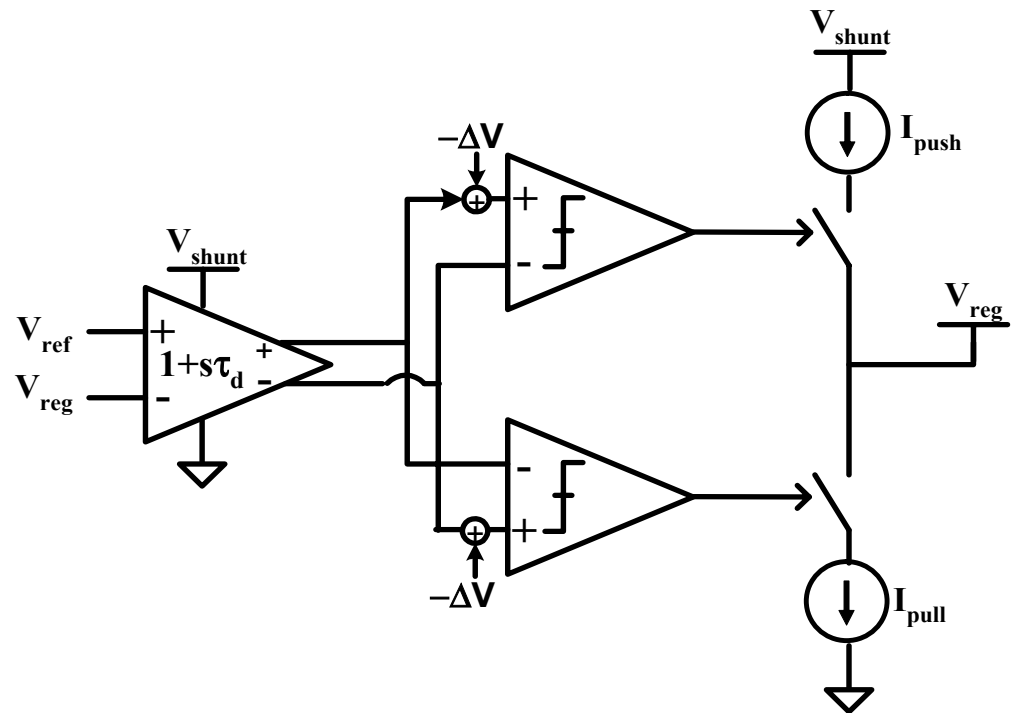
- But region of sliding behavior is small



Test-Chip Details



- 65nm SOI AMD test-chip
- Regulator uses same power distribution scheme as processor
 - With reallocation for V_{shunt}
- On-chip noise generator and perf. monitor for testing

**Regulator
Circuits**

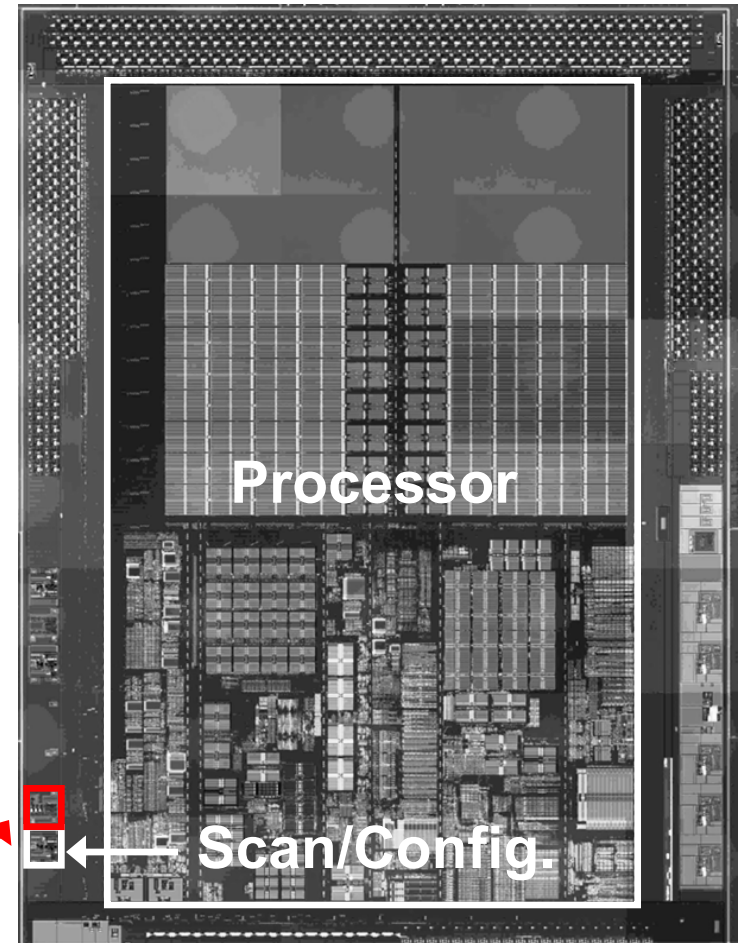

E. Alon and M. Horowitz, "Integrated Regulation for Energy-Efficient Digital Circuits," *IEEE Journal of Solid-State Circuit*, Aug. 2008.


Measured Results

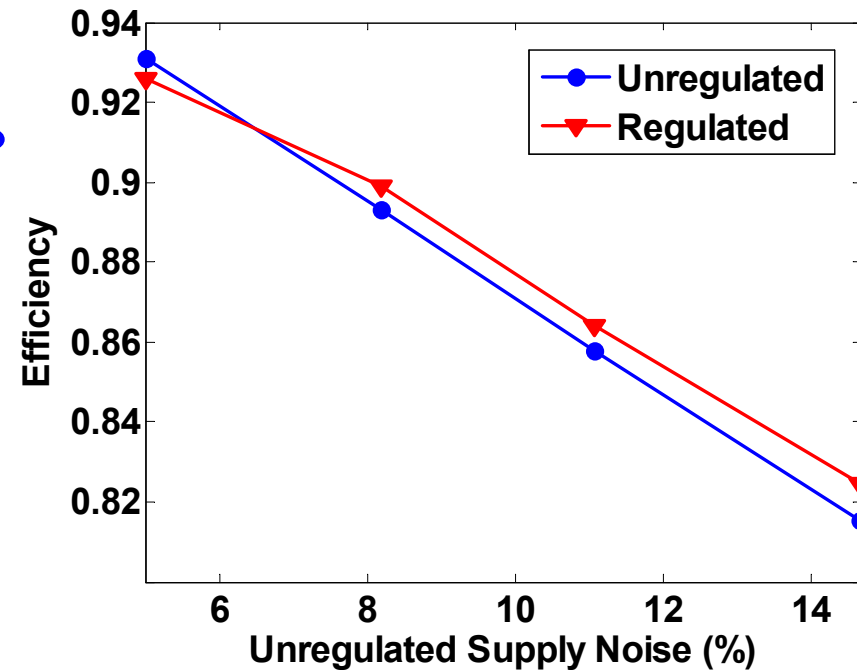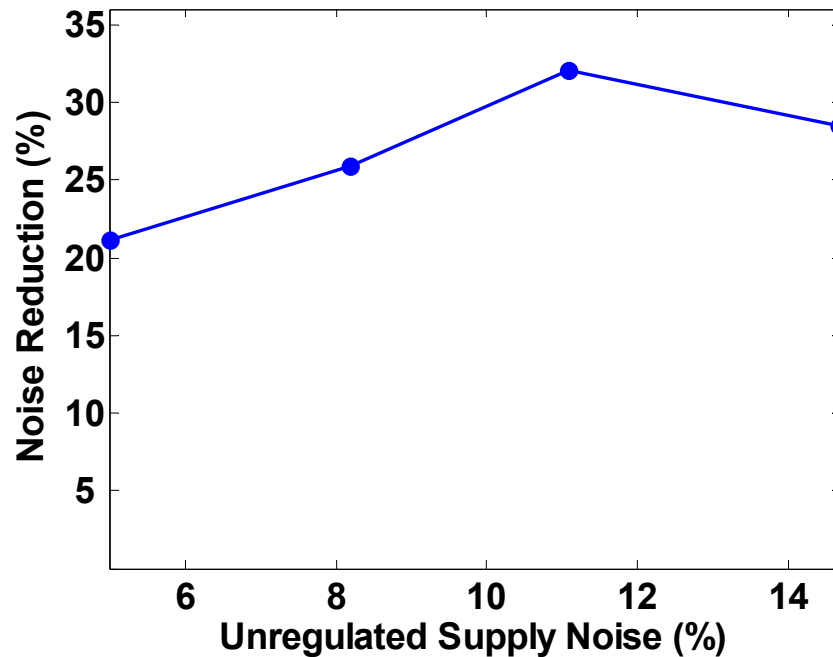

- Regulator reduces broadband noise by ~30%
- Total power dissipation actually reduced by up to ~1.4%

Impedance with Faster Process

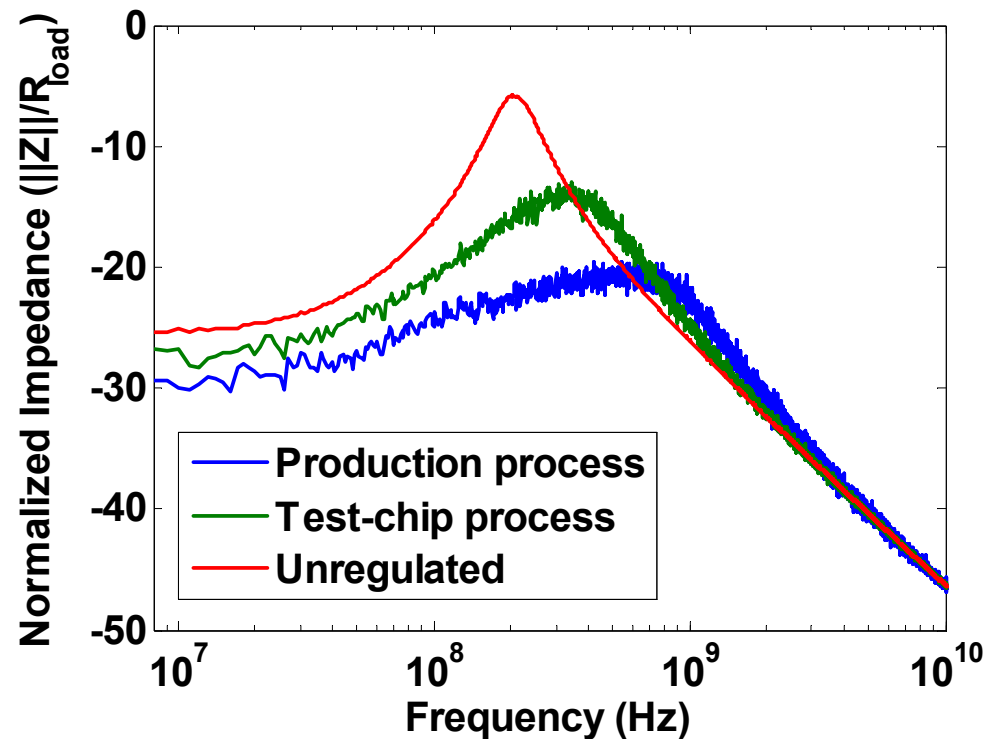- Process was in development
 - Low device f_t
- Measurement matches simulation with slower devices





- Expect to reach ~50% noise and ~4% power reduction in production process with higher f_t

Outline



- Motivation
- Linear Regulation and Power Efficiency
- **Implications on Integrated Conversion**
- Conclusions

Need for Local Power Supplies

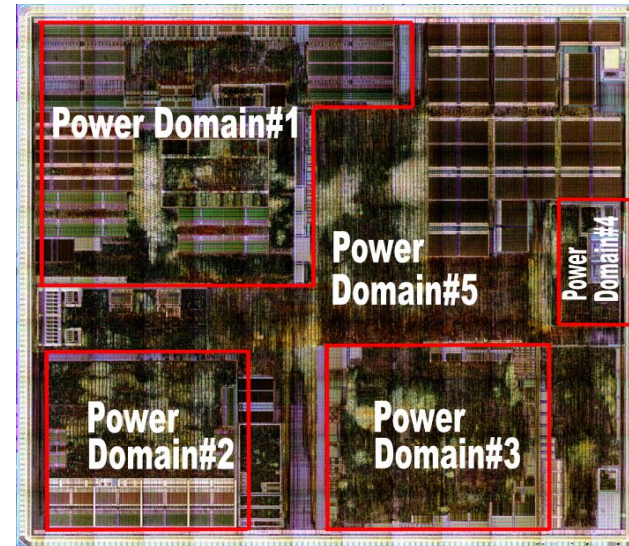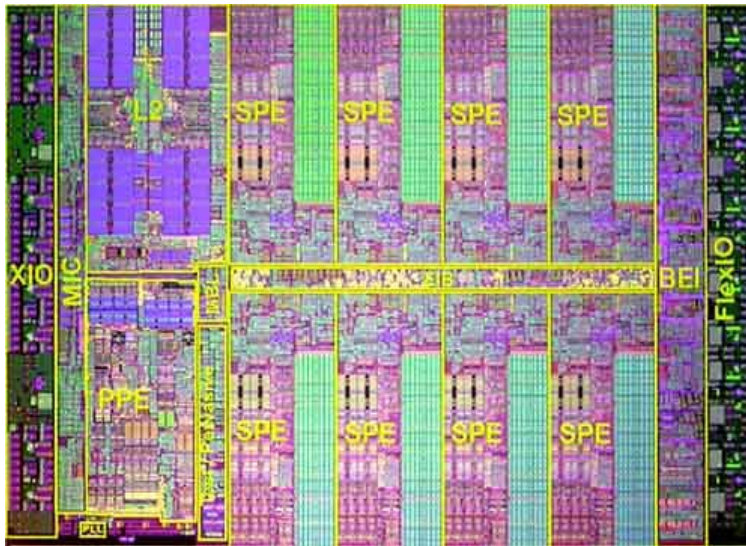


- **Clear need for many, local supply voltages**
 - Per core supply, dynamic voltage supplies for SRAM, etc.
- **But, can't sacrifice supply impedance**
 - Makes external DC-DC conversion difficult (split planes)

Converter Impedance and Efficiency

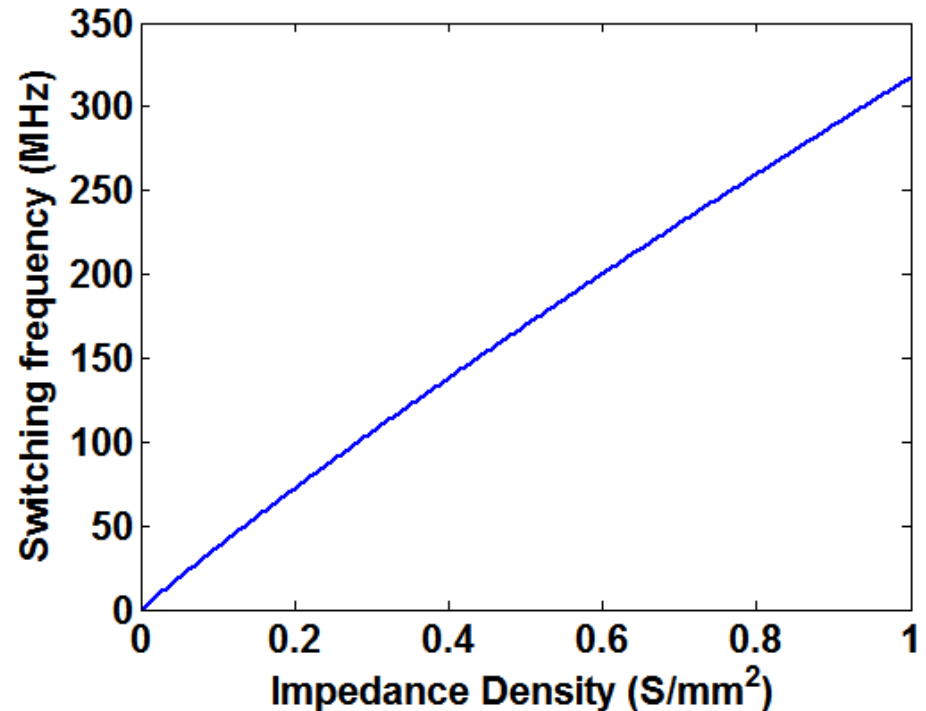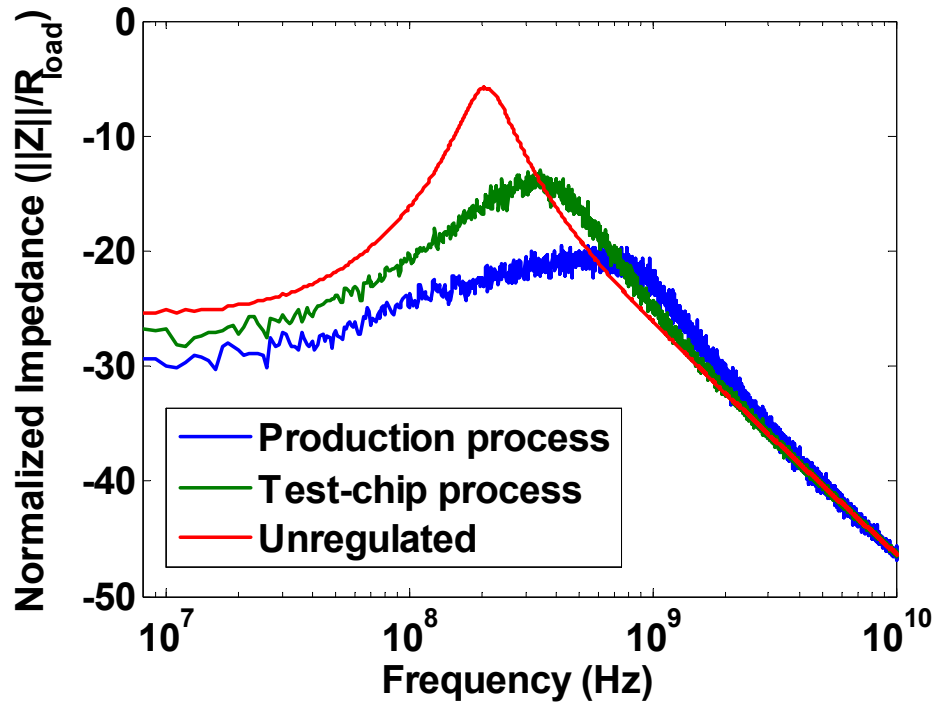

- **Supply noise very broadband...**
 - Significant noise content up to ~1GHz
- **Operate integrated switching converter at ~2GHz?**
 - Inefficient and impractical...

Proposed Power Delivery Architecture

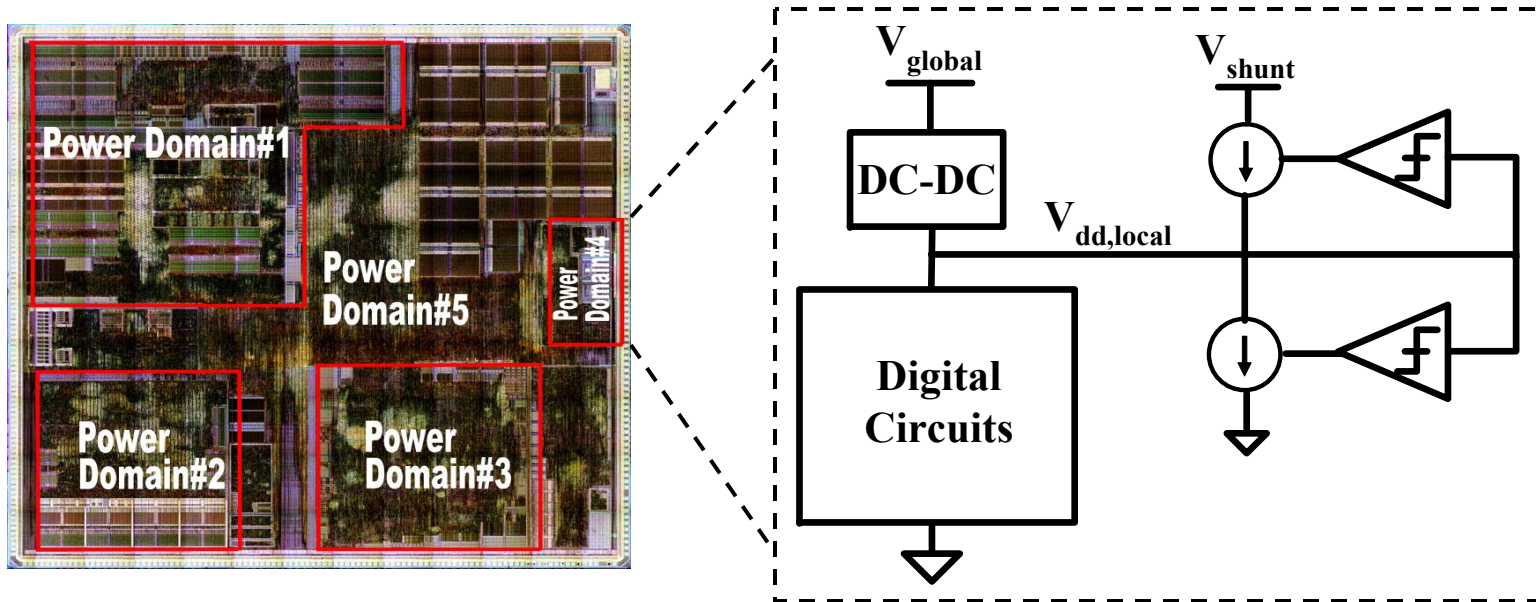

- **Split delivery of DC power from AC impedance**
 - DC-DC creates local supply
 - Parallel regulator handles transients (maintains V_{min})
- **Key question becomes conversion efficiency of integrated DC-DC**

Outline

- Motivation
- Linear Regulation and Power Efficiency
- Implications on Integrated Conversion
- **Conclusions**

Conclusions

- **Supply impedance is a key consideration in chip power delivery**
- **Digital circuits care about V_{\min}**
 - **Can leverage this to build power-neutral linear regulator**
 - **Measured 30% noise reduction and actually improved power by ~1.4%**
- **Leverage efficient delivery of low impedance for integrated converters**
 - **Low dynamic impedance and high efficiency hard to attain simultaneously**