
 


# What About Switched Capacitor Converters?

Grad Students: Michael Seeman, Vincent Ng, and  
Hanh-Phuc Le  
Profs. Seth Sanders and Elad Alon  
EECS Department, UC Berkeley
 
# Switched Capacitor Power Converters



- Only switches and capacitors
- Simple low freq model as an ideal transformer with Thevenin impedance
  - neglects freq dependent loss and leakage
  - Would model leakage, dynamic losses with shunt imped.
- Using no inductors has advantages:
  - Simplified full integration potential
  - Works well over a wide power range
    - Single mode, can adjust clock rate
    - No minimum load
  - No inductive switching losses
- Open-loop loadline regulation:
  - Output impedance has R-C characteristic, with R naturally designed to meet efficiency spec



# Why Not S-C ?

- Difficult regulation?
- Not suited for high current/power?
- Lots of difficult gate drive details?
- Interconnect difficulty for many caps?
- Voltage rating of CMOS processes?
- Magnetic-based ckts = higher performance?

# SC Analysis: Simplest Example

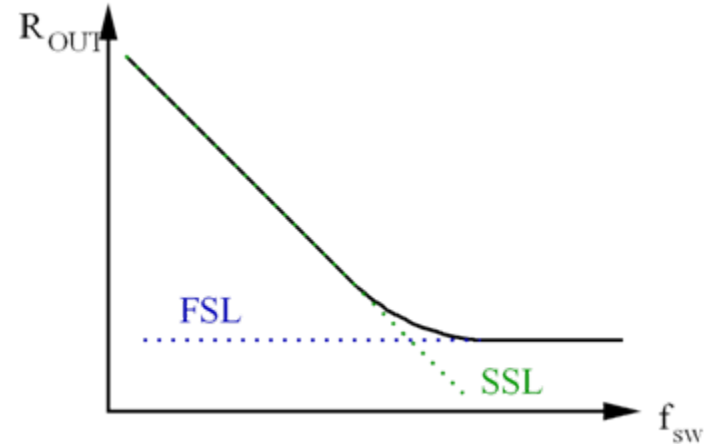 

- Slow Switching Limit (SSL):
  - Impulsive currents (charge transfers)
  - Resistance negligible (assume  $R = 0$ )
  - This (SSL) impedance is the switching loss!
- Fast Switching Limit (FSL):
  - Constant current through switches
  - Model capacitors as voltage sources ( $C \rightarrow \infty$ )

$$i = f_{sw} \Delta q = f_{sw} C \Delta v$$

$$i = \frac{1}{4} \frac{1}{R} \Delta v$$

$$(\Delta v = V_{IN} - V_{OUT})$$

# Comparing Converters

Need a metric to compare converters of different types!

Example: How much power can we get out of a converter with 10% voltage drop?

$$P_{OUT} = I_{OUT} V_{OUT} = (0.1 G_{OUT} V_{OUT}) V_{OUT} = 0.1 \cdot G_{OUT} V_{OUT}^2$$

Power performance related to  $GV^2$

We can make a unitless performance metric by comparing converter  $GV^2$  to component  $GV^2$

SSL Metric:

$$\frac{G_{OUT} V_{OUT}^2}{f \sum_{caps} C_i v_{c,i}^2(rated)}$$


FSL Metric:

$$\frac{G_{OUT} V_{OUT}^2}{\sum_{switches} G_i v_{r,i}^2(rated)}$$

# Analysis via Charge Multipliers

Capacitor Charge Multiplier:

$$a_{c,i}^j = \frac{\text{charge flow in cap } i, \text{ phase } j}{\text{output charge flow, both phases}}$$

 

**Phase 1:**


$$a_c^1 = \frac{1}{2}$$

$$a_{r,1} = \frac{1}{2}$$

$$a_{r,3} = -\frac{1}{2}$$

Switch Charge Multiplier:

$$a_{r,i} = \frac{\text{charge flow in switch } i, \text{ when on}}{\text{output charge flow, both phases}}$$

 

**Phase 2:**

$$a_c^2 = -\frac{1}{2}$$

$$a_{r,2} = \frac{1}{2}$$

$$a_{r,4} = -\frac{1}{2}$$

# Output Impedance ~ Power Loss

M. Seeman, S. Sanders, IEEE T-PELS, March 2008

- An SC converter's power loss is the sum of component energy (power) losses:

$$P_{SSL} = f_{sw} \sum_{\text{capacitors}} \Delta q_i \Delta v_i = R_{SSL} i_{OUT}^2 \quad P_{FSL} = \frac{1}{2} \sum_{\text{switches}} R_i (2q_i f_{sw})^2$$

- The converter's output impedance can be determined in terms of just the charge multiplier components:

$$R_{SSL} = \sum_{\text{capacitors}} \frac{(a_{c,i})^2}{C_i f_{sw}} \quad R_{FSL} = 2 \sum_{\text{switches}} R_i (a_{r,i})^2$$

# Output Impedance and Optimization

Tellegen's theorem and energy conservation used to find  $R_{OUT}$ :

$$\text{SSL: } R_{OUT} = \frac{1}{f_{sw}} \sum_{i \in \text{capacitors}} \frac{(a_{c,i}^1)^2}{C_i} \quad \text{FSL: } R_{OUT} = 2 \sum_{i \in \text{switches}} R_i (a_{r,i})^2$$

Minimize output impedance while keeping component cost constant:

**Cost constraint**

**Optimized components**

**Optimized output impedance**

$$E_{TOT} = \frac{1}{2} \sum_{\text{capacitors}} C_i v_{c,i(\text{rated})}^2$$

$\Rightarrow$

$$C_i^* \propto \left| \frac{a_{c,i}}{v_{c,i(\text{rated})}} \right|$$

$$R_{SSL}^* = \frac{1}{2E_{TOT} f_{sw}} \left( \sum_{\text{capacitors}} |a_{c,i} v_{c,i(\text{rated})}| \right)^2$$

$$A_{TOT} = \sum_{\text{switches}} G_i v_{r,i(\text{rated})}^2$$

$\Rightarrow$

$$G_i^* \propto \left| \frac{a_{r,i}}{v_{r,i(\text{rated})}} \right|$$

$$R_{FSL}^* = \frac{2}{A_{TOT}} \left( \sum_{\text{switches}} |a_{r,i} v_{r,i(\text{rated})}| \right)^2$$

In the optimal case:


Capacitor voltage ripple and switch voltage drop are proportional to rated voltage

Output impedance proportional to the square of the *sum of the component V-A products*




# Comparison with Magnetic Designs


Ladder-type switched-cap converter

 

Transformer-bridge converter

 

Boost or Buck converter

 


**Switch sizes optimized for a given conversion ratio  $n$  for all converters**

# Switch Utilization – Conduction Loss Comparison

- Performance compared with switch GV2 metric:

$$\frac{G_{OUT} V_{OUT}^2}{\sum G_i v_{r,i(rated)}^2}$$

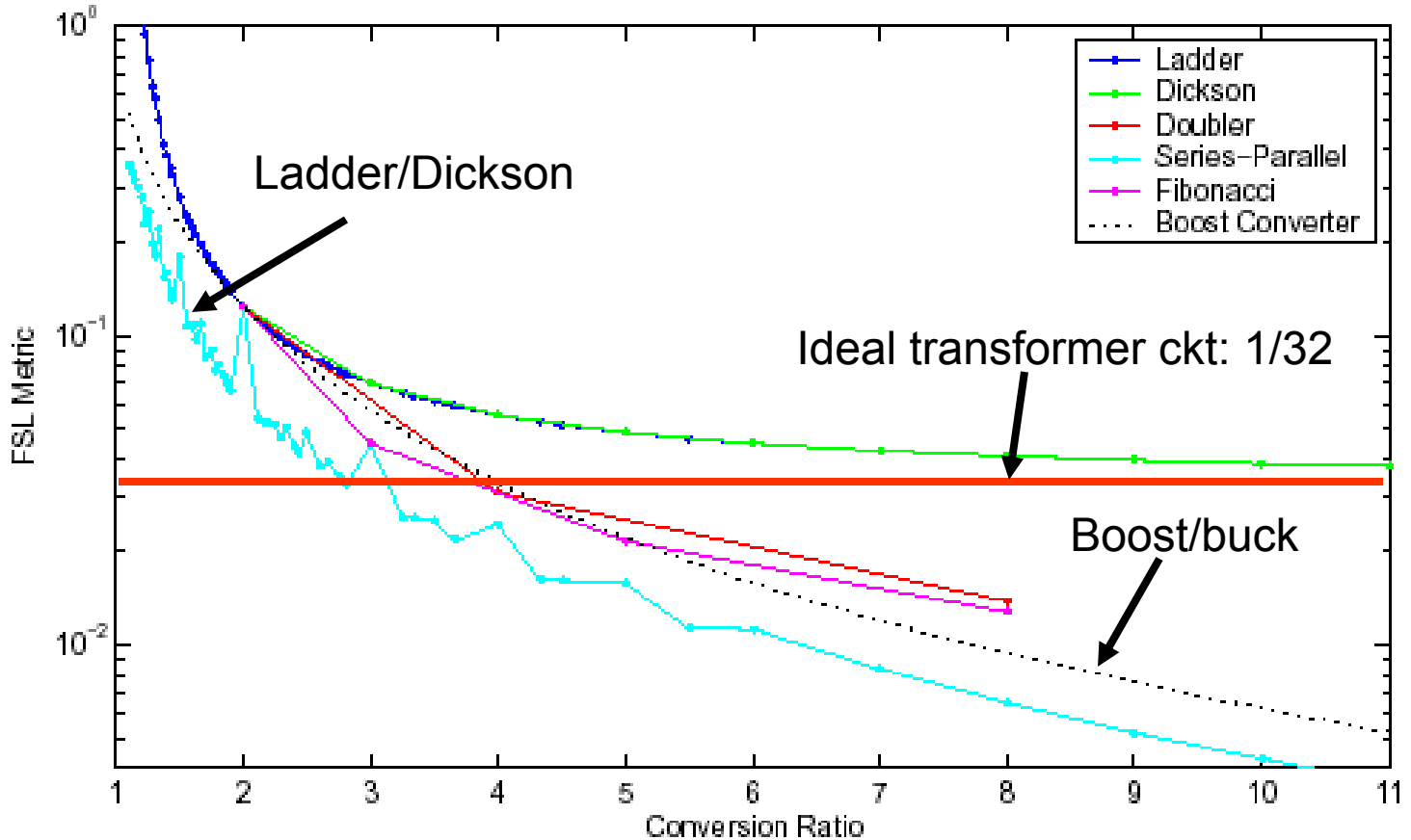- Magnetic components modeled with *zero* conduction loss, and *no* switching loss impact



# D.H. Wolaver, PhD dissertation, MIT, 1969 proves fundamental thms on dc-dc conv.:

*G = voltage or current gain*

- Switches (*resistors*):

$$- \sum_{k \in dc\text{-active}} \overline{v_k} \overline{i_k} \geq \frac{G-1}{G} P_o$$

$$- \sum_{k \in ac\text{-active}} (\overline{v_k} - \overline{v_k}) \bullet (\overline{i_k} - \overline{i_k}) \geq \frac{G-1}{G} P_o$$

- *Ladder/Dickson are optimal*

- Reactive Elements:


$$\frac{1}{2} \sum_{k \in reactive} |\overline{v_k i_k}| \geq \frac{G-1}{G} P_o$$

*Meaning for 2-phase ckts:*

$$\sum_{k \in C} V_k q_k + \sum_{k \in L} I_k \lambda_k \geq \frac{1}{f} \frac{G-1}{G} P_o$$
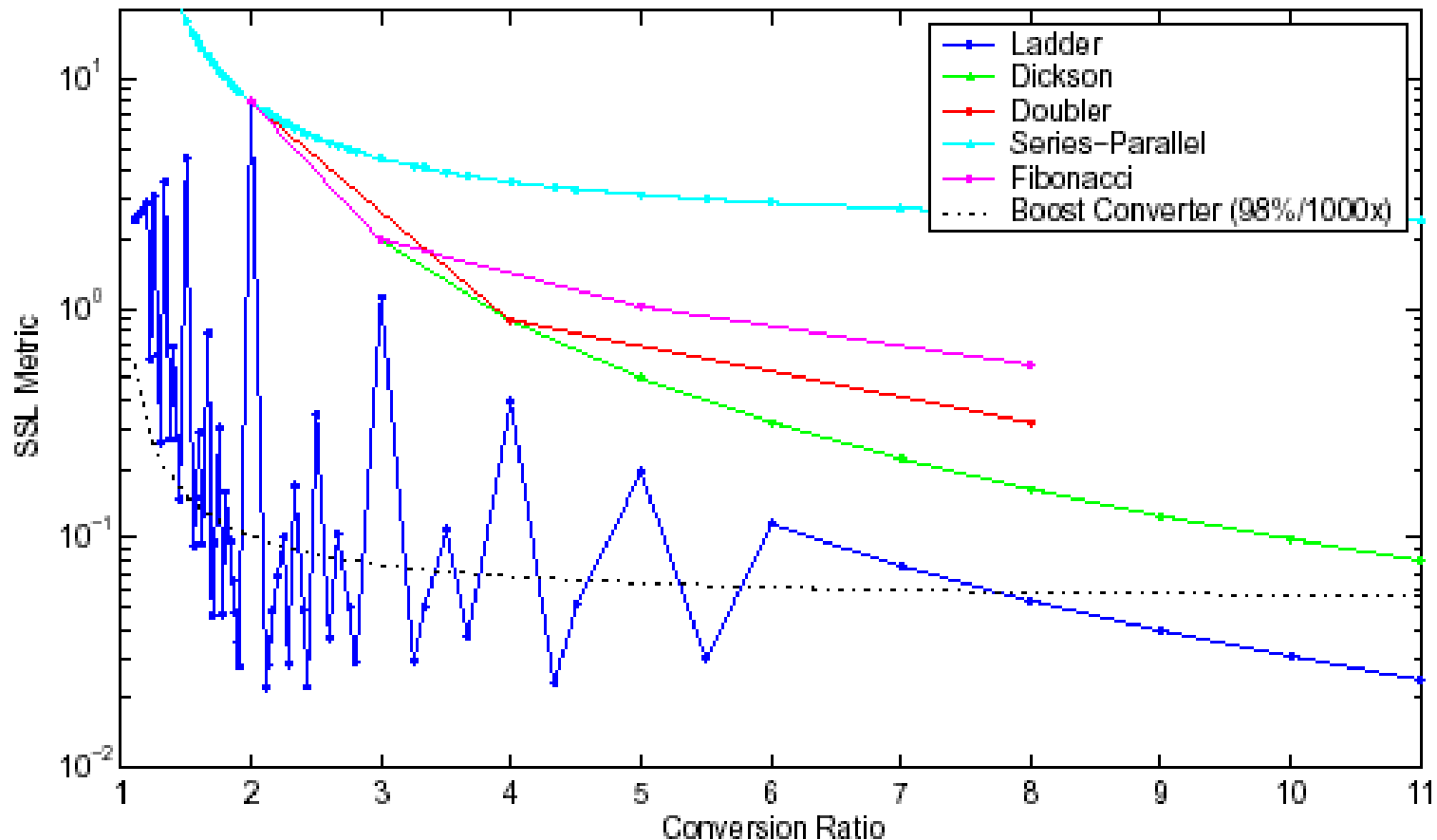
# Utilization of Reactive Elements:

- For boost or buck, derate inductor by 1000x relative to cap due to practical energy density, assert that S-C examples exhibit 2% voltage drop relative to mag ckts




# The Submicron Opportunity

- Rate device by ratio:  $G_s V_s^2 / C V_g^2$ 
  - Essentially an Ft type parameter for a power switch reflecting power gain, exposes opportunity in scaling
- Suggests that we should look for opportunities to build our ckts with scaled CMOS based devices, but:
  - Low voltage rating per device
  - Inadequate metal/interconnect for high current?


# Regulation Considerations

- *Open-Loop* Loadline Regulation
  - Droop matching resistive output impedance effective for loadline VR type reg.

Dominant First  
Order  
Dynamics

 


 
Simulation Example:  
8-phase 2-to-1  
converter



- Tap Changing for Line Regulation – Feedforward
- Multi-mode Operation for Apps like Voltage Scaling
 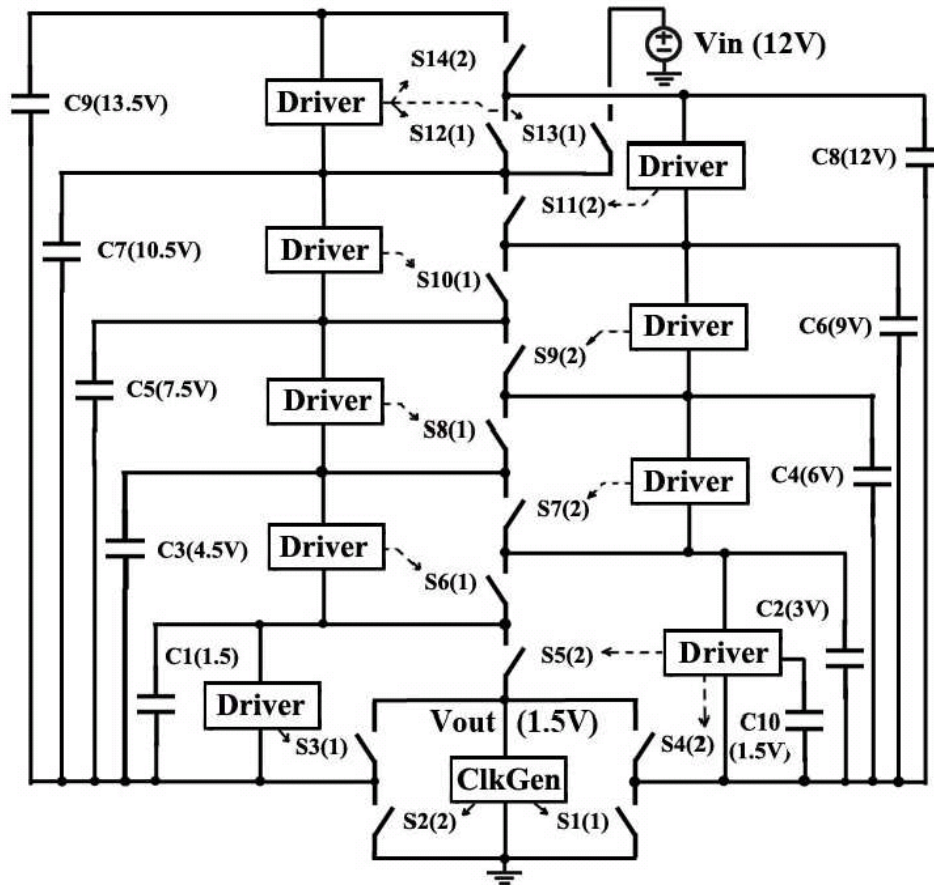
# Example 1 – Point-of-Load:12V-to-1.5V Dickson Circuit


Illustrates “tap-changing” technique for line regulation.



Regulation scheme against line variations

V.W. Ng, A 98% peak efficiency 1.5A 12V-to-1.5V Switched Capacitor dc-dc converter in 0.18  $\mu m$  CMOS technology, Master Thesis Report, EECS Dept, UC Berkeley, Dec. 2007.

# Layout in Triple-Well 0.18 um CMOS

 


AREA OF DIFFERENT COMPONENTS IN DIE LAYOUT

	area in layout
3V switches	$0.57mm^2$
3V switch buffers	$0.1mm^2$
1.5V switches	$0.5mm^2$
1.5V switch buffers	$0.06mm^2$
Other circuits	$0.13mm^2$
decoupling capacitors	$1.56mm^2$
<b>Total active area</b>	<b><math>3mm^2</math></b>
Total area excluding pads	$6.7mm^2$
<b>Total area including pads</b>	<b><math>9mm^2</math></b>




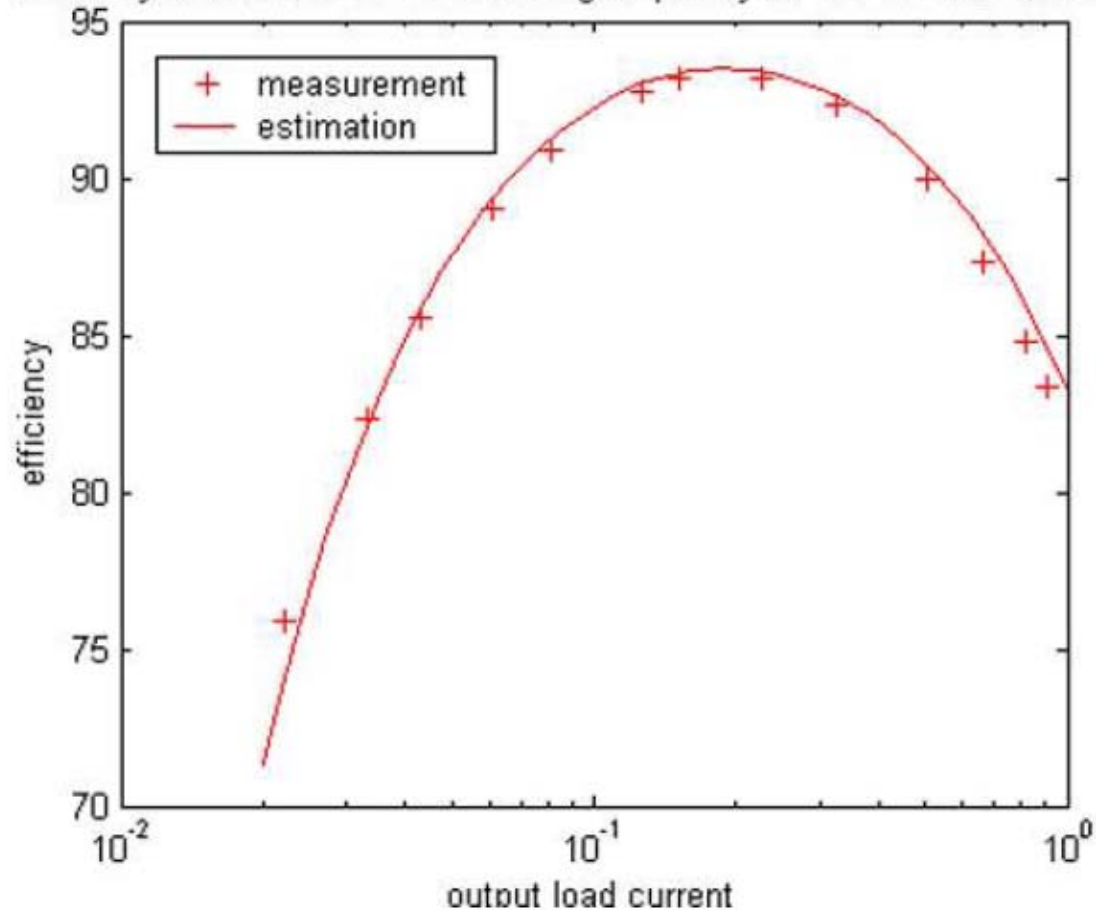
# Design vs. Performance

efficiency versus load 1MHz switching frequency for 12V-to-1.5V conversion



1.5V cap	2.2 $\mu$ F
3V cap	2.2 $\mu$ F
4.5V cap	1 $\mu$ F
6V cap	1 $\mu$ F
7.5V cap	0.68 $\mu$ F
9V cap	0.68 $\mu$ F
10.5V cap	0.47 $\mu$ F
3V switch width	16mm
1.5V switch width	75mm
Contribution to conduction loss	
all switches	51m $\Omega$
onchip metal	39m $\Omega$
capacitor $R_{ESR}$	15m $\Omega$
bondwire resistance	65m $\Omega$
Fixed loss	1.3mW
Freq-dep switch loss	7mW
<b><math>R_{OUT}@1MHz</math></b>	<b>211m<math>\Omega</math></b>
  
# POL Design 2: Flip Chip Packaging Scheme




# Cost and PCB Area Comparison

COMPARISON WITH OTHER WORKS IN INDUSTRY AND LITERATURE

	input	output	peak eff	> 80% eff	switch area	dominant passive	PCB area	height	L,C cost
1-st design (this work)	12V	1.5V	93% at 200mA	25mA-1A	1mm <sup>2</sup>	~1μF caps x10	13mm <sup>2</sup>	0.8mm	\$0.11
2-nd design (this work)	12V	1.5V	95% at 1 A	100mA-5A	4mm <sup>2</sup>	~3μF caps x 8	11mm <sup>2</sup>	0.8mm	\$0.09
SC converter (TI, [6])	5V	1.5V	85%	2mA-200mA		~1μF caps x 2	3mm <sup>2</sup>	0.8mm	\$0.02
buck (National, [7])	12V	0.8V	75%	-		10μH inductor	34mm <sup>2</sup>	2.8mm	\$0.47
buck (Linear, [9])	12V	3.3V	85%	0.1A-2A		4.7μH inductor	36mm <sup>2</sup>	2mm	\$0.17
buck (Maxim, [8])	12V	3.3V	86%	3mA-1.5A		10μH inductor	34mm <sup>2</sup>	2.8mm	\$0.47
buck (Literature, [5])	12V	1.3V	89%	1A-10A	15mm <sup>2</sup>	2μH inductor	156mm <sup>2</sup>	6.5mm	\$0.76
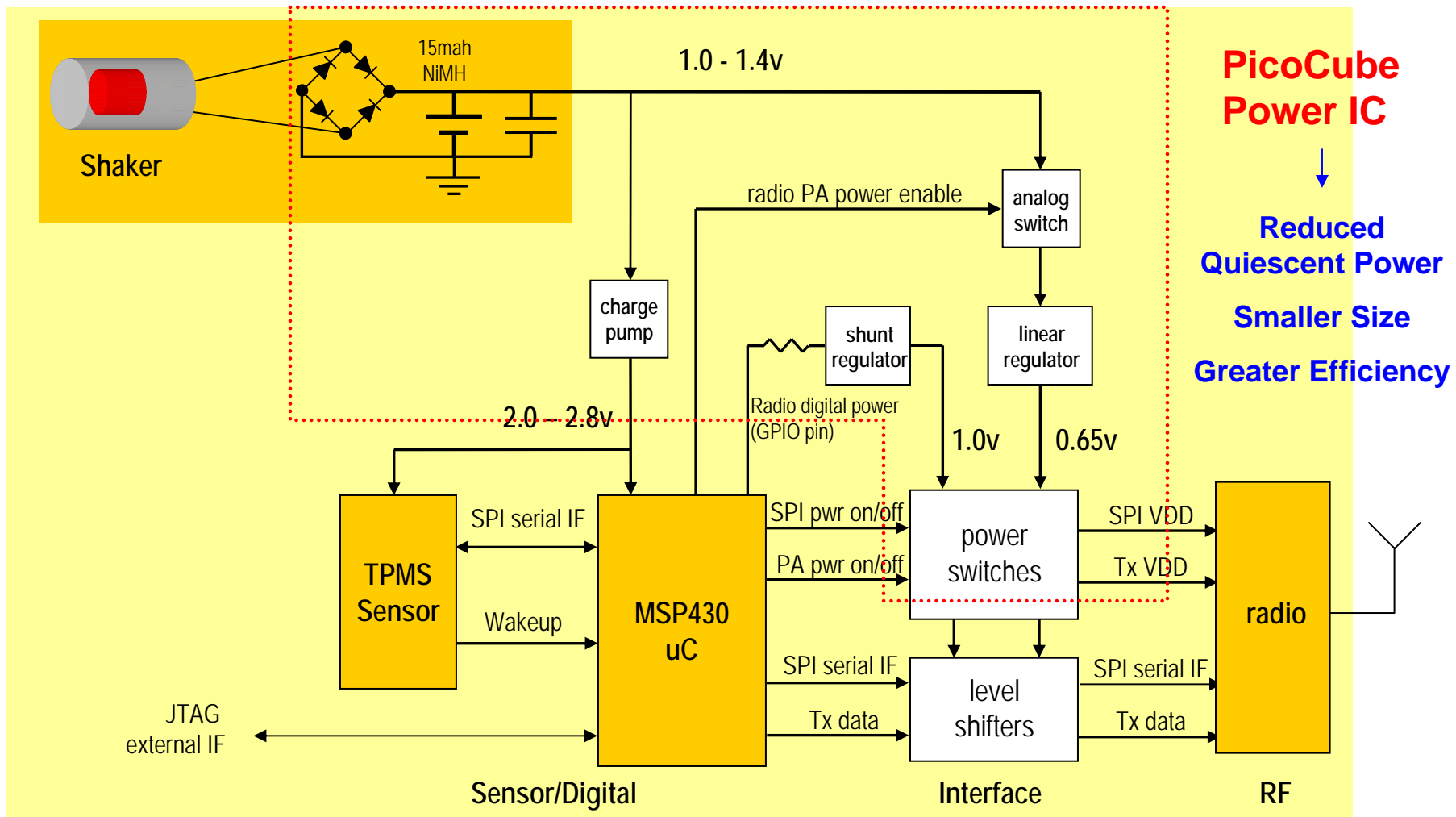
# Ex. 2 - Ultra-low-power Conversion in PicoCube Wireless Sensor Node




# PicoCube Power Management Chip Block Diagram


Analog/Control Circuits

Shaker

Power Circuits

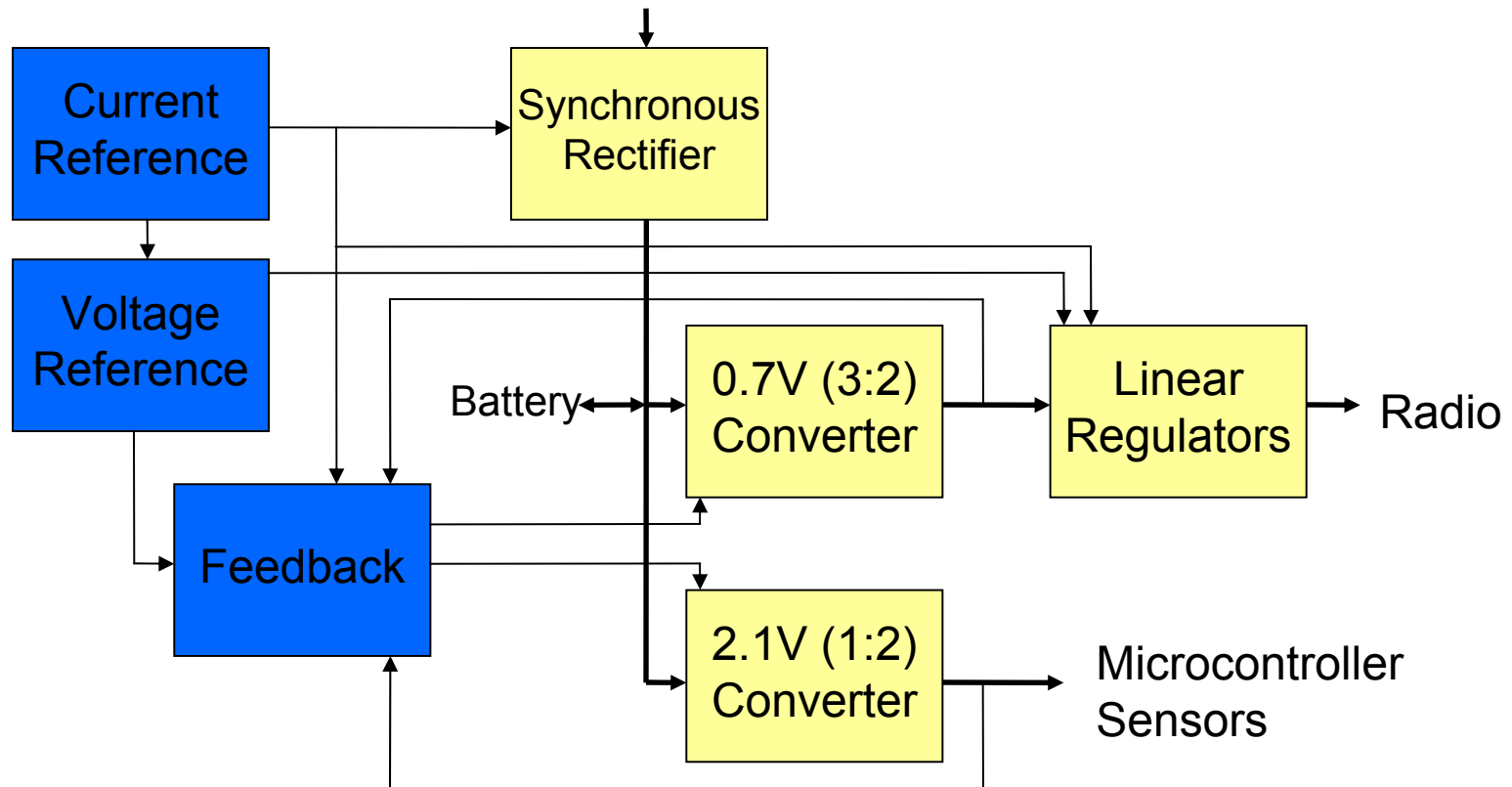



# PicoCube Converter Topology

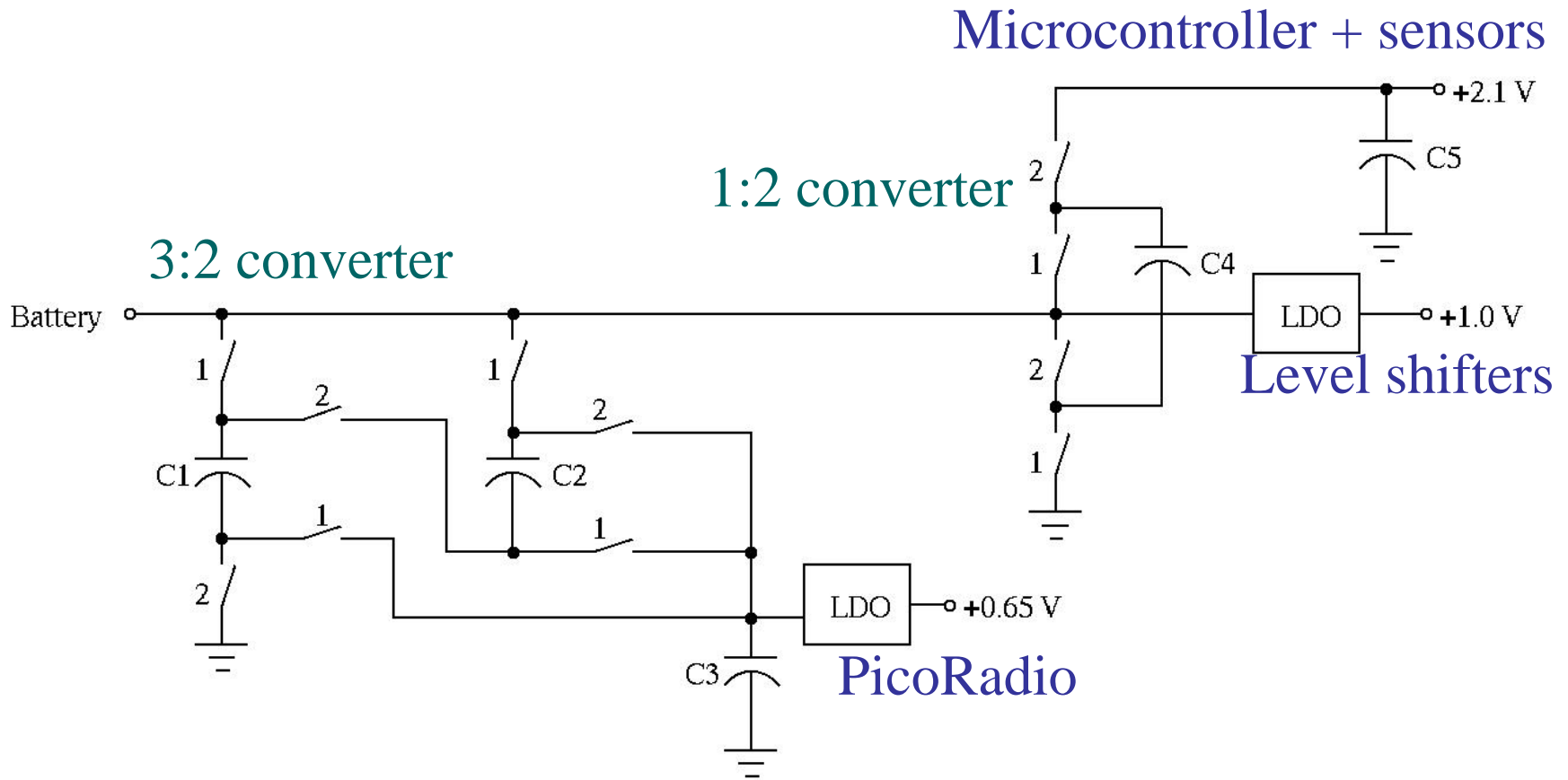

Linear Regulators (LDOs) further regulate and reduce ripple on outputs

 
 
# Hysteretic Feedback

- Regulates output voltage
  - On/off clocking control
  - Thermostat-type control
  - Improves efficiency by reducing  $f_{sw}$  for small loads



Converter leaves regulation for only large loads




# Converter Performance

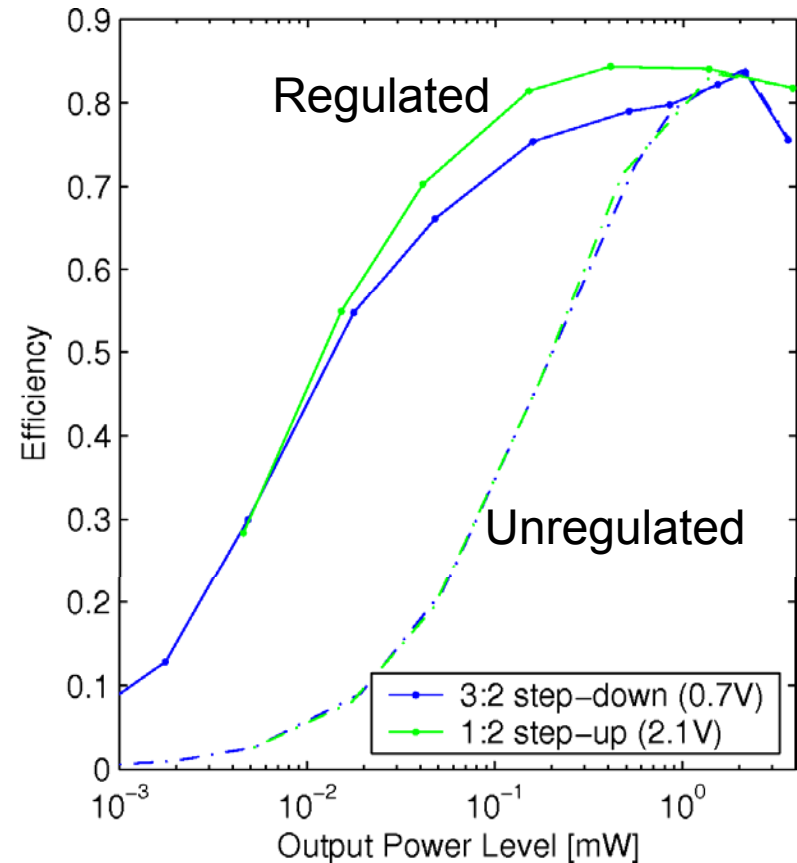 

Regulation is effective at controlling output voltage and increasing efficiency at low power levels!




# Ex. 3: Microprocessor SC Converter

 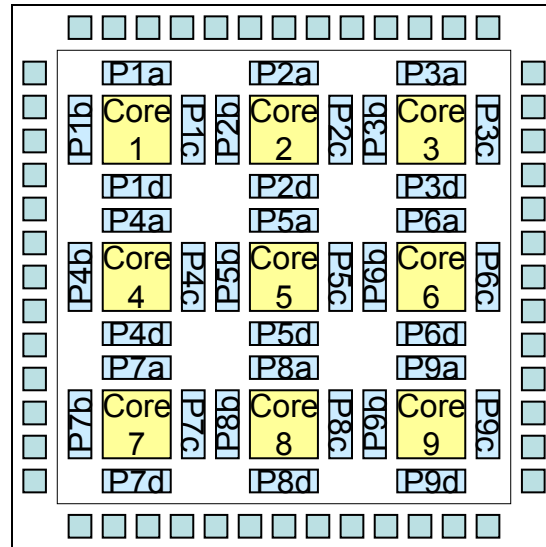 

- A power density of 1 W/mm<sup>2</sup> is achievable in 65nm process.
- A tiled design improves output ripple and ESR performance
- Creates a scalable IP platform
- Ideal for microprocessor supplies:
  - Ultra-fast transient response
  - Package I/O at higher voltage/lower current
  - Independent core voltage control
 
# Design Optimization Example: 0.4 W/sq.mm


- Representative 0.13um tech
- 2.4-to-1.2V Conversion
- 1 sq mm M-I-M cap (2 nF)
- Losses
  - SSL (main caps)
  - FSL (conduction)
  - Gate cap
  - Cap Bottom plate
  - Junction cap


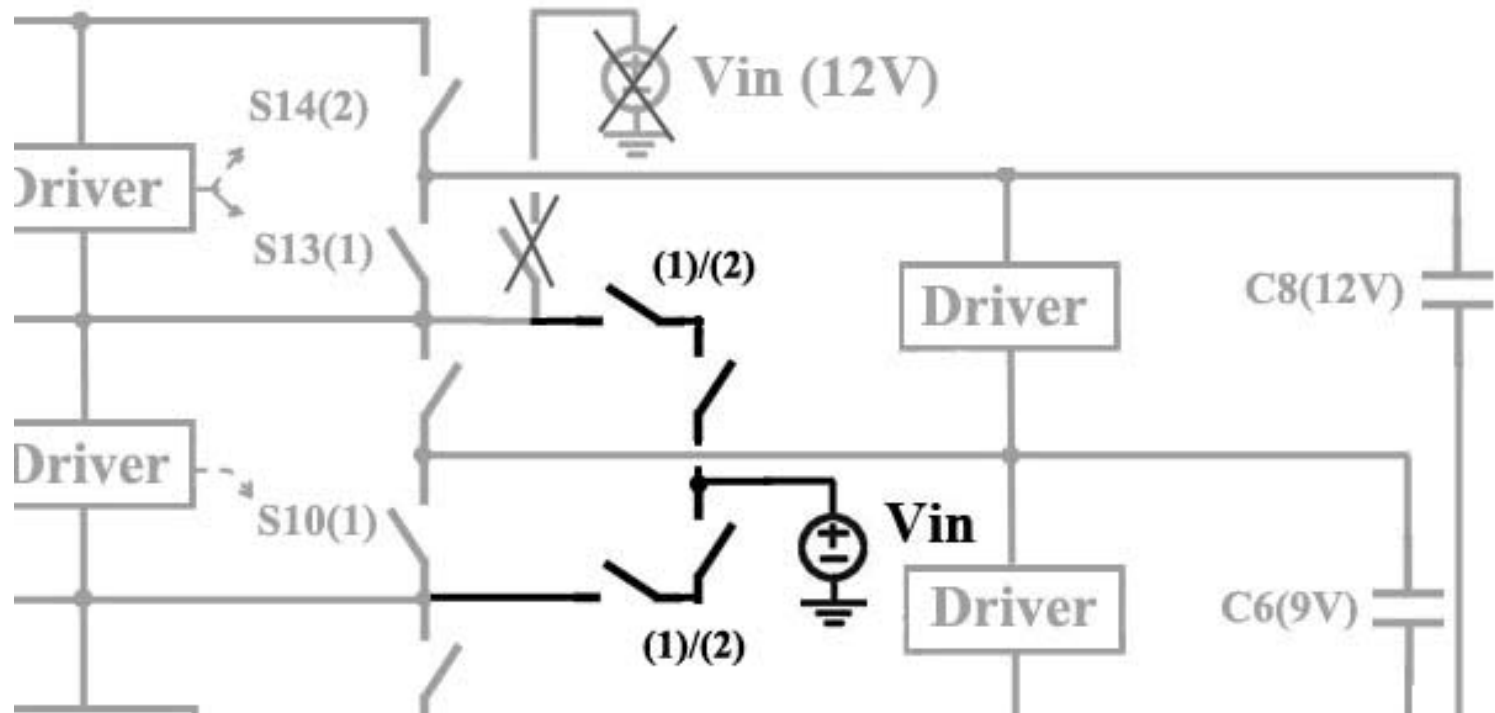
# Switched Cap Take-Aways

- Theoretical performance exceeds magnetic-based converters, and this is being realized in research
- Very simple low power operation – reduce clk
- Integration convenient for v. low power app's to v. high current app's
- Moderate (high) voltage capability by stacking devices – triple-well, SOI
- Regulation challenges – nominal fixed ratio, but can operate with multiple Taps
- Further on-chip integration via aggressive clk scaling

- Tap Changing for Line Regulation – Feedforward



- Multi-mode Operation for Apps like Voltage Scaling

# Conduction Loss Comparison

M. Seeman, S. Sanders, IEEE T-PELS, March 2008

- Performance compared with switch  $GV^2$  metric:

$$\frac{G_{OUT} V_{OUT}^2}{\sum G_i v_{r,i(rated)}^2}$$

- Since converters are bi-directional, graph applies equally to step-down converters

- Magnetic components modeled with *zero* conduction loss, and *no* switching loss impact

