



# **Integrated inductive DC/DC down conversion for integrated power management using a two-die approach**

Henk Jan Bergveld, Kasia Nowak, Ravi Karadi  
September 24, 2008

# Outline

- ▶ Introduction
  - Why integrated power management?
  - Two-die approach for integration
- ▶ First demonstrator
  - Design aspects
  - System-in-Package (SiP) construction
  - Measurement results
- ▶ Second demonstrator
  - Improvements with respect to first demonstrator
  - Design aspects
  - Measurement results for active die
- ▶ Conclusions and future outlook



# **Introduction**

# Why integrated power management?

- ▶ Energy-source voltage  $\neq$  load voltage
- ▶ Drive for **efficient voltage conversion**
  - ...for increased run time in mobile devices
  - ...for reduced petrol consumption in automotive
  - Switched-mode conversion: Ls and/or Cs
- ▶ Drive for **smaller size/integration of power supplies**
  - Package integration; low L,C, high  $f_s$
  - Enables integration of power supply with load: system integration
  - System integration would allow increased power efficiency
- ▶ Integrated power management: **small form-factor highly efficient DC/DC converters**

# Integrated DC/DC conversion

- ▶ Integrated capacitive converters
  - Advantage
    - Avoid integration of inductor
  - Disadvantages
    - Limited control of output voltage
    - Multi-ratio converters require many capacitors
- ▶ Integrated inductive converters
  - Advantages
    - Limited number of passives
    - Good control of output voltage
  - Disadvantage
    - Integration of inductor difficult
- ▶ Approach:
  - Integrated inductive down conversion using planar air-core inductor
  - 100-mW output power range

# Two-die approach for integration

## ► Rationale:

- **Actives** integrated in **nm-CMOS** with the load
- **Passives** in low-mask-count optimized **passive-integration process (PICS)**

## ► Pros

- High-density capacitors, low area for  $C_{in}$  and  $C_{out}$  (10-100 nF)
- Low height (<600  $\mu\text{m}$ )

## ► Cons


- Need copper for reasonable Q factor inductor
- Planar technology, relatively large foot print coil (e.g. 10 nH costs 1  $\text{mm}^2$ )

# **Results for the first demonstrator (\*)**

(\*) H.J. Bergveld, R. Karadi, K. Nowak, 'An inductive down converter System-in-Package for integrated power management in battery-powered applications', IEEE Power Electronics Specialist Conference, PESC08, pp. 3335-3341, Rhodes, Greece, June 16-18, 2008
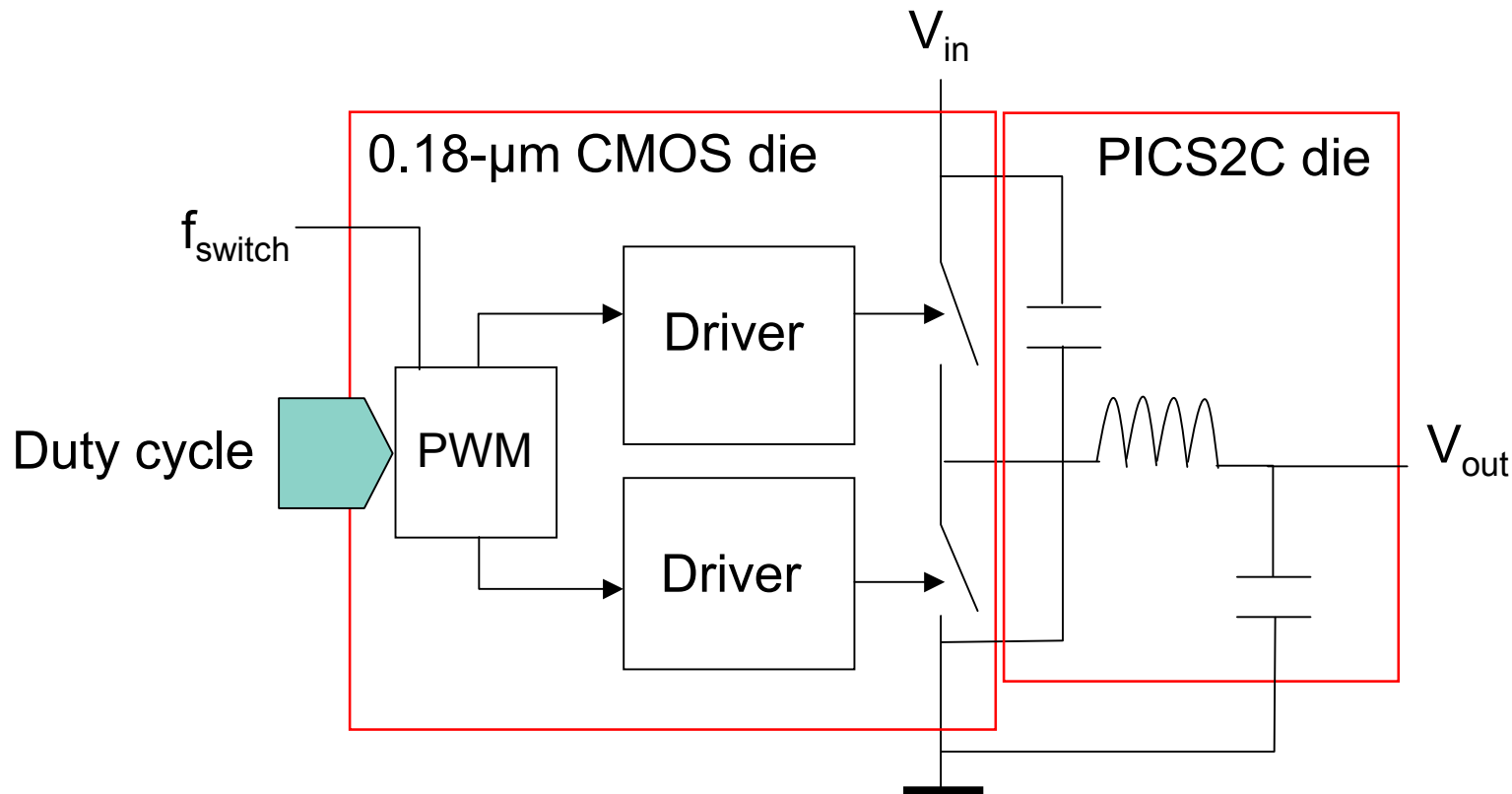
# Design aspects active die

- System block diagram of synchronous DC/DC down converter




No closed-loop control! Focus on power stage and two-die approach



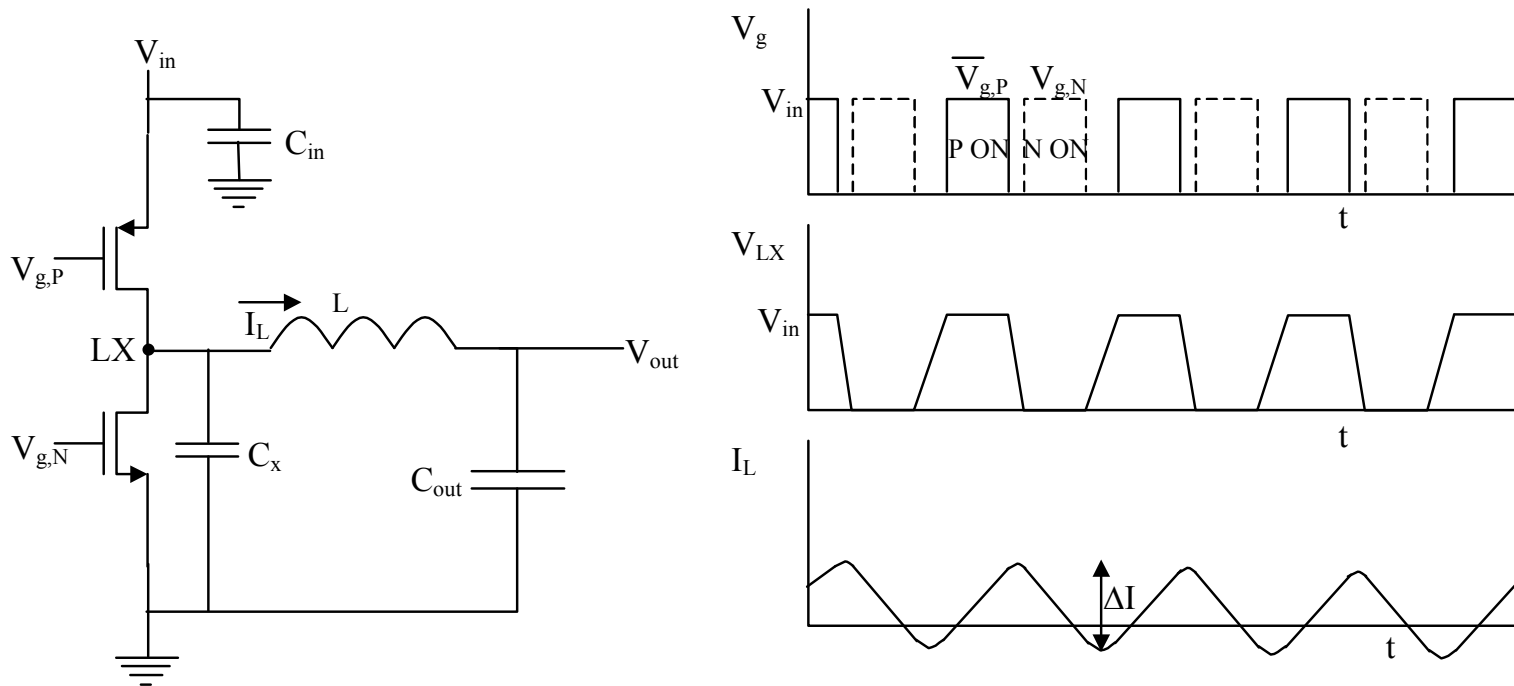
# Design aspects active die

- ▶ Zero-Voltage-Switching (ZVS) concept (Continuous Conduction Mode)



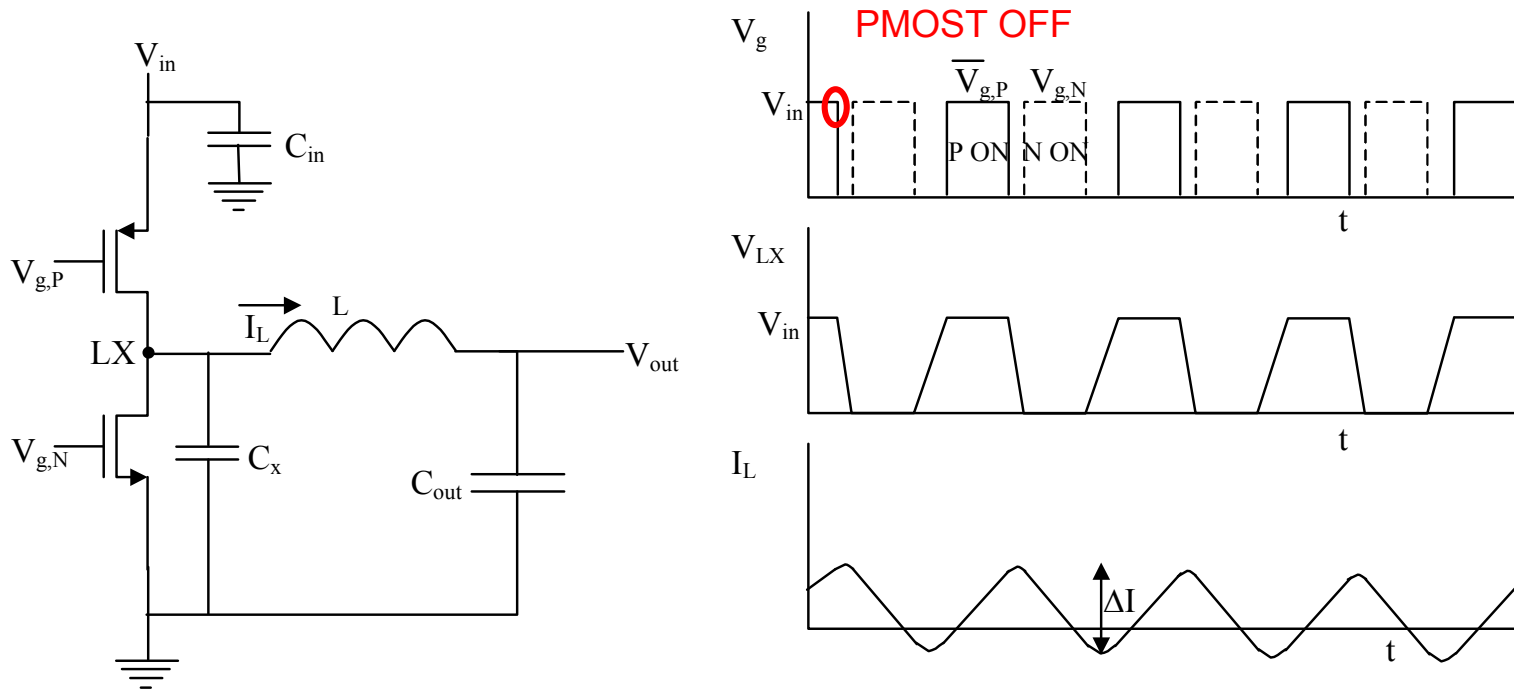
# Design aspects active die

- Zero-Voltage-Switching (ZVS) concept (Continuous Conduction Mode)



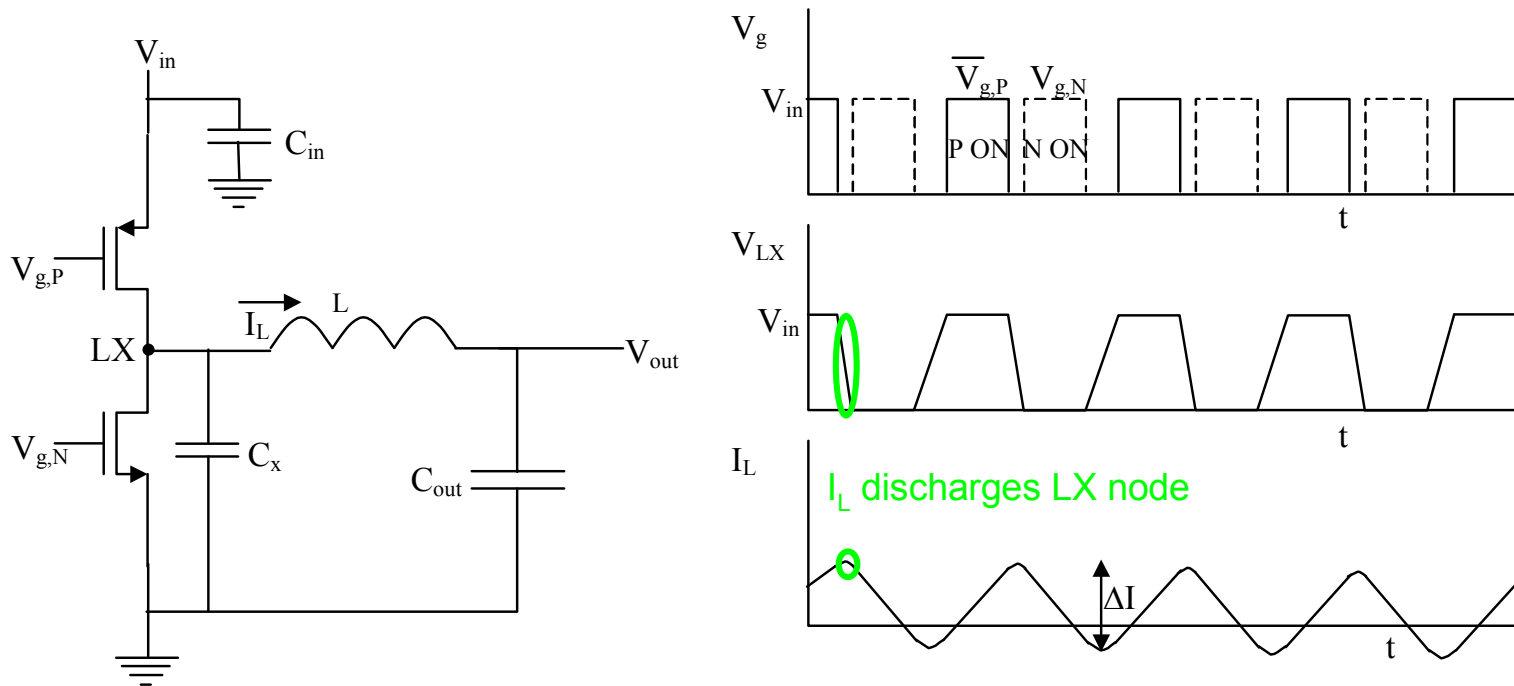
# Design aspects active die

- ▶ Zero-Voltage-Switching (ZVS) concept (Continuous Conduction Mode)



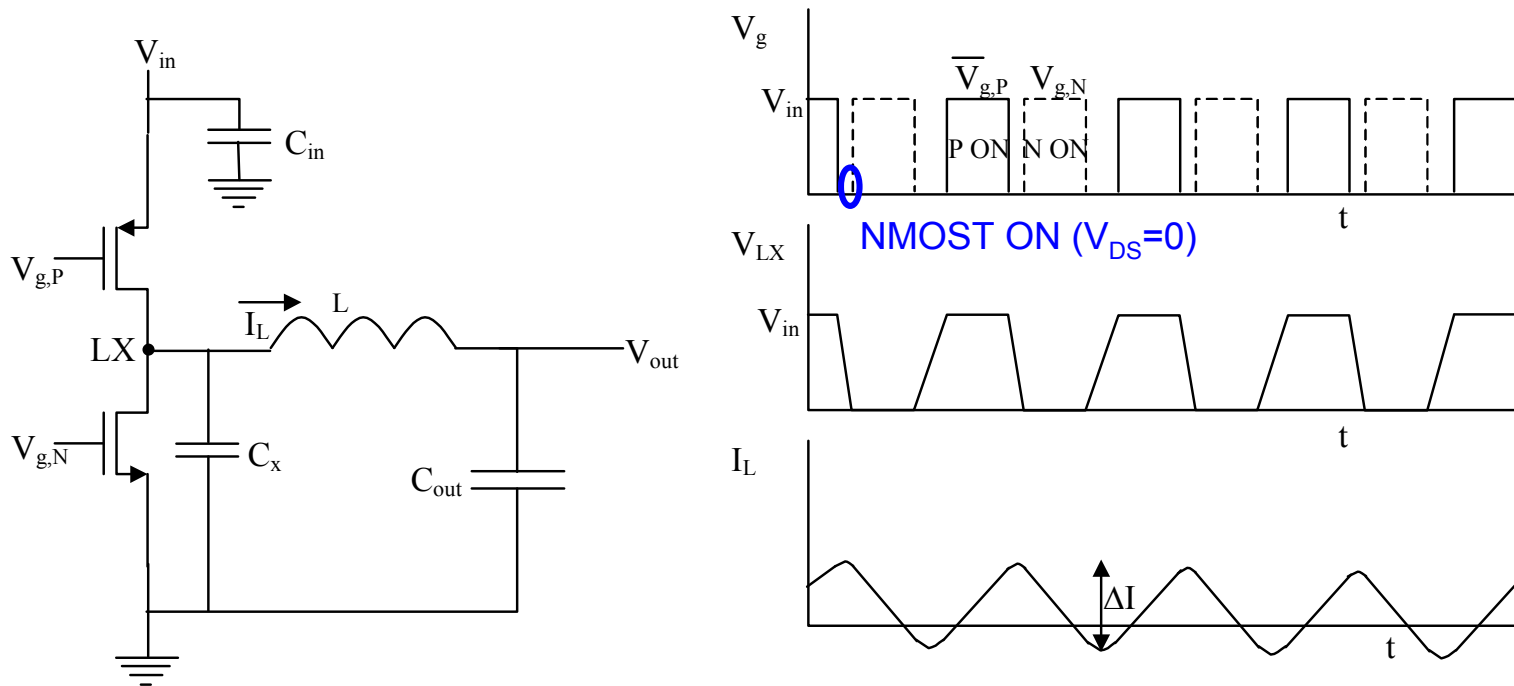
# Design aspects active die

- Zero-Voltage-Switching (ZVS) concept (Continuous Conduction Mode)



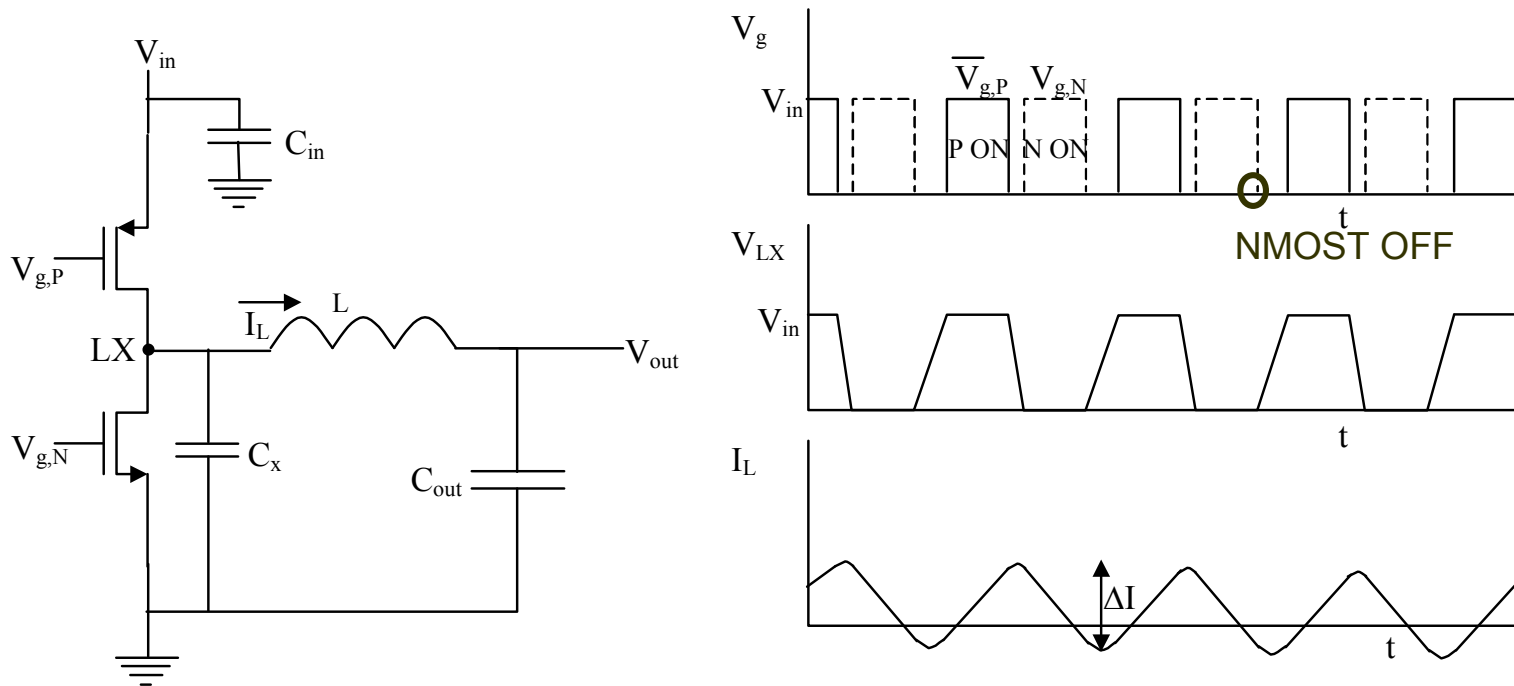
# Design aspects active die

- ▶ Zero-Voltage-Switching (ZVS) concept (Continuous Conduction Mode)



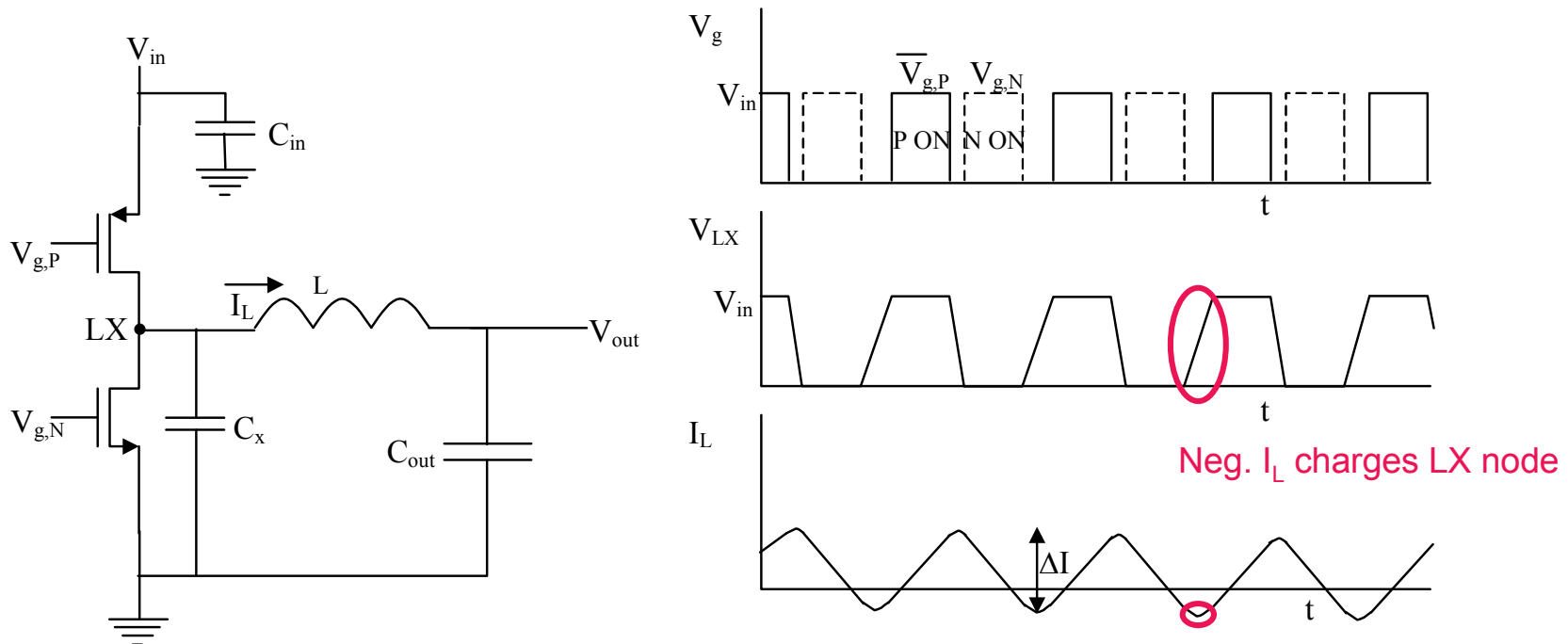
# Design aspects active die

- Zero-Voltage-Switching (ZVS) concept (Continuous Conduction Mode)



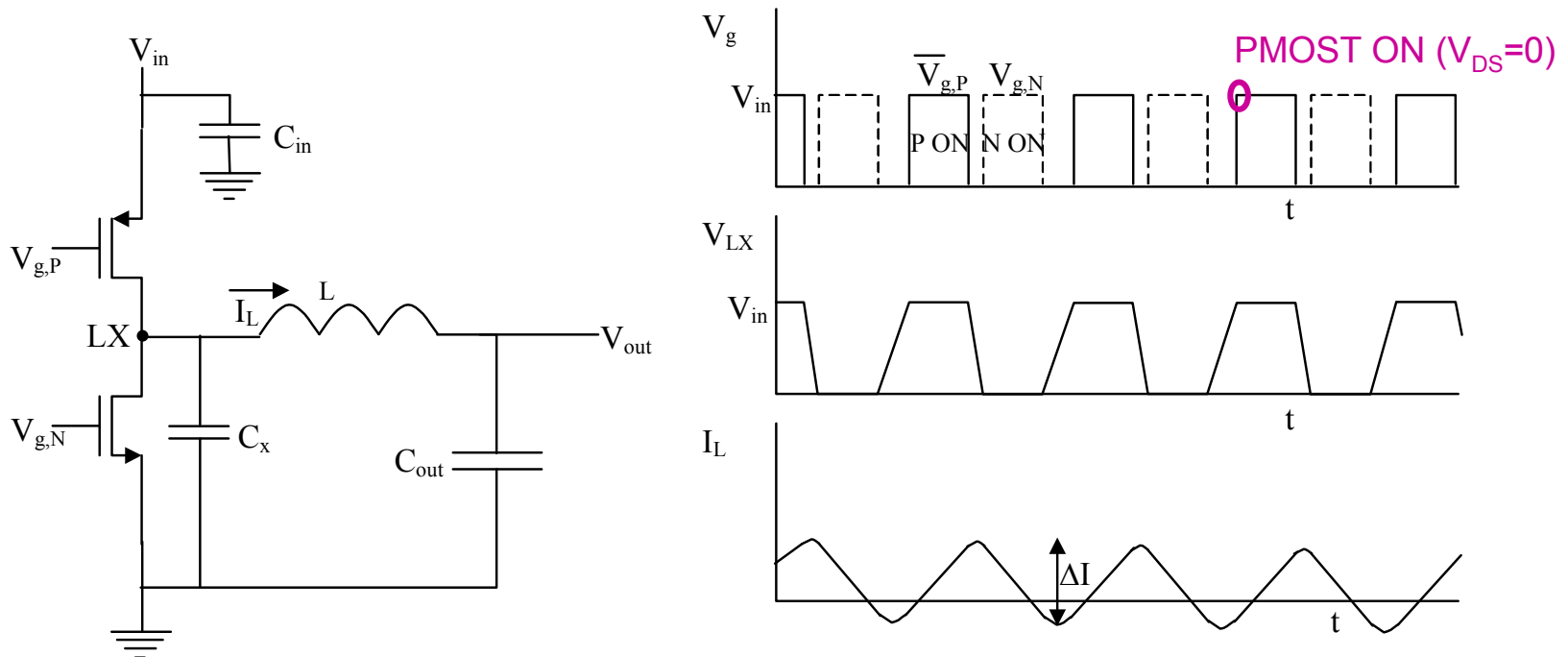
# Design aspects active die

- Zero-Voltage-Switching (ZVS) concept (Continuous Conduction Mode)


 
# Design aspects active die

- ▶ Zero-Voltage-Switching (ZVS) concept (Continuous Conduction Mode)




- Need adaptive dead-time control
- $V_{in}=1.8\text{ V}$ ,  $P_{out}=100\text{ mW} \rightarrow$  Simple ZVS



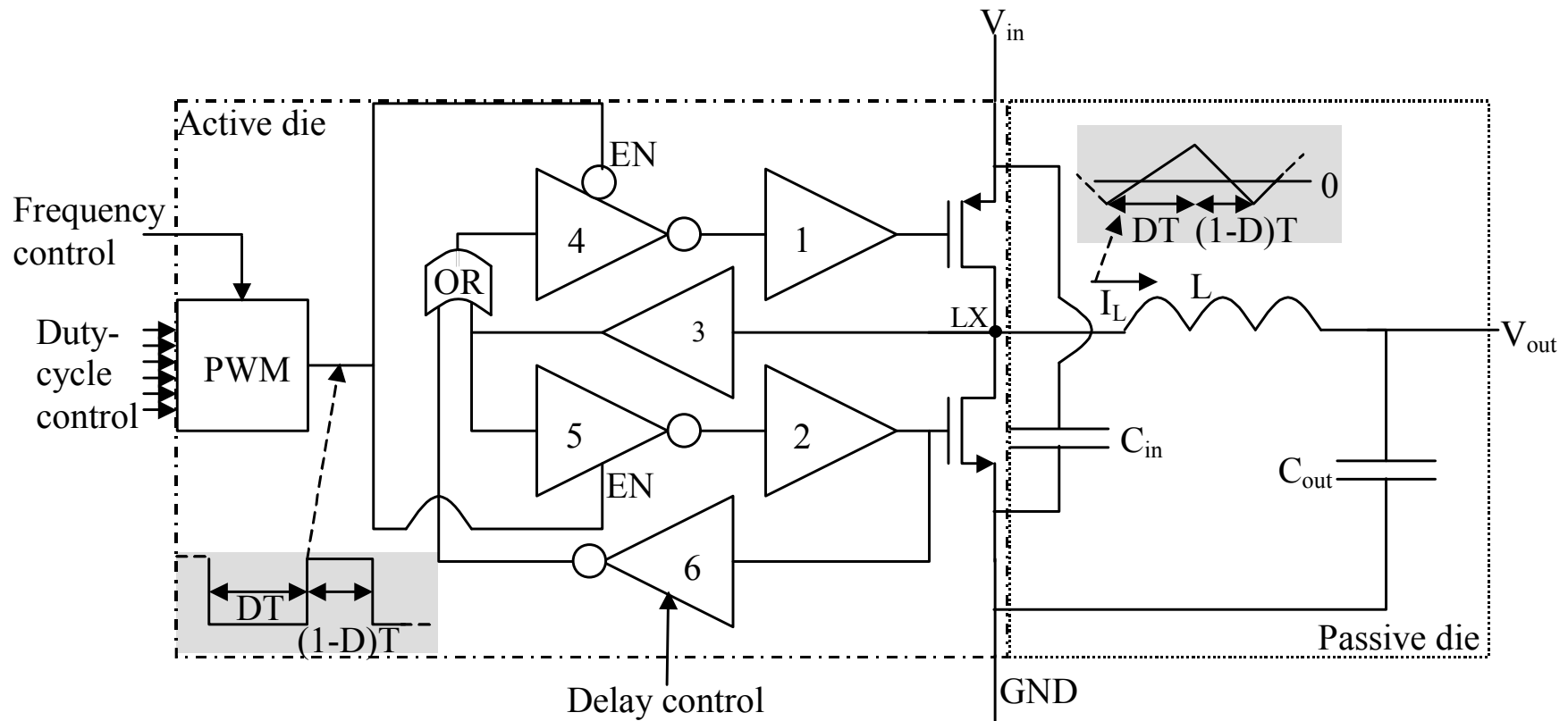
# Design aspects active die

- System block diagram incl. ZVS implementation



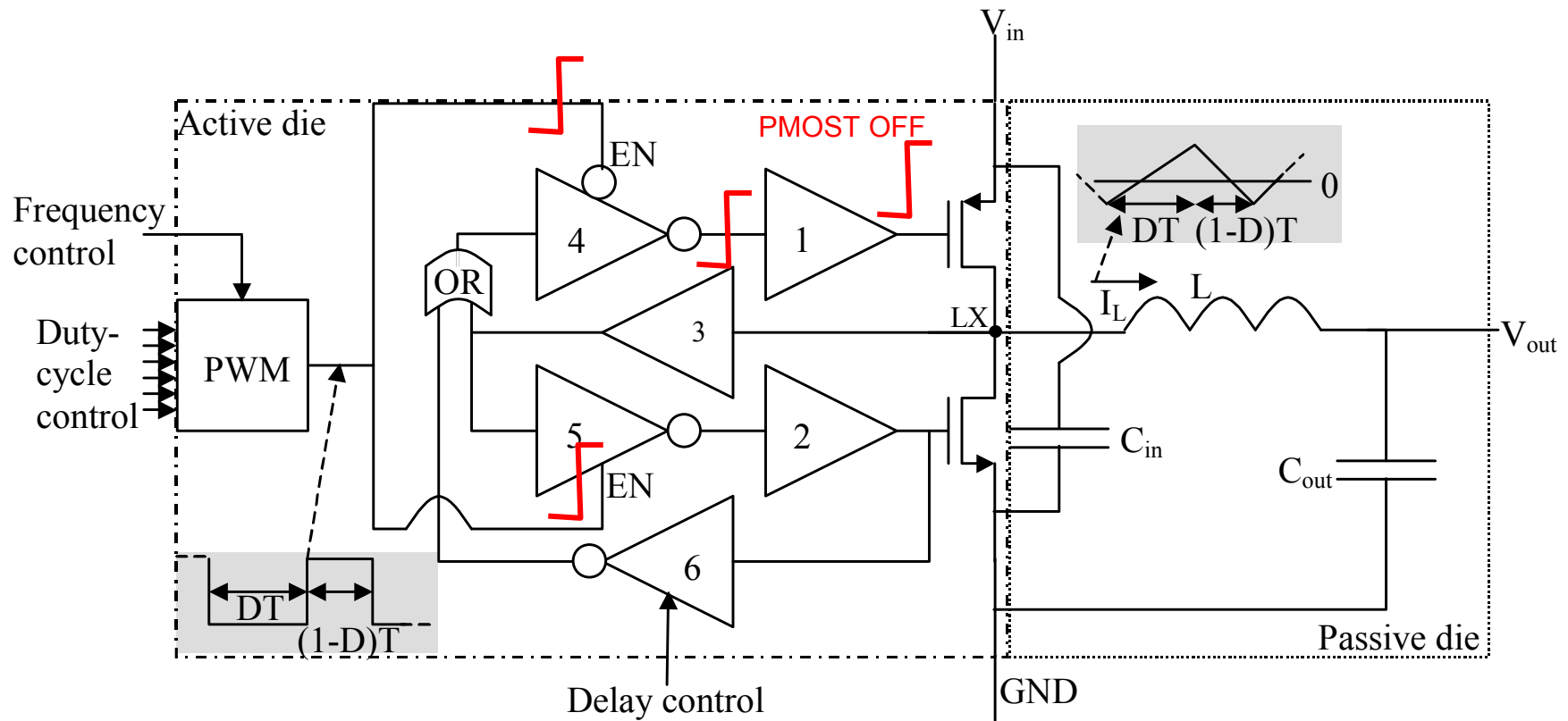
# Design aspects active die

- System block diagram incl. ZVS implementation


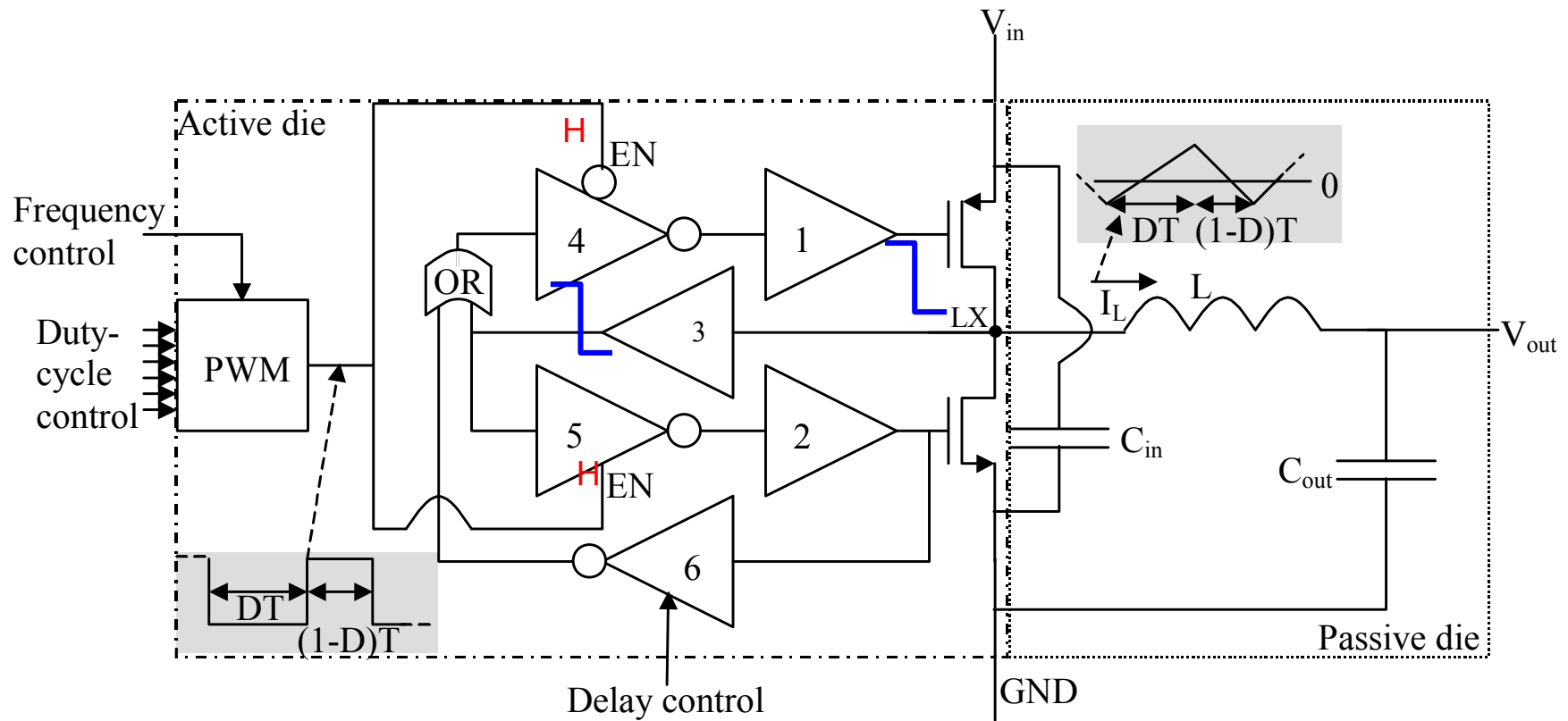
# Design aspects active die

- System block diagram incl. ZVS implementation




- System block diagram incl. ZVS implementation



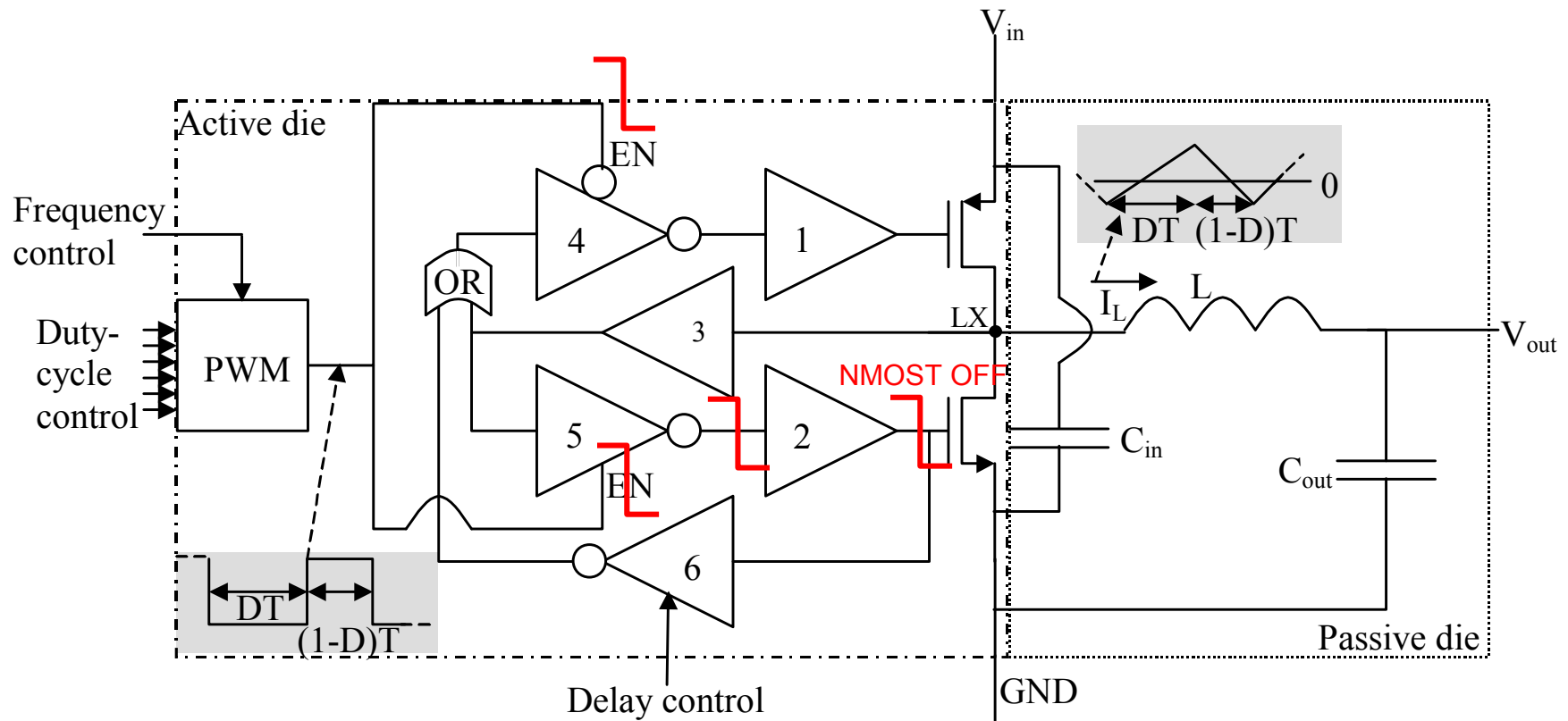
# Design aspects active die

- System block diagram incl. ZVS implementation



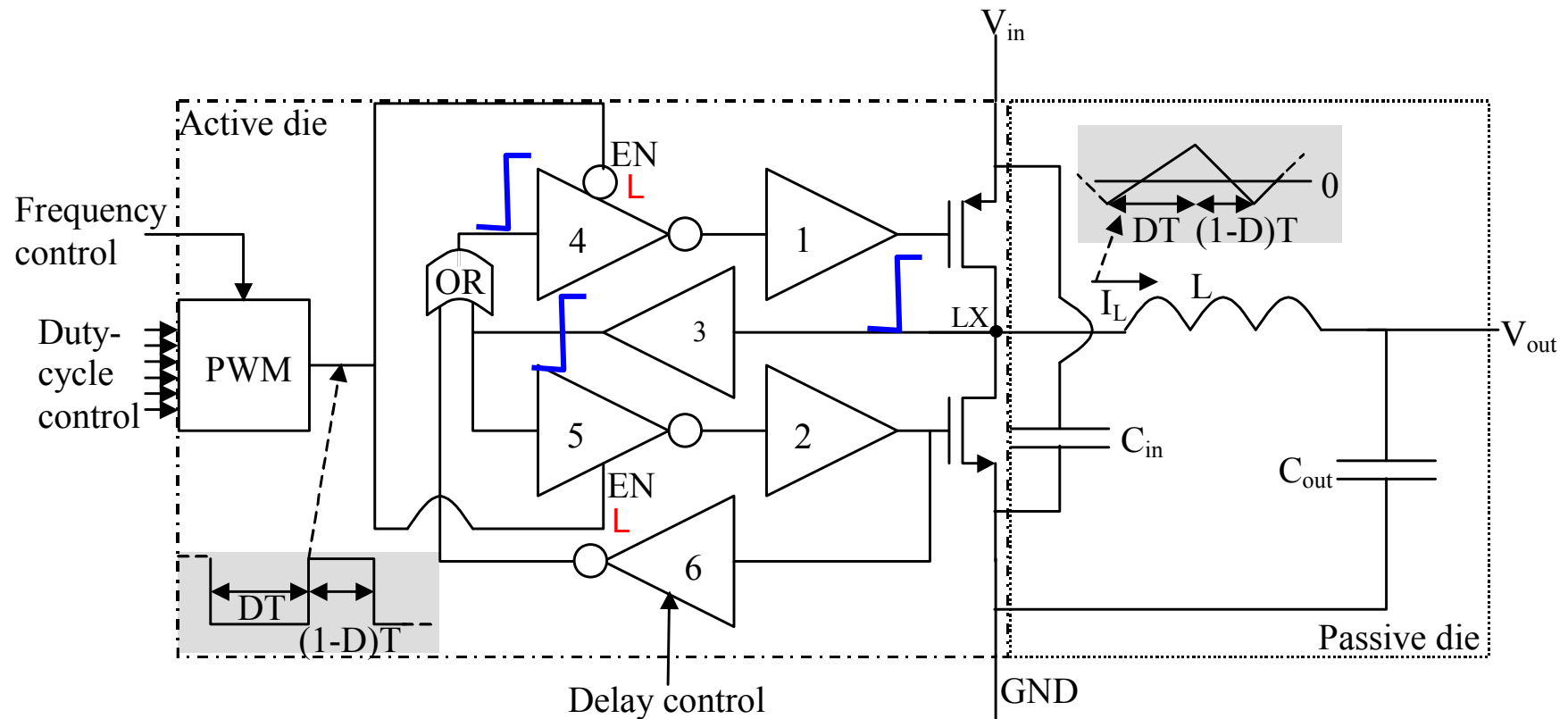
# Design aspects active die

- System block diagram incl. ZVS implementation


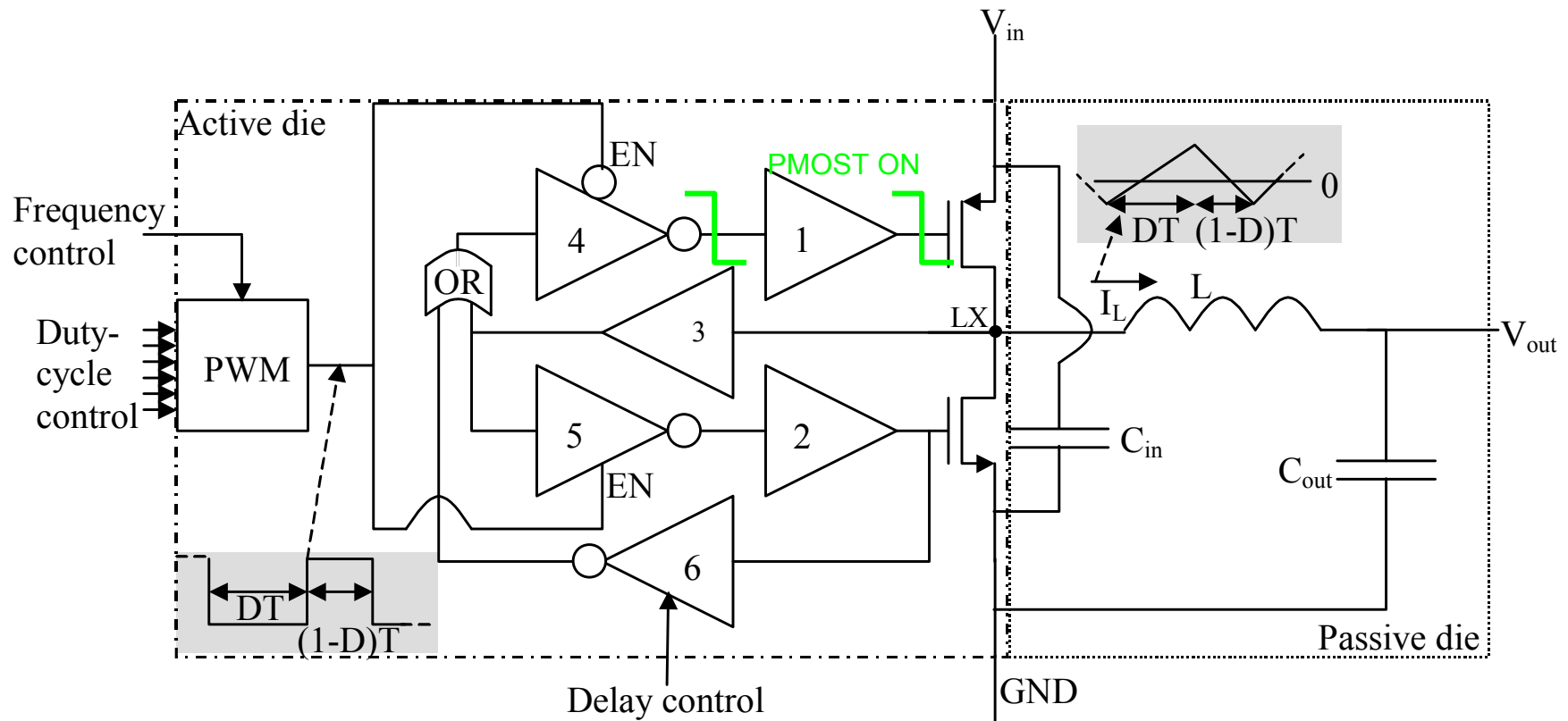
# Design aspects active die

- System block diagram incl. ZVS implementation




- ▶ System block diagram incl. ZVS implementation





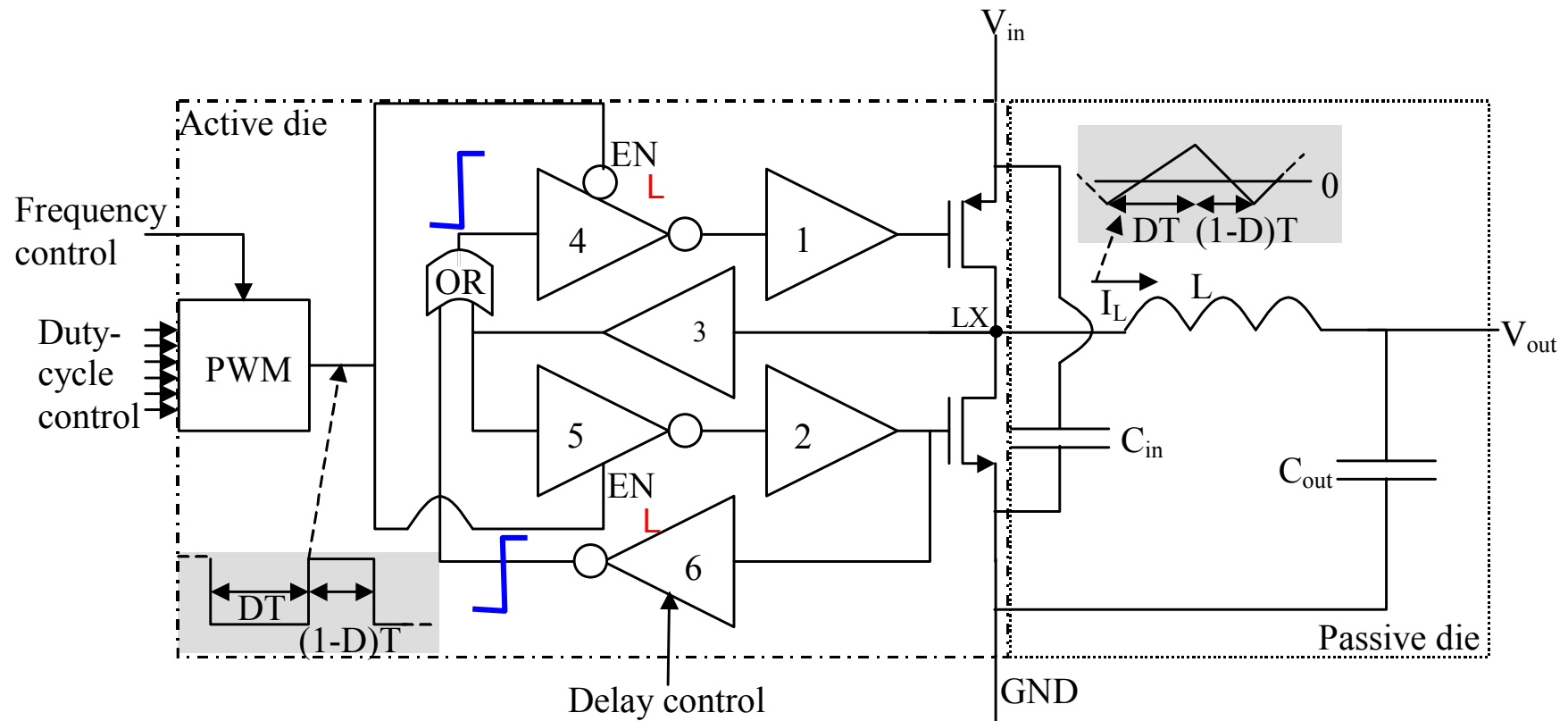
# Design aspects active die

- System block diagram incl. ZVS implementation



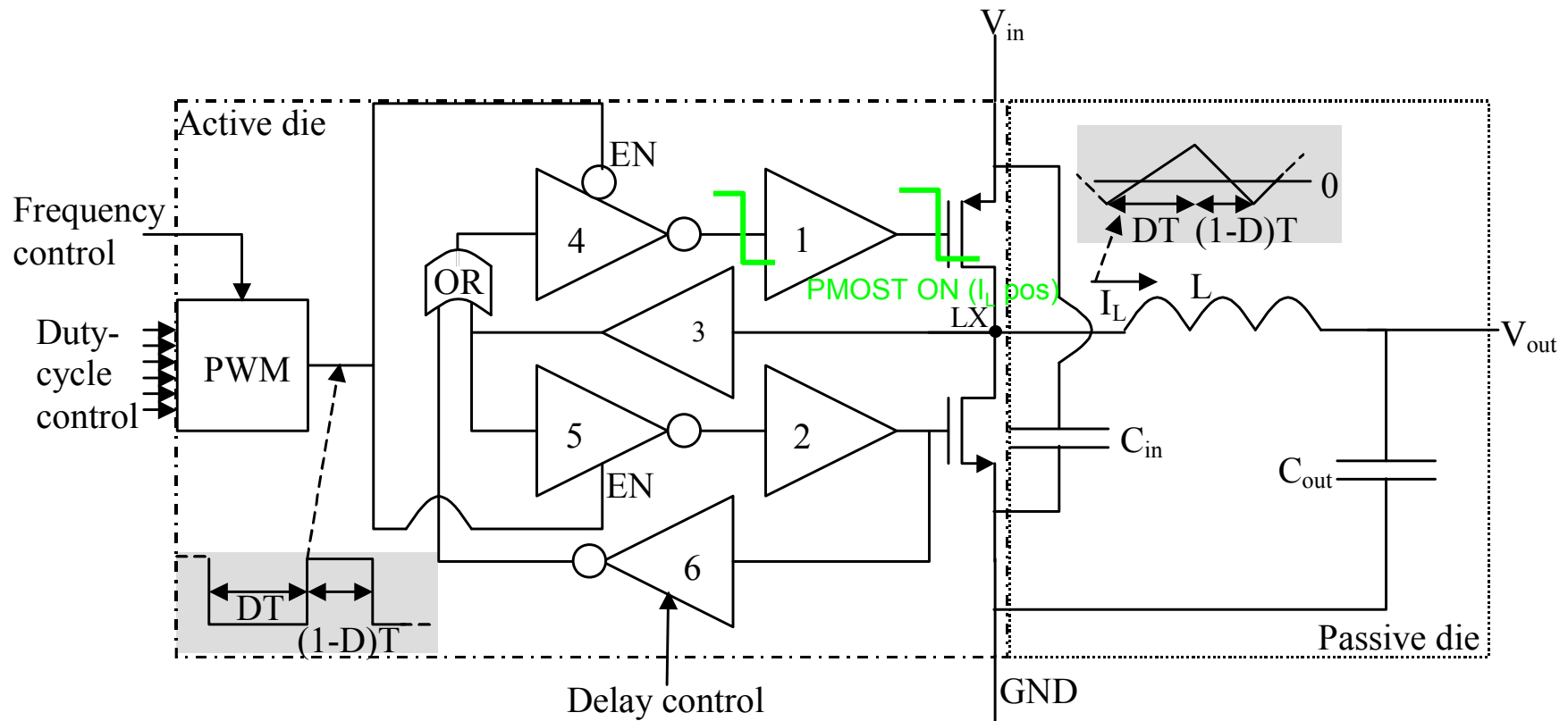
# Design aspects active die

- System block diagram incl. ZVS implementation


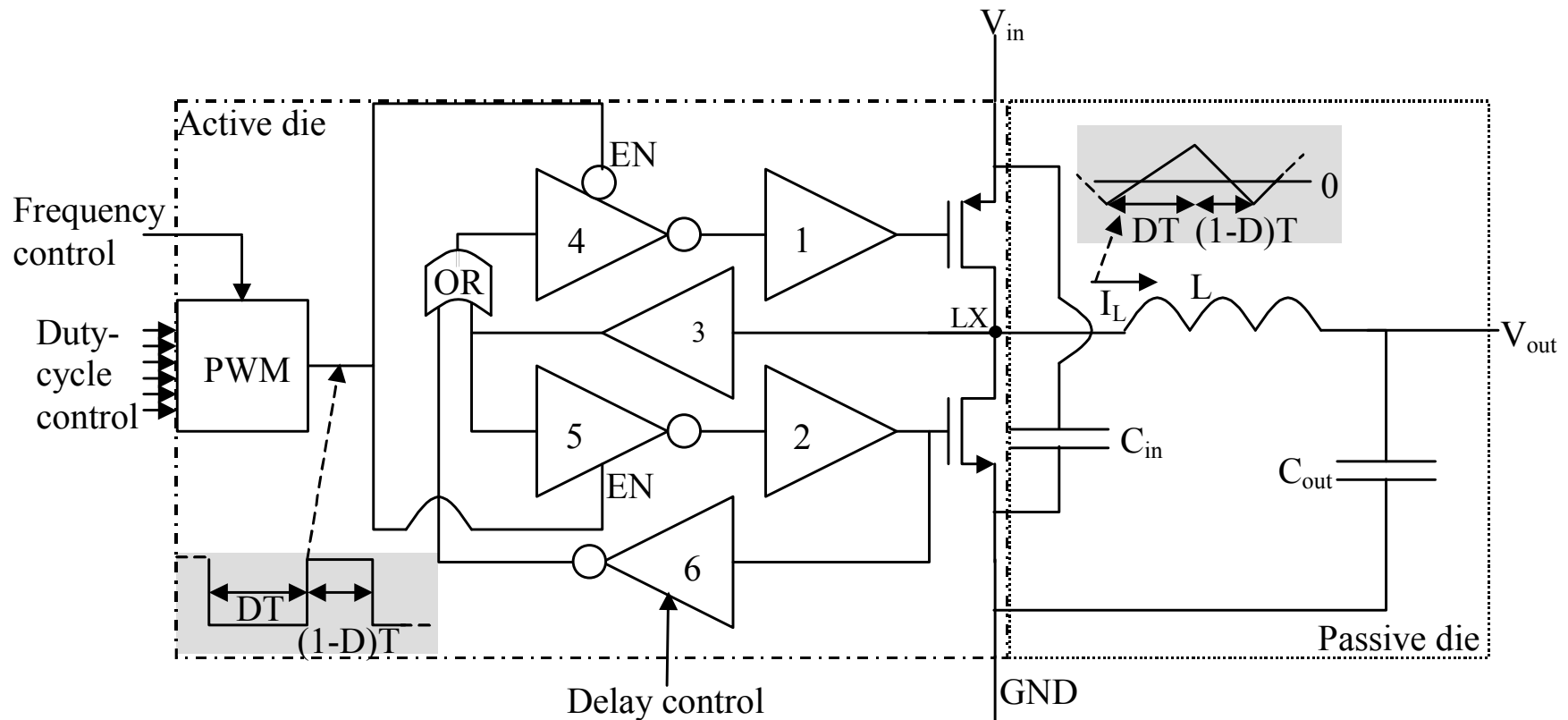
# Design aspects active die



- System block diagram incl. ZVS implementation



- Switches optimized for  $f=50$  MHz,  $I=100$  mA,  $L=20$  nH
- Driver tapering factor and number of stages optimized

  
# Design aspects passive die

- ▶ Passive process: Passive-Integration Connective Substrate
  - Silicon-based platform for integrating R, L, C
  - High capacity density: 80 nF/mm<sup>2</sup> in used version,  $V_{BV}=15.5$  V
  - Two metal layers
    - First-level aluminium
    - Second-level 8- $\mu$ m copper: inductor




# Design aspects passive die

## Inductor design

 


 - Fit  $C_{out}=75$  nF (15 mV<sub>pp</sub> ripple) inside
- $L=20$  nH:  $N=3$ ,  $w=80$   $\mu$ m,  $s=8$   $\mu$ m
- Underpass: balance R and  $f_{res}$  (1 GHz)
- Various test structures for probing



# Design aspects passive die



## Total die design

 

- $C_{out}$  connections
  - Thin parallel stripes: low losses
  - Copper routing (low ESR)
  - GND underpass: balance ESR and  $f_{res}$
- Thick supply lines (250  $\mu m$ )
- $C_{in}=300$  nF
  - Complete area active die (3.8x3.8 mm<sup>2</sup>)
- Total passive-die area: 6.6x6 mm<sup>2</sup>






# SiP construction

  




- Flip-chip: Thermo compression gold stud bumps
- Sandwich wire-bonded in QFP64 package

# Measurement results: LC filter

   




# Measurement results: LC filter

   

Plot inductors\_pics\_w8/compare/duts\_80u/L

C:19 freq=10.00 MHz, Y(2)=20.47n

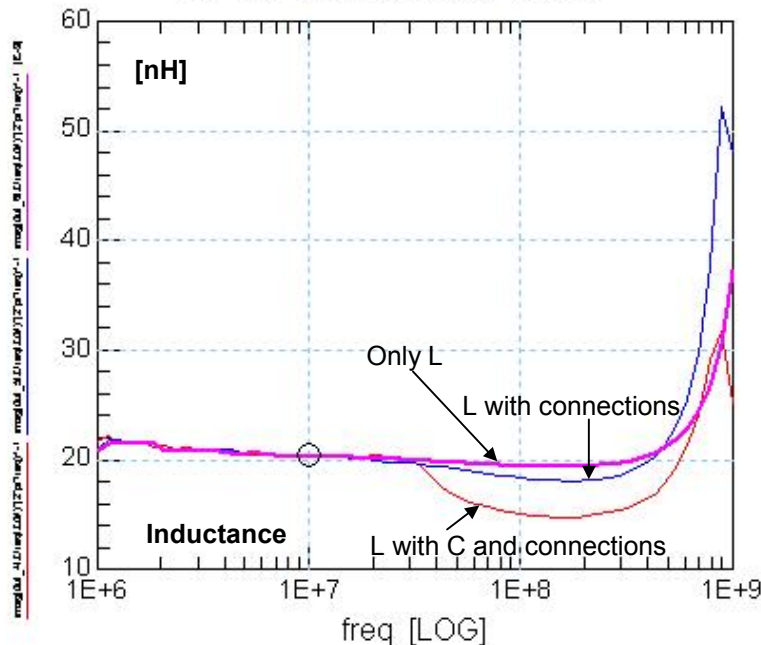


PO  
A

X  
Y

Plot inductors\_pics\_w8/compare/duts\_80u/Z




C:33 freq=54.56 MHz, Y(0)=2.014

 

PO  
A


X  
Y

# Measurement results: LC filter

   

Plot inductors\_pics\_w8/compare/duts\_80u/L

C:19 freq=10.00 MHz, Y(2)=20.47n

 


PO  
A

X  
Y

Plot inductors\_pics\_w8/compare/duts\_80u/Z




C:33 freq=54.56 MHz, Y(0)=2.014

 

PO  
A


X  
Y

# Measurement results: LC filter

   

Plot inductors\_pics\_w8/compare/duts\_80u/L

C:19 freq=10.00 MHz, Y(2)=20.47n

 


PO  
A

X  
Y

Plot inductors\_pics\_w8/compare/duts\_80u/Z

C:33 freq=54.56 MHz, Y(0)=2.014

 


PO  
A

X  
Y

 
# Measurement results: complete converter

Measured efficiency for  $V_{in}=1.8\text{ V}$ ,  $V_{out}=1.1\text{ V}$ , minimum delay



 
# Measurement results: complete converter

Measured efficiency for  $V_{in}=1.8\text{ V}$ ,  $V_{out}=1.1\text{ V}$ , minimum delay



 
# Measurement results: complete converter

Measured efficiency for  $V_{in}=1.8\text{ V}$ ,  $V_{out}=1.1\text{ V}$ , minimum delay



 
# Measurement results: complete converter

Measured efficiency for  $V_{in}=1.8\text{ V}$ ,  $V_{out}=1.1\text{ V}$ , minimum delay


 
# Measurement results: complete converter

Measured vs simulated efficiency at  $f=80$  MHz




- LC-filter model fitted to measurements
- Extracted power switch resistance added
- **Ohmic losses dominant** (large  $\Delta I$  and  $R$ )


 
# Measurement results: complete converter

LX node voltage ( $f=50$  MHz,  $I=15$  mA)



- Supply decoupling effective (ringing caused by probe)
- ZVS functional, no body diode losses



## **Results for the second demonstrator**

# Improvements with respect to first demo

## ► Decrease ohmic series resistance

- Move  $C_{out}$  out of middle L
  - No eddy-current losses
  - L area minimized
- Decrease switch connection resistance
  - Fewer bond pads in parallel
  - Optimized switch placement
- No bond wires: double flip-chip
- Solder bumps (no gold stud bumps)

## ► Smaller active die

- One DC/DC converter, less I/O pads
- More routing space on passive die

## ► Smaller package

- HVQFN40


## ► Move to newer CMOS technology node

- 65-nm CMOS (load integration)
- $V_{in}=1.2$  V (65-nm CMOS limit)

# Optimize design for efficiency (Matlab™)

High-level modeling, design-space exploration



## Input

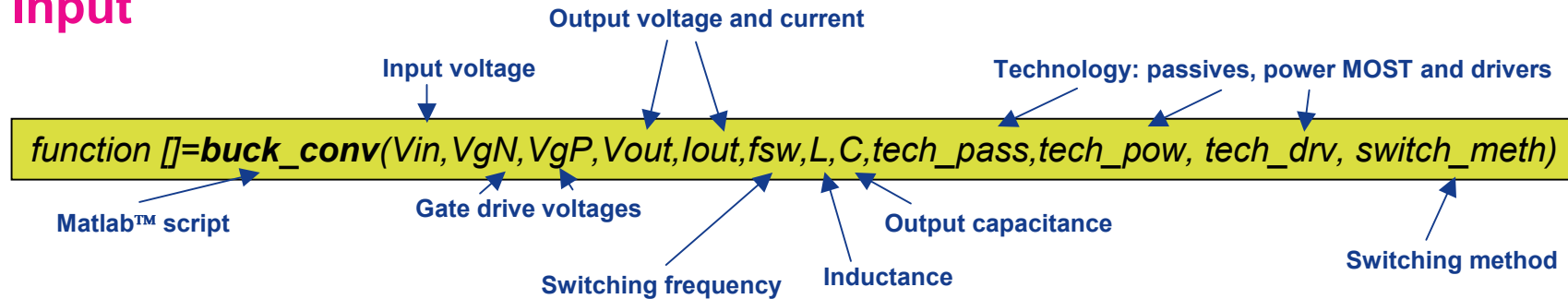
  
## Output

```
=====
=>Maximum efficiency theta=71.51%
=>Optimum switching frequency fsw=100MHz
=>Optimum inductor size Lind=16nH
=>NMOST size WN=6337.93um
=>PMOST size WP=6361.44um

=>Duty cycle D=0.333333
=>Output power Pout= 300mW
=>Total loss power Ploss=119.525mW
=>Power loss breakdown:
=>MOSFET conduction=39.7627mW (NMOS: 14.4935mW, PMOS: 25.2691mW)
=>MOSFET switching =39.7627mW (NMOS: 14.4935mW, PMOS: 25.2691mW)
=>Inductor losses =40mW
=====
```




# Design aspects

- ▶ No ZVS implementation
  - At  $V_{in}=1.2$  V ZVS implementation costs more efficiency than it saves
- ▶ Design optimization active die
  - $V_{in}=1.2$  V
  - $V_{out}=0.85$  V ( $\eta_{LDO}=71\%$ )
  - $I_{out}=100$  mA
  - $f=100$  MHz
  - Simulated efficiency: 84.9 %
  - No closed-loop control
- ▶ Design optimization passive die
  - $L=10$  nH ( $N=3$ ,  $w=50$   $\mu$ m,  $s=8$   $\mu$ m,  $area \approx 1$  mm<sup>2</sup>,  $R_{DC} \approx 0.4$   $\Omega$ ,  $R_{100\text{ MHz}} \approx 0.5\Omega$ )
  - $C_{out}=30$  nF (12.5 mV<sub>pp</sub> ripple)
  - $C_{in}=21$  nF (underneath active die and slightly beside it)
 
# Measurement result active die (stand-alone)

HVQFN14 package, external passives,  $L_{\text{tot}}=10 \text{ nH}$



Optimization point:

$$V_{\text{in}}=1.2 \text{ V}$$

$$V_{\text{out}}=0.85 \text{ V}$$




$$I_{\text{out}}=100 \text{ mA}$$

$$f=100 \text{ MHz}$$

$$\underline{\eta_{\text{meas}}=84.4\%}$$

$$\underline{\eta_{\text{sim}}=84.9\%}$$

# SiP construction (September 2008)

  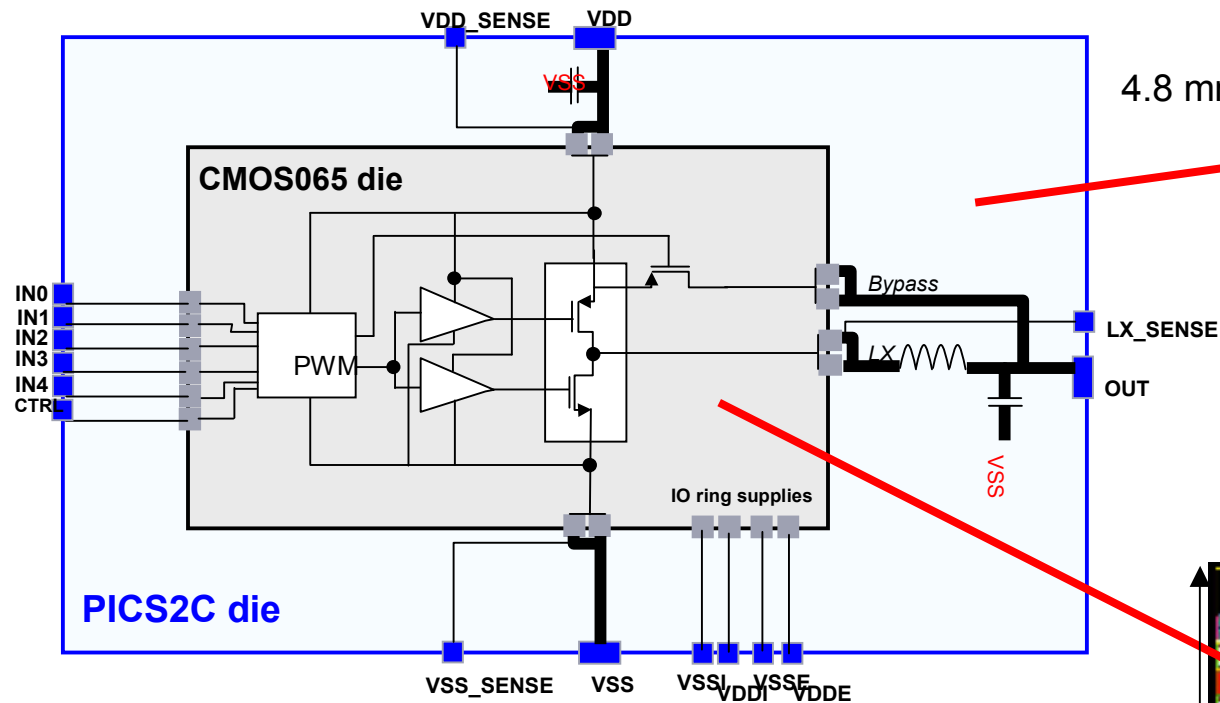



Expected peak efficiency of SiP: 82%




# SiP construction (September 2008)

## *Assembly pictures*



Passive wafer

  



Double flip-chip

 

Active-on-passive-die sandwich

  

HVQFN40

  



The background features a large yellow area on the right, a blue vertical bar on the left, and green triangular shapes at the top-left and bottom-left corners.

## **Conclusions and future outlook**

# Conclusions

- ▶ Two-die approach feasible for integrated DC/DC conversion
- ▶ No external components, higher efficiency than linear regulators
- ▶ Integration with load enables system integration of power management
- ▶ Future Outlook
  - Direct Li-ion battery connection
    - Cascoding at high frequencies with low-power ZVS implementation
  - Even higher capacitive densities
    - Even beyond 400 nF/mm<sup>2</sup>, ref. Fred Roozeboom et al

# Acknowledgements

- ▶ NXP Eindhoven, Netherlands
  - Stefan Menten, Ralf Pijper, Luuk Tiemeijer
- ▶ NXP Caen, France
  - Jorge Ferreira, Lionel Guiraud, Sebastien Iochem, Sophie Ledain, Dick Mapanao, Eric Pieraerts, Mickael Pommier
- ▶ Philips Research, Eindhoven
  - Derk Reefman
- ▶ INSA Lyon, France
  - Bruno Allard, Malal Bathily, Nicolas Degrenne, Jerome Saby

