



Integrated High Frequency Power Conversion using GaAs pHEMTs


T. Paul Chow, Mona Hella, Vipindas Pala, Han Peng
Rensselaer Polytechnic Institute,
Troy, NY

Power Converters for Portable Electronics

- Battery Capacity
- IC Voltage Scaling
- Miniaturization
- Integration

System Trends


Efficient POL Power Conversion

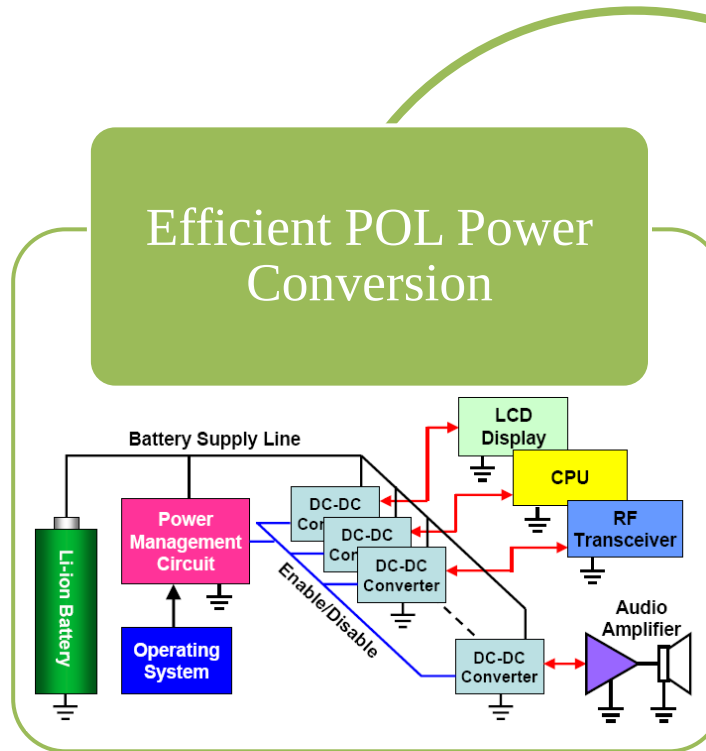

- Bandwidth +
- Efficiency +
- Footprint

SMPS

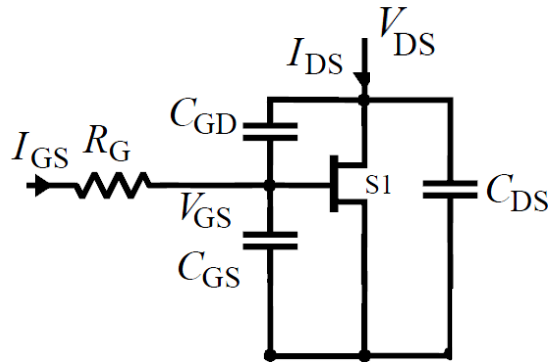Switch Power Losses for Hard Switched Converters



- Gate capacitance charging loss and output switching loss limit the switch gate width
- Product of R_{ON} and Q_G still determines minimum switch power loss

$$P_{CON} = I_{DS}^2 R_{DS,ON}$$

$$P_{SW} = \frac{1}{2} V_{Batt} I_{DS} (t_{ON} + t_{OFF}) \times Freq$$

$$\approx V_{Batt} I_{DS} \frac{Q_G}{I_G} Freq$$

$$P_{GD} = Q_G V_{GS,ON} Freq$$

$$P_{OSS} = \frac{1}{2} Q_{DS1} V_{Batt} Freq$$

$$P_{Min} = 2 \sqrt{\bar{I}_L^2 R_{ON,SP} Df \left(\frac{\bar{I}_L}{I_G} Q_{G,SP} V_{Batt} + Q_{G,SP} V_{DD} + \frac{1}{2} Q_{DS,SP} V_{Batt} \right)}$$

$$\Rightarrow FOM = R_{ON} \times Q_G$$

FOM : Low-Voltage High Frequency Switches

$$FOM = R_{ON} \times Q_G$$

$$(R_{CH} + R_D + R_{EXT}) * (Q_{CH} + Q_D) = \left(R_{EXT} + \frac{L_{CH}}{W\mu_{CH}Q_{CH}} + \frac{L_D}{W\mu_DQ_D} \right) \times (Q_{CH}L_{CH}W + Q_DL_DW)$$



Channel Scaling to improve these

- R_{EXT} : Contact, Access, Metallization resistance become critical

Wide Bandgap Advantage limited to these two terms only

Comparison of Device Technologies



- HEMT : Higher mobility, NMOS : Smaller access resistance
- GaAs : Higher channel and drift mobility compared to GaN, Si
- GaN : Higher voltage supporting capability, but for low voltages, the drift region contribution is small, so other resistance components dominate

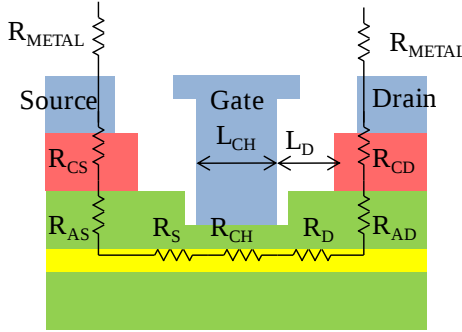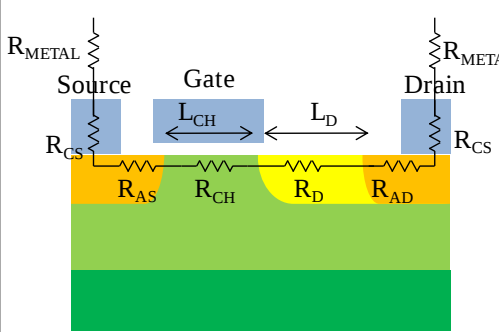Device	HEMT		Lateral NMOS
Structure			
Material	AlGaAs/InGaAs/ AlGaAs	GaN	Silicon
μ_{CH} (cm ² V ⁻¹ s ⁻¹)	6000	1500	500
μ_D (cm ² V ⁻¹ s ⁻¹)	6000	1500	1200
$E_{C,Lat} = BV / L_D$	25V/ μ m	150V/ μ m	15V/ μ m
Contact + Access Res.	0.2 Ω .mm	0.2 Ω .mm	0.1 Ω .mm

Power Device for High Frequency Switching


- Silicon approach :
 - Migrate to Nanometer gate lengths to reduce capacitance
 - Below 5V : Cascoded nm-CMOS
 - Below 20V : LDD NMOS
 - Above 20-30V: LDMOS
- Our approach : Schottky gated AlGaAs/InGaAs/AlGaAs pHEMTs on GaAs substrates
 - Bandgap + Mobility Advantage
 - Low FOM without small feature size processes

First Order Comparison of FOM

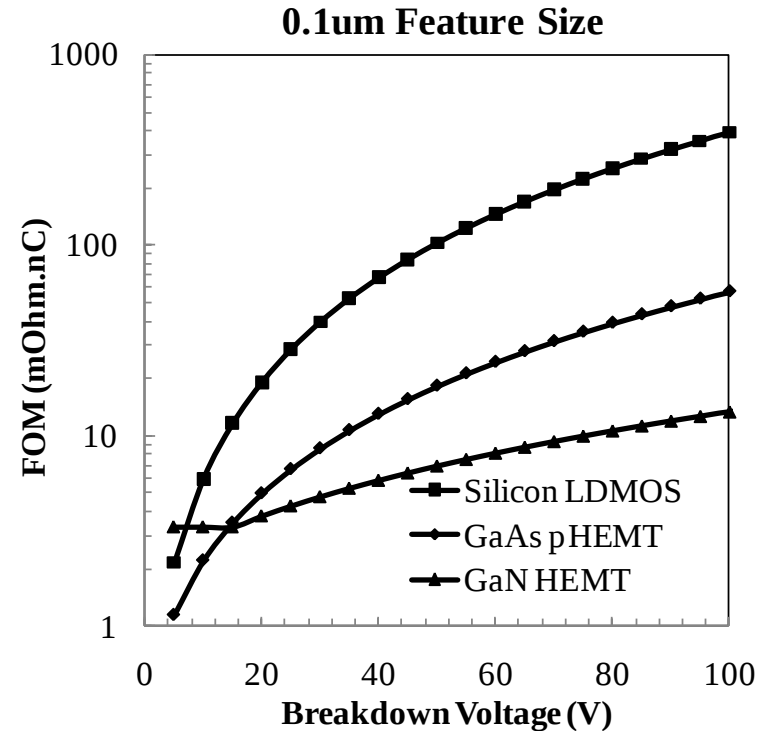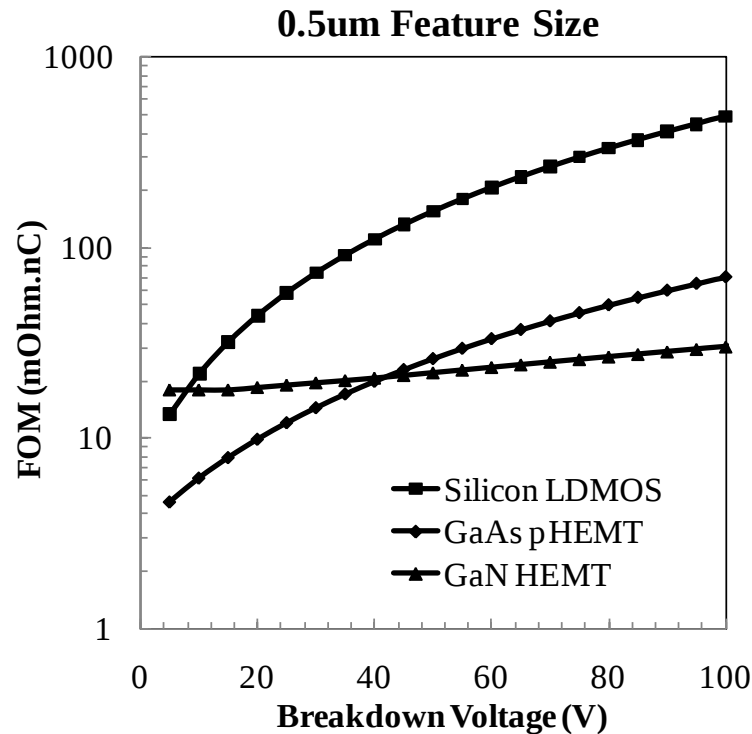



- Mobility and Bandgap advantage for GaAs pHEMTs
- Best for under 20V

0.5 μ m E-Mode GaAs pHEMT Switch

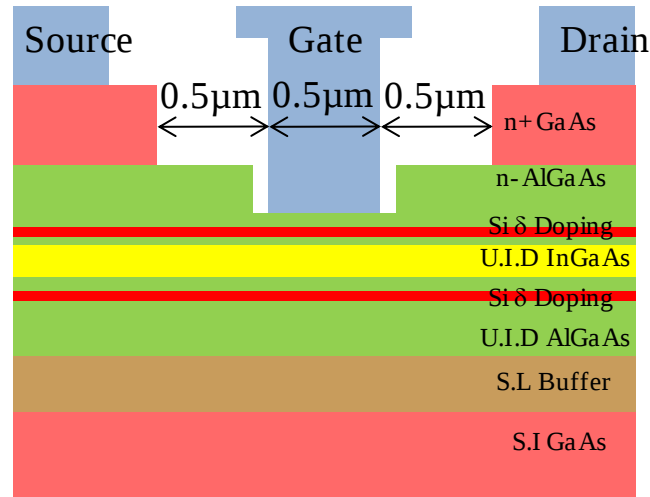


- pHEMTs ubiquitous in RF MMICs
- Mature Process technology
- Double recessed commercially available E-pHEMT process (TriQuint TQPED)
 - For RF switches and front ends : Not-optimized for power switching
- InGaAs 2DEG Channel
- Threshold Voltage = +0.36V, Maximum $V_{G,ON}$ =0.8V
- Semi-insulating substrate : High side operation

Device Characteristics

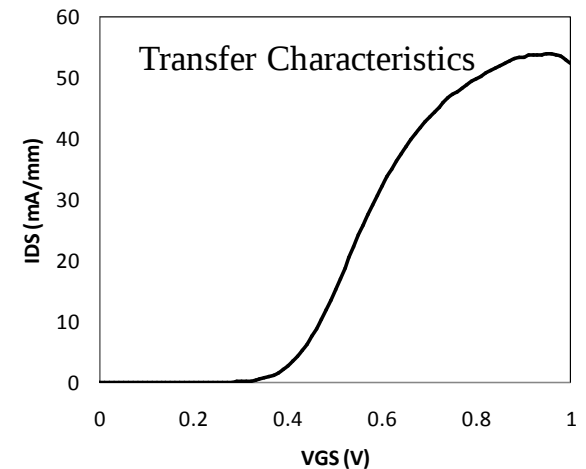
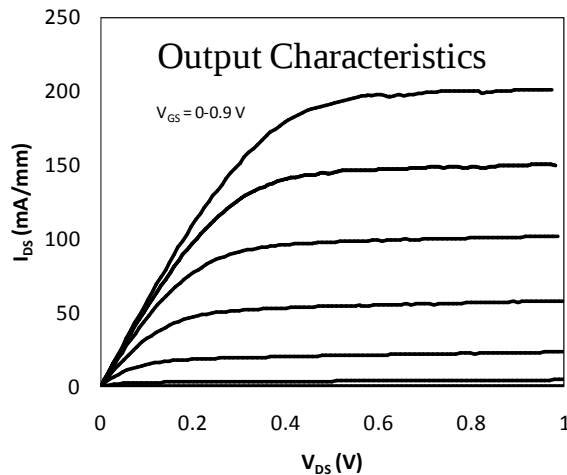


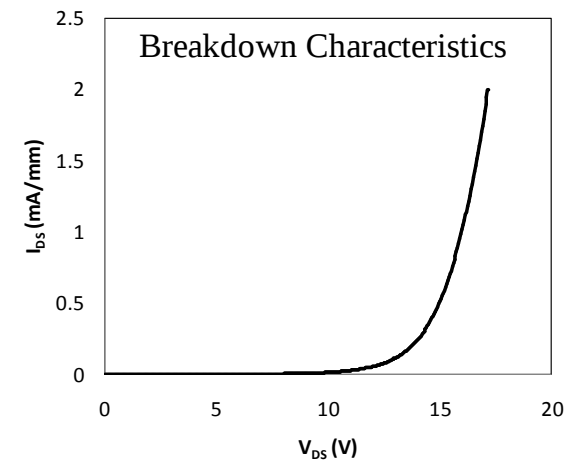- Threshold Voltage = +0.36V, Maximum $V_{G,ON}=0.8\text{V}$
 - Low Leakage at $V_G=0\text{V}$, $V_{DS}=5\text{V}$: 20nA/mm
 - No negative voltage generator required in standby mode
 - $P_{ON} / P_{OFF} = 10^5$
- Breakdown Voltage 11V (at $V_{GS}=0\text{V}$) (10uA/mm)
 - Limited by leakage
 - Avalanche breakdown only at ~25-30V



Intrinsic FET Characteristics


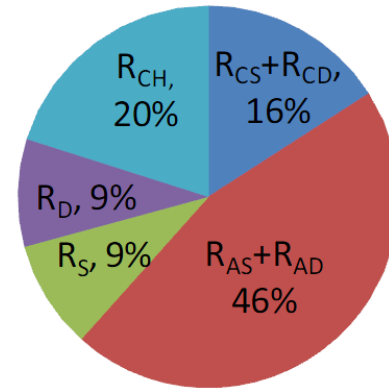
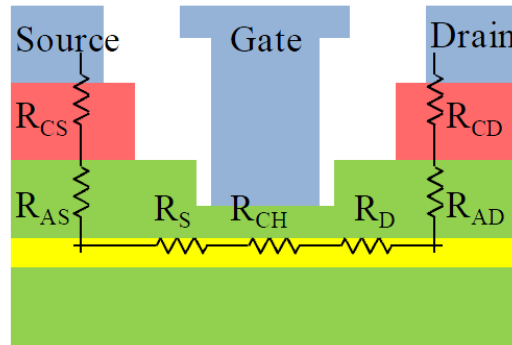
TLM Measurements : Single Finger FET (100 μ m)



- Intrinsic Specific R_{ON} (Measured on single Finger 100 μ m wide FET= 1.48 Ohm.mm)
 - Dominated by Contact and Access
 - Intrinsic Specific R_{ON} (Measured on single Finger 100 μ m wide FET= 1.48 Ohm.mm)
- Specific Gate Charge (From Capacitance Models) : 3.1pC/mm
- Intrinsic FOM : 4.6 m Ω .nC


Metallization and Packaging Effects

Three Level Interconnect + Flip Chip

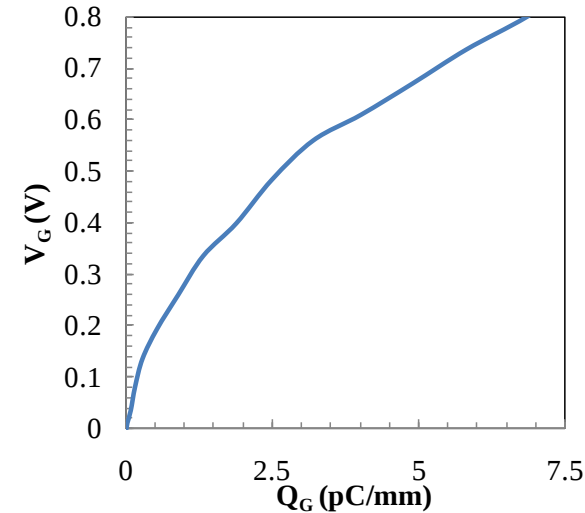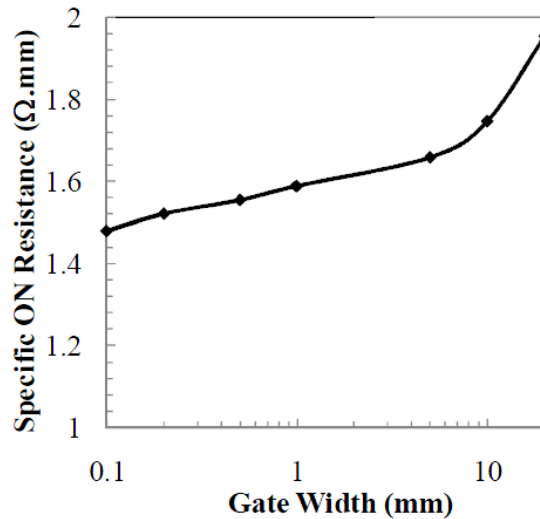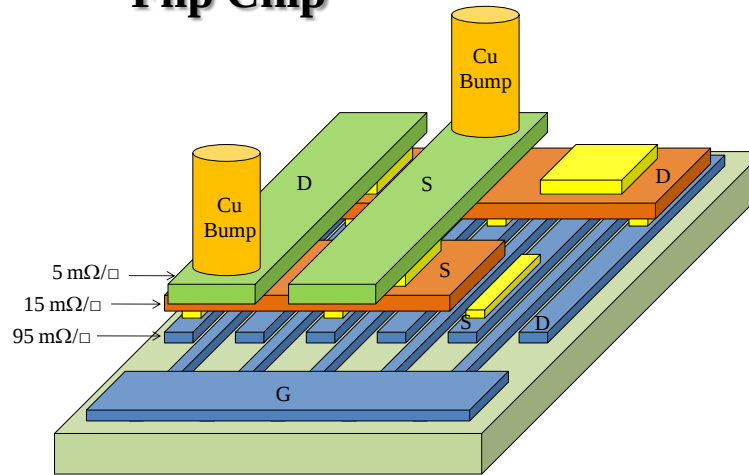

- Metallization resistance further degrades resistance for multi-fingered devices
- 10mm gate width: $R_{ON} = 1.75\text{m}\Omega$, $Q_G = 70\text{pC}$
- FOM=12 mΩ.nC
 - Compared to 27.5 mΩ.nC for Silicon 0.5um, 11V LDMOS (GWS24N07)

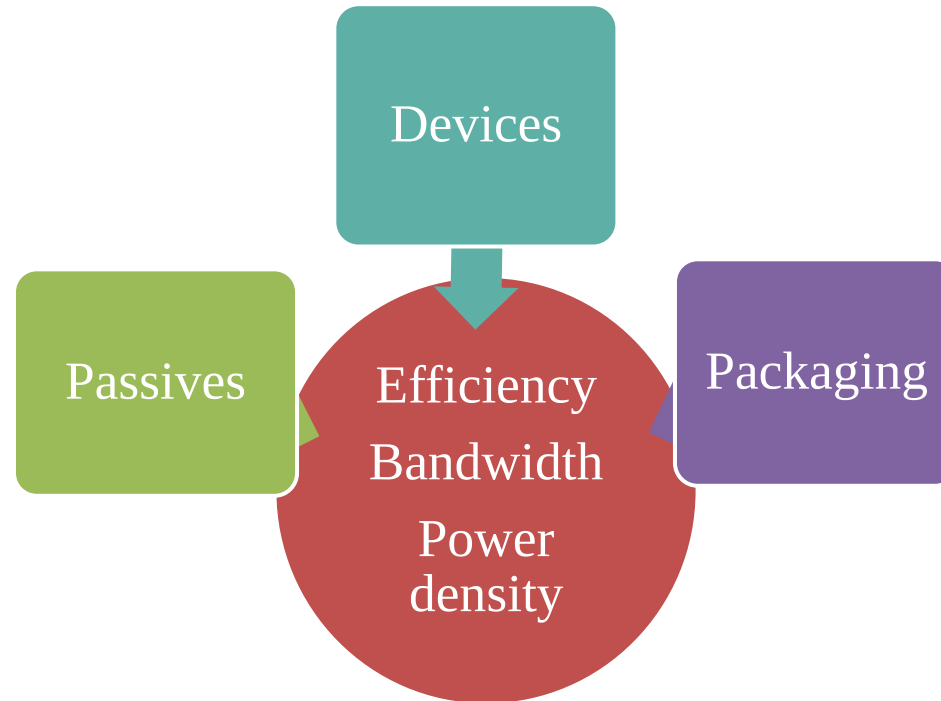
Key Technologies for High Frequency Power Conversion



Device is only part of the story !!



Passive Technology : Thick Cu Inductors on GaAs

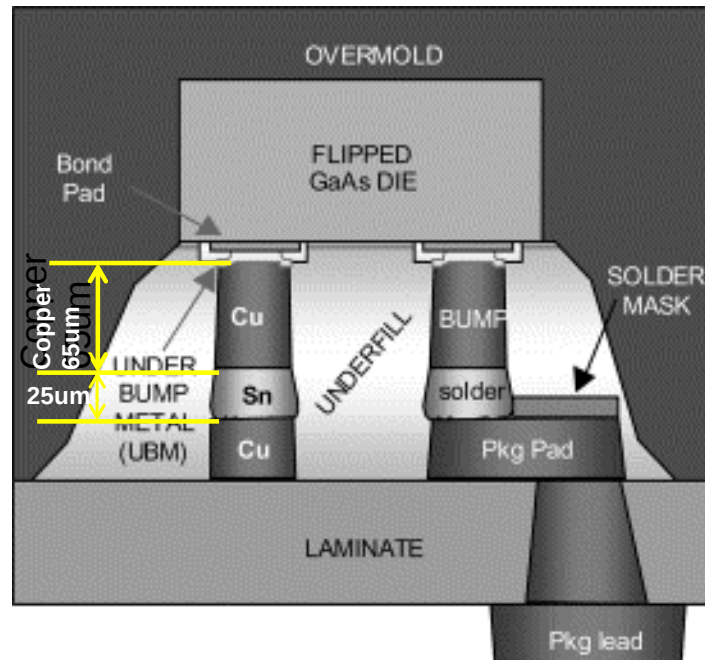- Air core inductors for switching above 100 MHz
- Thick Cu (65 μ m tall) spirals with spacing of 30-45 μ m
- Solder bumps on top, flip chipped to laminate
- Bump height (25 μ m) prevents Eddy current losses to laminate interconnect





Passives for DC-DC Conversion

- Tall Cu : Low DCR, High Q

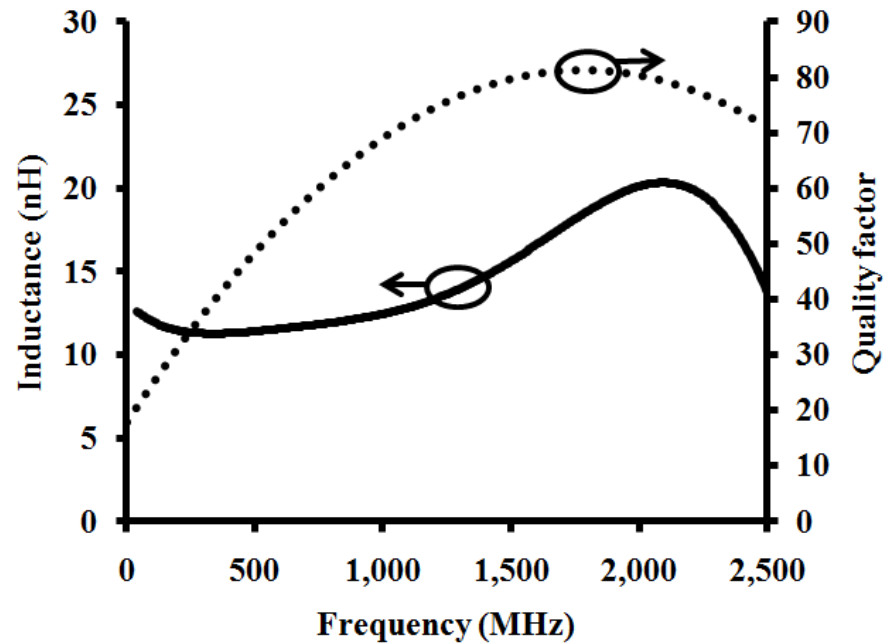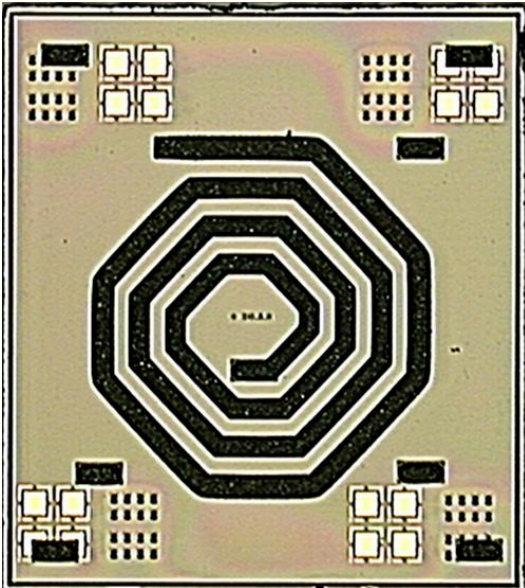

Inductor Coupling for Multiphase Converters

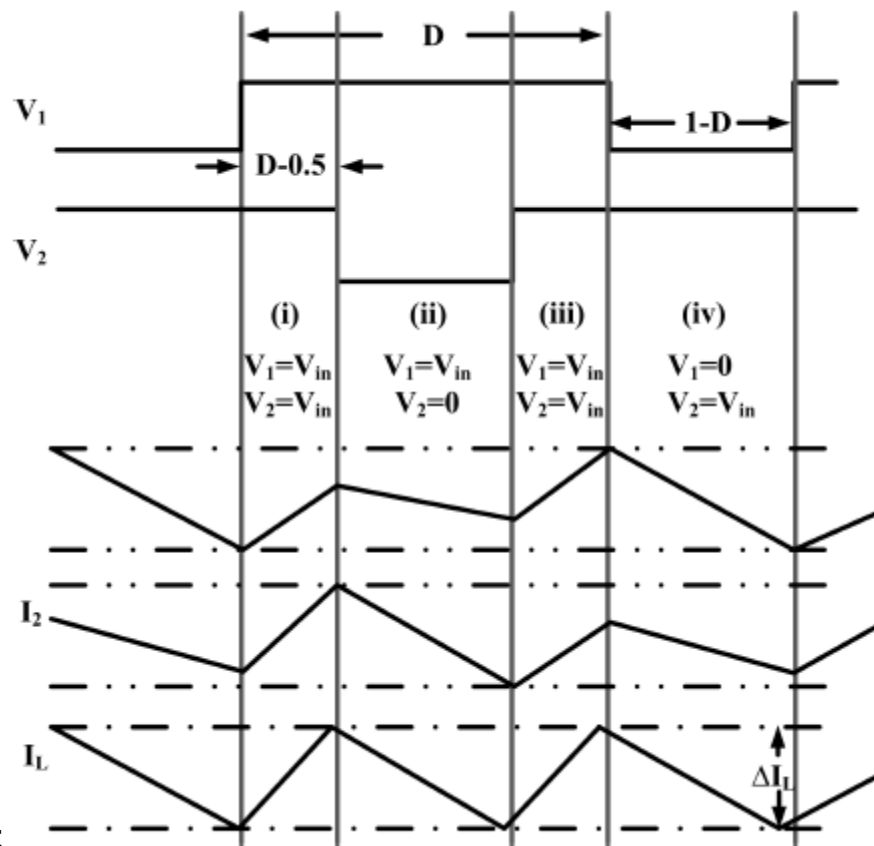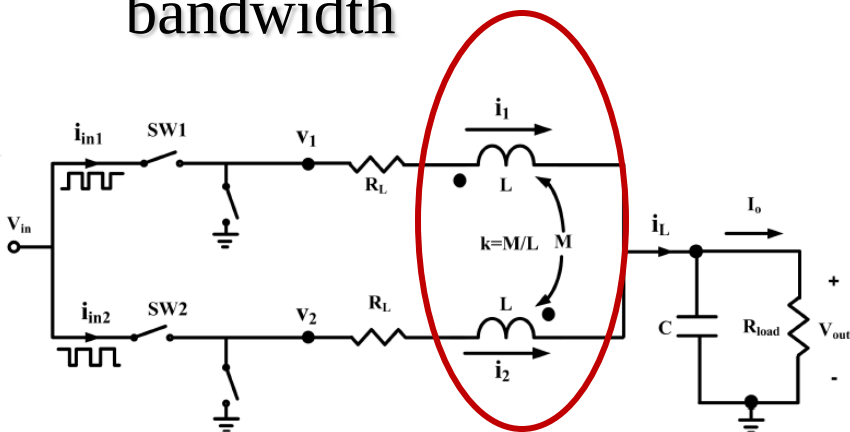- Can use smaller inductors for same ripple : improved efficiency, bandwidth




Optimal Coupling Factor


$$k_{opt} = \begin{cases} \frac{1-D}{D} \left(\sqrt{1 - \left(\frac{D}{1-D} \right)^2} - 1 \right) & \text{for } D \leq 0.5 \\ \frac{D}{1-D} \left(\sqrt{1 - \left(\frac{1-D}{D} \right)^2} - 1 \right) & \text{for } D > 0.5 \end{cases}$$

Coupling : Ripple and Bandwidth enhancement

Current Ripple Reduction with Duty Ratio

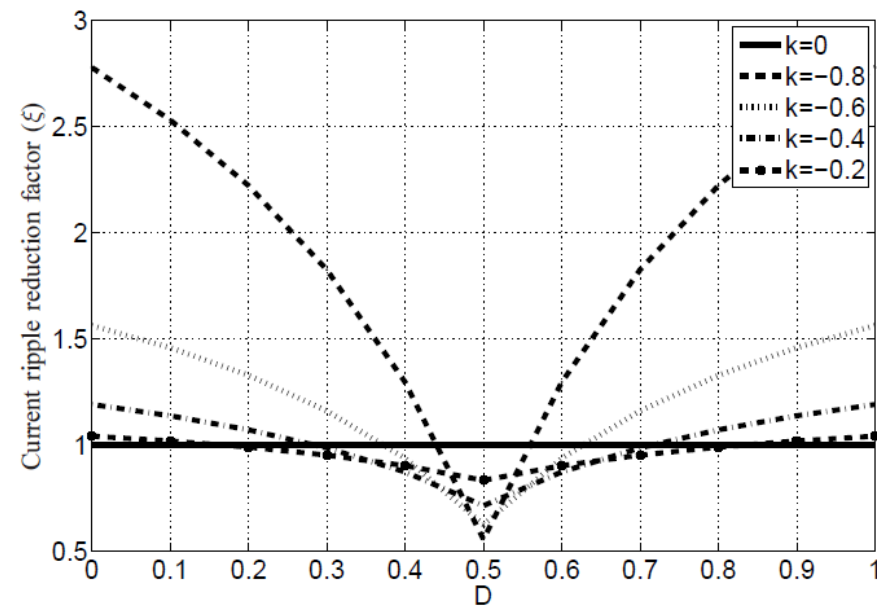

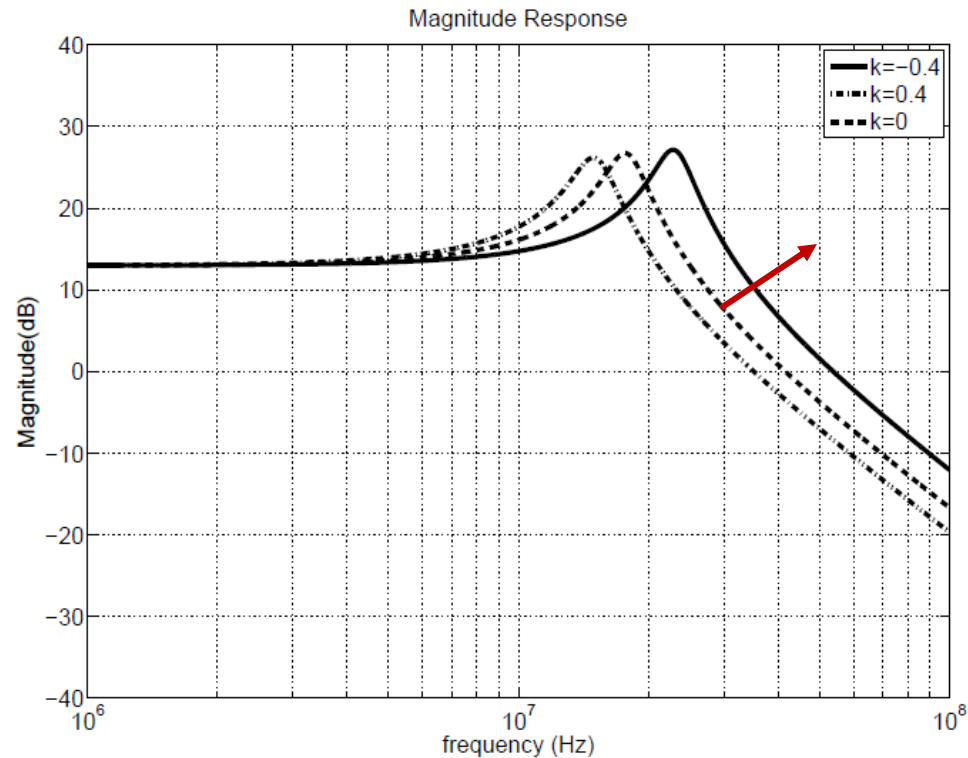Bandwidth enhancement with negatively coupled spirals




Coupling : Ripple and Bandwidth enhancement

- Coupled Thick Cu Inductors on GaAs





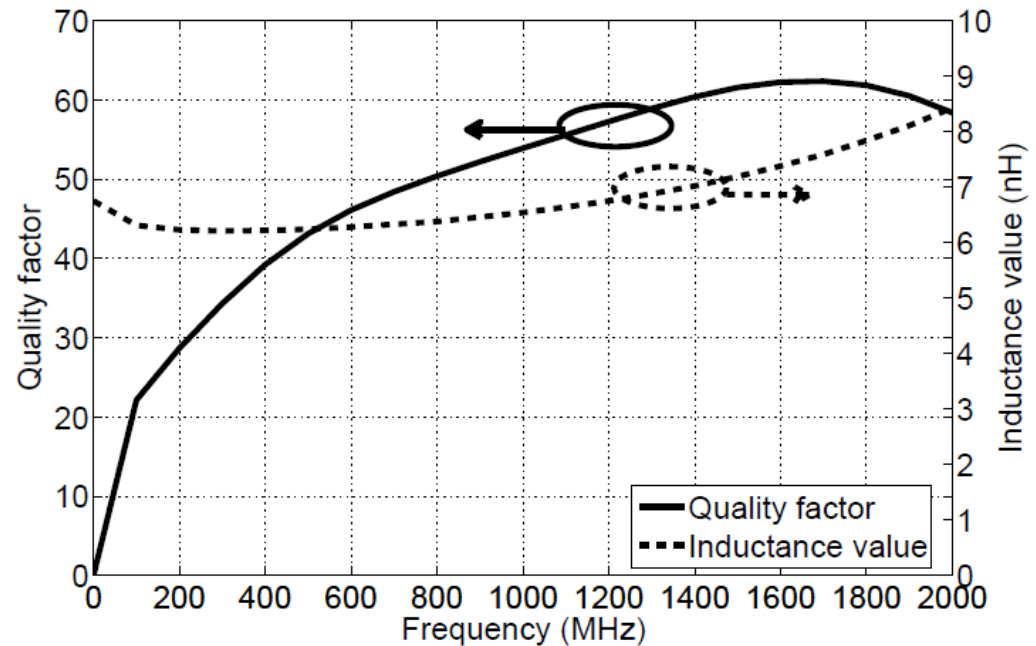Coupling Factor : -0.4 for
65% conversion Ratio





Packaging : Multi-chip Module

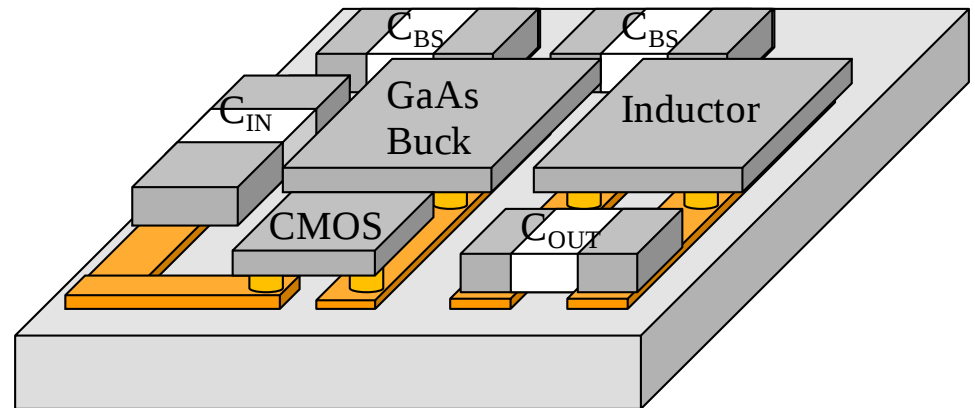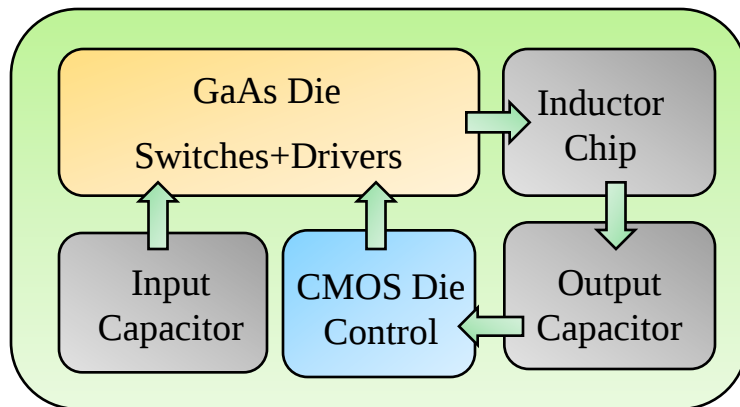- Use best technology for each component :
 - GaAs pHEMT– High Frequency Switch + Drivers
 - Inductor Chip– Thick Cu on bare semi-insulating GaAs / SMD
 - CMOS – Control and Logic





Flip Chip Bonding

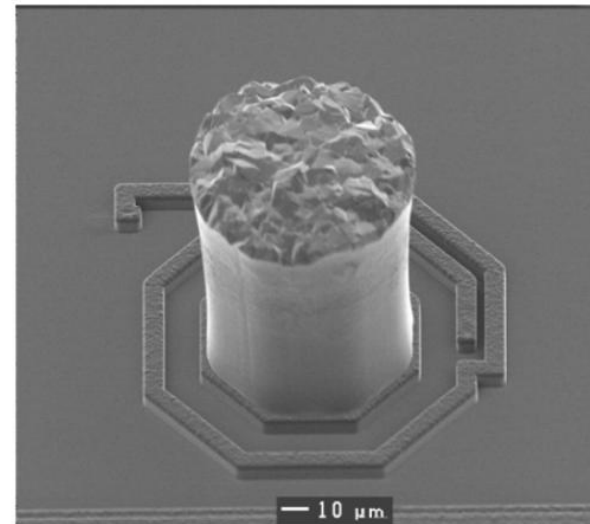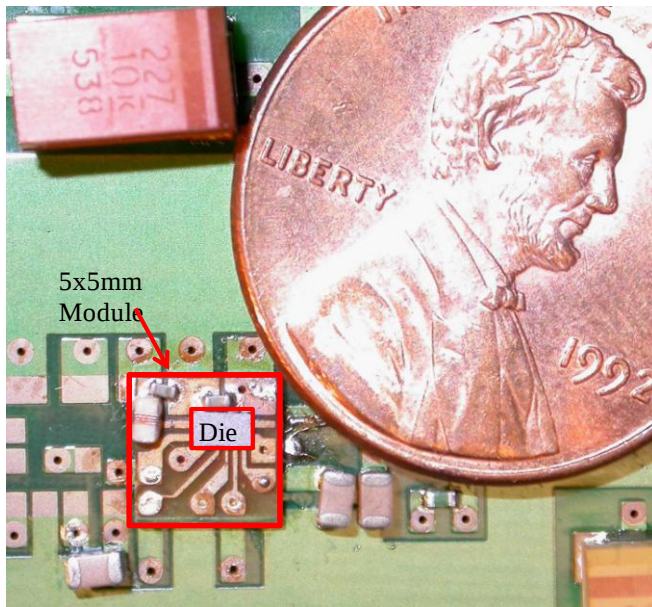- Solder on Copper bumps
- Can place bumps on active FET area : spreading resistance reduced
- No bondwire parasitics : lower wire inductance, resistance
- Eliminates the need for ON-chip de-coupling
- High throughput, low assembly cost




Design Example A

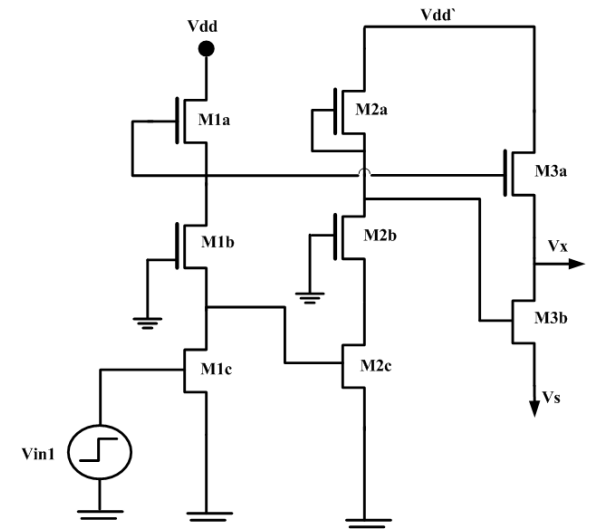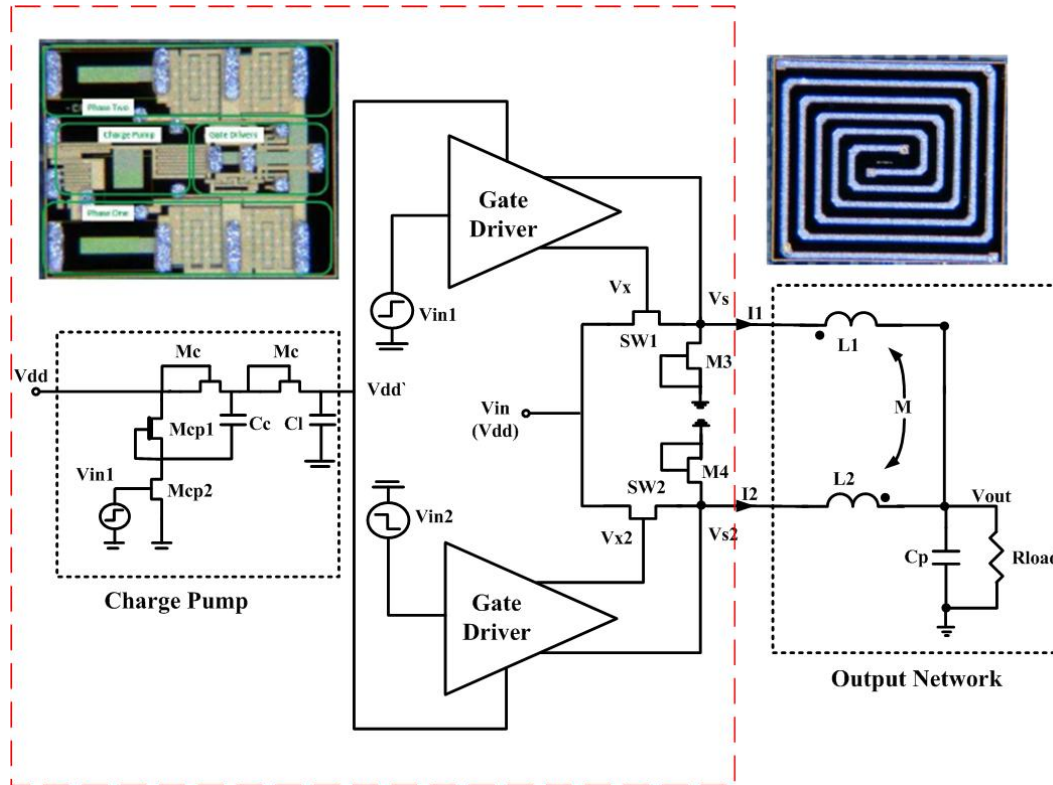- 150 MHz 2 Phase Interleaved Buck with Coupled Inductors
- Switches + Drivers on GaAs pHEMT
- 4.5V Input : 1.5-3.3V Output, 0.5A per Phase





Measurements

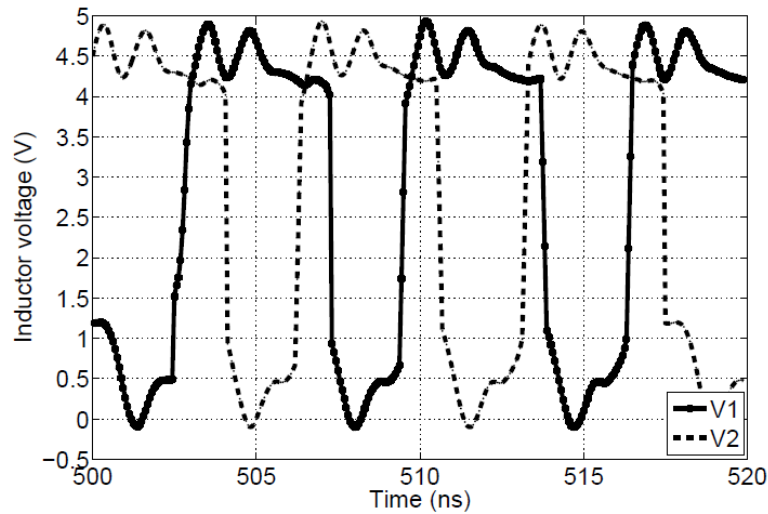


MEASURED PERFORMANCE SUMMARY

Technology	0.5 μ m GaAs p-HEMT
Circuit Area	4.22mm ²
Inductor Area	5.94mm ²
Inductance Value	8.77 nH
Coupling Factor	0.46
Q at 150MHz	26
Input Voltage	4.5 V
Output Voltage	3.3 V
Output Current	1 A
Switching Frequency	150 MHz
Peak Efficiency	84%
Voltage Ripple	116 mV

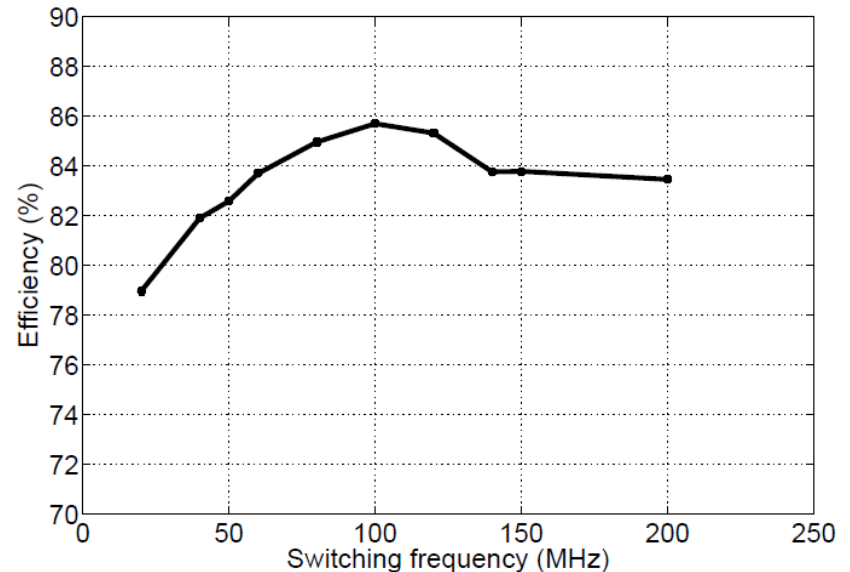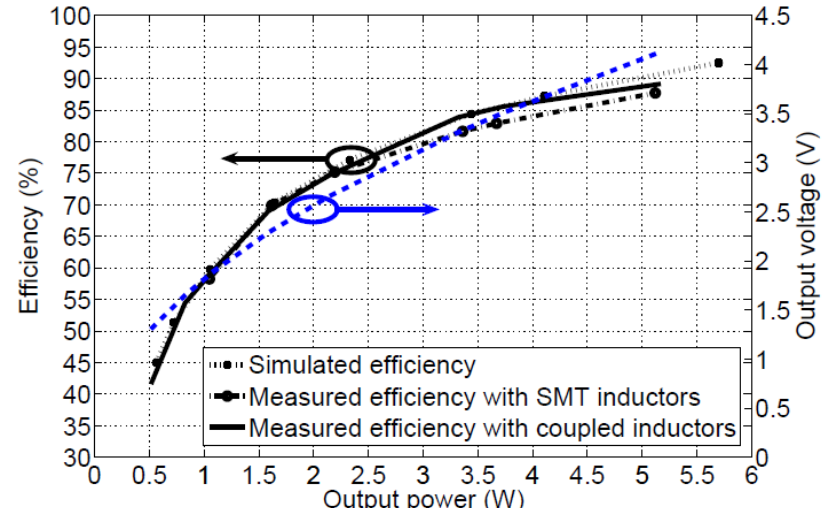

Design Example B

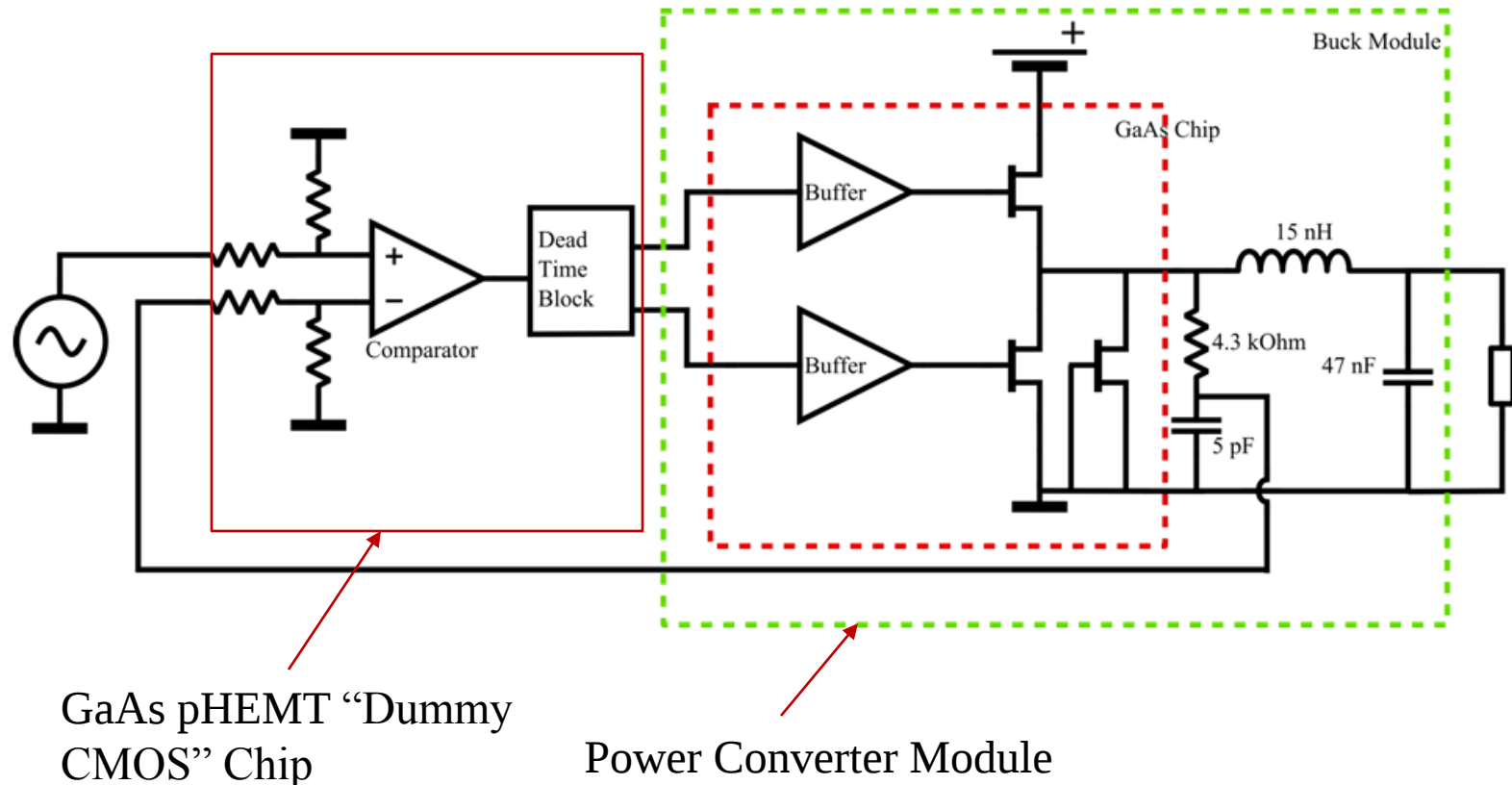
- ~100MHz DC-DC Converter for Power Amplifiers
- Single Phase , GaAs pHEMT Output Stage + 0402 Air Core inductors from Coilcraft




Design Example B : GaAs Output Stage

- Synchronous Buck Converter
- High Side Bootstrapped driver for N-type device
- 100MHz switching frequency at full power (switching frequency varies with load)

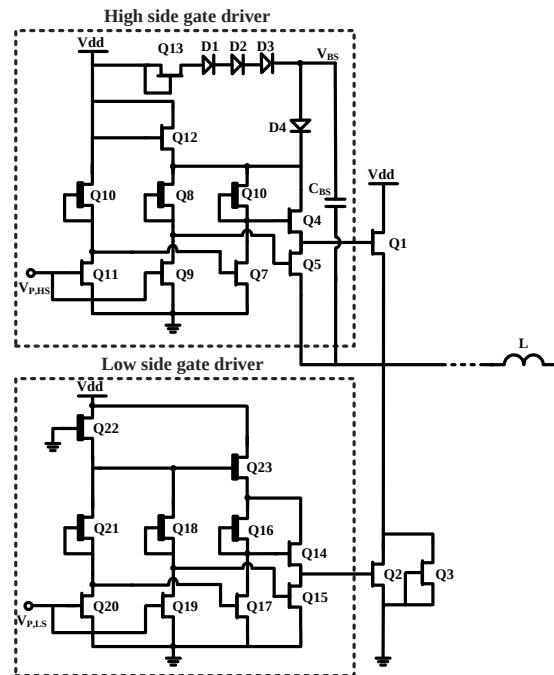GaAs Buck Circuit + Bootstrapped Gate Driver




Chip Photograph
Single Phase Used

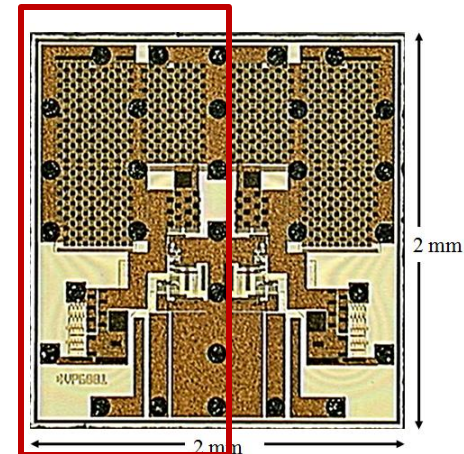


Measurements

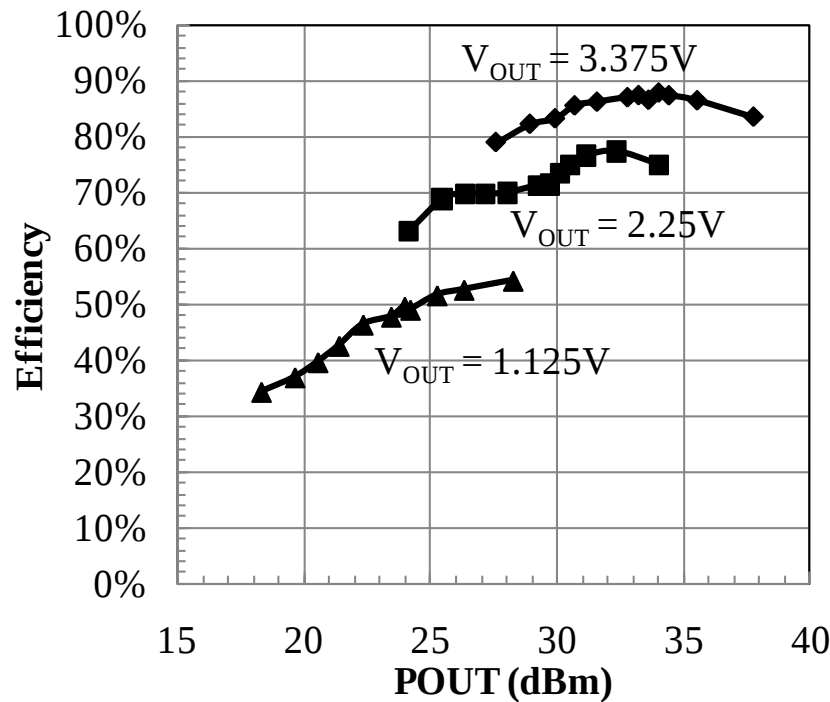- Efficiency : 88% at 4.5V input, 3.375V output, 1A
- Efficiency degradation at low power due to GaAs gate driver power loss





Simulated Power Loss Components

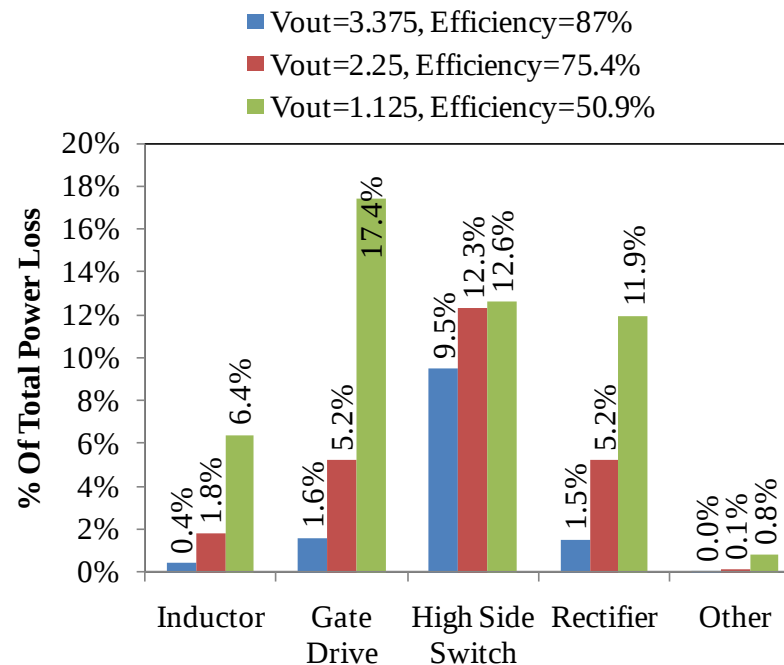
- At low power, GaAs gate driver loss degrades efficiency considerably
- GaAs has no PMOS like device, hard switched drivers are lossier than CMOS



Transient Response and Bandwidth

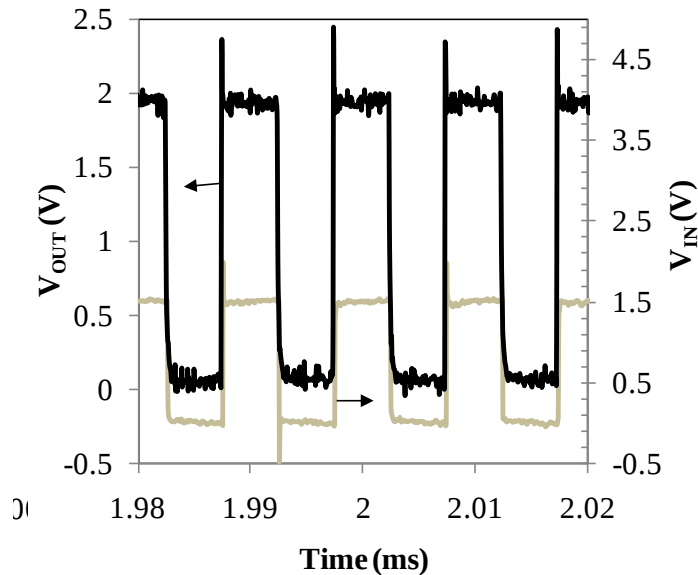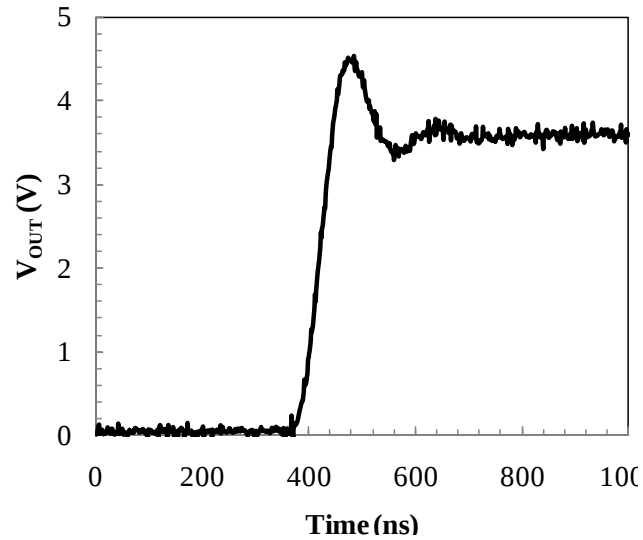

Amplitude Response

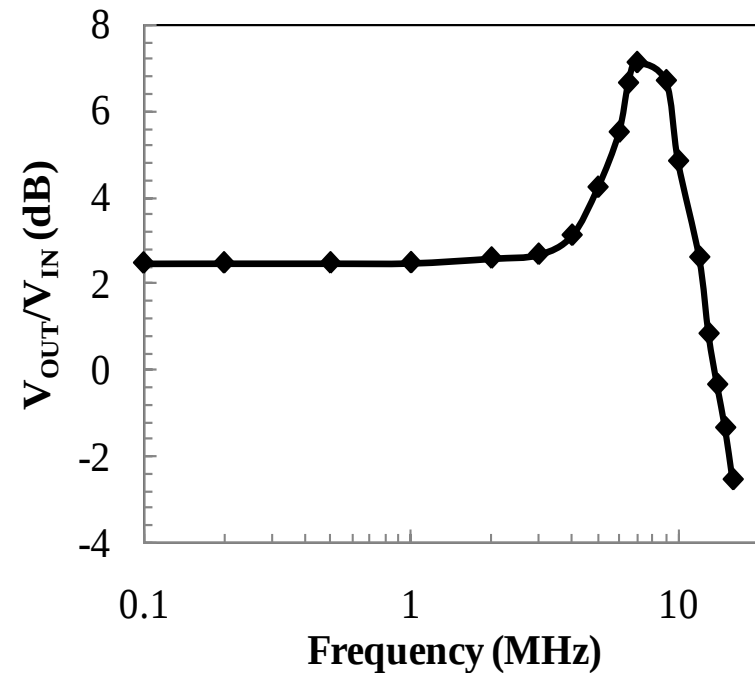

Summary

- GaAs Technology platform for high frequency switching
 - Device :
 - E-pHEMTs with superior FOM, Breakdown and Ruggedness
 - 3 Layer Interconnect
 - Thick Cu Air core planar inductors for integration
 - Passive
 - Thick Cu high Q air core planar inductors on GaAs
 - Coupling to achieve bandwidth + efficiency improvement
 - Packaging
 - Flip Chip Interconnects : Low parasitic inductances, reduced de-coupling, integration
 - Multi-chip modules : pHEMT Power + GaAs Passive + CMOS Control
- Design Examples
 - 150MHz interleaved Converter with coupled inductors, 84% Efficient
 - 100 MHz Single Phase, 1A output – 88% Efficient, 3dB bandwidth – 14.5 MHz

Future Work

- Output Stage :
 - 0.25 μ m GaAs E-pHEMT process : Gate Charge Advantage
 - Resonant drivers : Reduce driver loss, improve switching time and thus reduce switching loss
- Adding CMOS based controller for PA power supply modulation up to 10-15 MHz
- E-Mode power pHEMT processes for higher voltages : 20V, 30V rated devices



chowt@rpi.edu
palav@rpi.edu
hellam@ecse.rpi.edu
pengh2@rpi.edu