
Gate-Charge Recovery for Light-Load Efficiency Improvement in High-Frequency DC-DC Converters

O. Trescases, Y. Wen
Energy Systems Group
Department of Electrical and Computer Engineering
University of Toronto, Canada
www.ele.utoronto.ca/~ot


Oct. 14, 2010



Outline


- Motivation: light-load efficiency in mobile devices
- Existing gate-drive power optimization techniques (fixed/variable frequency)
- Proposed gate charge recycling using output capacitor as the storage element
- Precision closed-loop calibration of gate driver timing for charge recycling in 0.13 μm CMOS
- Conclusion

SMPS Landscape

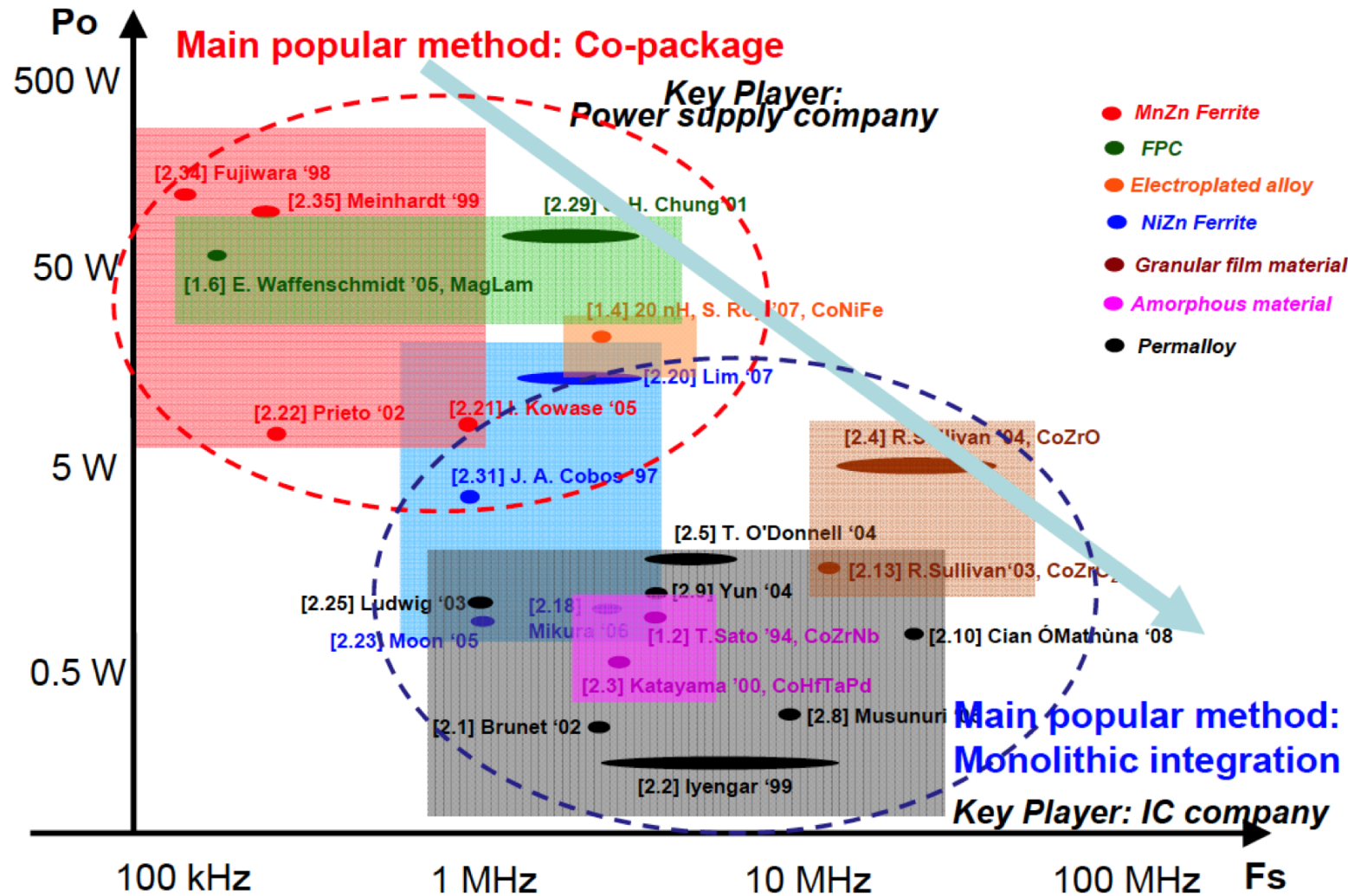


Light-Load Efficiency of 20 MHz Buck Converter

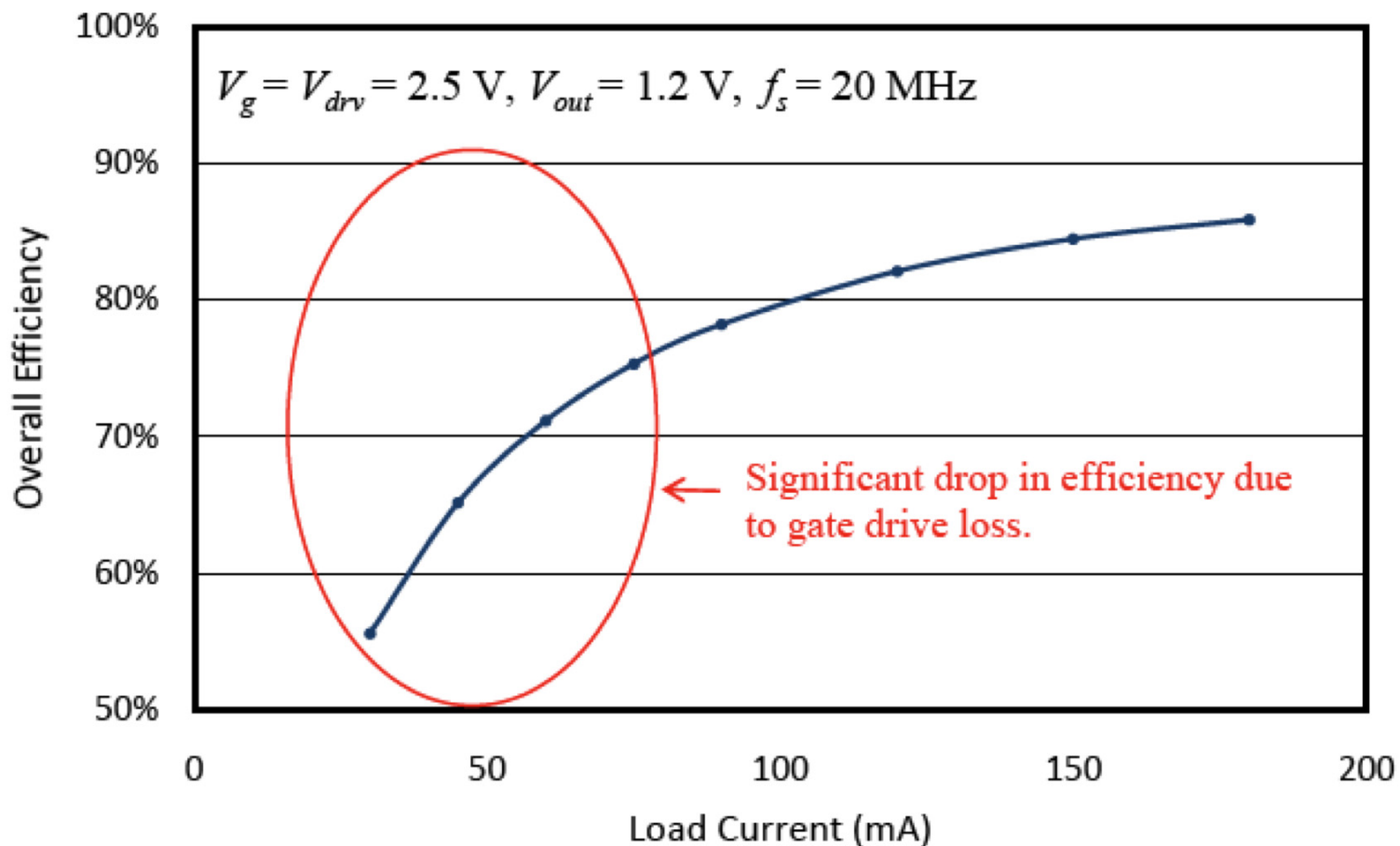- Simulated light-load efficiency of 20 MHz buck converter designed in 0.13 μm CMOS technology. Significant efficiency drop below 100 mA.



Gate Drive Loss Limits Converter Efficiency

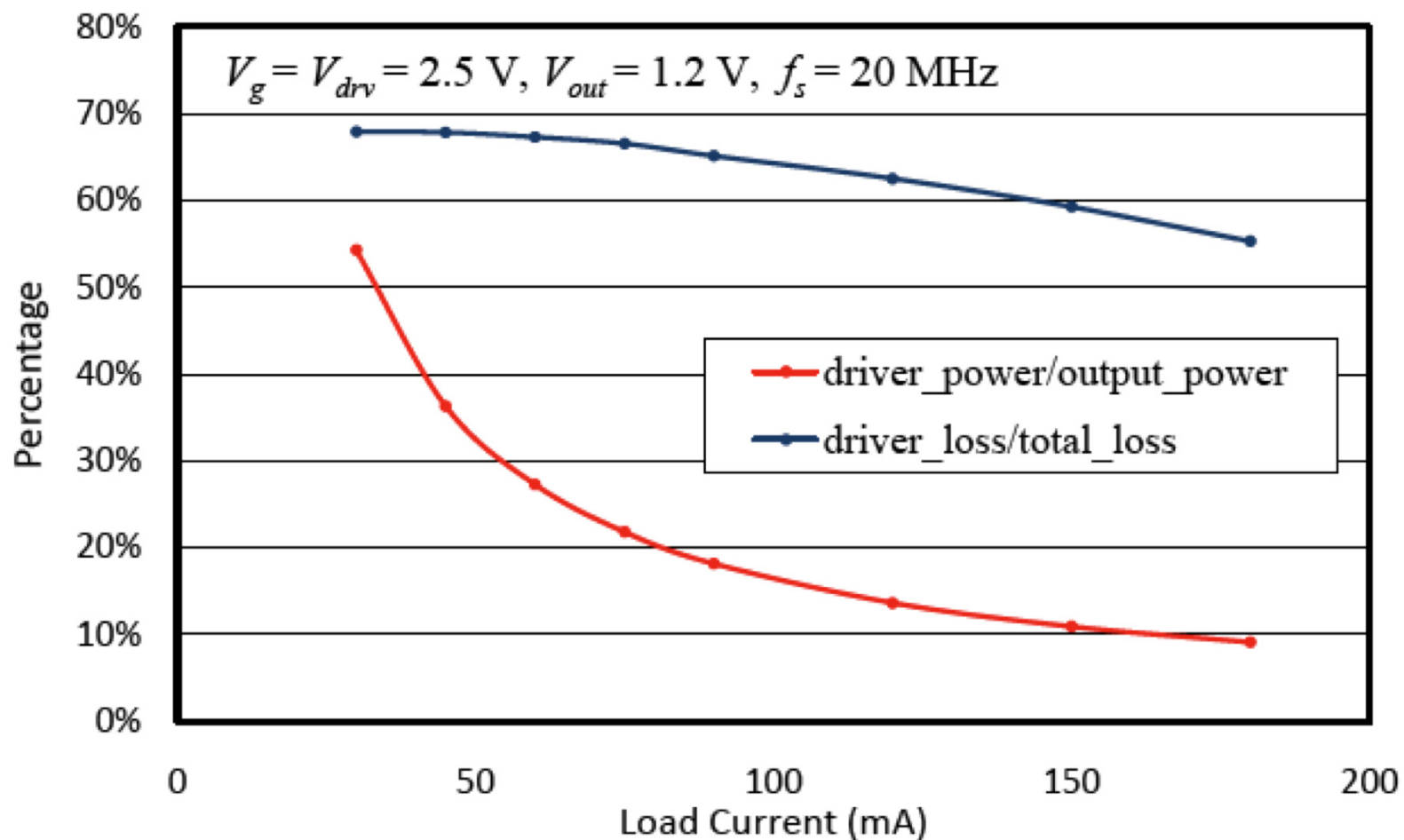
- At light load, > 60% of the total loss is gate drive loss!



Light Load Efficiency Improvement Techniques

- Light-load efficiency improvement techniques are divided into 2 categories
- Certain applications do not permit variable frequency operation (EMI)


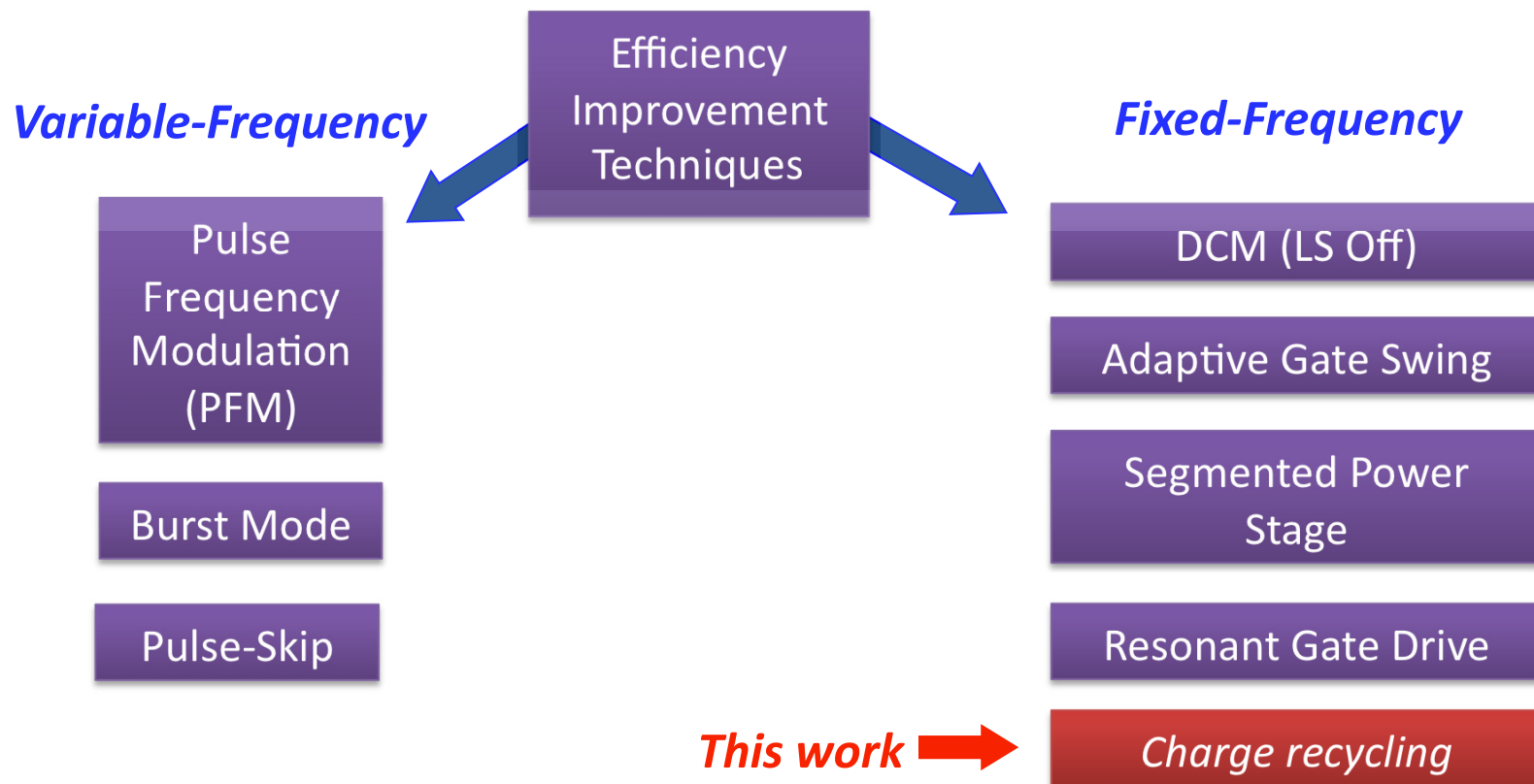
$$P_{gate} = Q_{gate} \cdot V_{dr} \cdot f_s$$



Adaptive Gate Swing (AGS)

- Adaptive gate charge control using RC timing circuit:


$$V_{g,opt} = \sqrt{\frac{D\Delta i_L^2}{3kC_g V_{in} f_s}} + |V_{th}|$$

 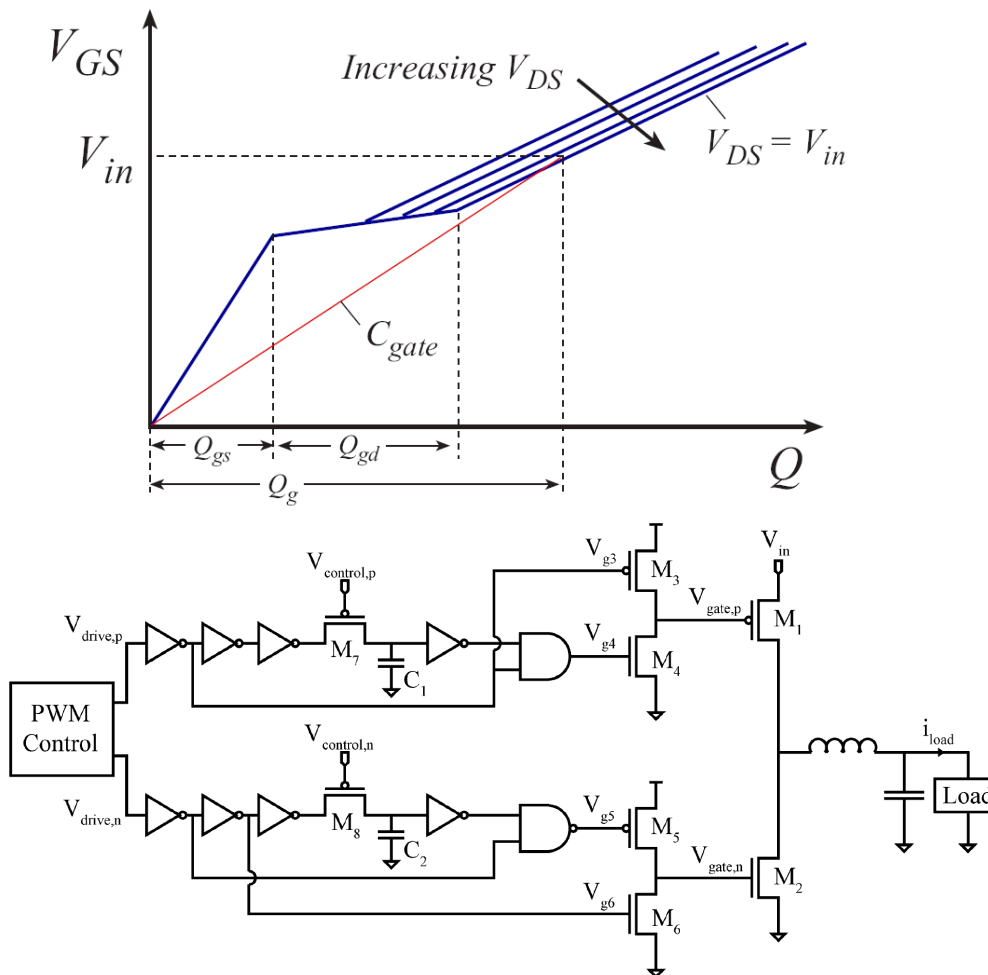


Source: Mulligan et. Al. IEEE Power Electronic Letters 2005

Segmented Power Stage (SPS)

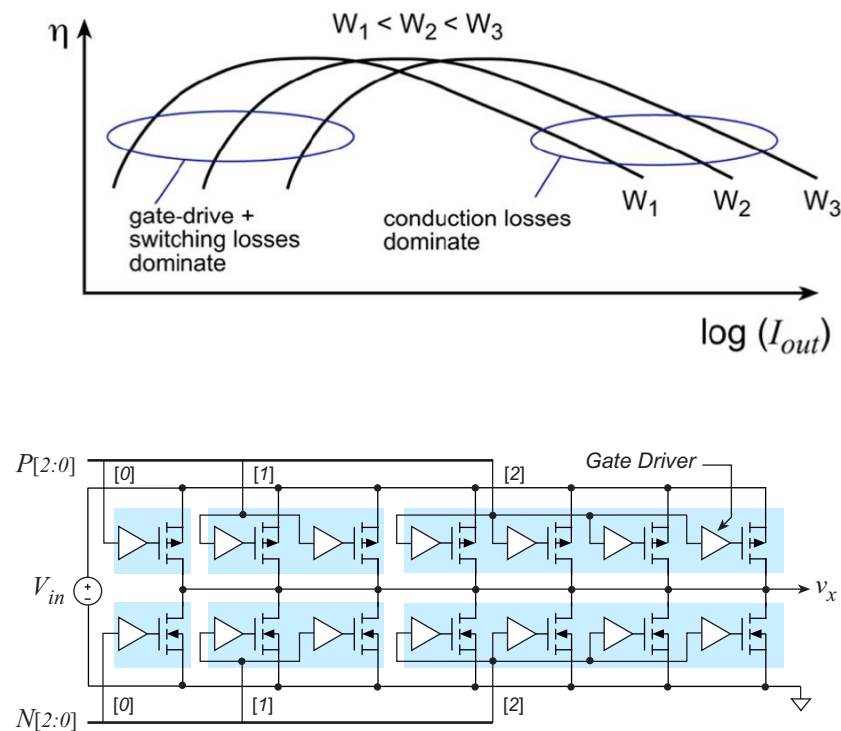- 3-bit, binary weighted segmentation at 4 MHz:





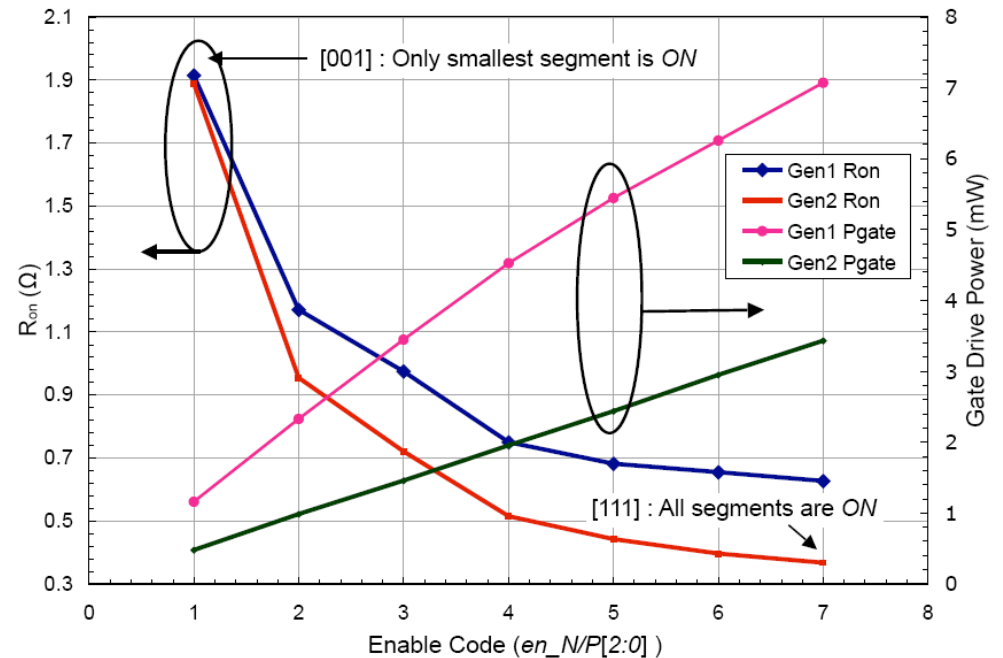- P_{gate} is reduced by 6.3x
- $R_{on,N}$ increased by 2.4x, $R_{on,P}$ increased by 3.1x




Segmented Power Stage (SPS)

  - Experimental efficiency for 3-bit, binary weighted segmentation at 4 MHz






Dynamic Segment Control in Closed-Loop

 


Fuji Electric CSM

 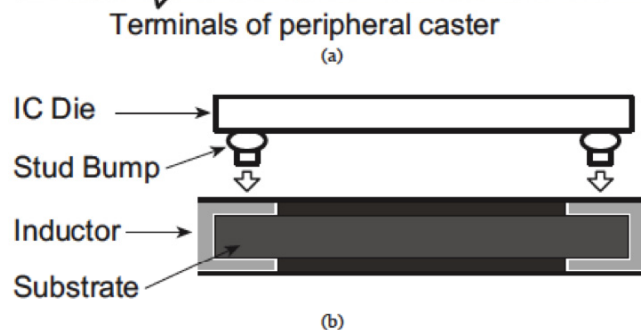 - Chip scale module for HF DC-DC converter



System Power Management with SPS



- Application in digital class-D audio:

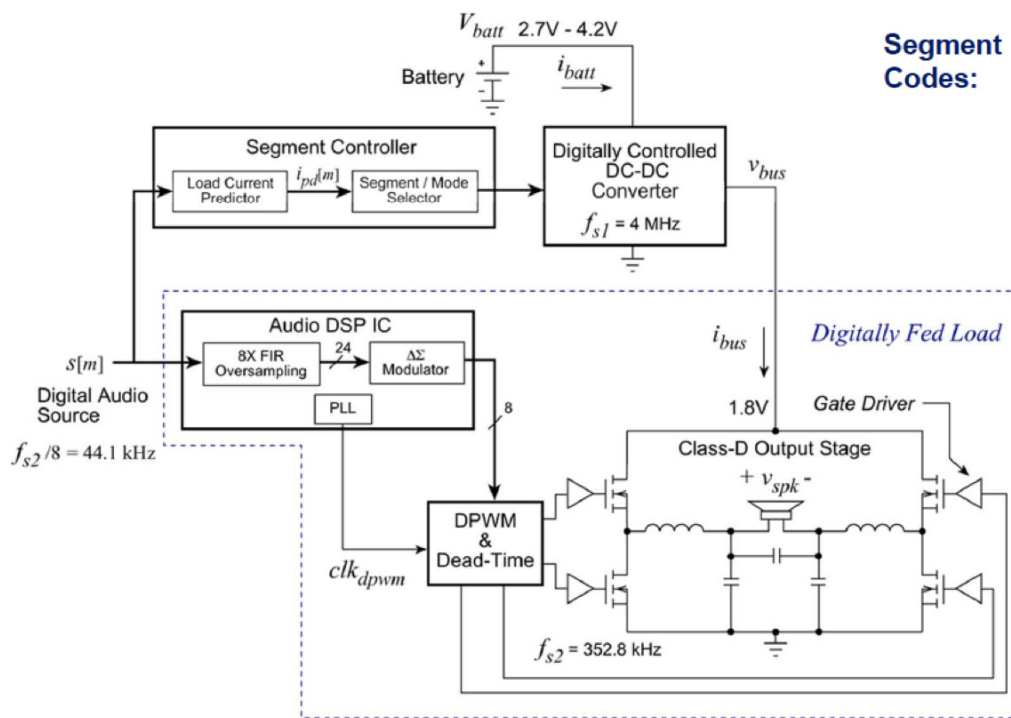

Predicted
Current:

Speaker
Voltage:



Segment
Codes:

 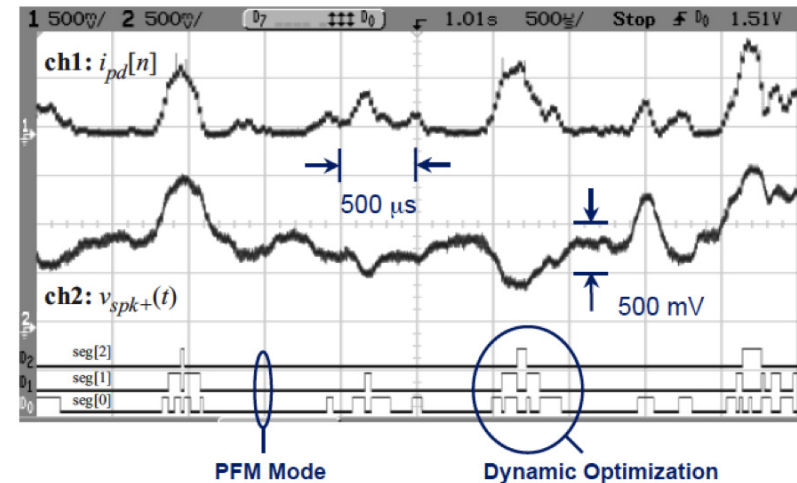

Source: Trescases et. al.TPE'08




Resonant Gate Drive

- Original resonant gate driver:

  


Charge Recovery

 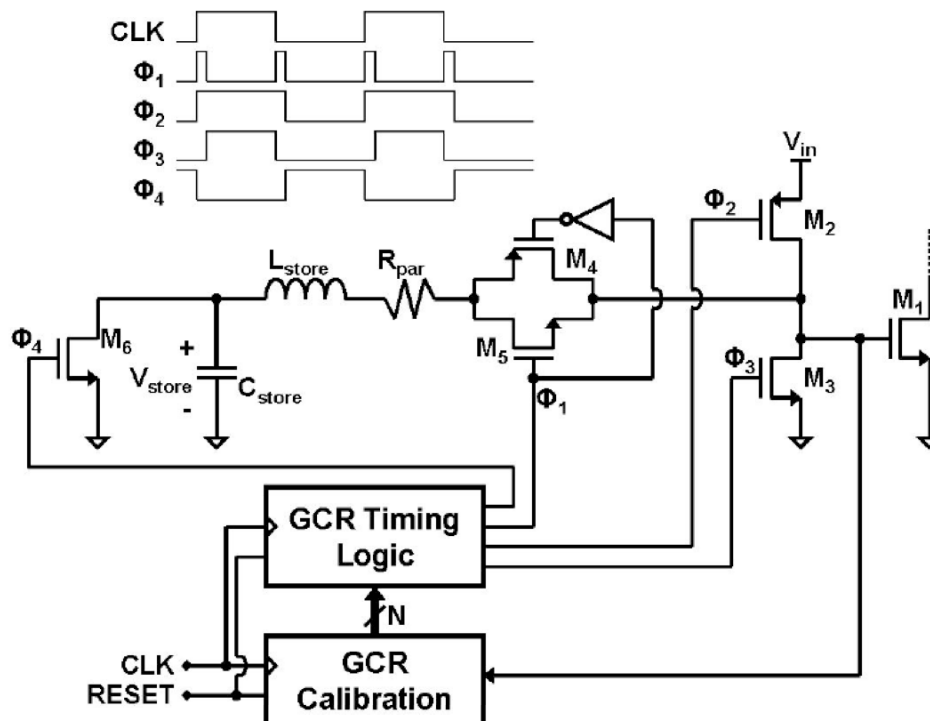 - Uses on-chip C_{store} (85 pF + 35 pF total) + L_{store} (22 nH x2)
- Approx 5 % efficiency improvement at 3 MHz operation
- Additional energy storage components dominate the layout



Source: Mulligan et. al. ISSCC'07

Existing Gate-Charge Recycling Technique

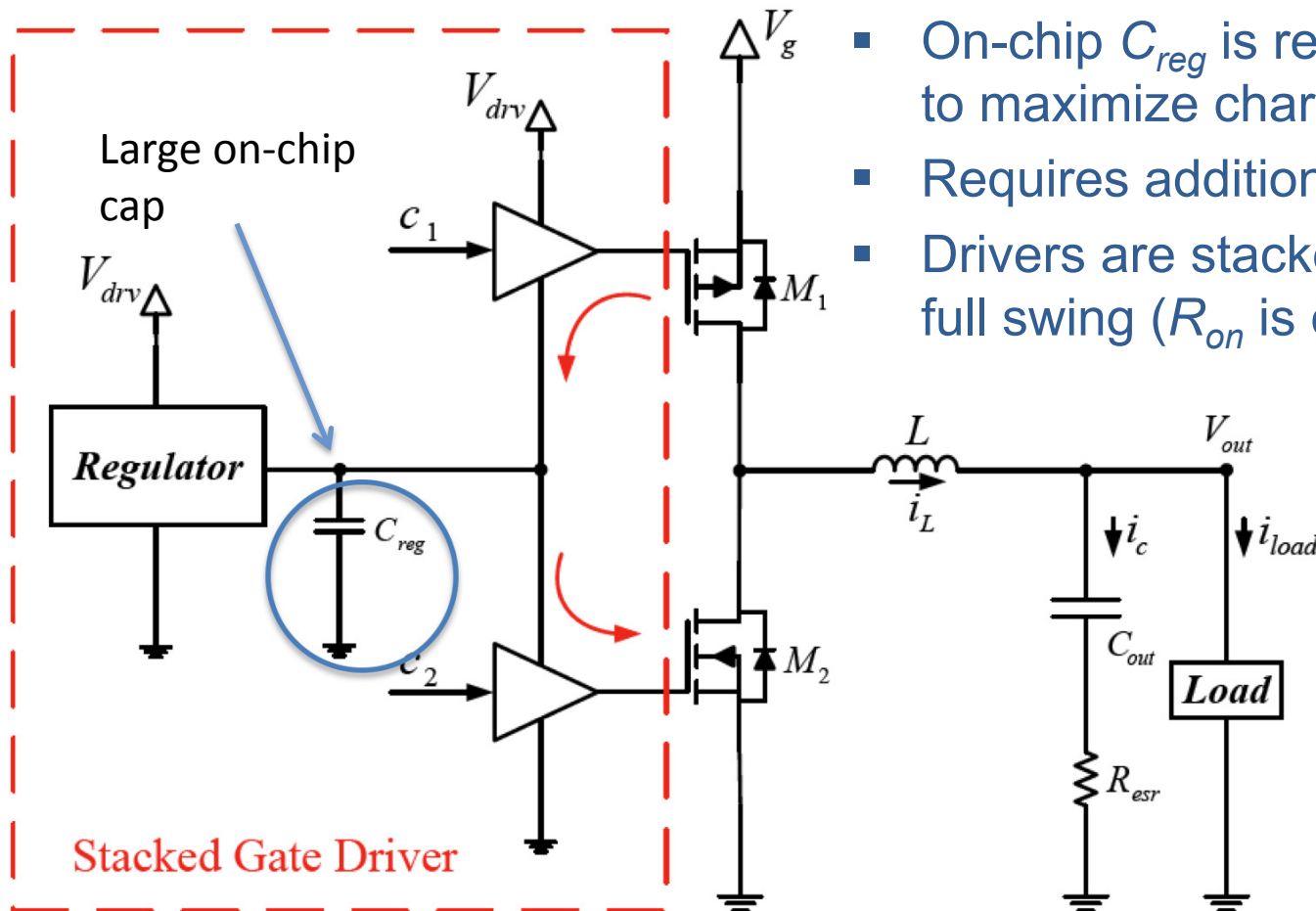


- On-chip C_{reg} is regulated at mid-rail to maximize charge recycling
- Requires additional linear regulator
- Drivers are stacked and don't reach full swing (R_{on} is compromised)

[1] J. Xiao et. al. JSSC 2004.



[2] M. Alimadadi, et al. IEEE PESC 2008.

Proposed Gate-Charge Recycling Technique

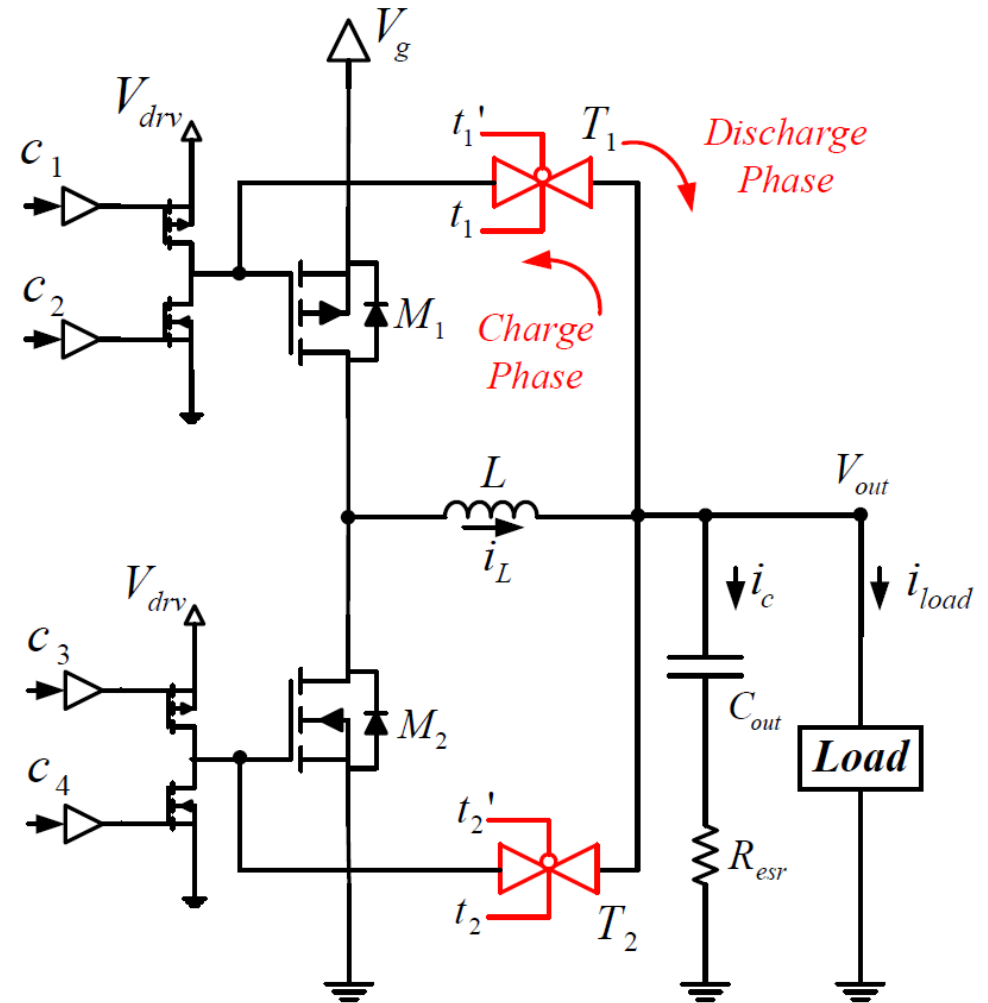- No on-chip energy storage needed
- C_{out} is used as energy storage
- No additional linear regulator required
- Additional dynamic power consumption due to transmission gates
- Main drivers can be reduced in size
- Power savings depends on V_{out}




Proposed Gate-Charge Recycling Technique

 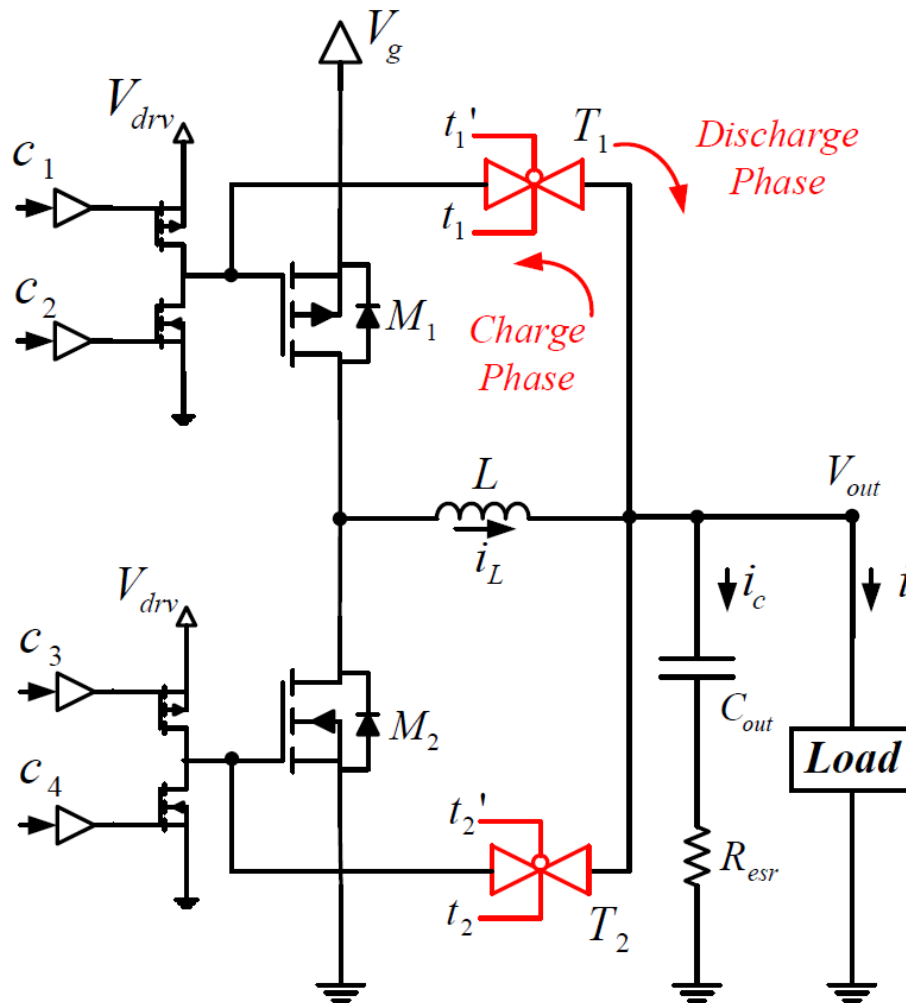


Proposed Gate-Charge Recycling Technique

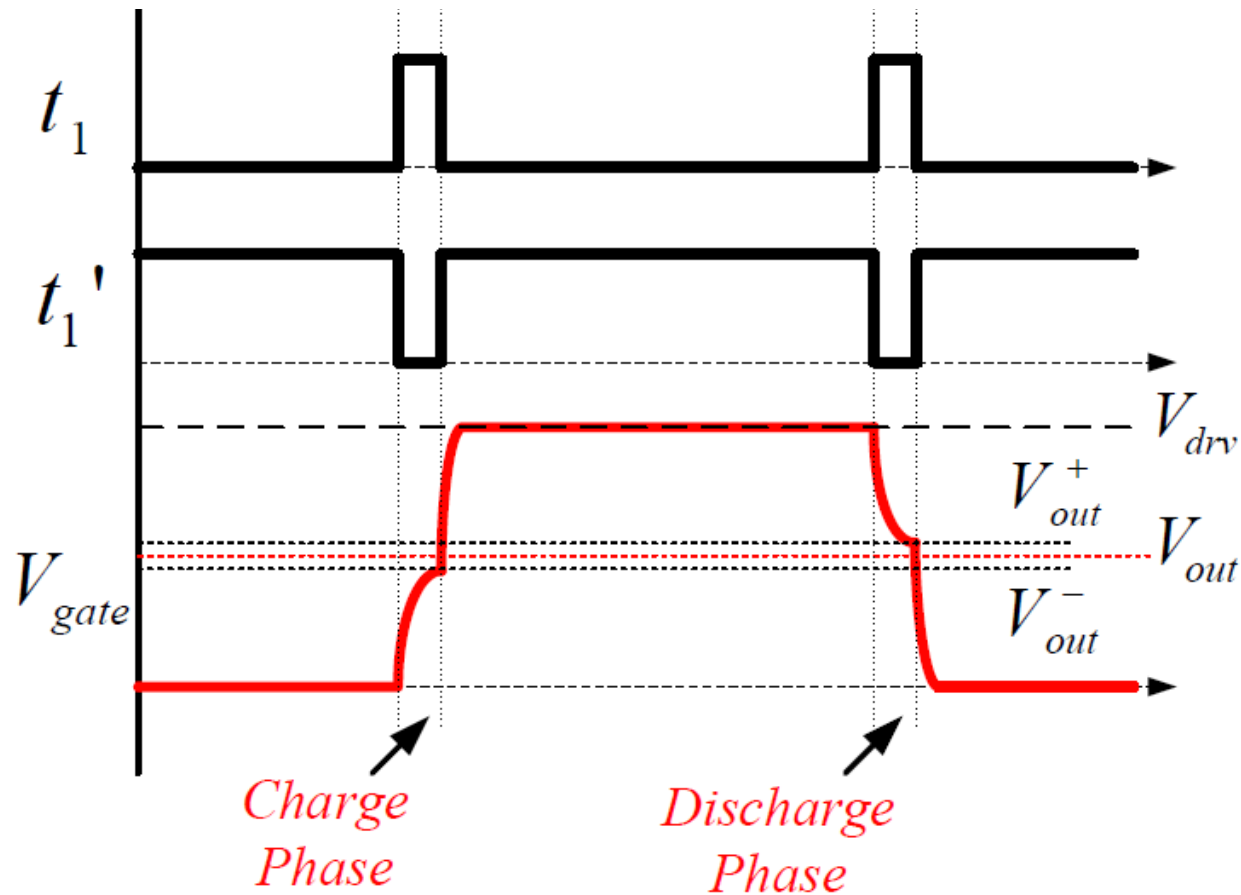- Basic control scheme: adjust t_1 so that V_{gate} reaches:
 - V_{out-} at the end of the charge phase
 - V_{out+} at the end of the discharge phase




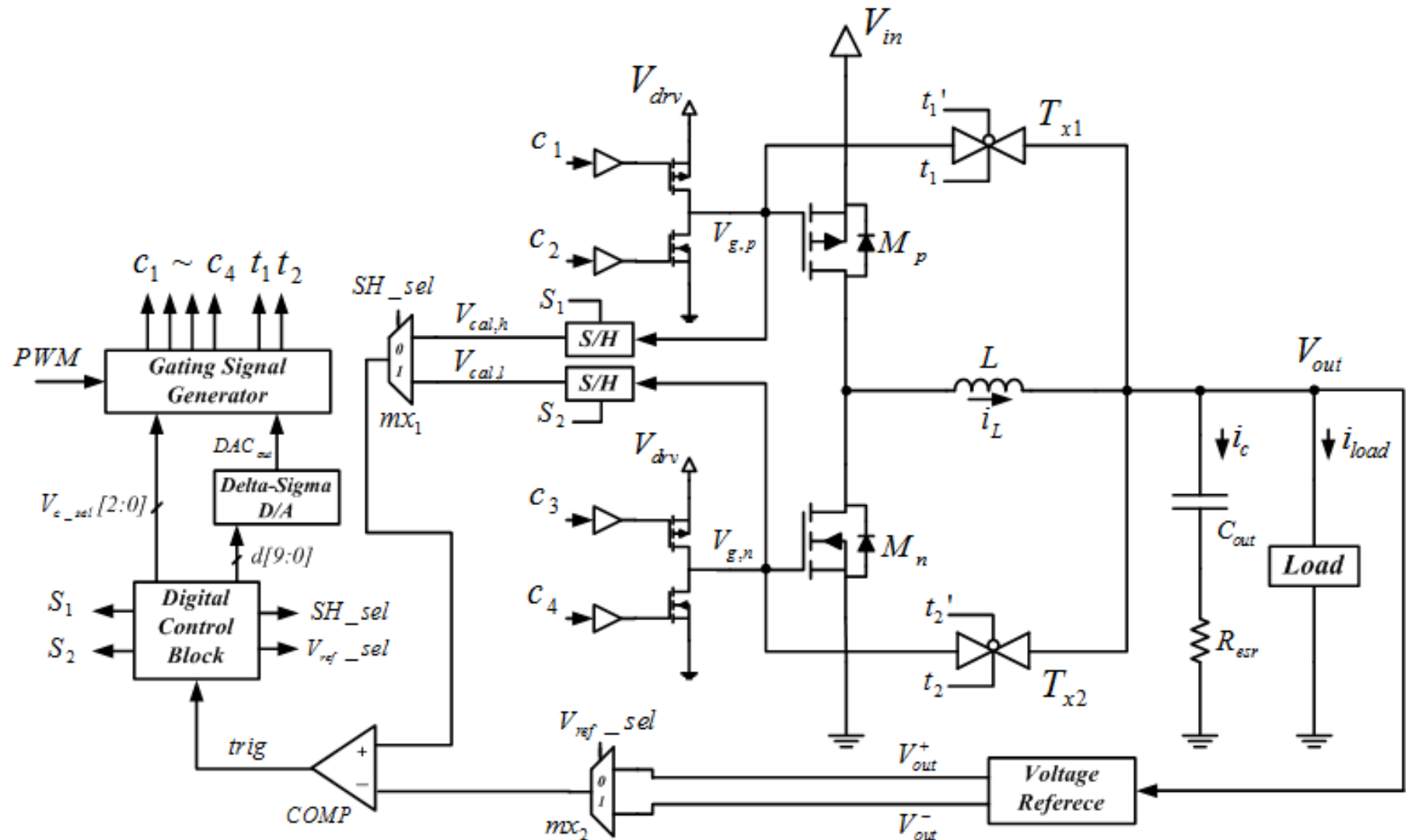Full System Architecture with Calibration




Gating Signal Generator

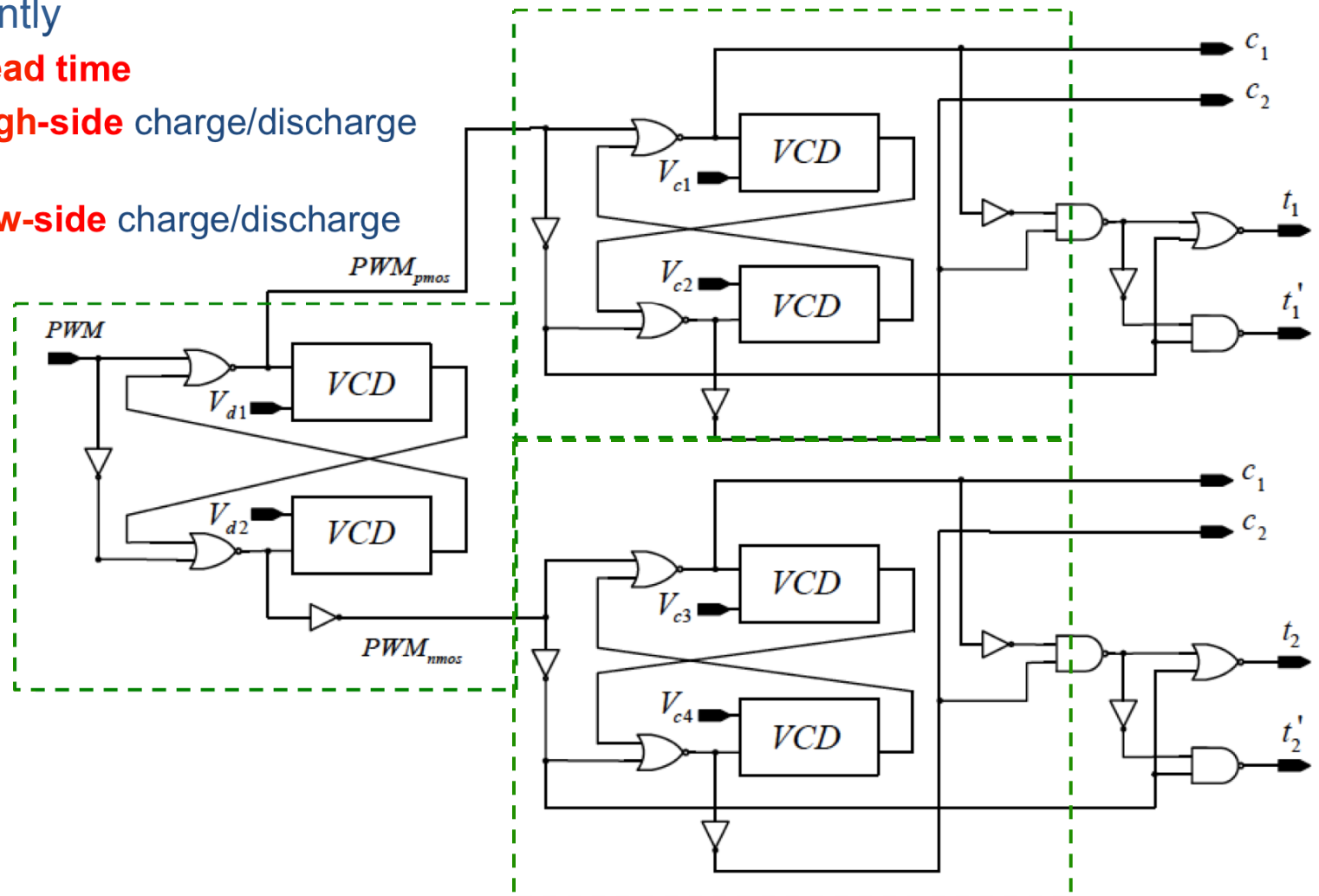
- Total of 6 VCDs are calibrated independently
 - 2 for **dead time**
 - 2 for **high-side** charge/discharge timing
 - 2 for **low-side** charge/discharge



Voltage Controlled Delay

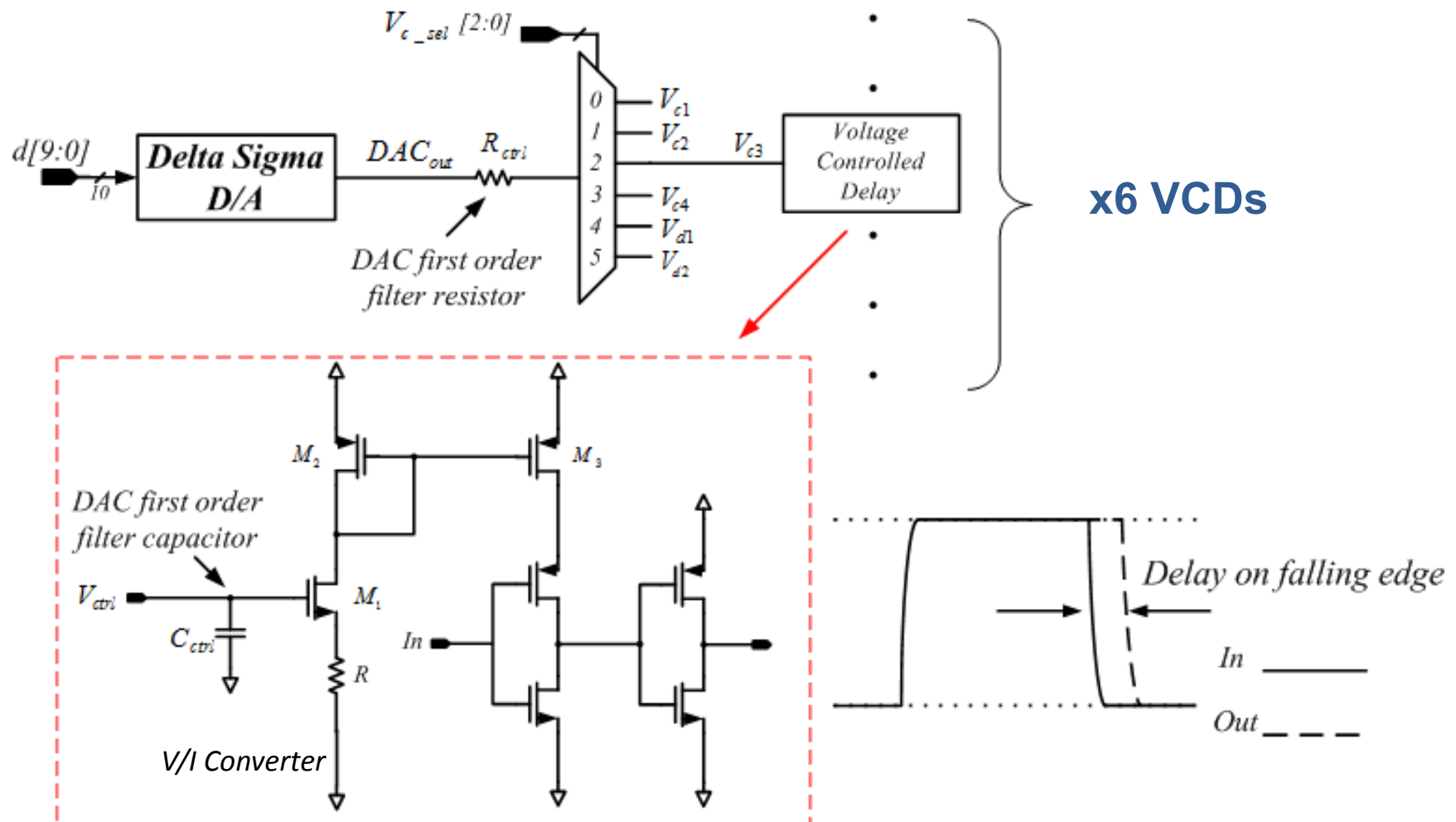

Charge Recycling Calibration Scheme

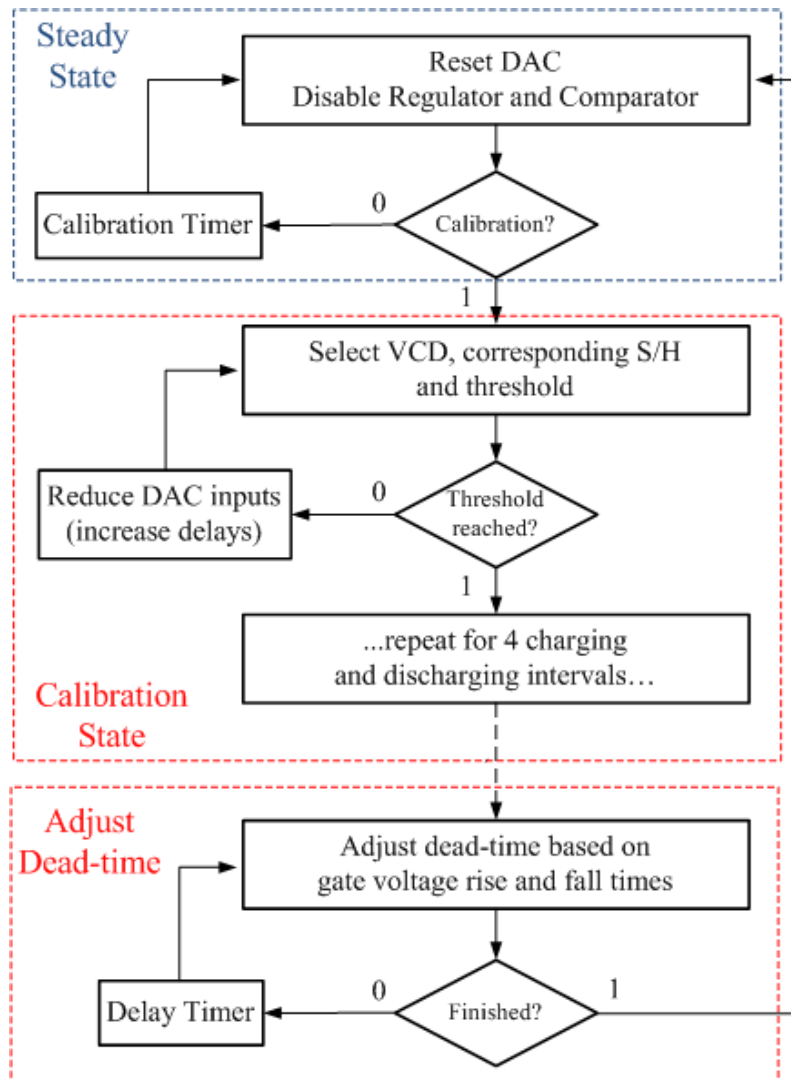

→ Charge recycling circuitry is put into sleep mode

→ Charge recycling circuitry is operational, which includes:

- Comparator
- Voltage reference
- Delta Sigma D/A

Converter Specification (designed in 0.13 μm CMOS)

Specification	Value	Units
Input Voltage, V_g	2.5	V
Driver Voltage, V_{drv}	2.5	V
Output Voltage, V_{out}	0.8 to 1.6	V
Rated Load, I_{load}	300	mA
R_{on} for $M_{1,2}$	185, 90	$\text{m}\Omega$
Q_{gate} for $M_{1,2}$ @ 2.5V	230, 120	pC
R_{on} for T_{x1} pmos, nmos	1.4, 2.5	Ω
R_{on} for T_{x2} pmos, nmos	2.8, 3.5	Ω
Output Capacitor C_{out}	1	μF
Total Capacitor ESR R_c	10	$\text{m}\Omega$
Filter, L	1.5	μH
Inductor DCR, R_L	100	$\text{m}\Omega$
Switching Frequency, f_s	20	MHz
DAC Clock Frequency, DAC_{clk} , adjustable	67 to 140	MHz
VCD Range	0.2 to 1.5	ns
Dead-time Range	0.5 to 2	ns
Total calibration time	< 20	μs
Re-calibration period	5	ms

T_{x1} and T_{x2} are
< 10x smaller
than M_p and M_n

requires
calibration
every 5 ms



Simulation Results: Before Calibration

High-side MOSFET
Gate drive waveforms:



TX off too soon
(partial charge sharing)

$$V_{cal,h} < V_{out}^-$$

$$V_{cal,h} > V_{out}^+$$

  

Transmission gate
Control:

  

Simulated Waveforms: After Calibration





High-side MOSFET
Gate drive waveforms:

Proper control of TX

$$V_{cal,h} = V_{out}^-$$


$$V_{cal,h} = V_{out}^+$$

Transmission gate
Control:

    




Simulated Overall Efficiency Improvement

 - Efficiency vs. load current from 15-180 mA (closed loop control)
- 25 %** reduction in gate-drive power – 5 % efficiency improvement






Deeper Look: Power Savings vs. V_{out} , I_{out}

   - $V_{out} < \sim V_g/2$:
 - Net charge transfer from V_{drv} to V_{out}
 - Power from V_g is reduced
- $V_{out} > \sim V_g/2$
 - Net charge transfer from V_{out} to V_{drv}
 - Power from V_g is increased




Power Savings with Discharge Phase Only

  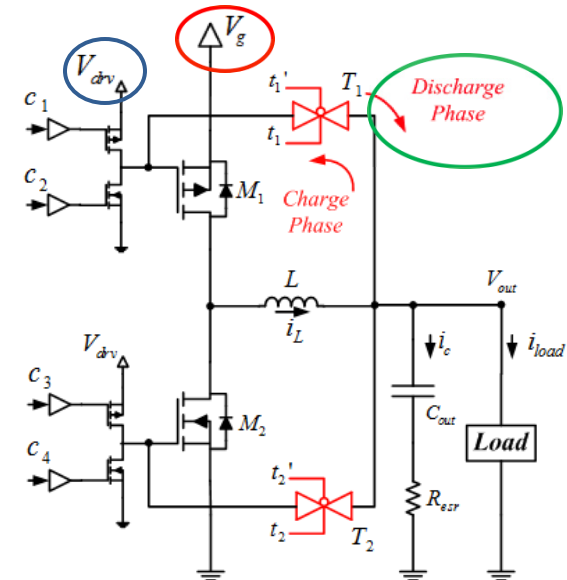- Discharge phase provides no savings in driver power
- TX gate is only used once per cycle (potential savings)
- Input power is reduced since the driver power is transferred to the output



With Discharge Phase Mode Only

 - Light-load efficiency curve with discharge phase operating only



Conclusions

- Gate-drive loss becomes significant for dc-dc converters that operates beyond 10 MHz.
 - Over 60% of total loss is gate-driver loss in this 20 MHz converter design
- Gate-charge recycling needs to be achieved by a close-loop control scheme to provide optimal power savings at various operating conditions.
- Compatible with
 - variable frequency techniques (PFM, burst-mode, etc.)
 - adaptive gate swing to achieve further power savings
- The proposed technique provides a solution without additional magnetic components with 5% overall efficiency improvement and equivalent of 25% in driver power saving, without increasing R_{on}
- Conducted EMI from gate driver is moved from input to output
- On-chip experimental results coming soon