

# Deep Trench Capacitors for Switched Capacitor Voltage Converters

Jae-sun Seo, Albert Young,  
Robert Montoye, Leland Chang

*IBM T. J. Watson Research Center*

3<sup>rd</sup> International Workshop for Power Supply on Chip


Nov 17<sup>th</sup>, 2012

# Outline

- **Motivation**
- **Switched-capacitor voltage converter with deep trench capacitor technology**
- **Design Tradeoffs for Efficiency and Current Density**
- **Chip floorplanning / Application**
- **Summary**


# Power Delivery w/ 2:1 Step Down

Today

 

Proposal

Reduce current delivery by 2x

 


$I^2R$  Loss  
Reduces by 4x

$Ldi/dt$   
Reduces by 2x  
Net improvement: 4x  
(including conversion)

$C4$  current  
Reduces by 2x
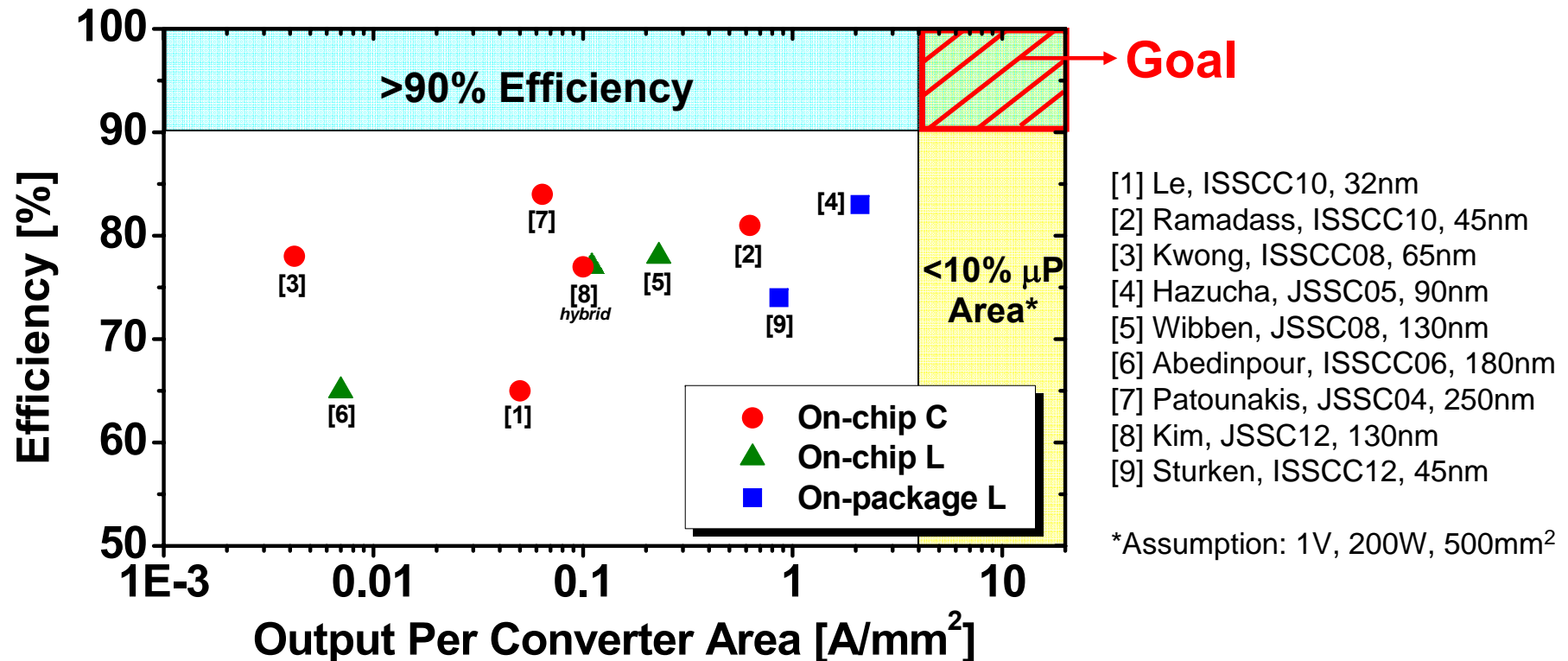
# Previous Work on On-Chip Voltage Conversion



- Typically 3 approaches : (1) linear (2) switched-capacitor (3) buck
  - Linear regulator not suitable for high-voltage power delivery
- Difficult to achieve high efficiency & current density simultaneously


# Why Switched-Capacitor Converters?

- **High-voltage power delivery**
  - Offers strong benefits especially for high-current applications or when significant package loss exists
  - Achievable by switched-capacitor voltage converters with fixed ratio step-down
  - Linear regulator : no high-voltage delivery benefit
- **Low-cost on-chip integration with existing technology**
  - Buck converter : on-chip inductor material with high-enough Q not quite there, external inductors not good for integration
- **With dense deep trench capacitors, switched-capacitor converter can achieve high-efficiency and high current density**

# Outline


- Motivation
- **Switched-capacitor voltage converter with deep trench capacitor technology**
- Design Tradeoffs for Efficiency and Current Density
- Chip floorplanning / Application
- Summary

# 2:1 Switched-Capacitor Converter

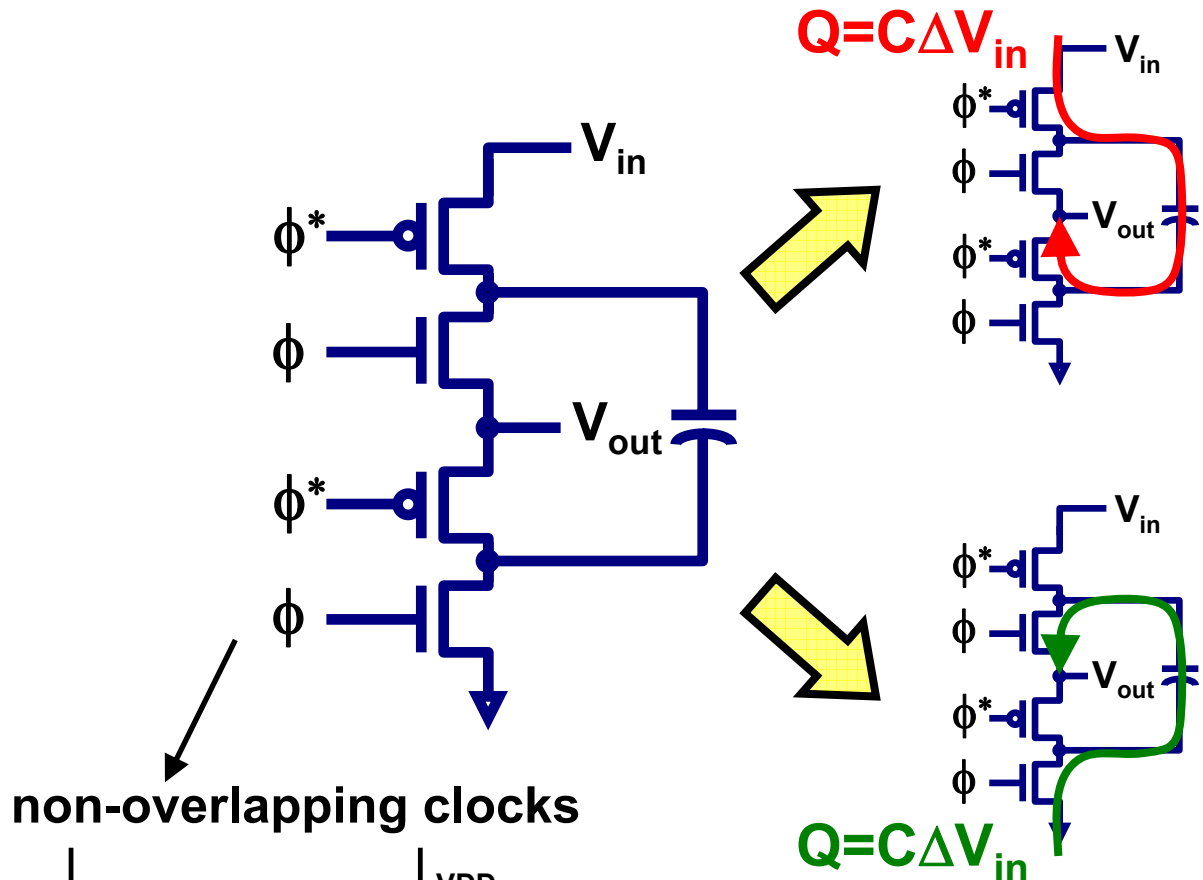

- $V_{out} = \frac{1}{2} V_{in}(1-\Delta)$
- $I_{out} = 2\Delta C V_{in} f$
- Intrinsic efficiency =  $(1-\Delta)$

non-overlapping clocks

 


- Small  $\Delta$  offset in  $V_{out}$  generates current
- With traditional capacitor, cannot really achieve intrinsic efficiency or sufficient output current

# Deep Trench Capacitor Technology
 
## High performance SOI CMOS


- Yields low loss switch
- Floating body FET with buried oxide isolation
  - Facilitates stacking of thin-oxide devices for high voltage conversion



## Deep trench capacitor


- High density, low loss vs. MOS capacitor:
  - Area efficiency: >25× better density
  - Conversion efficiency: >10× better parasitics
- High-κ storage node dielectric introduced in 32nm, metal liner mitigates poly depletion

32nm SOI eDRAM  
(Wang, IEDM 2009)

 





# Scaling Trend of Deep Trench Capacitor

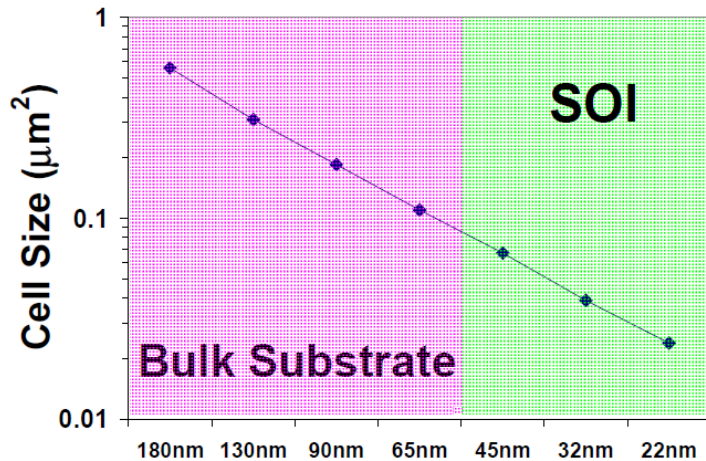


- IBM's embedded DRAM implemented with deep trench capacitor
- Since 180nm, cell size reduced ~60% every node

Wang, IEDM 2009

  

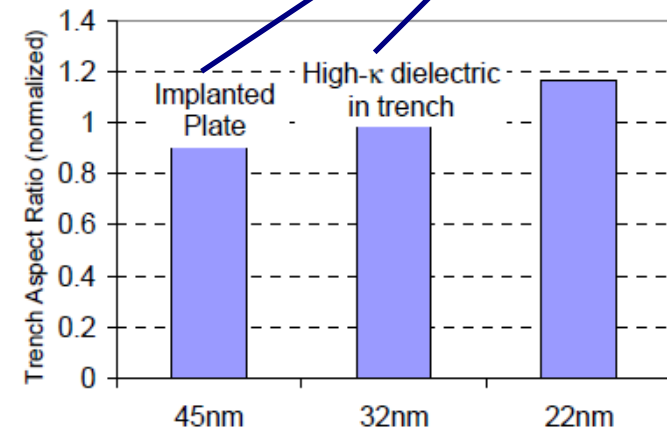
- eDRAM cell capacitance density scales well, path shown for 22nm





- New technology elements + modest increase in trench AR → optimal storage capacitance

# Multiple Conversion Ratios (3:1, 3:2, ...)

Ramadass, ISSSCC 2010

 

Le, ISSSCC 2010

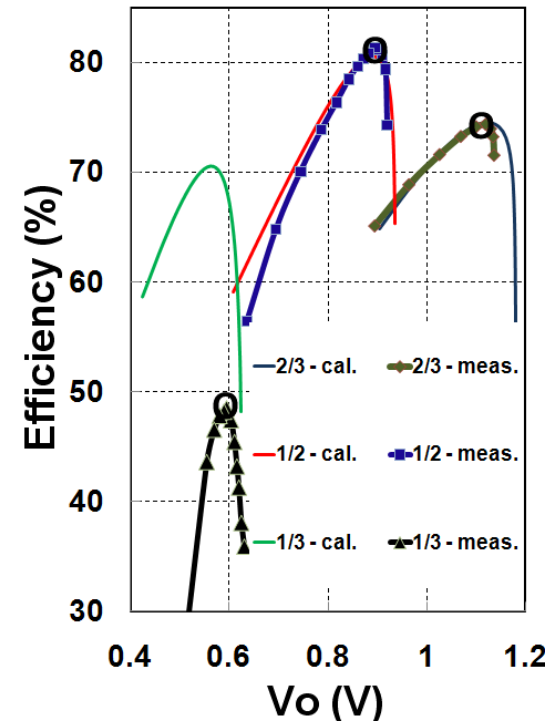 


- Different conversion ratios, reconfigurable converters, hybrid conversion schemes are possible
- However, they require more area (than 2:1), not necessarily favorable in terms of current density for high-current microprocessors
  - Depends on whether the application requires a continuously wide range of output voltages

# Outline


- Motivation
- Switched-capacitor voltage converter with deep trench capacitor technology
- **Design Tradeoffs for Efficiency and Current Density**
- Chip floorplanning / Application
- Summary
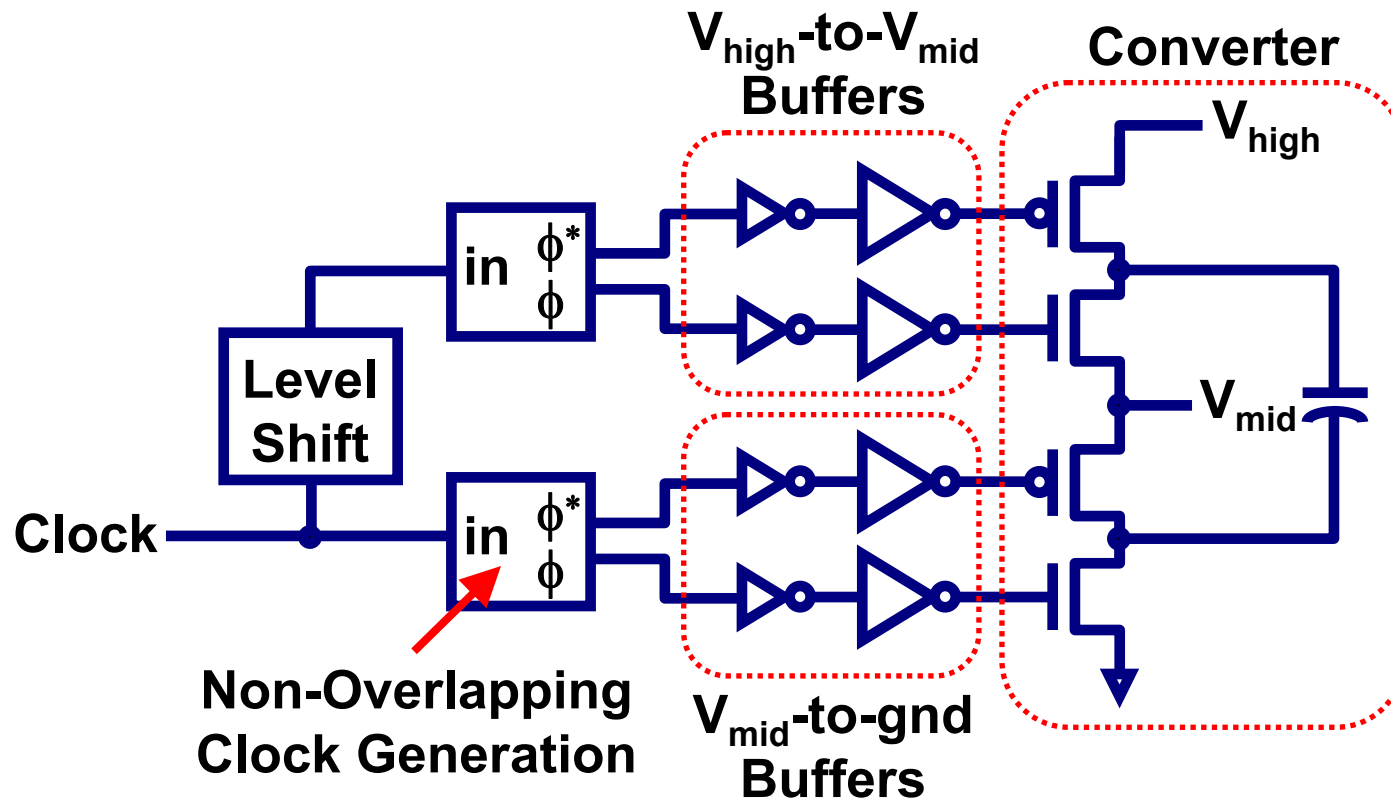
## 2:1 Switched-Capacitor Converter Circuits




- Using level shifters / stacked buffers, no thick-oxide devices required
- External supplies of negligible current for  $\phi/\phi^*$  generation
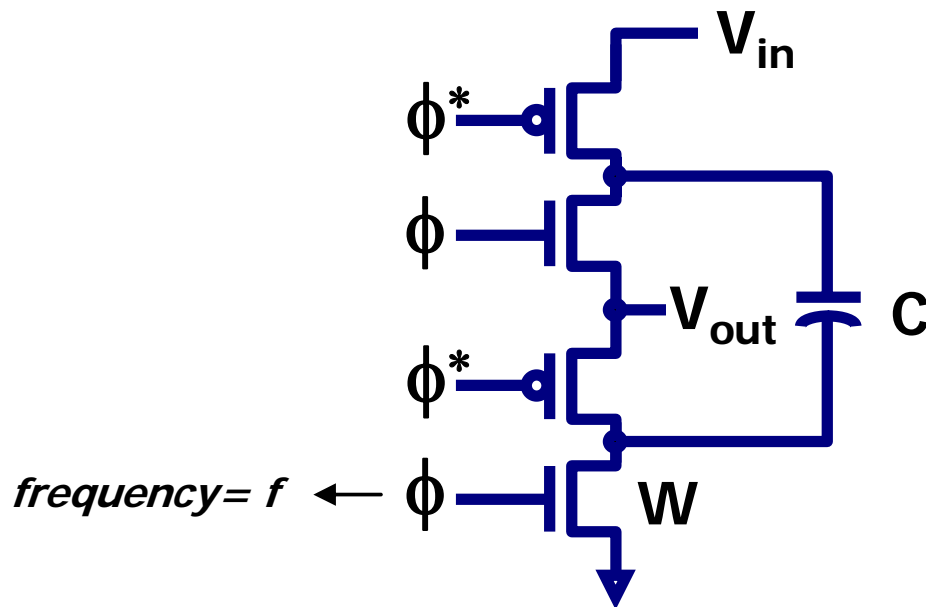
## 2:1 Switched-Cap Single-Phase Design Point




- $V_{out} = \frac{1}{2} * V_{in} * (1 - \Delta)$
- $I_{out} = 2 * C * V_{in} * \Delta * f$
- **Efficiency =  $1 - \Delta - k * W * f$**
- **Trade-off in efficiency, area, output current by selecting  $V_{in}$ ,  $C$ ,  $W$ , frequency, etc.**
- **Objective: high efficiency with that satisfies required output current for an application**

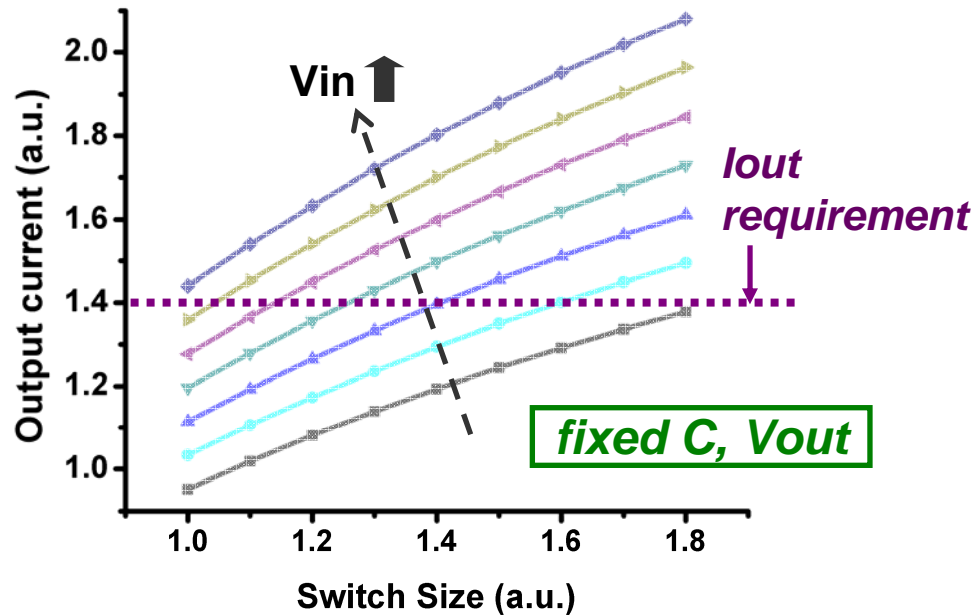
# Efficiency / Output Current Optimization



 - For a certain application, following specs will be fixed
  - Target supply voltage
  - Required output current
  - Allowable area for SC converters → fixed flying cap
- Still, designers have freedom on the following to optimize efficiency
  - $V_{in}$  ( $\Delta$ )
  - Switch sizes
  - Frequency
  - Need to keep balance between  $\Delta$  losses and switching ( $W$ , freq.) losses




# Measurements of 45nm 2:1 SC Converter

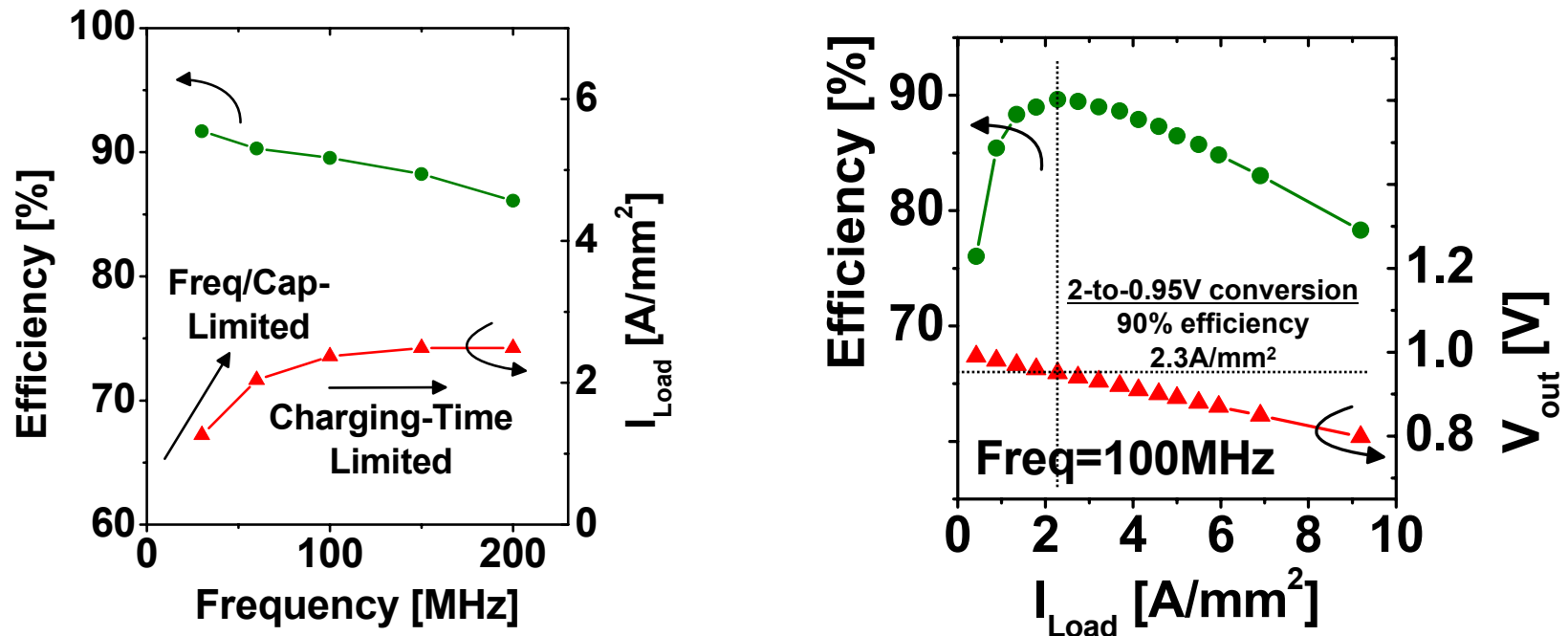

Chang, VLSI Symp. 2010

- Output current is bounded by flying cap charge (when freq. is low), and RC of switch (when freq. is high)
- Achieved 90% efficiency ( $\Delta \sim 5\%$ , clock losses  $\sim 5\%$ ) with 2.3A/mm<sup>2</sup>
  - Higher current density achievable by trading off efficiency

# Tradeoff: Efficiency vs. SC Area

 


- Once the output current requirement is set, spending more area for SC converters (flying capacitors) increases power efficiency
- But eventually saturates due to minimum switching loss and  $\Delta$ -related loss



# Outline


- Motivation
- Switched-capacitor voltage converter with deep trench capacitor technology
- Design Tradeoffs for Efficiency and Current Density
- **Chip floorplanning / Application**
- Summary

# Interleaved Switched-Cap Converters

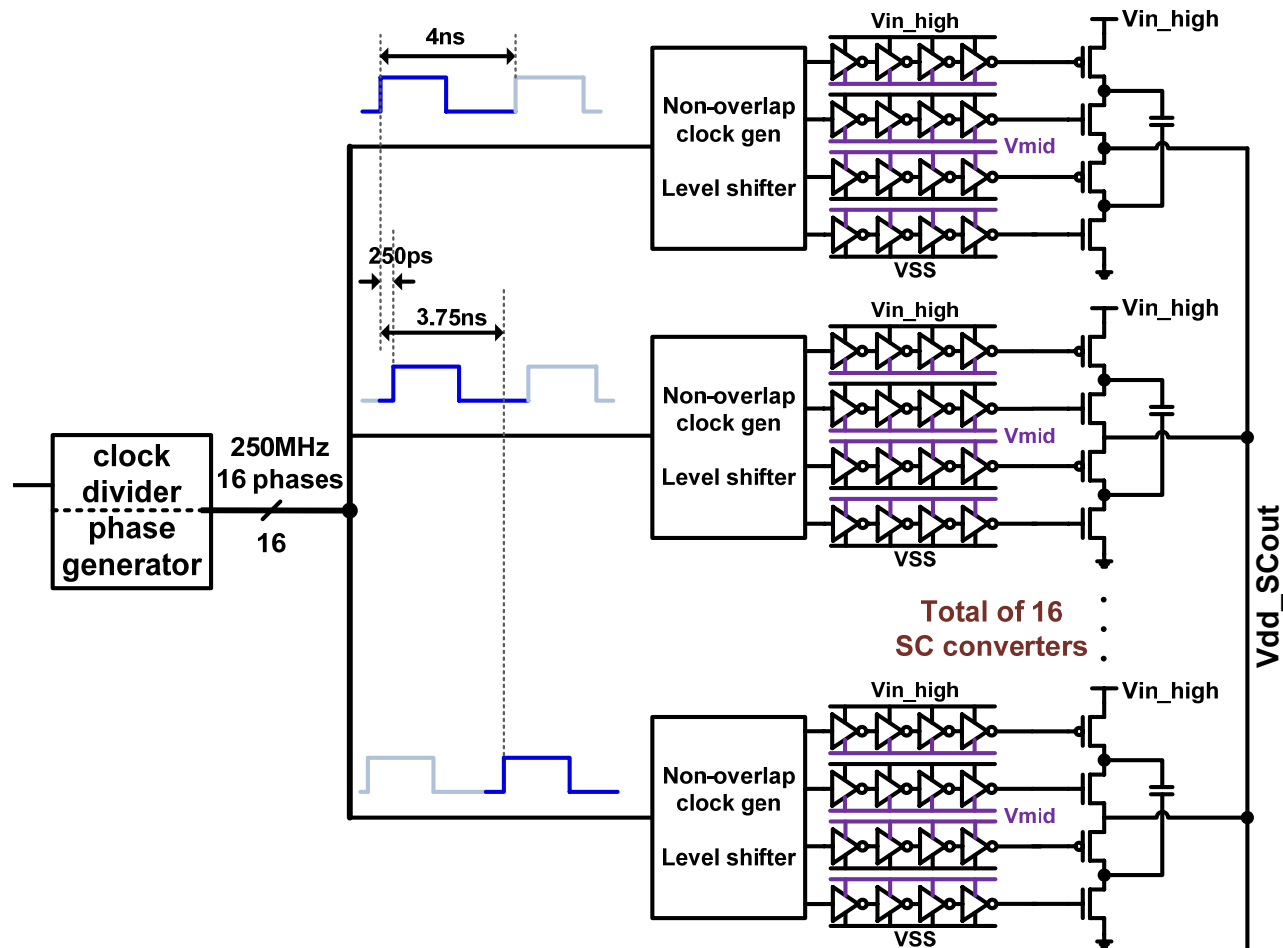

- Reduce output ripple
- Main processor clock could be tapped and divided for multiple phases


# Chip Floorplanning

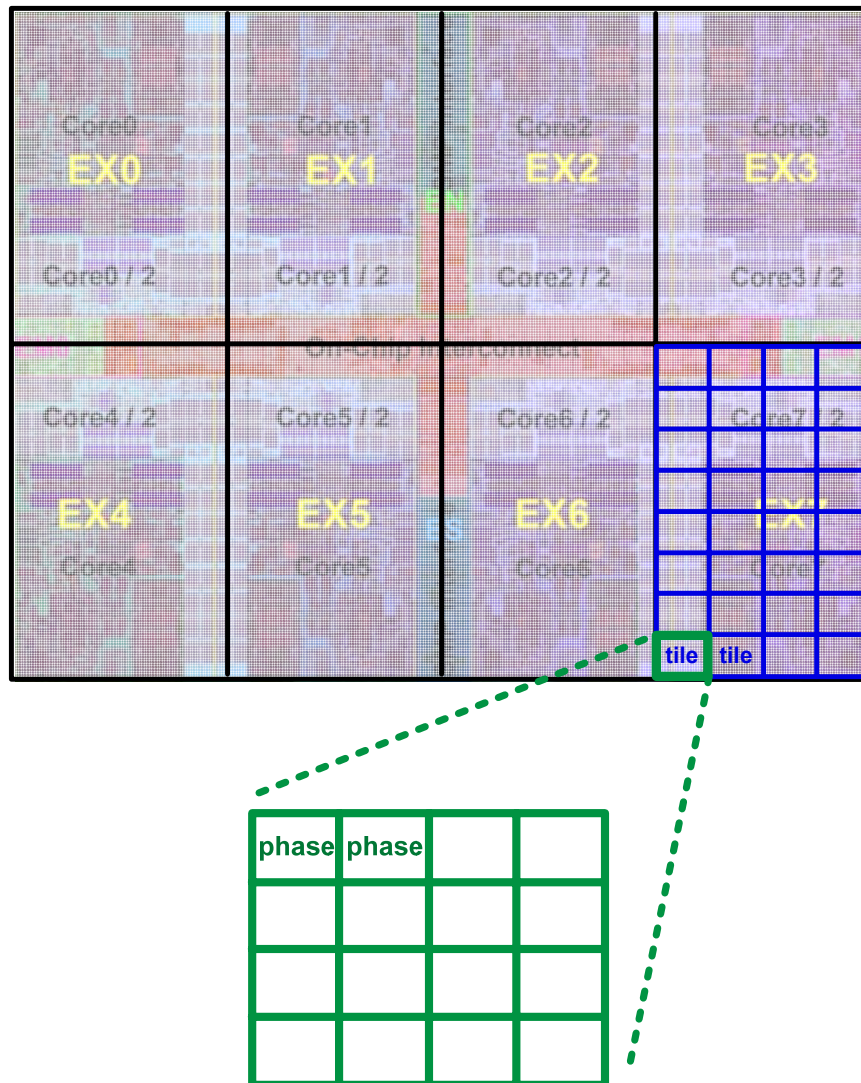


- One switched-capacitor tile consists of multiple interleaved SC converters
- Multiple switched-capacitor tiles could be placed across a processor
- Each tile has its own SC control, enable, duty cycle
  - Output could be all tied together
  - SC converters near hot spots would be turned on more frequently than idle spots
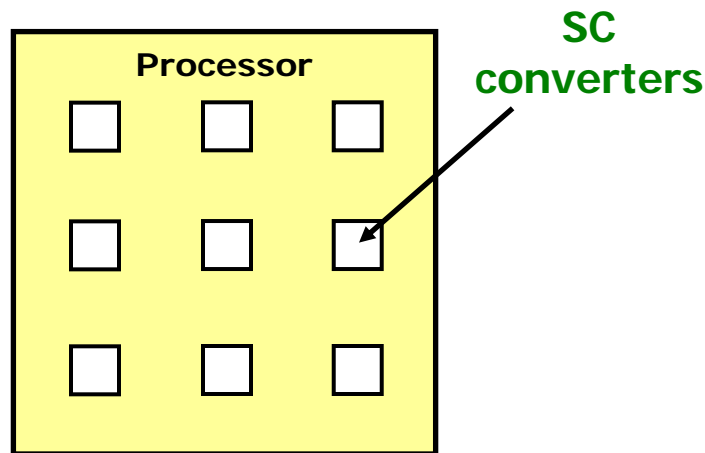
# 2-D / 3-D Implementation Options

***2-D implementation:***  
 Allocate certain area for SC



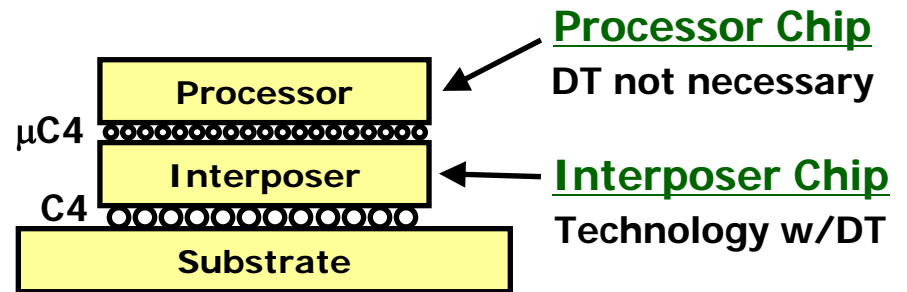
***3-D implementation:***  
 Interpose chip for voltage conversion/regulation



- Implementation depends on system requirements, area availability

# Fast Switched-Cap Strategy for Processors


## Open-loop operation

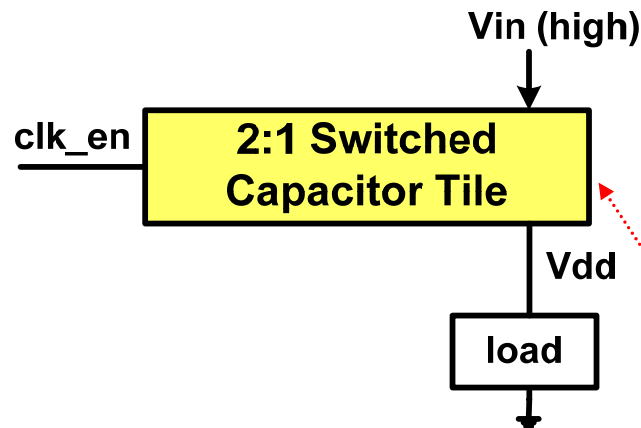

- If SC is fully ON, Vdd varies linearly with load current
- SC could be turned on with a certain duty cycle depending on output load current

DT flying capacitors also act as decoupling caps for Vin and Vdd

## Closed-loop regulation

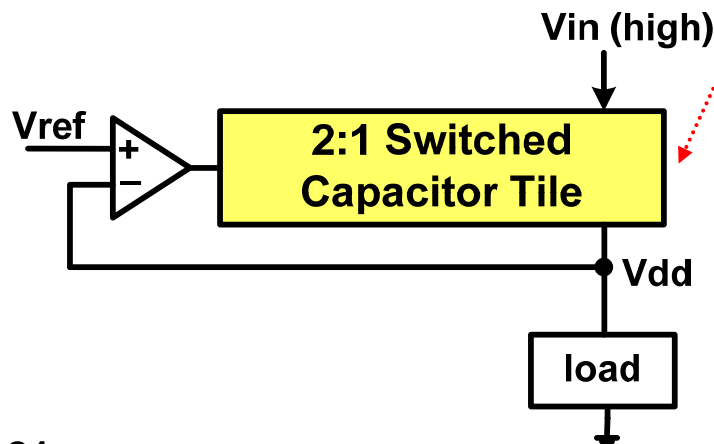


- Needs accurate reference voltage
- Overall closed-loop latency is critical for noise reduction
- Input voltage noise largely handled against load fluctuations

Ramadass JSSC10, Kim JSSC12

# Another Application – Stacked I/O

- Stacked I/O for low voltage signaling

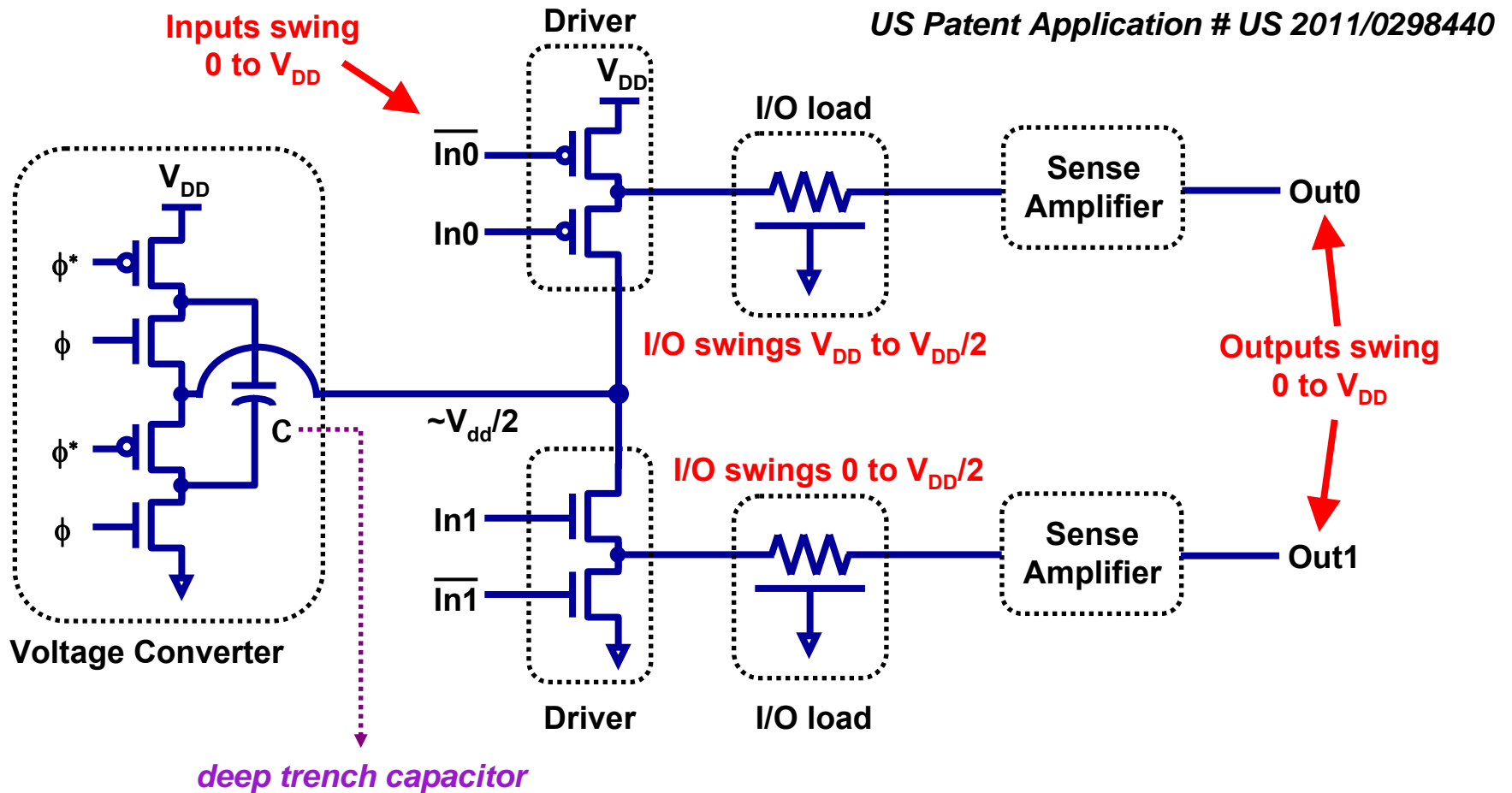

# Summary

- **High-voltage power delivery is beneficial to reduce power distribution losses, which could be achieved with switched-capacitor down-conversion**
- **Deep trench capacitors enable switched-capacitor converter to achieve high efficiency and high output current**
- **Clear scaling path is shown for deep trench capacitors towards 22nm and beyond**
- **Design tradeoff exists between efficiency, area, output current**
- **DT-based switched-capacitor circuits offer solutions for highly-efficient voltage regulation modules for various applications**

**Thank you!**