

# Mixed-Signal IC Controllers and Low-Volume SMPS Topologies

Prof. Aleksandar Prodić

[prodic@ele.utoronto.ca](mailto:prodic@ele.utoronto.ca)

Laboratory for Power Management and Integrated SMPS

University of Toronto, E. Rogers ECE Department



University of Toronto, Rogers ECE Department

## A Low Power (Portable) Application – Rogers Portable Radio




- Allowed a large number of households to have daily access to information
- Reduced power consumption by using more efficient electronic tubes


Main motivation: to reduce the volume and weight of the power supply, by far the largest part of previous radios


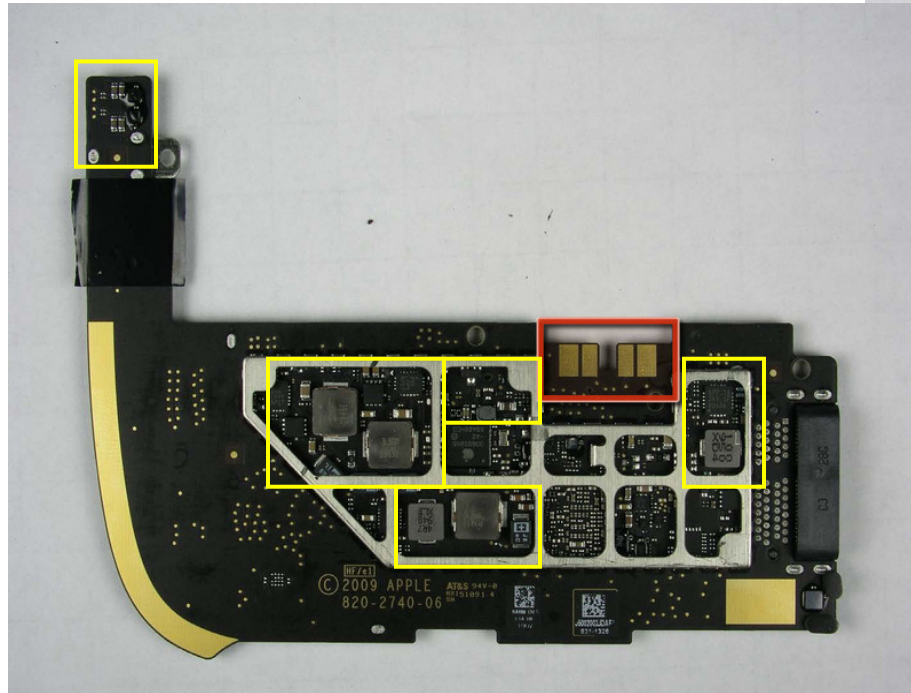
## Low Power SMPS in Portable/Consumer Electronics



iPad - teardown

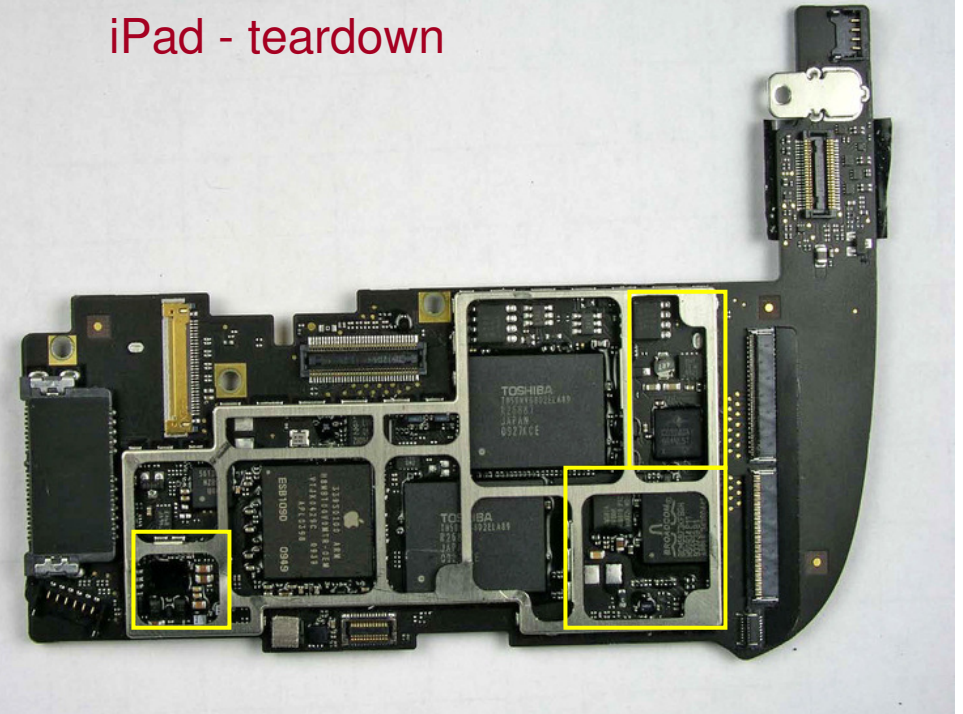


<http://www.ifixit.com/Teardown/iPad-FCC-Teardown/2197/1>

- Dc-dc SMPS occupy between 20% and 80% of the total volume in modern electronics devices, communication equipment, computers...
- Most of the volume occupied by passives and heat sinks




## Outline: Two Parts of Presentation

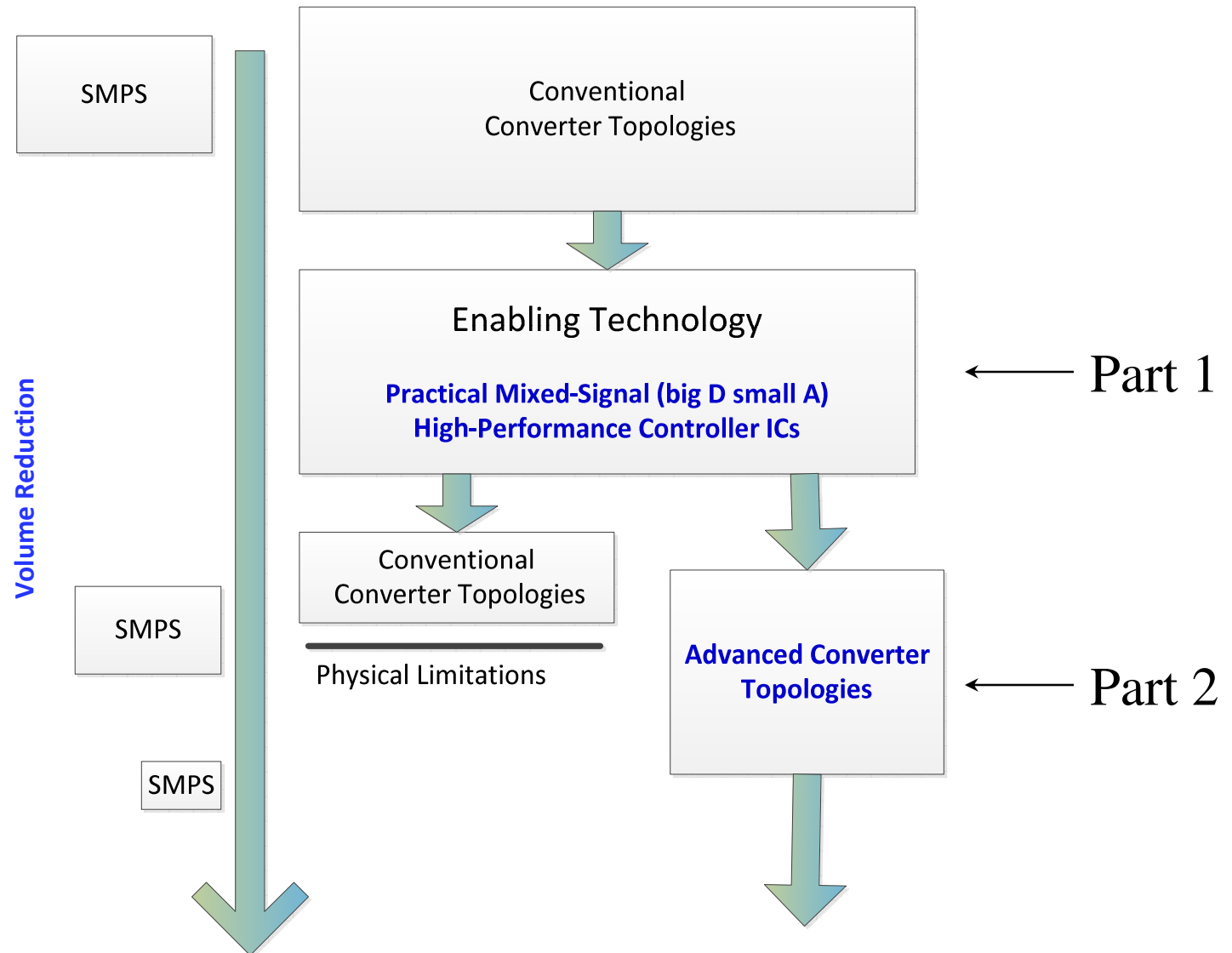
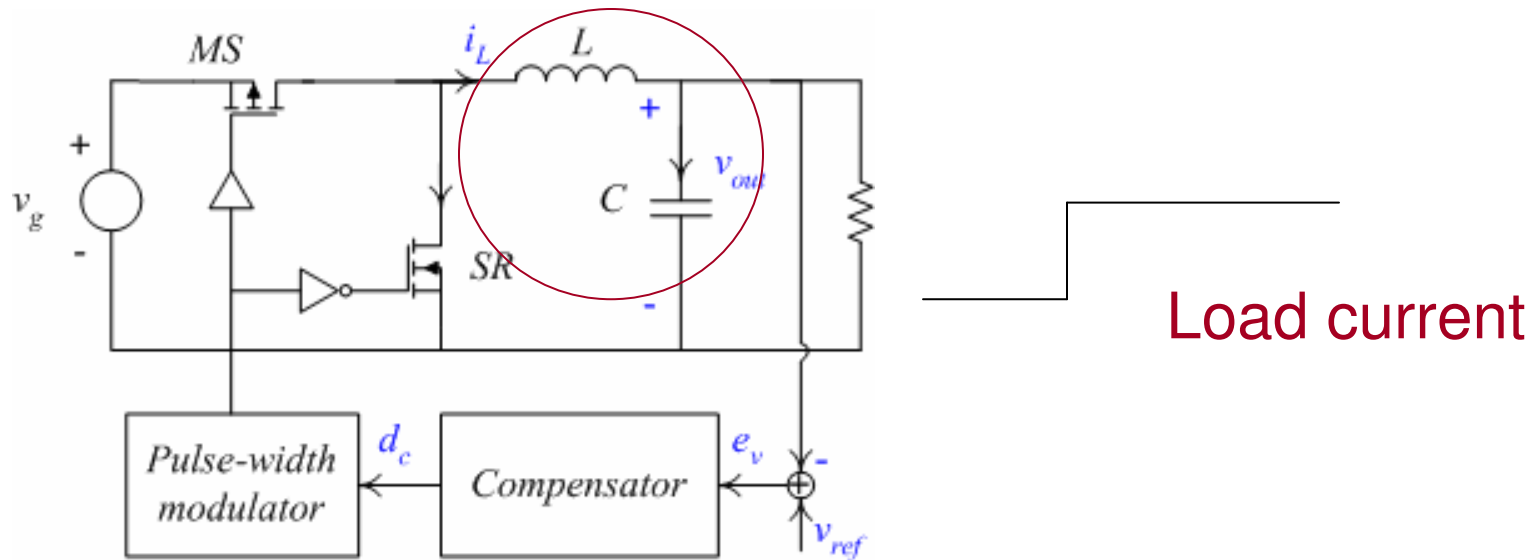
## Conventional Methods for Volume Minimization

- Operation at high switching frequencies
- Efficiency optimization = flat and high efficiency curve
- Fast dynamic response of the controller + plug and play operation





All three of these goals can be accomplished




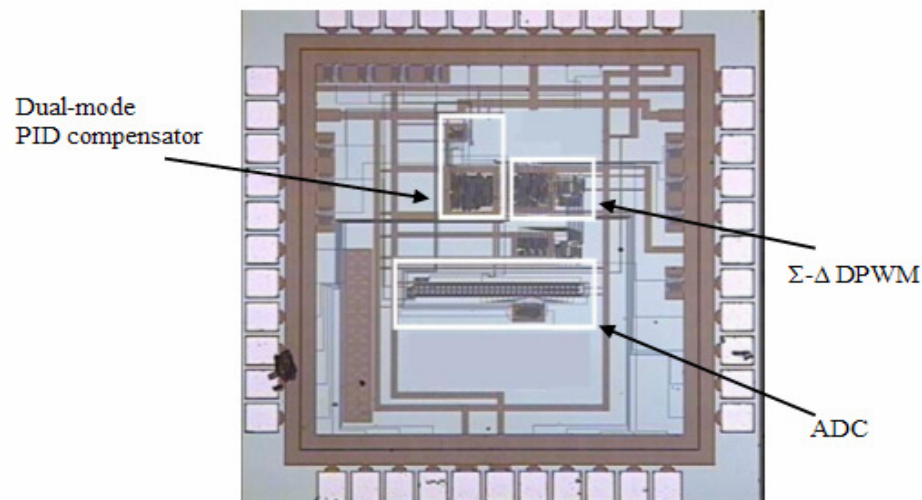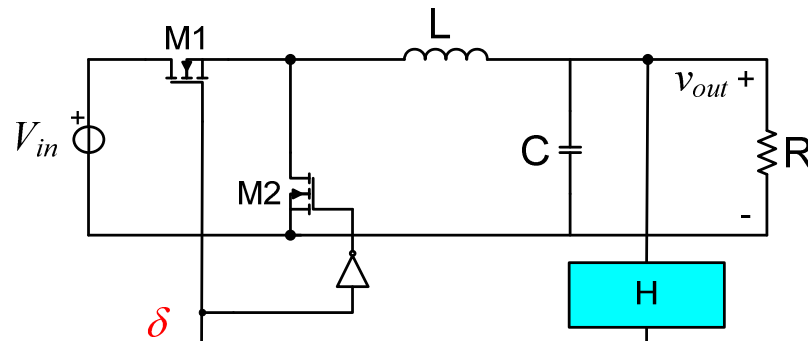
# Ultra High-Frequency High-Resolution Digital Controller IC





- The duty ratio of a core resolution (high-frequency) DPWM is varied over several switching cycles to achieve high effective resolution.
- The averaging is performed by the switching converter itself (LC filter)
  - The output measured with a moving windowed ADC producing just few error signals
- Processing unit reduced since it also operates over a small error range




[1] Z. Lukic, N. Rahman, A. Prodić, "Multibit  $\Sigma$ - $\Delta$  PWM Digital Controller IC for DC-DC Converters Operating at Switching Frequencies Beyond 10 MHz," IEEE Transactions on Power Electronics, Vol.22, Issue.5, October 2007, Pg. 1693-1707 (.pdf).

# Ultra High-Frequency Digital Controller IC Results


DPWM switching frequency	Programmable, 400 kHz to 150 MHz
DPWM effective resolution	10-bit
Controller area	0.14 mm <sup>2</sup>
$\Sigma$ - $\Delta$ Modulator current consumption	Sub 10 $\mu$ A/MHz

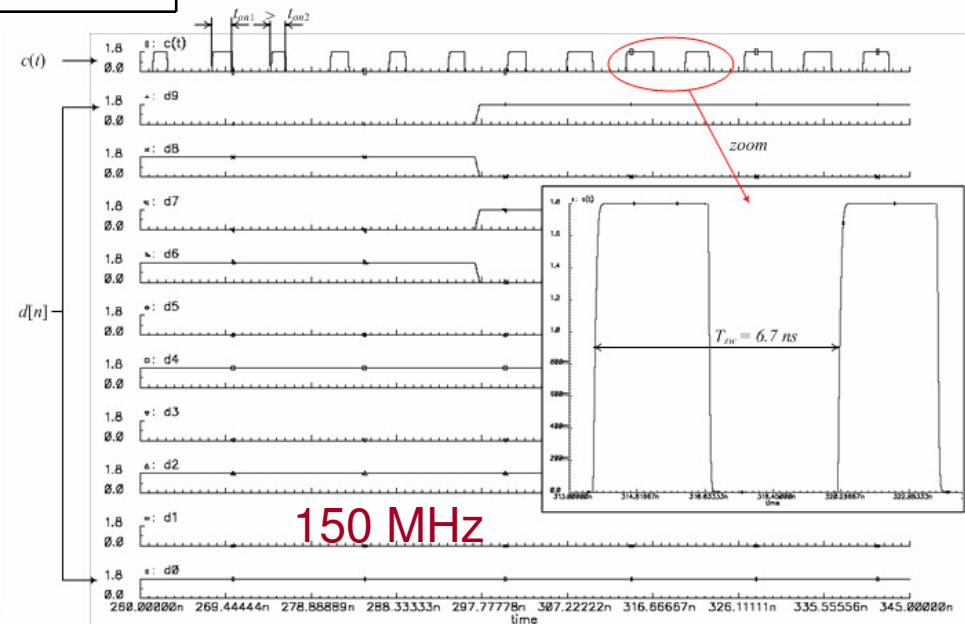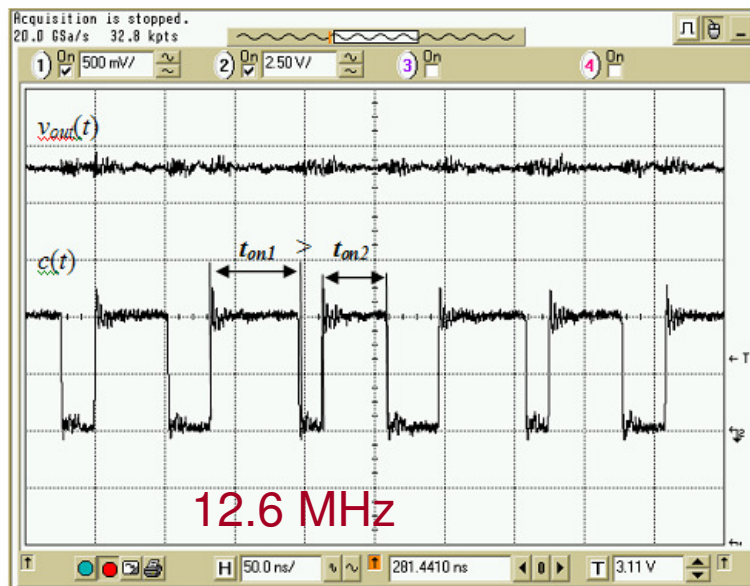

# Minimum Deviation Controller IC [2]

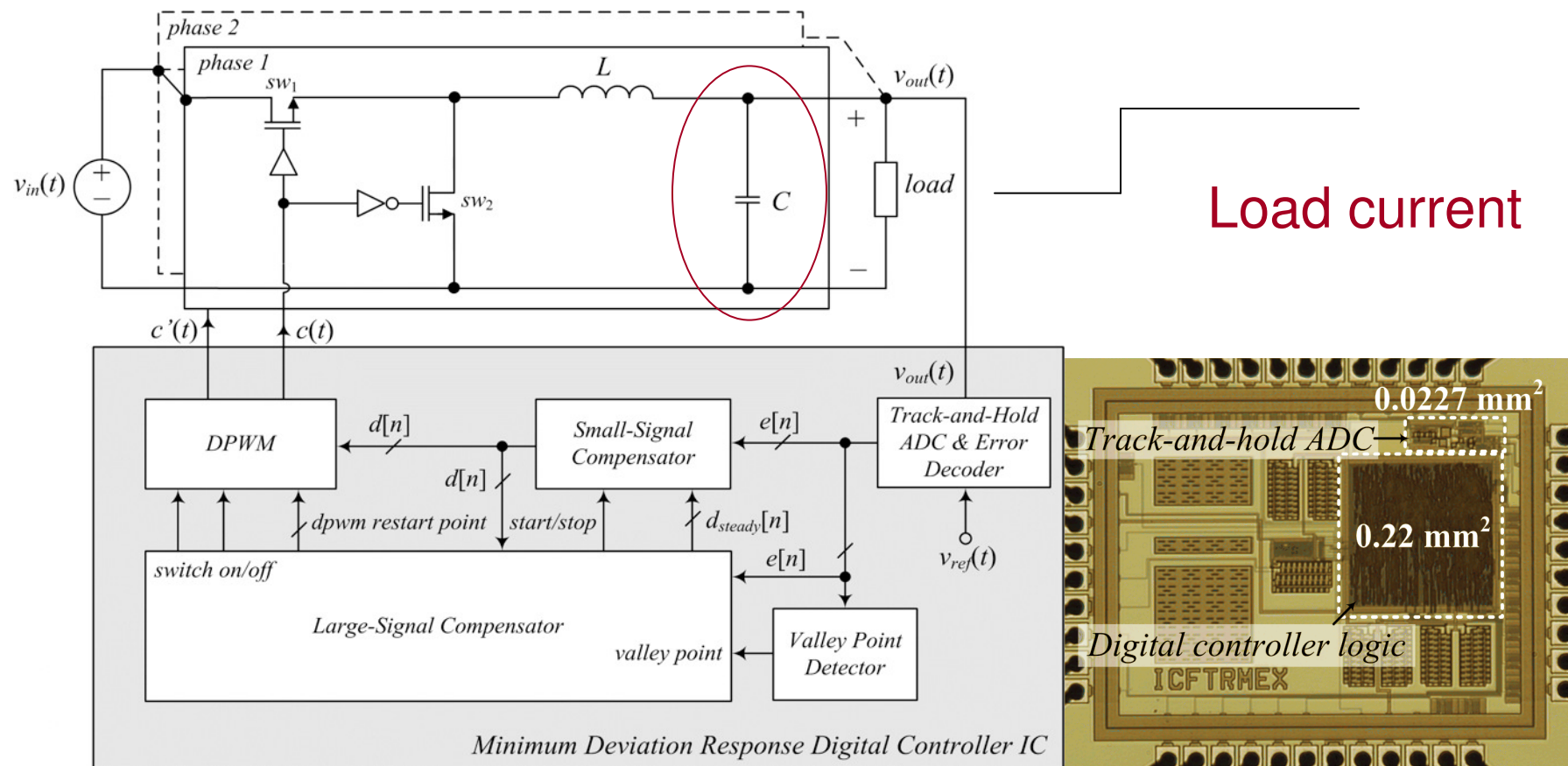


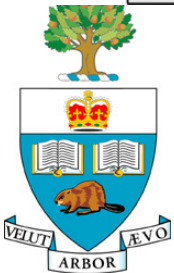[2] A. Radic, Z. Lukic, A. Prodic, and R. de Nie, "Minimum Deviation Digital Controller IC for DC-DC Switch-Mode Power Supplies," IEEE Transactions on Power Electronics, Vol.28, Issue.2, February 2013.







# Conventional Controller Design

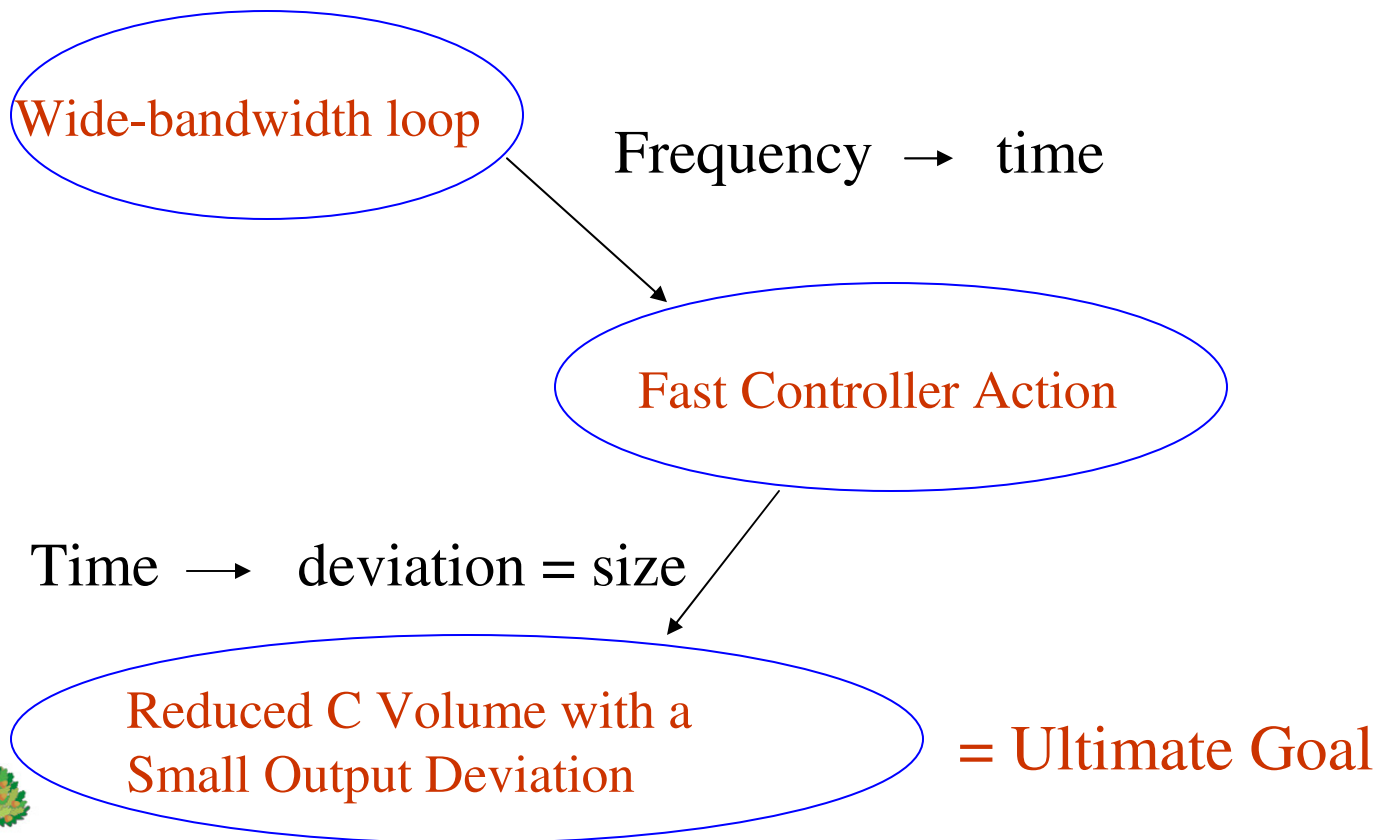

## Time-Optimal Controller

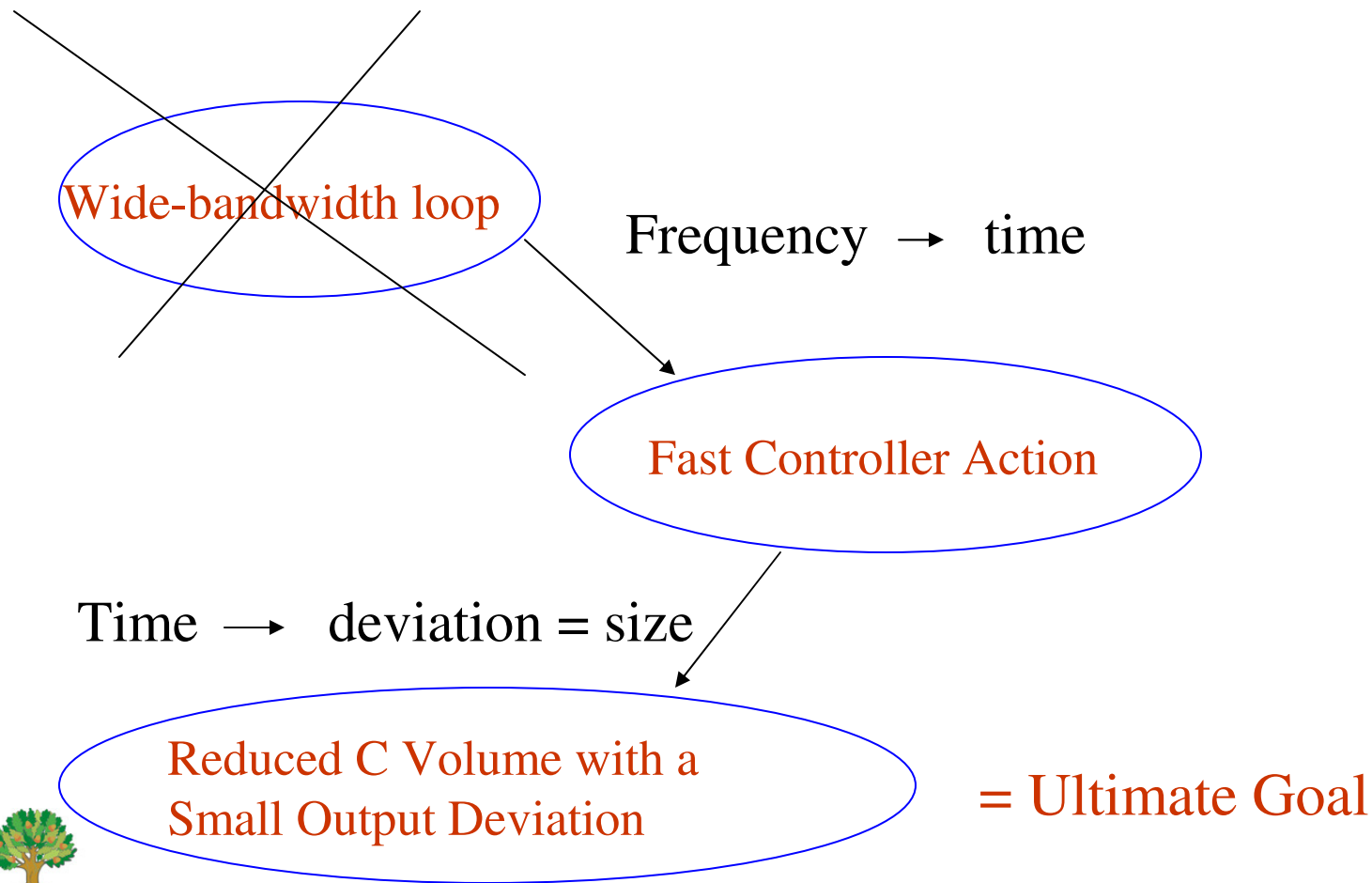

# Time-Optimal Control

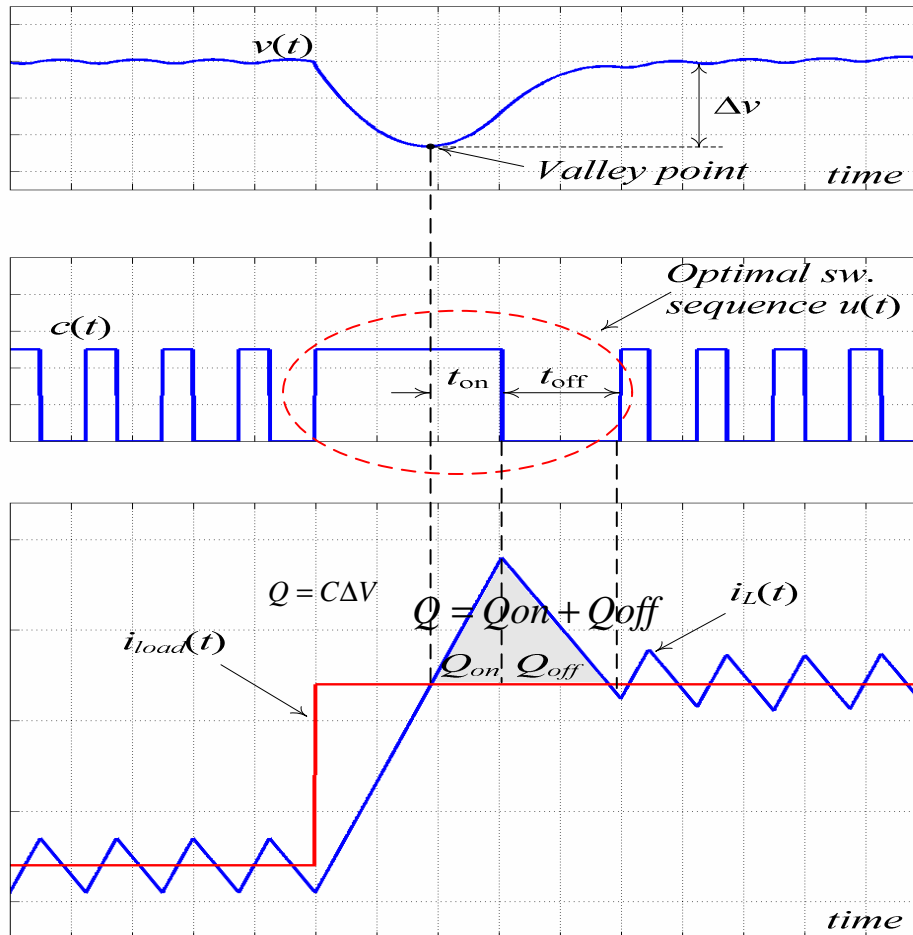

❑ Overly large peak inductor current, i.e. inductor might need to be oversized


❑ Fairly complex calculations

❑ Need to know LC values


❑ Very sensitive to time delays



# Minimum Deviation Controller

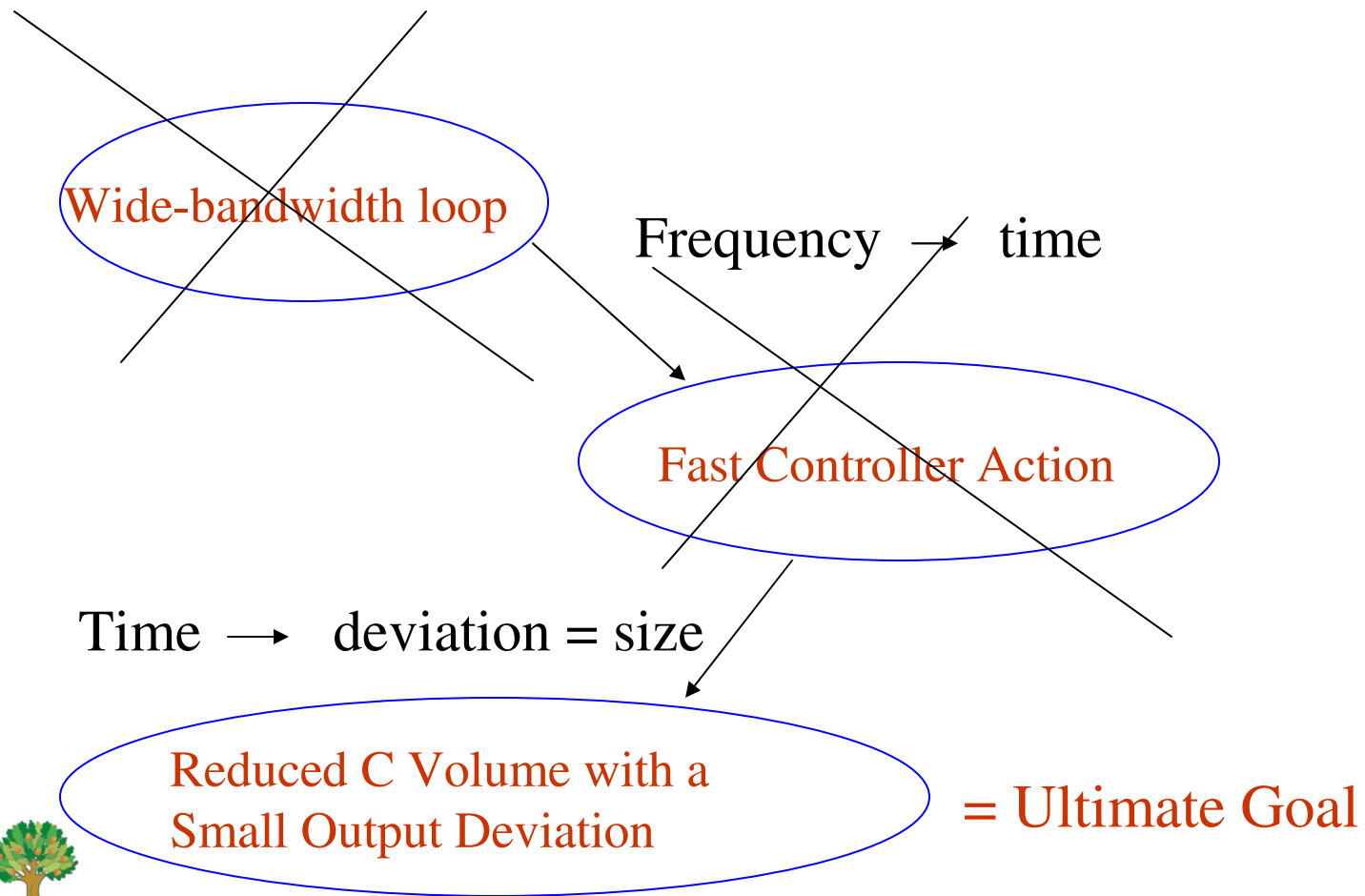
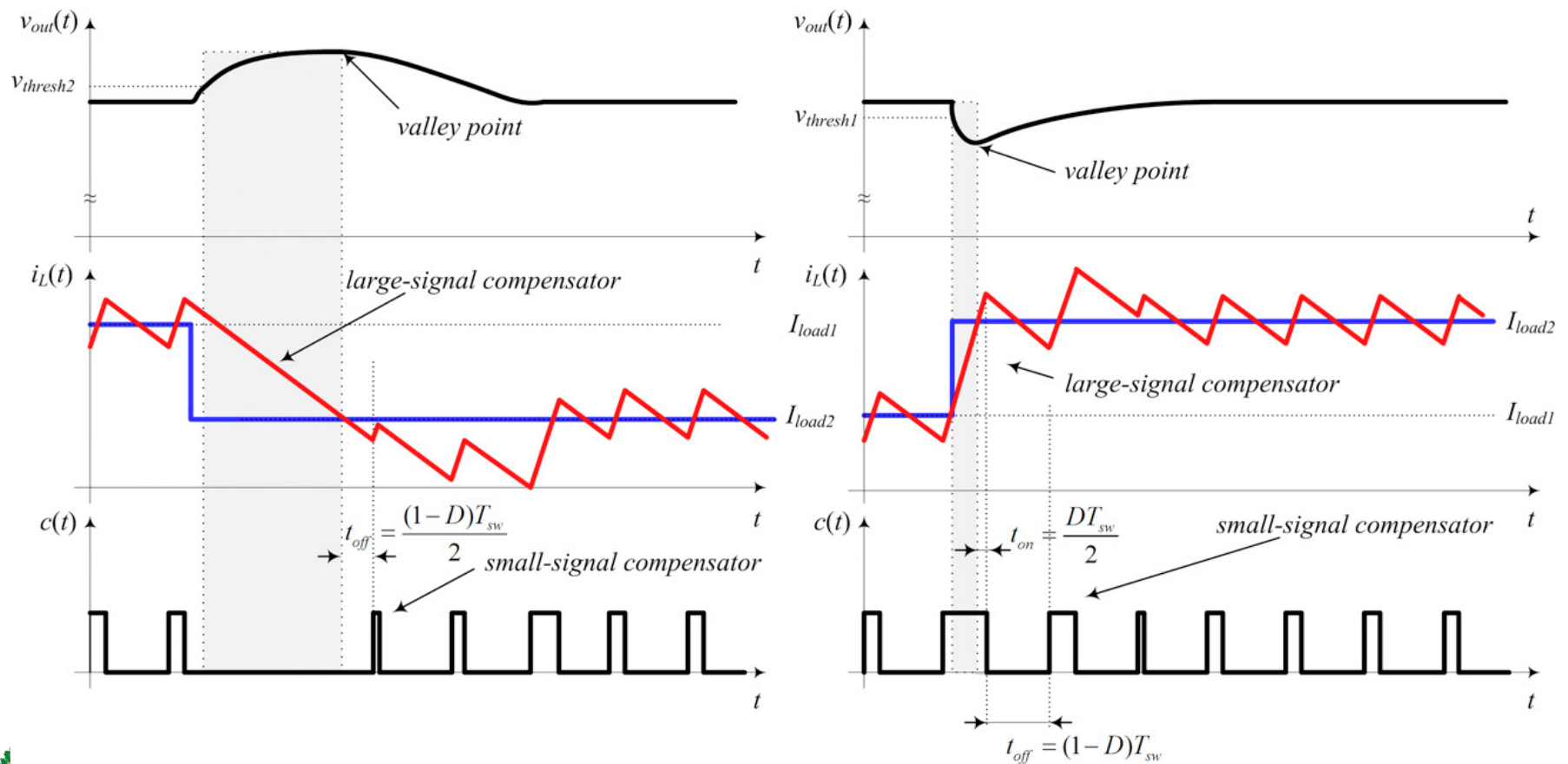
## Minimum (Optimum) Deviation Controller




- No current overshoot, no need to know converter parameters, simple calculations





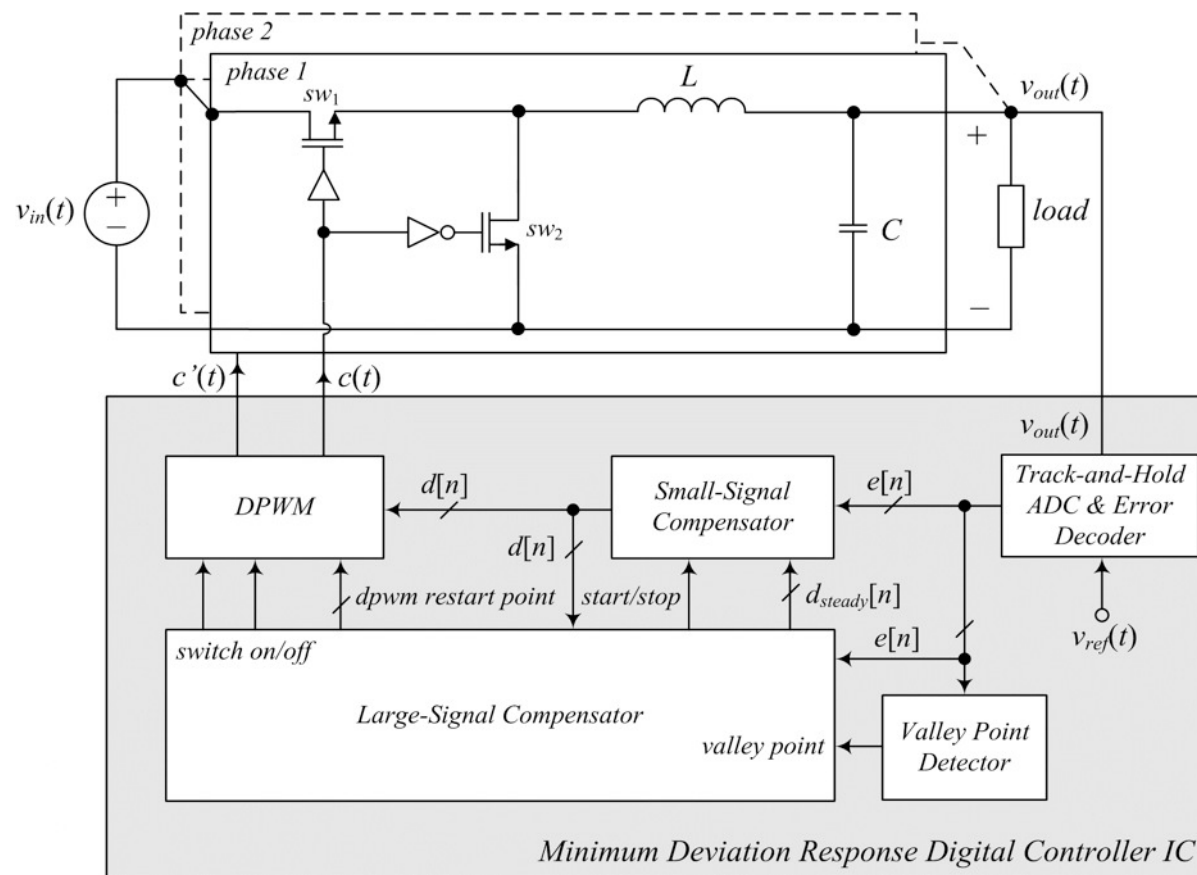
## Minimum (Optimum) Deviation Controller




□ Only needs to remember  $D$  before transient




# Self-Calibrating SAR Track & Hold ADC

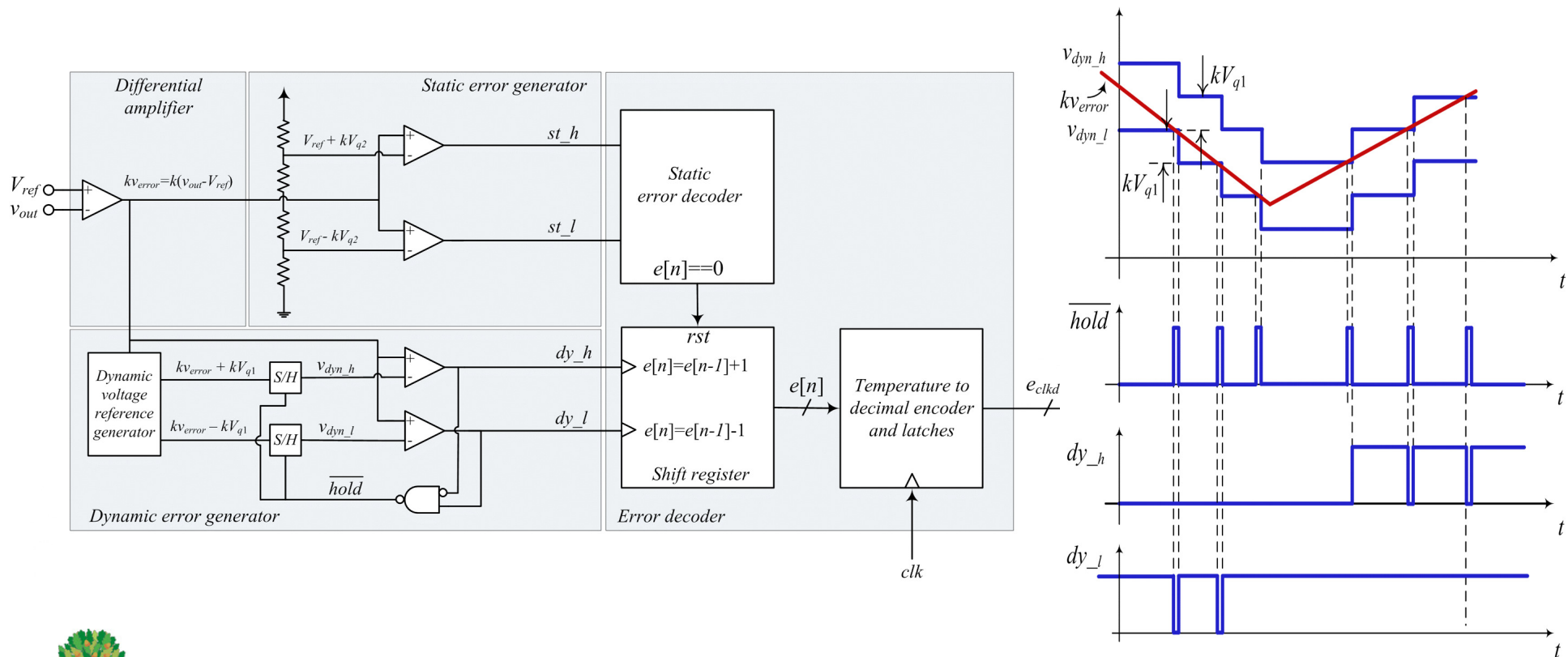

## Dual Sampling Mechanism

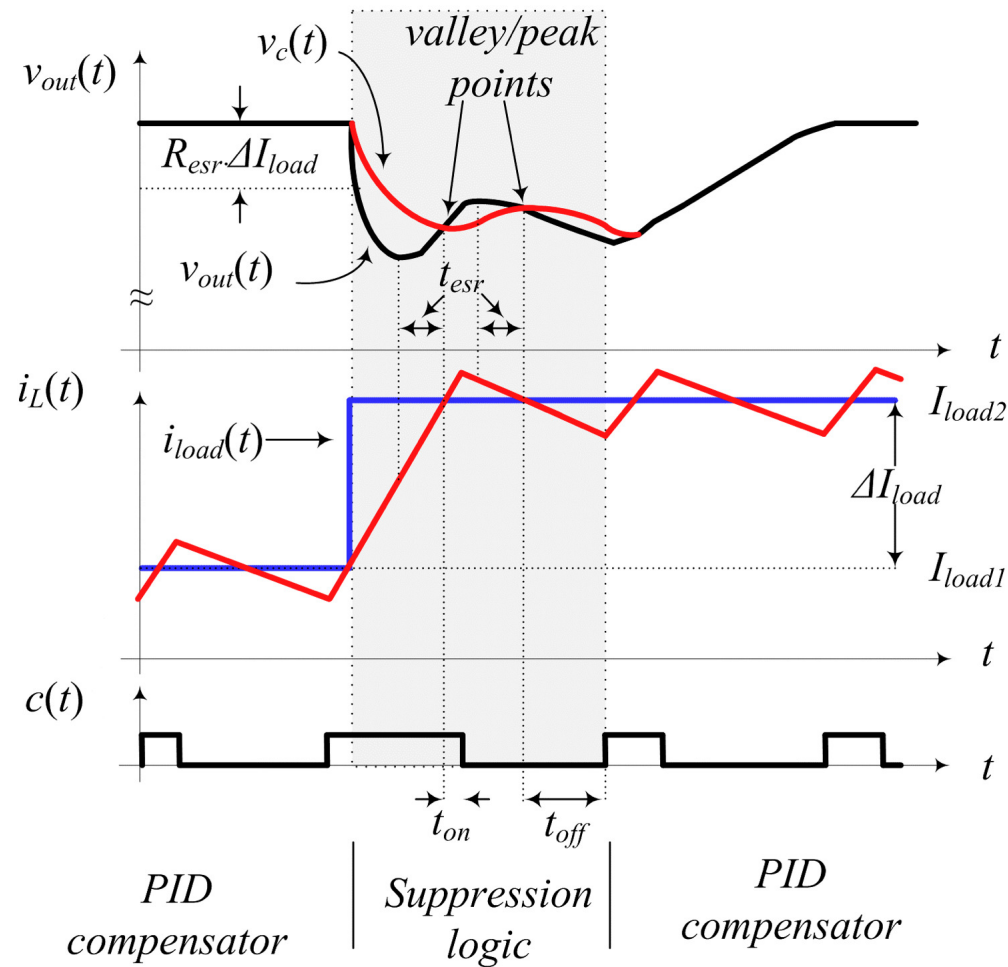

# Practical Implementation (500 kHz VRM)


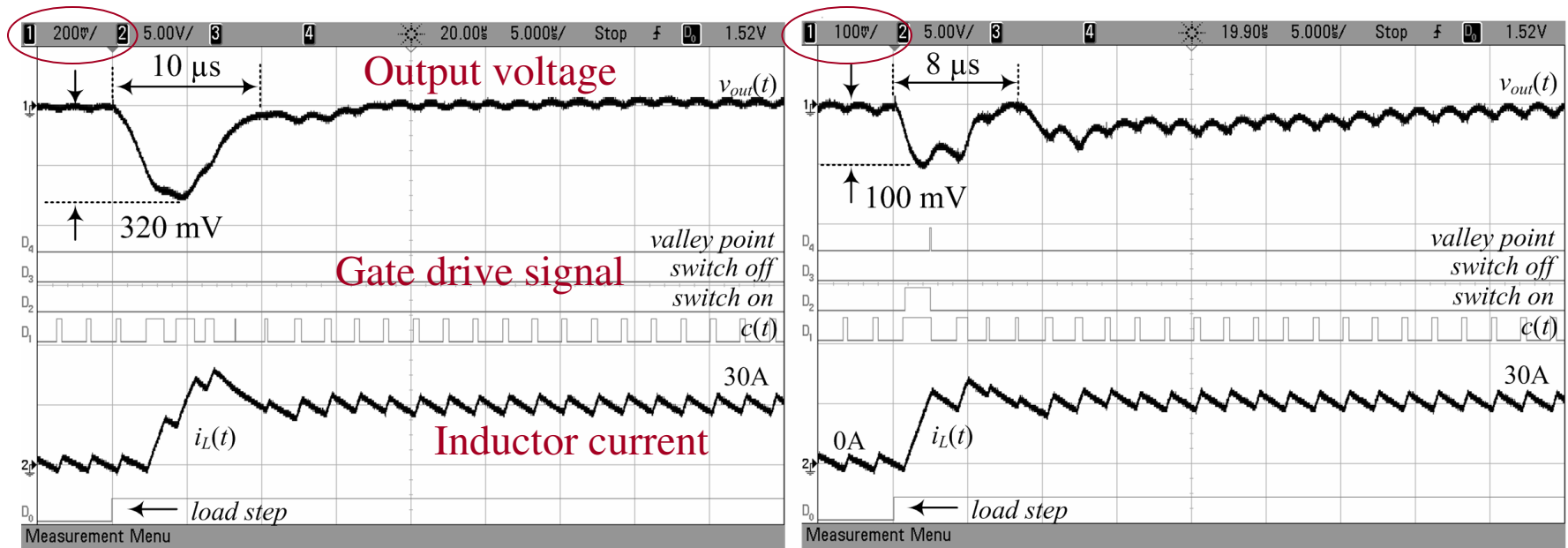


↑  
Fast PID

↑  
Optimum Deviation



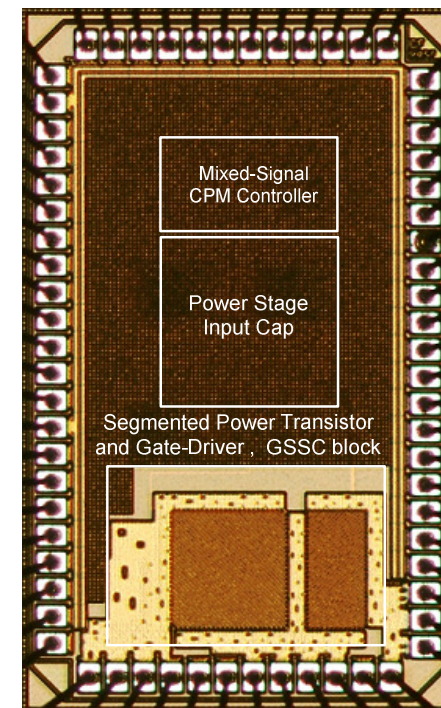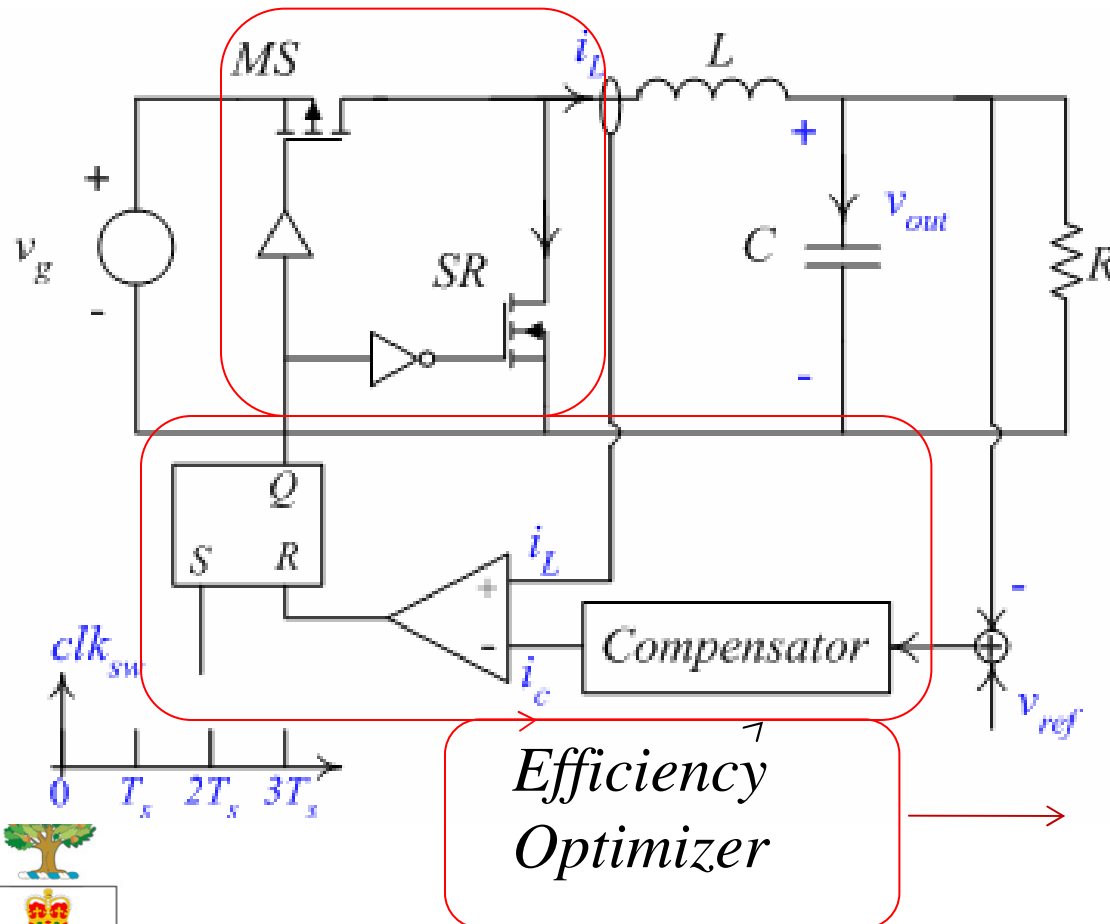
# 10 MHz Mixed Signal CPM Power Module with Instantaneous Efficiency Optimization [3]



[3] A. Parayandeh, B. Mahdavi-khah, S.M. Ahsanuzzaman, A. Radic, A. Prodic, "A 10 MHz mixed-signal CPM controlled DC-DC converter IC with novel gate swing circuit and instantaneous efficiency optimization," in Proc. IEEE ECCE, 2011, Pg. 1229-1235



*Incorporates:*

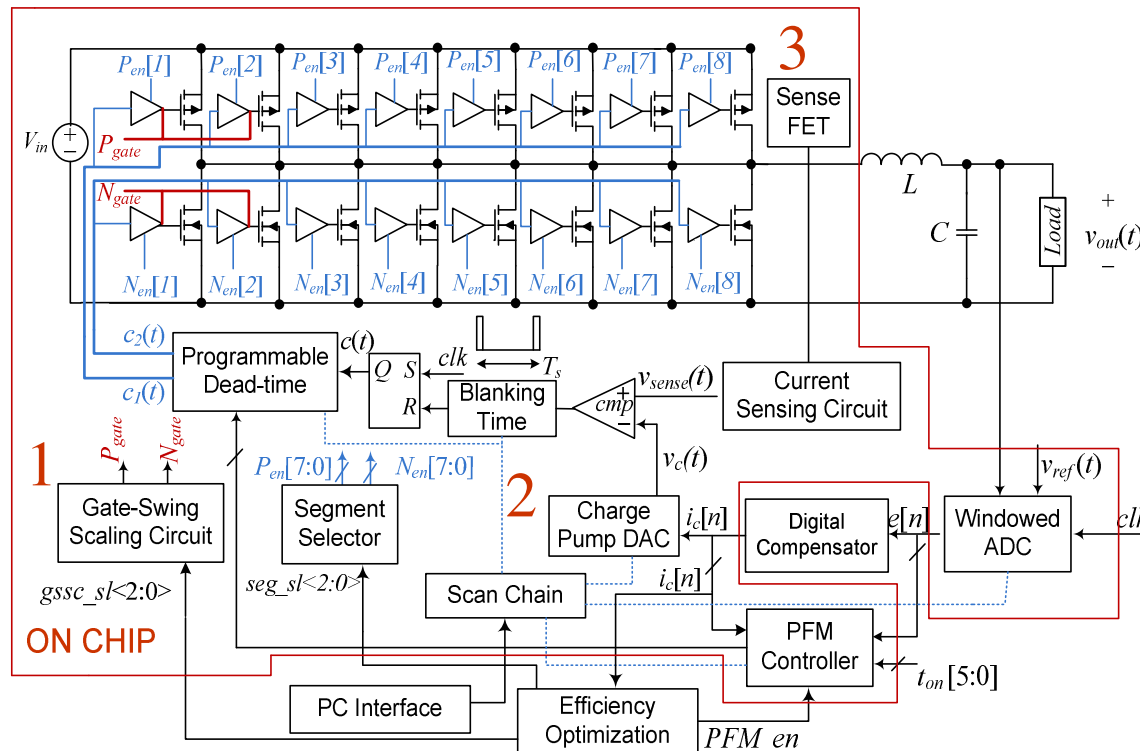


## 2. Modified high-resolution charge-pump based DAC

### 3. Optimized design of current sensing circuit (senseFET)




## Low-Power High-Frequency SensFET

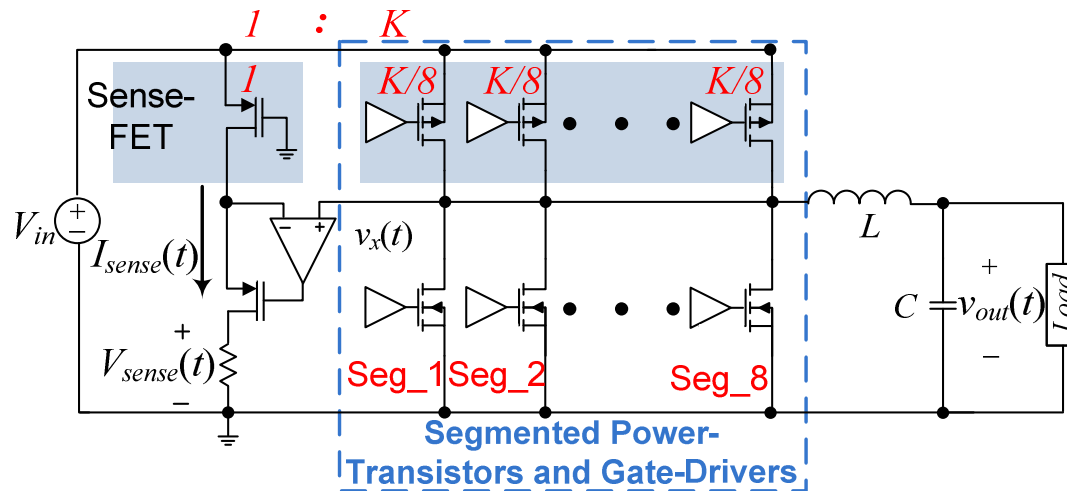

*GBW reduced since the amplitude is always relatively large (but not the losses)*




# IC-Implementation

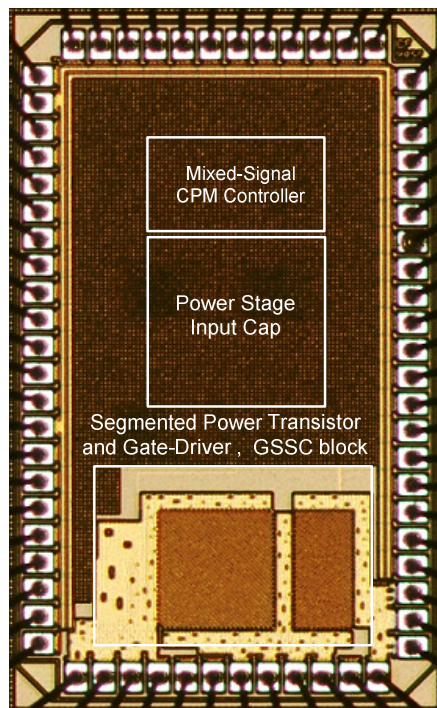


Specifications	Value	Units
CMOS Process	0.13	$\mu\text{m}$
Area	2.5	$\text{mm}^2$
Input Voltage	2.5	V
Output Voltage	0.8-1.3	V
Rated Load	500	mA
Filter L,C	400, 0.9	nH, $\mu\text{F}$
Switching Frequency ,	10	MHz
Ron Pmos , Nmos	0.26 , 0.234	$\Omega$
Supply Analog , Digital	1.2, 2.5	V
Peak Efficiency	83	%
CPM Controller Current	500	$\mu\text{A}$
PFM Controller Current	10	$\mu\text{A}$
Digital Core	200	$\mu\text{A}$



## Experimental Results

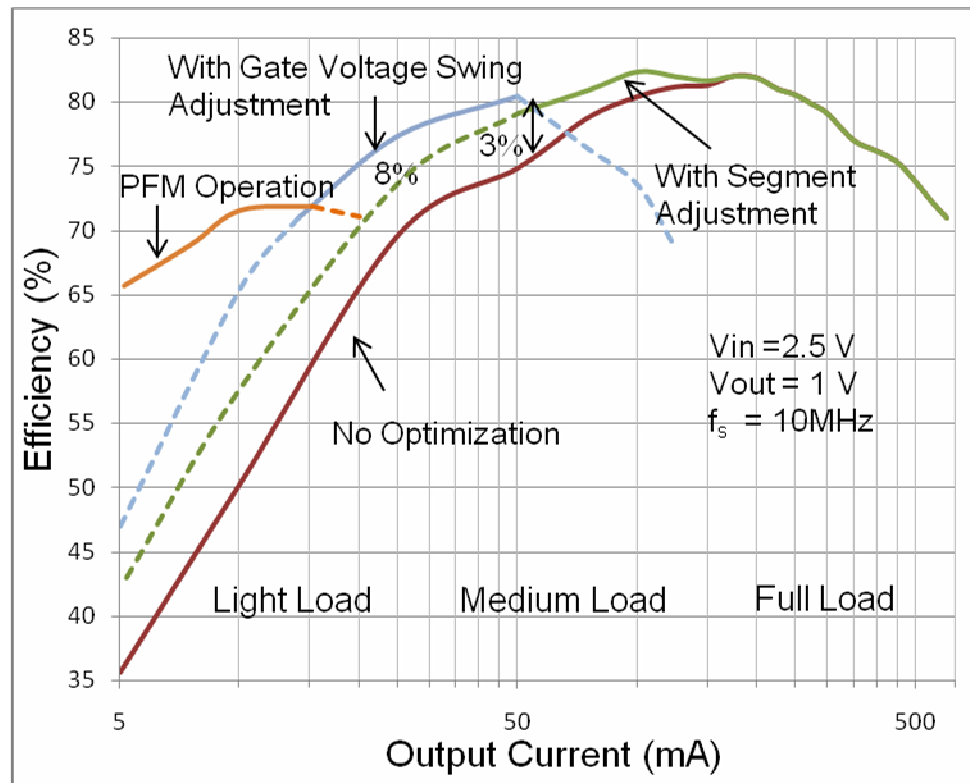
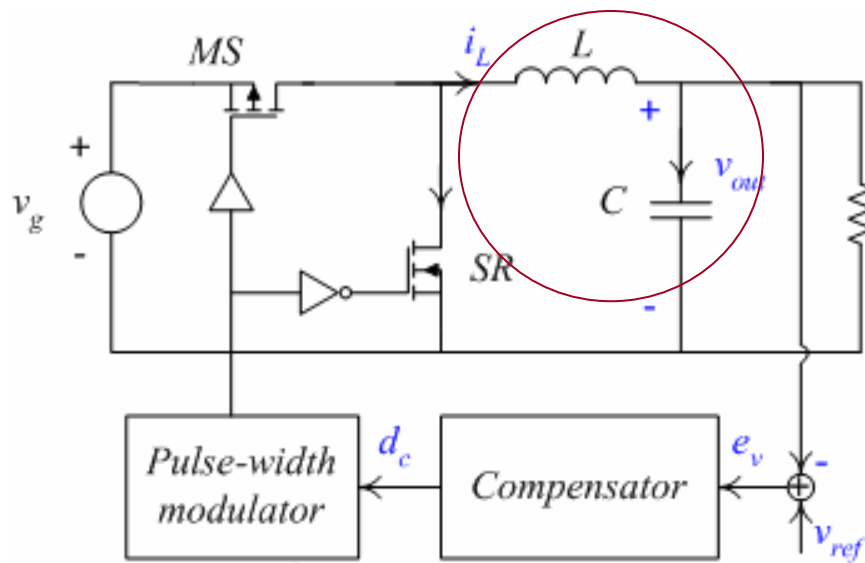
## Reaching the Physical Limitations Through Hardware-Efficient Mixed-Signal ICs



Load current

- ✓ High-frequency of operation
- ✓ Optimal response with plug and play operation
- ✓ Relatively flat efficiency curve even during load changes






# **Moving Forward**

## *Advanced Low-Volume SMPS Topologies*



## Moving Forward

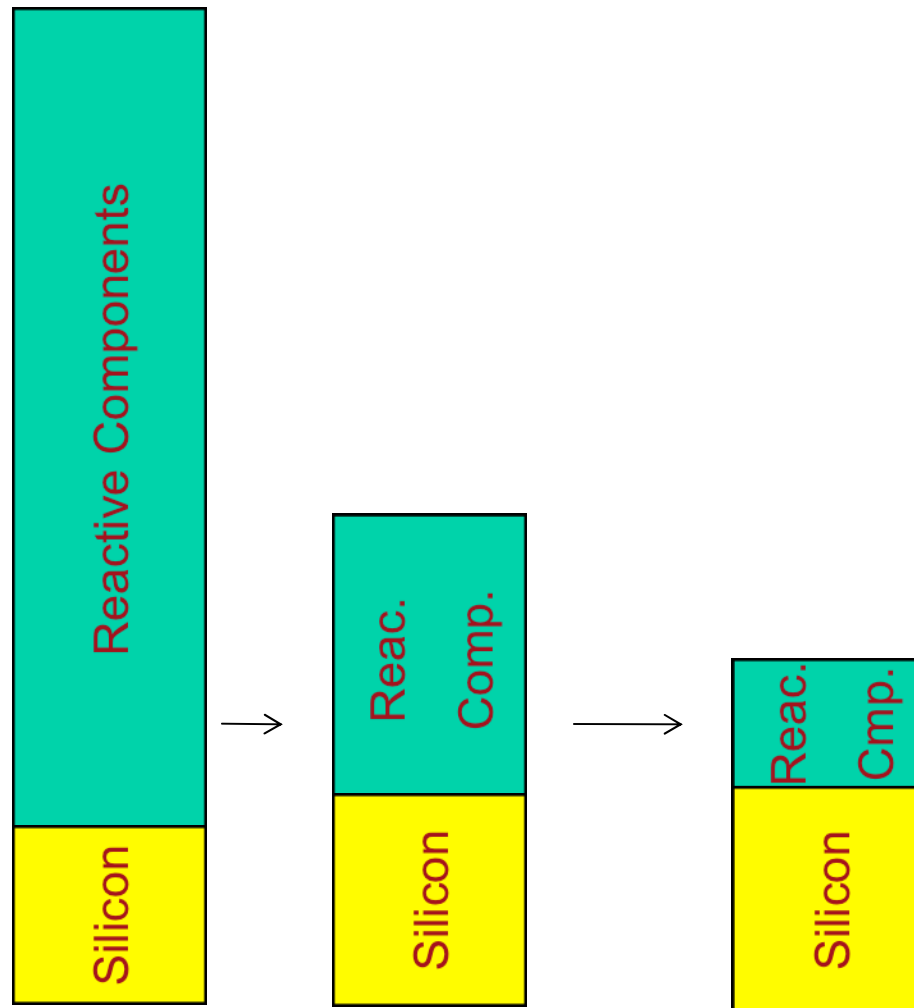

Overall volume (weight) contribution

- ❑ Reduce volume of reactive components through advanced converter and control topologies
- ❑ Allow weight (cost) distribution where the silicon are will be larger than today but the overall volume smaller
- ❑ No penalty in efficiency




## Flyback Transformer Based Buck (FTBB) with Transient Energy Recycling [4]



[4] Jing Wang; Prodić, A.; Wai Tung Ng, "Mixed-Signal-Controlled Flyback-Transformer-Based Buck Converter With Improved Dynamic Performance and Transient Energy Recycling," IEEE Transactions on Power Electronics, Vol. 28, Issue. 3, February 2013.

University of Toronto, Rogers ECE Department

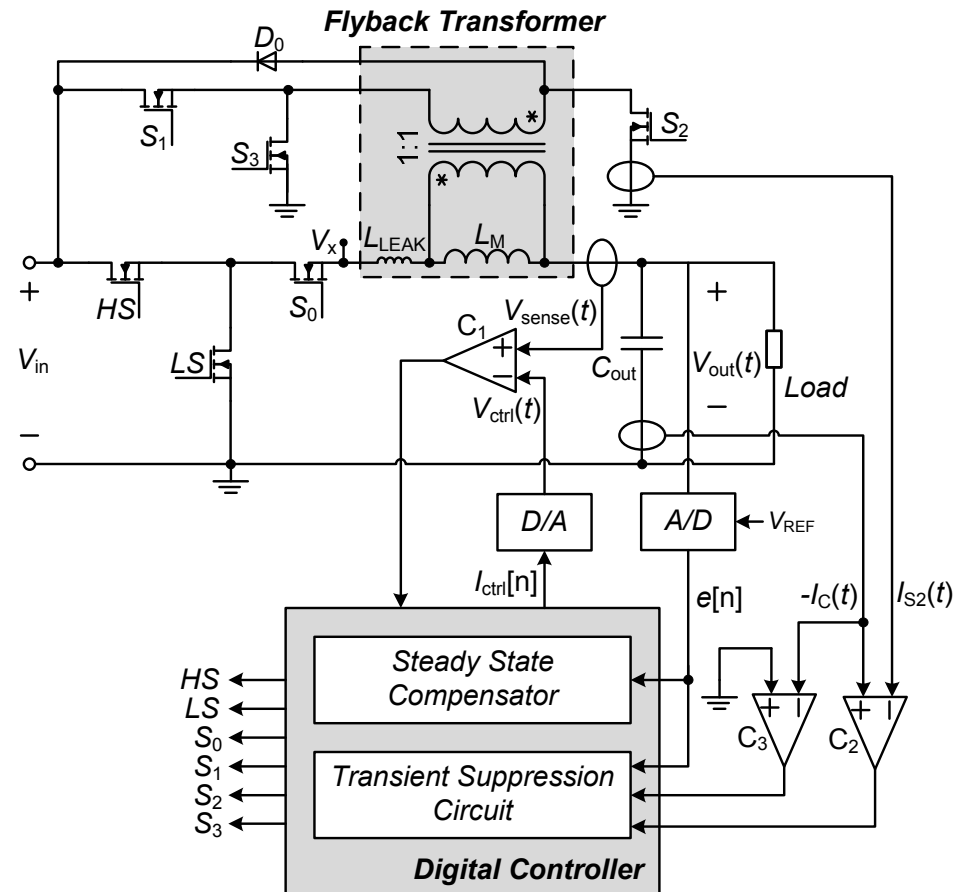
# Flyback Transformer Based Buck with Transient Energy Recycling



The buck inductor is replaced with a flyback transformer, and a single extra switch inside the conduction path




## FTBB – Principle of Operation

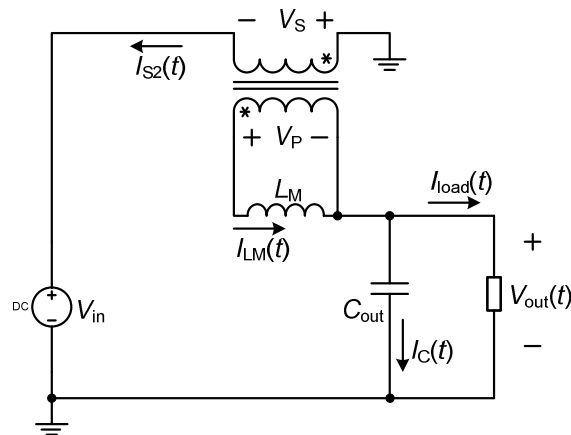

Current slew rate of magnetizing inductance is  $-V_g/L_m$  rather than  $-V_{out}/L_m$

*Also, the transient energy is recycled back to the source – two fold effect*

*Heavy-to-light*

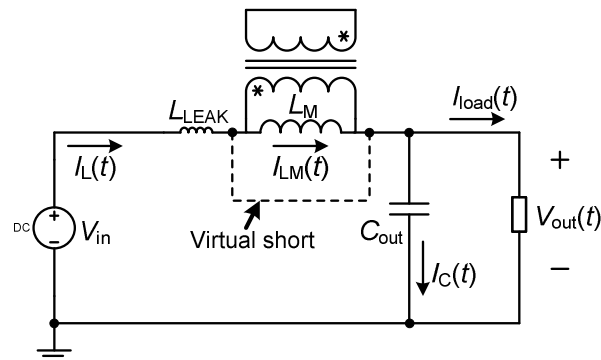




The inductance is reduced to its leakage value

*Light-to-heavy*




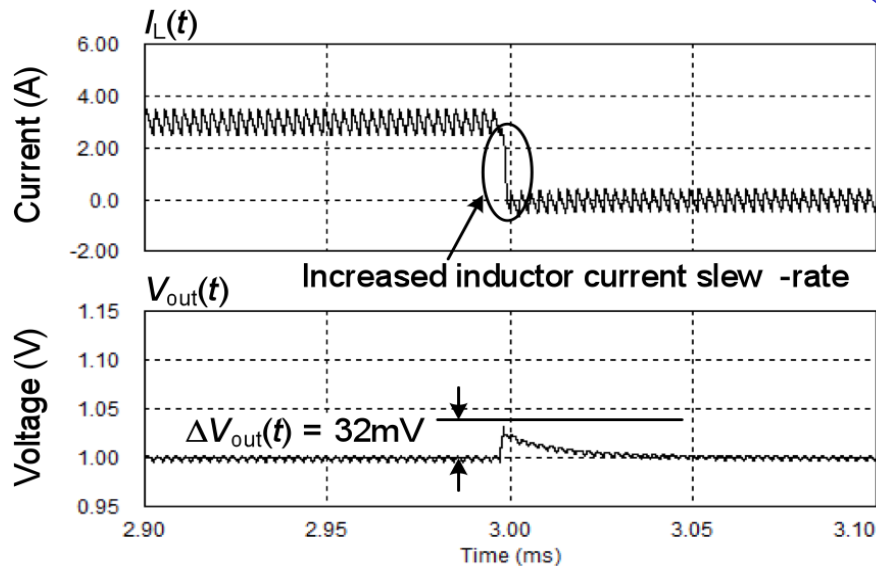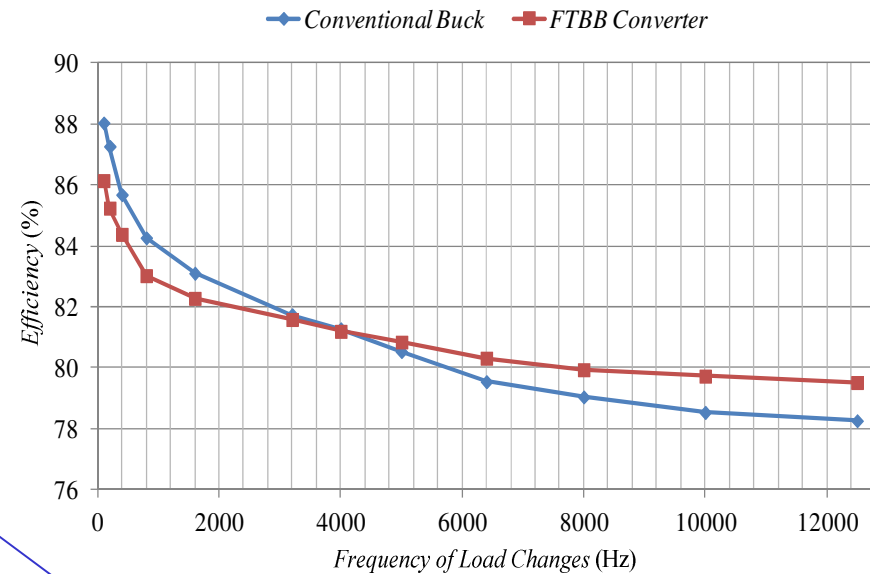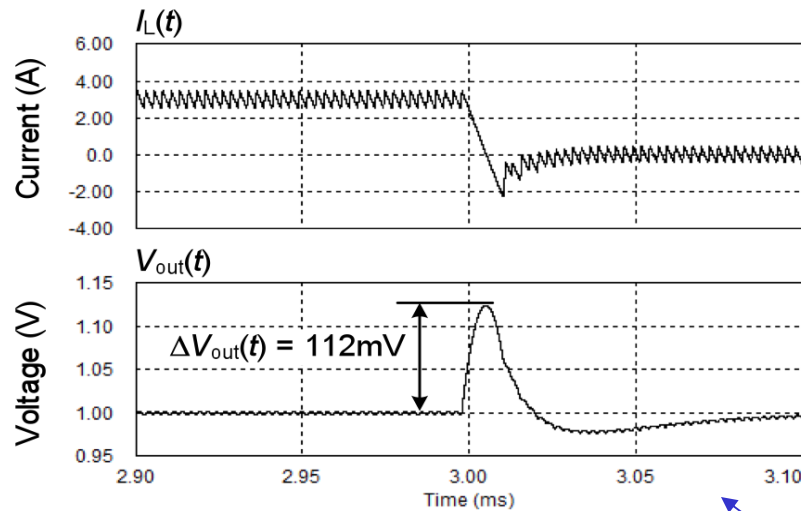
## Conventional Minimum-Deviation vs. FTBB



Conventional buck


FTBB converter

# Load-Interactive Steered-Inductor DC-DC Converter with Transient Energy Recycling <sup>[5]</sup>



[5] S.M. Ahsanuzzaman, A. Parayandeh, A. Prodic, D. Maksimovic, “Load-interactive steered-inductor dc-dc converter with minimized output filter capacitance,” in Proc. IEEE Applied Power Electronics Conference (APEC '10), 2010, Pg. 980-985.

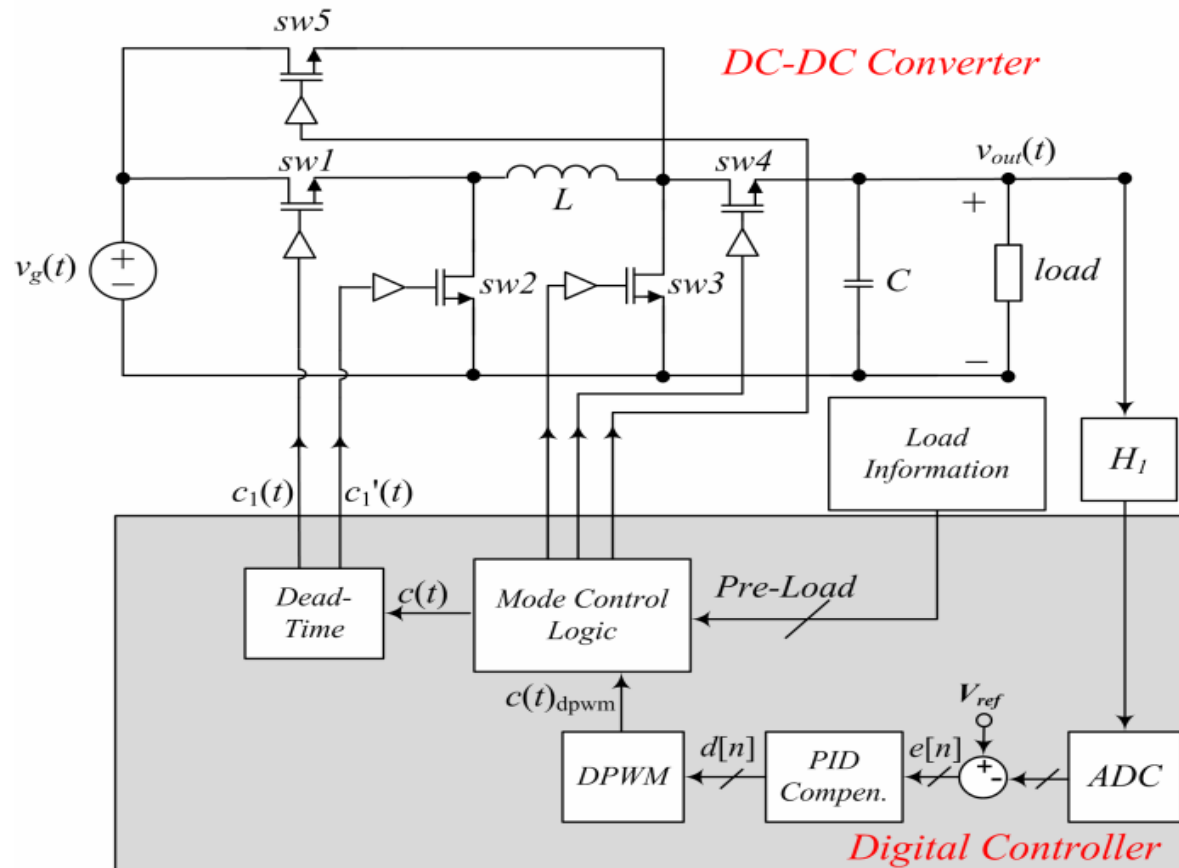
## Load Interactive SMPS with Current Steering




- Relies on improved interaction with the digital load
- Theoretically, allows selection of the output capacitor based on the output ripple criteria only.



## Steered Inductor Buck-Boost Converter

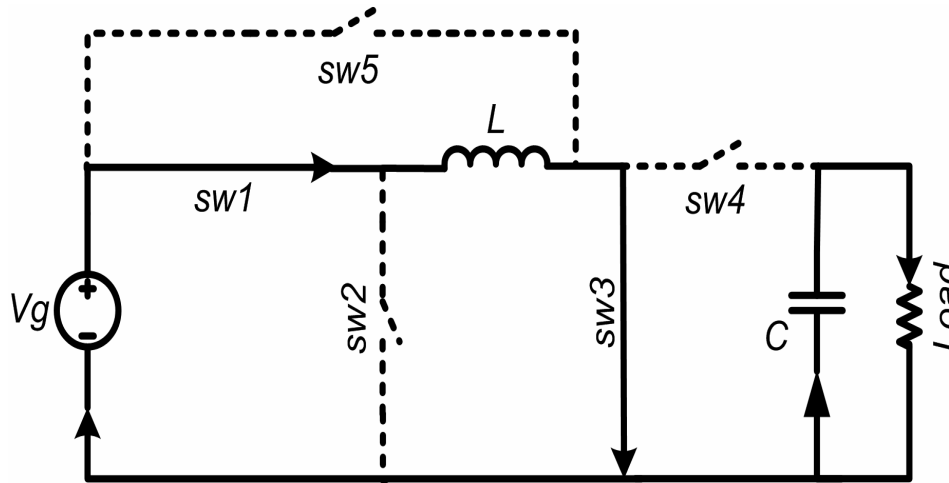


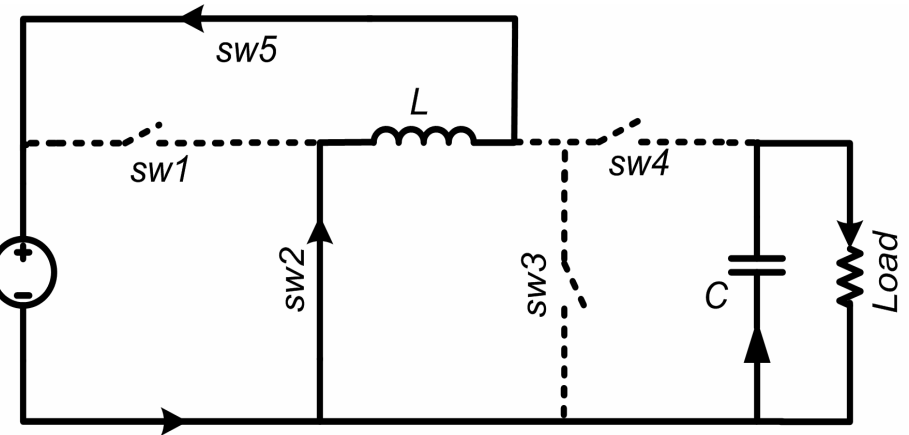
- Light-to heavy pre-transient condition current “pump-up”
- Slew rate is  $V_g/L$  vs  $(V_g - V_{out})/L$



- Heavy-to-light transient ,the current is steered away from the capacitor to the source)
- The current slew-rate is  $-V_g/L$  (was  $-V_{out}/L$  in buck mode)
- Energy recycled in this cycle



## Load Transient Performance

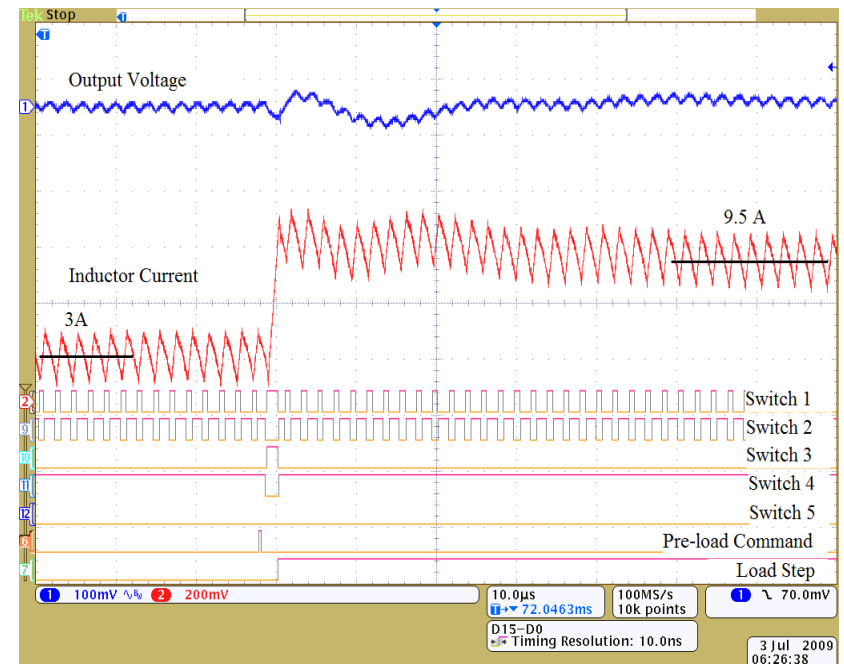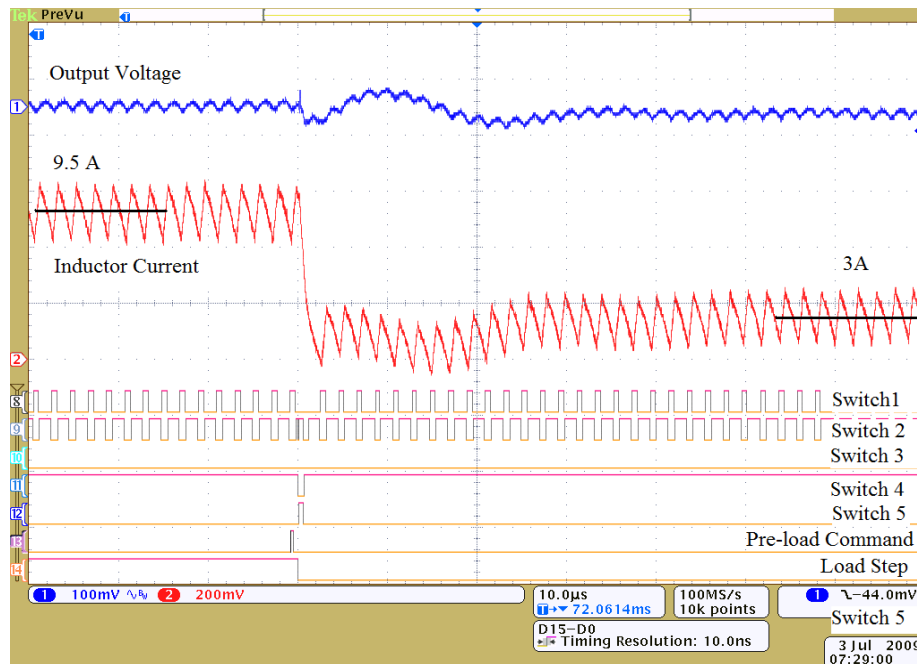

Theoretically, allows reduction of the output capacitor to ripple-limited value




## Buck Converter with Merged Capacitive Attenuator <sup>[6]</sup>



[6] A. Radic, A. Prodic, “Buck Converter With Merged Active Charge-Controlled Capacitive Attenuation,” IEEE Transactions on Power Electronics, Vol. 27, Issue. 3, March 2012.

University of Toronto, Rogers ECE Department
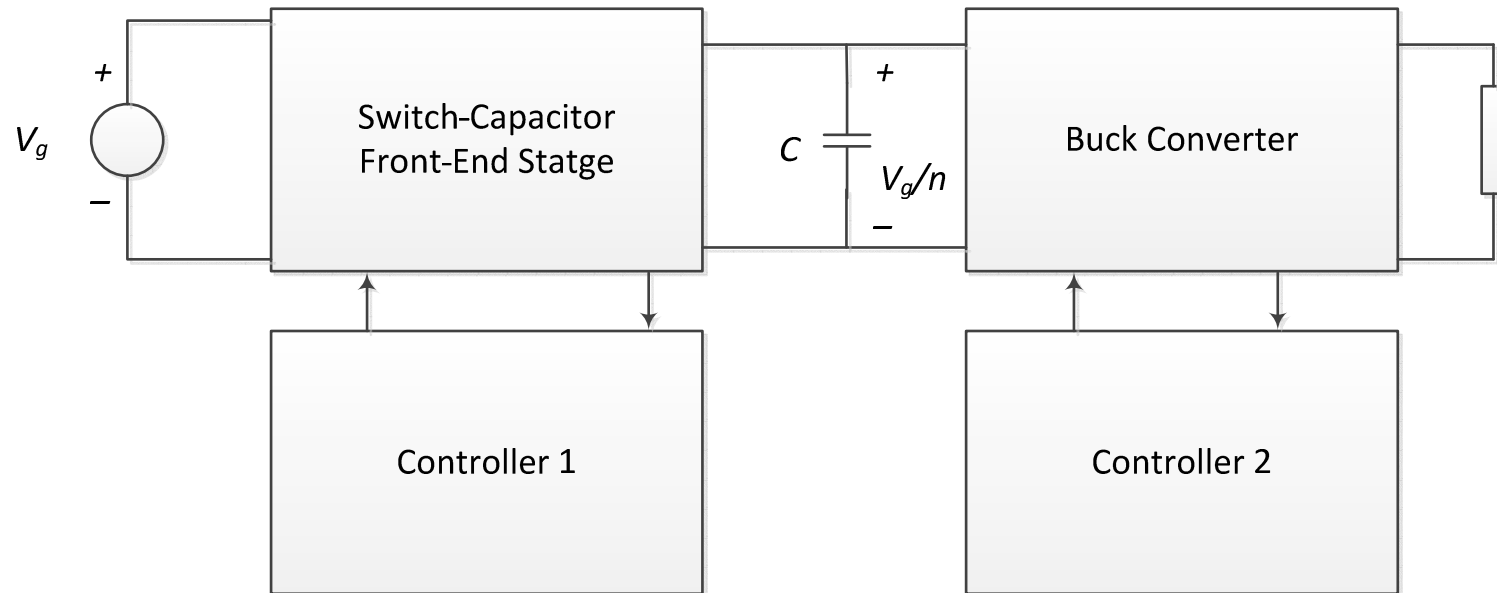
## Common Approach: Serial Connection of a Switch Cap Converter And a Converter with Inductor



*1. Reduced output filter volume*

*1. Bulky intermediate balancing cap*


*2. Extra switches in conduction path (at least 4) and at least 6 switches total*

*3. Requires two control loops*




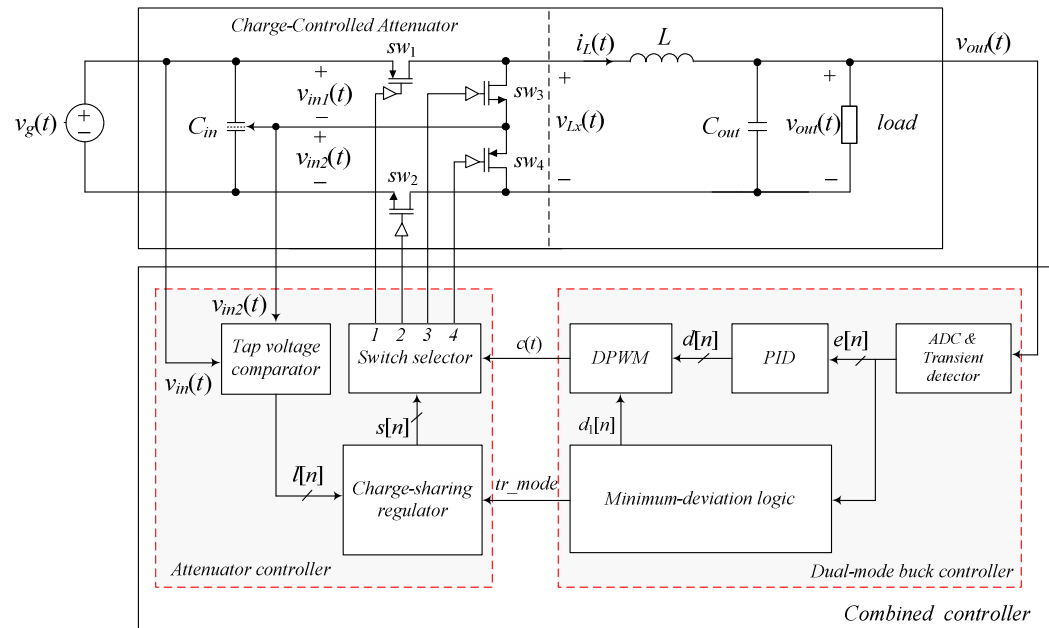
# Buck Converter with Merged Capacitive Attenuator



-All switches rated at  $\frac{1}{2} V_{max}$  of the conventional buck (no extra conduction losses)

-Switches are shared between the cap stage and buck



-Lower switching losses than of the conventional buck

-Centre tap voltage maintained constant with the help of buck inductor

- Better transient response than the time-optimal buck



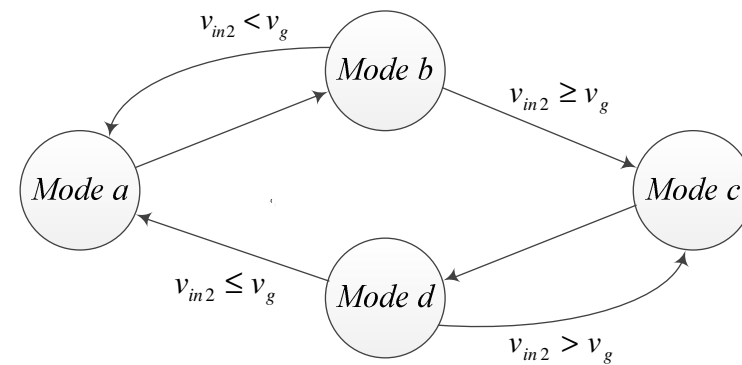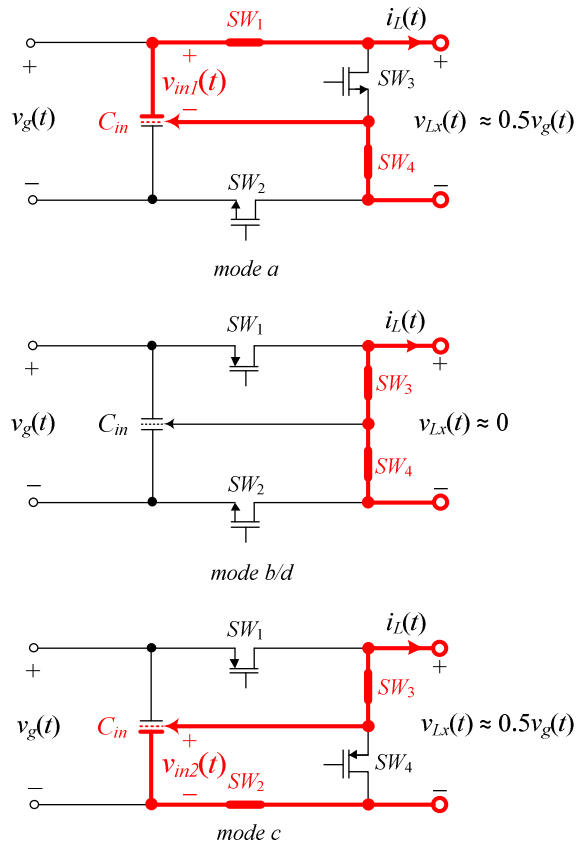
# Modes of Operation, Ideal and Practical System



*Centre-tap voltage controller operation. Skips regular sequence and takes the charge from the cap with larger voltage until balance is achieved.*




## Transient Mode

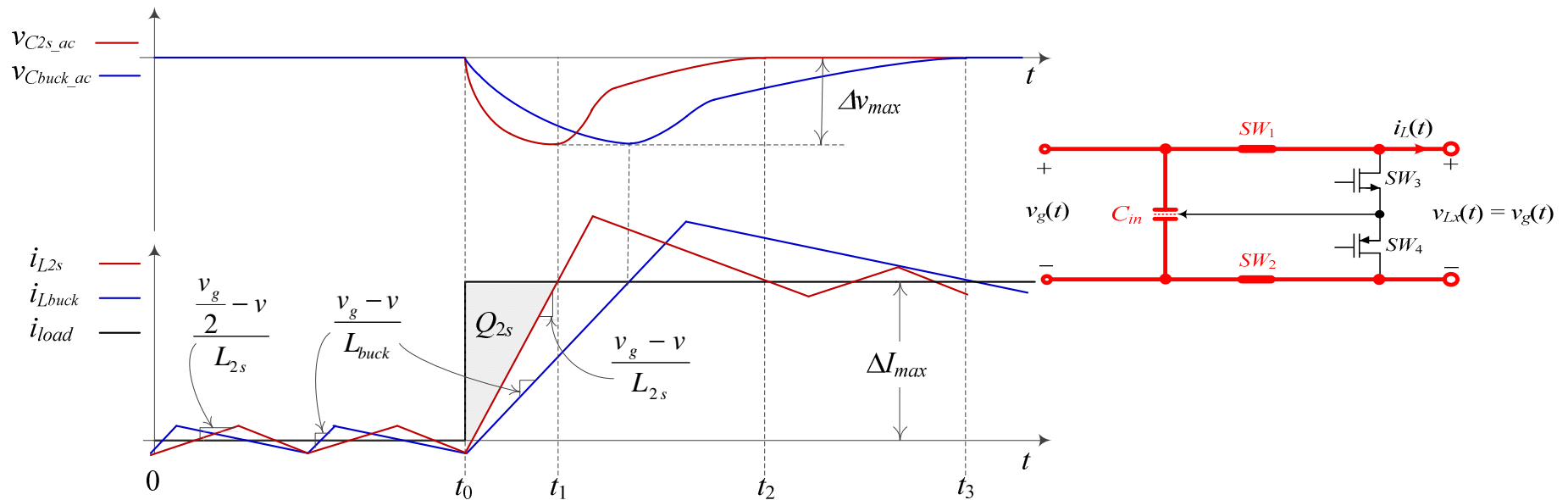

*Comparison with a conventional buck*




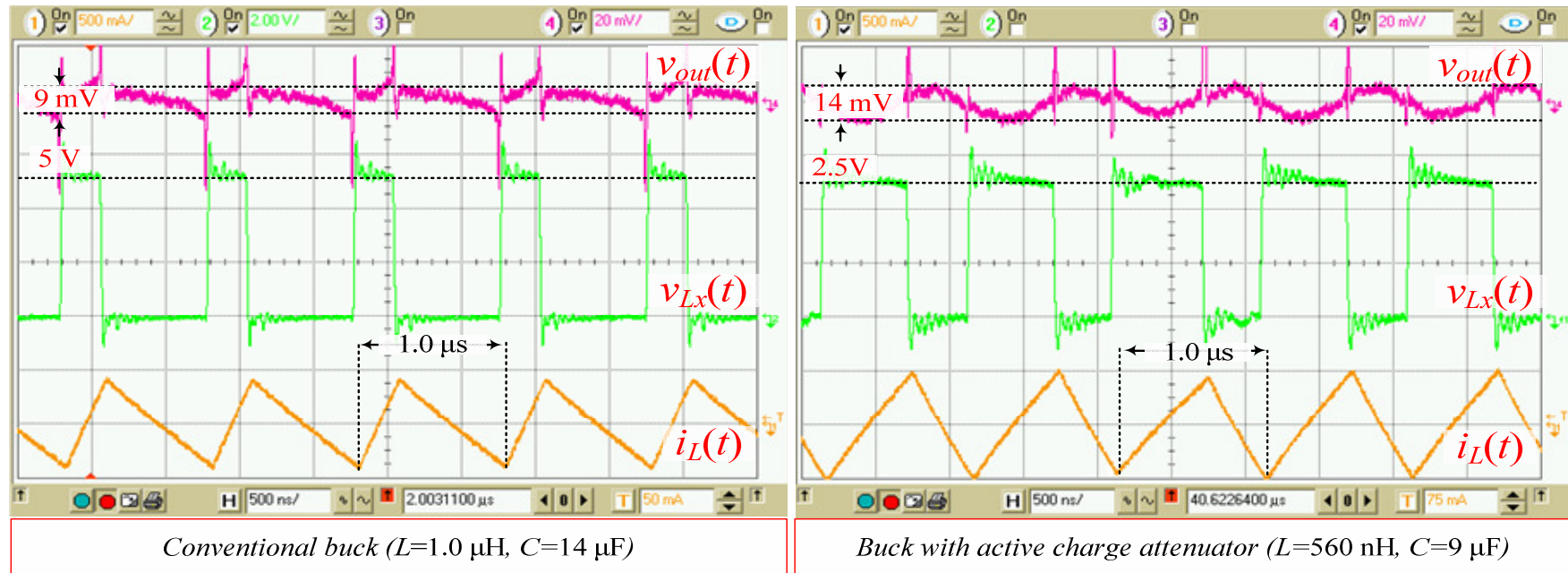
## Experimental Results: Comparison with Conv. Buck



*For a 5V to 1 V buck 44% smaller inductor and 35% smaller output capacitor*



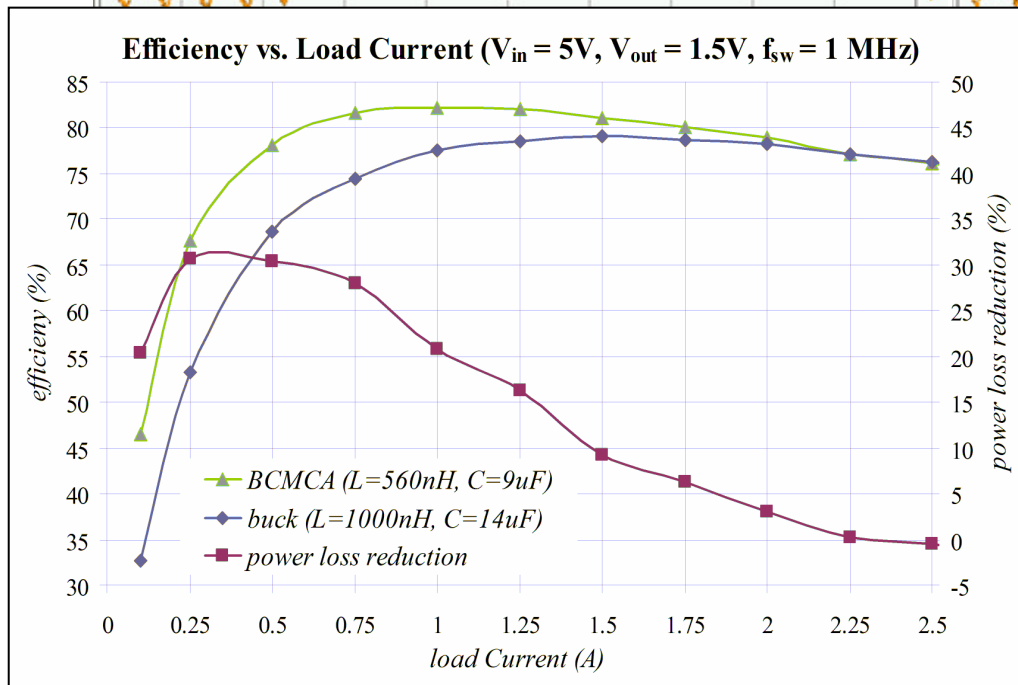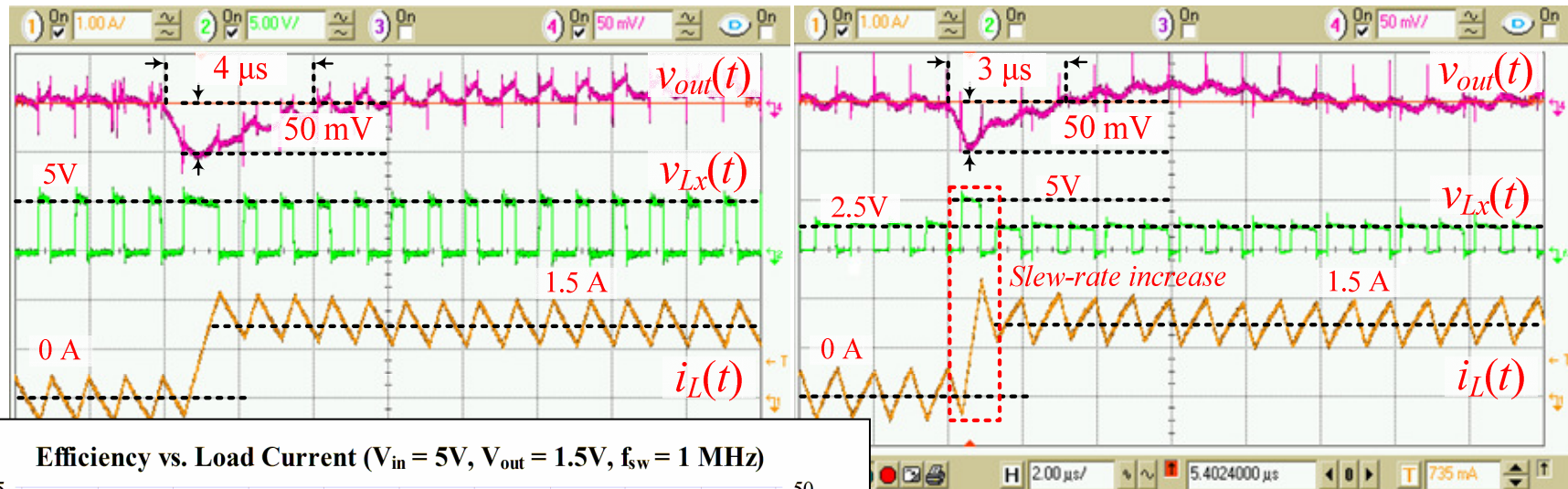
## Experimental Results: Comparison with Con. Buck



*Both transient response and efficiency improved*

## Extension to 2-Phase [7]

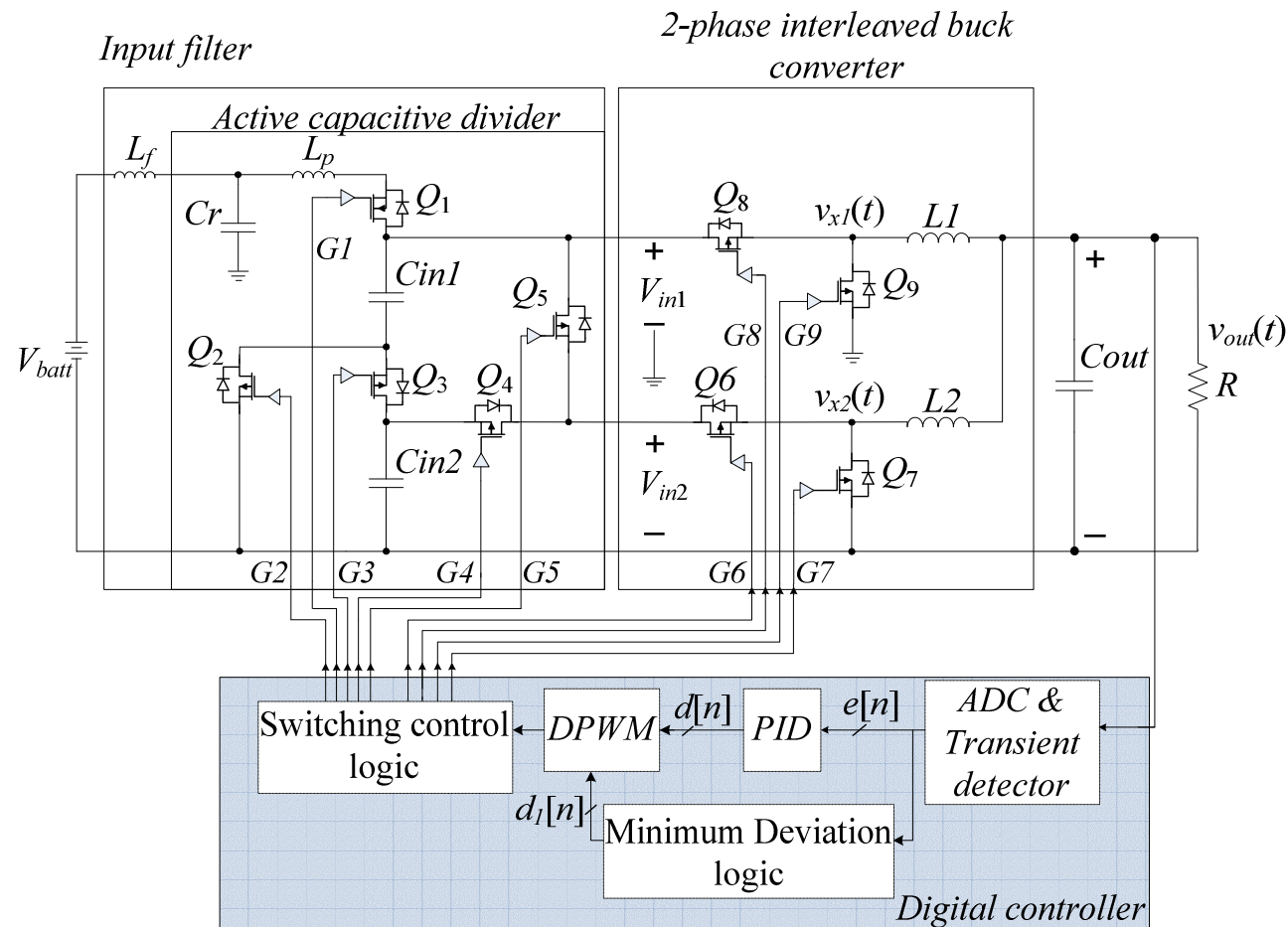

$L_1$  takes the charge from the top inductor and  $L_2$  from the bottom

[7] B. Mahdavihah, P. Jain, A. Prodic, "Digitally controlled multi-phase buck-converter with merged capacitive attenuator," Applied Power Electronics Conference and Exposition (APEC), 2012 Twenty-Seventh Annual IEEE , vol., no., pp.1083-1087, 5-9 Feb. 2012

University of Toronto, Rogers ECE Department



**Many other examples .....**





## Conclusion

*Digital control allows us to use advanced converter topologies and drastically reduce the volume of SMPS while improving efficiency at the same time.*



**Thank you**

