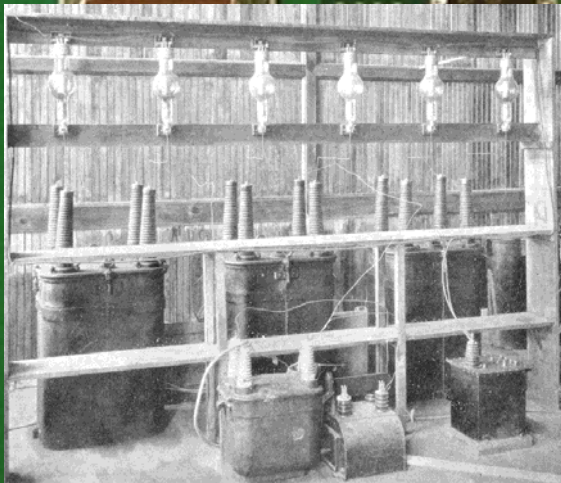


Miniaturized High-Frequency Integrated Power Conversion for Grid Interface

David J. Perreault Seungbum Lim David M. Otten


PowerSoC 2014
6 October 2014, Boston MA



20 kW Kenotron Rectifier, Circa 1926
(From Principles of Rectifier Circuits,
Prince and Vogdes, McGraw Hill 1927)



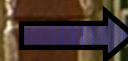Commercial LED Driver
Rectifier, Circa 2012




??

- Investigate the use of greatly increased switching frequencies to miniaturize *low-power, grid-interface* converters
 - HF frequency range, 3-30 MHz, 10-100x conventional
 - LED driver as an example



■ PowerChip Team (ARPA-E ADEPT)



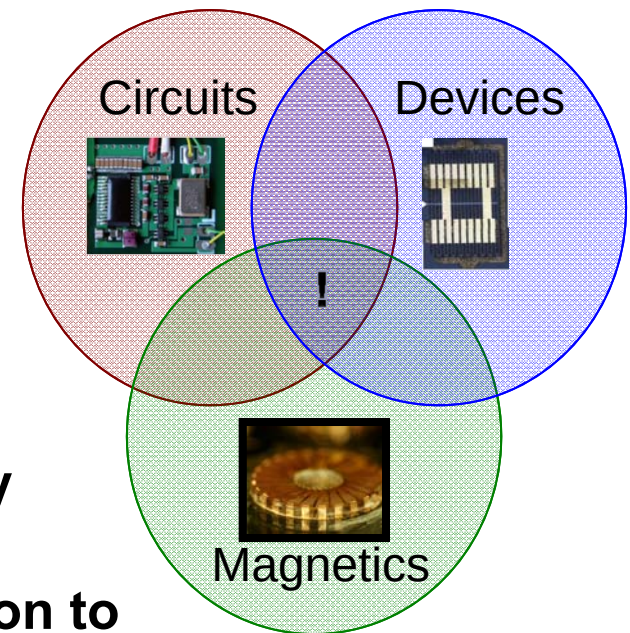- This talk describes:
 1. Application considerations and frequency constraints in this space
 2. System architecture and topology selection to address these considerations and constraints
 3. Design and performance of an experimental prototype demonstrating the proposed approach (Operation at 5-10 MHz at $> 50 \text{ W/in}^3$)




Example: Solid-State Lighting Drivers

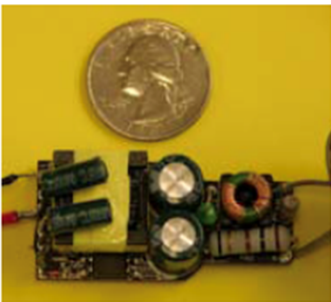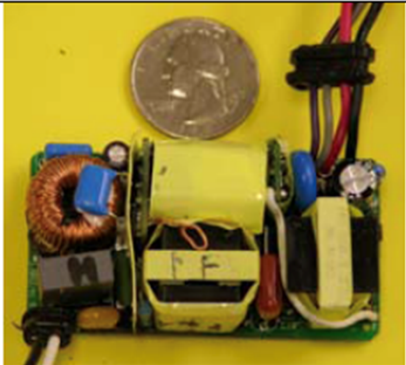Model	Polar-ray 6W		Cooper 1200 Series 24.8 W	
Output power	4.0 W		21.1 W	
Sw. Frequency	57 kHz		100 kHz	
Efficiency	64%		85%	
Converter Volume	1.27 in ³		4.76 in ³	

- **Today: $\eta \sim 60\text{-}90\%$**
- **power density of commercial designs $< 5 \text{ W/in}^3$**
 - ❑ Switching frequencies $< 150 \text{ kHz}$
 - ❑ Largest components are typically magnetic elements (inductors, transformers)
 - ❑ Second largest are usually electrolytic capacitors for twice-line-frequency energy storage
 - ❑ EMI filters also take up significant volume
- **Power factor / line-frequency energy buffering is also an important consideration**
 - ❑ EnergyStar: PF of 0.7 (residential) or 0.9 (commercial) is desired but mostly NOT achieved

■ Goals

- Miniaturization
- Integration

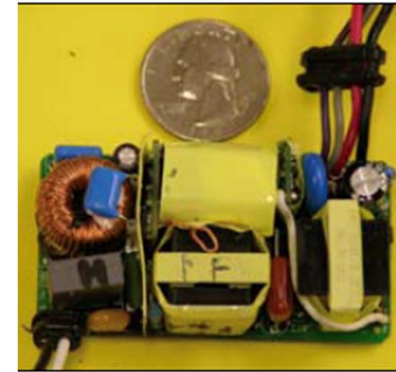



Commercial
LED Driver
100 kHz
21 W
85% eff
4.8 W/in³

- Passive energy storage components (especially magnetics) are the dominant constraint
- *Energy storage* requirements vary inversely with frequency: C,L proportional to f_{sw}^{-1}
- Volume can be scaled down with frequency
 - But, often scales down *slowly* with frequency
 - Magnetic core materials especially impact frequency scaling
 - Application constraints are also an important factor



Switching Frequency Limitations: Loss

- Loss mechanisms in power electronics limit switching frequencies
 - ❑ Relative importance of different losses depends on power, voltage
 - ❑ For this design space, switching loss and core loss dominate

■ Switching loss ($\propto f$)

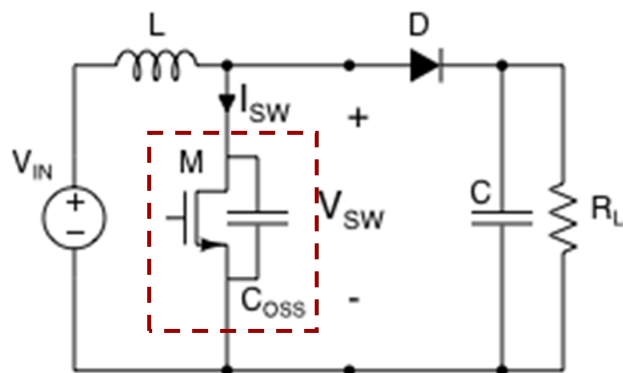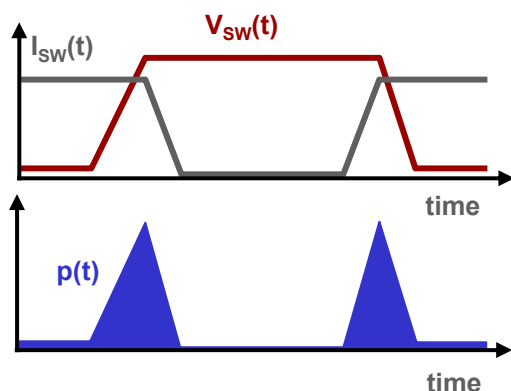

■ Magnetic core loss ($\propto f^k$)

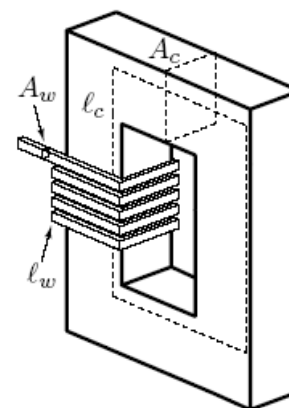
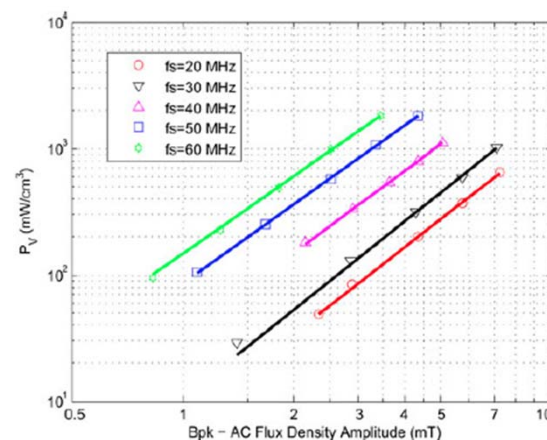


Switching Frequency Solutions



- Minimize frequency dependent device loss, switch fast enough to eliminate/minimize magnetic materials, enable PCB integration


- ZVS Soft switching

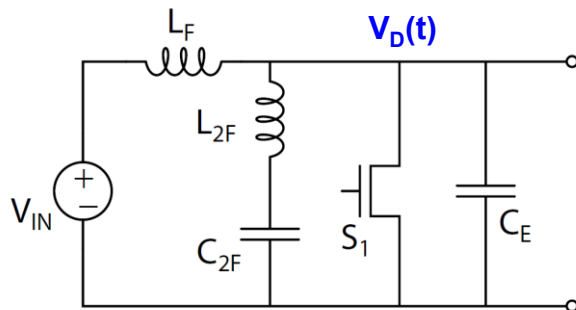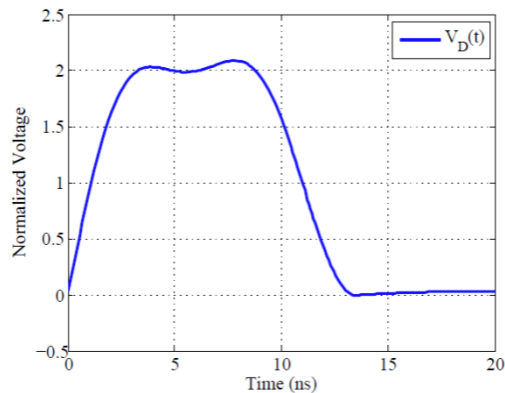

- Coreless magnetics in package or substrate



- Low-permeability RF magnetic materials

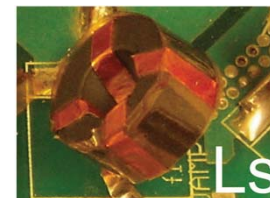


- **Application requirements also impose limits on miniaturization**
 - e.g., twice-line-frequency energy buffering requirements for interfacing single-phase ac to dc imposes size constraints

- **Device & component characteristics impact ability to scale frequency and miniaturize, separate from loss**
 - Component parasitics can limit the ability to scale frequency
 - e.g., at high voltage and low power, parasitic capacitance (e.g., device capacitance) imposes constraints

Twice-Line-Frequency Energy Buffering



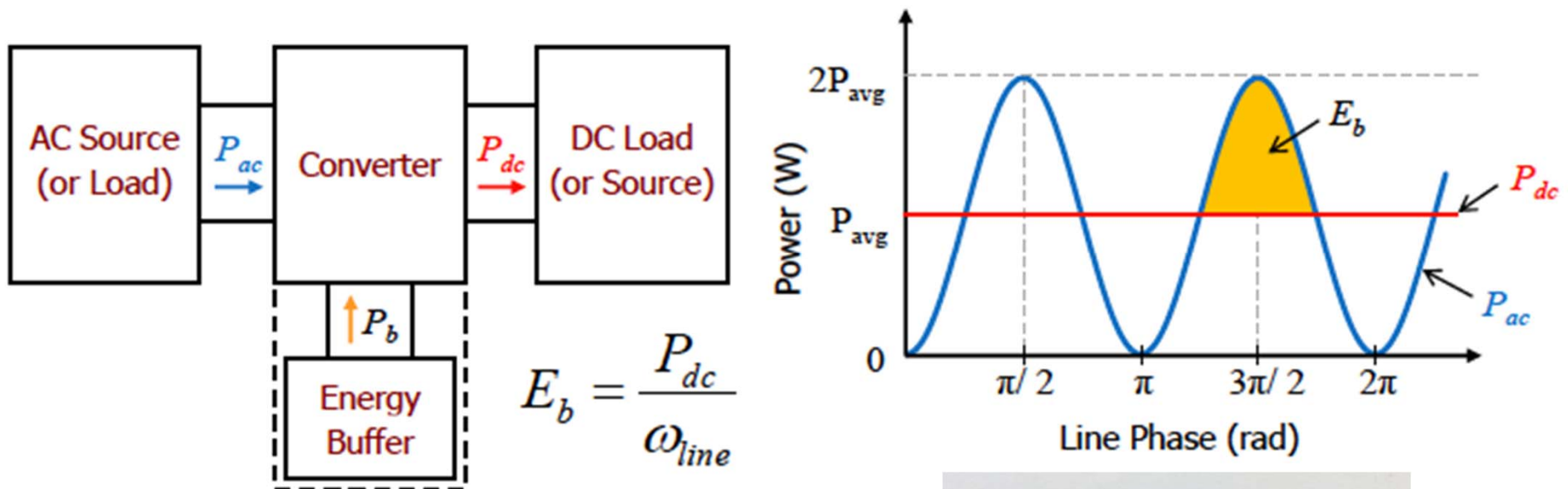- Interface between (continuous) dc and single-phase ac requires buffering of twice-line-frequency energy
 - Energy storage requirement is independent of switching frequency



- Electrolytic capacitors are energy dense but have temperature and lifetime limits




Added Goal: Achieve energy buffering (for high pf and continuous output) at high power density without electrolytics

- **Operation from ac-line-voltage inputs (to 200 V peak) to moderate outputs (~ 30 V) at low powers (~ 10 -50 W)**
 - Resonant circuits at high voltage and low current lead to small capacitance values and large inductor values
 - Increase in frequency reduces both L's, C's
- ***Minimum practical capacitances can limit frequency***
- **Design approach must be selected to require minimal magnetics/larger capacitances to enable greater frequency scaling**
 - Stacked architectures to reduce subsystem operation voltage
 - Multi-stage/merged conversion techniques
 - Topologies selected for small magnetics size


HF dc-dc Power Stage



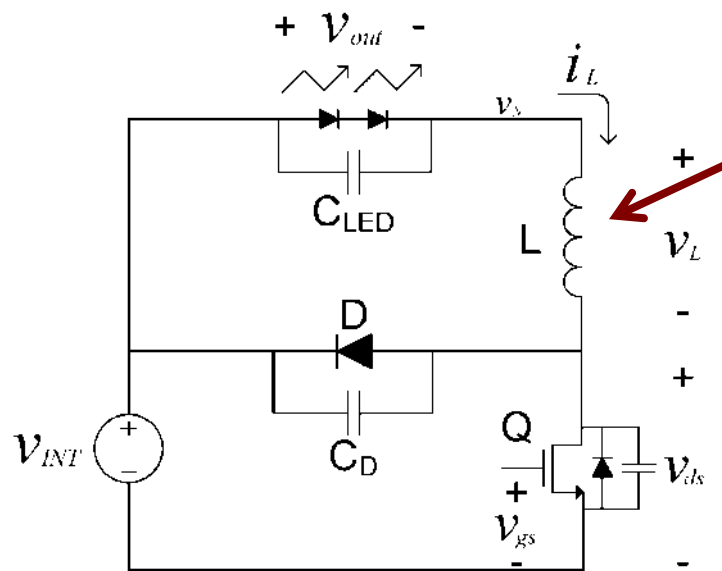- High-frequency dc-dc conversion block (50-100 V in, ~25-40 V out)






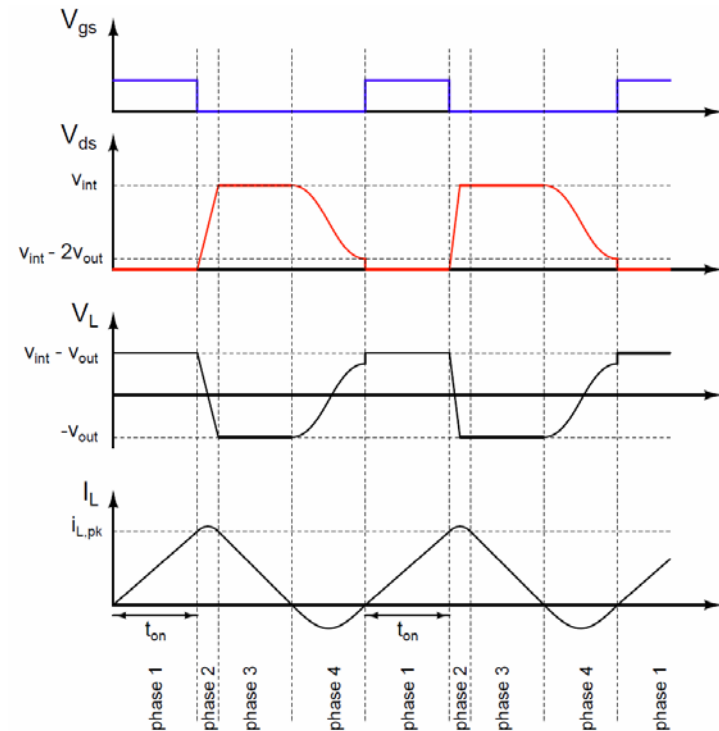Enables small Inductance and possible Integration!




- Resonant transition inverted buck circuit at edge of DCM
- ground referenced switch for HF switching operation (~5-10 MHz)
- Low voltage stress enables operation with significant device capacitance
- Near-minimum magnetics (700-1000 nH inductor for 100 V input at 10's of W)
- ZVS / near ZVS with PWM “on-time” control of output current

HF dc-dc Power Stage

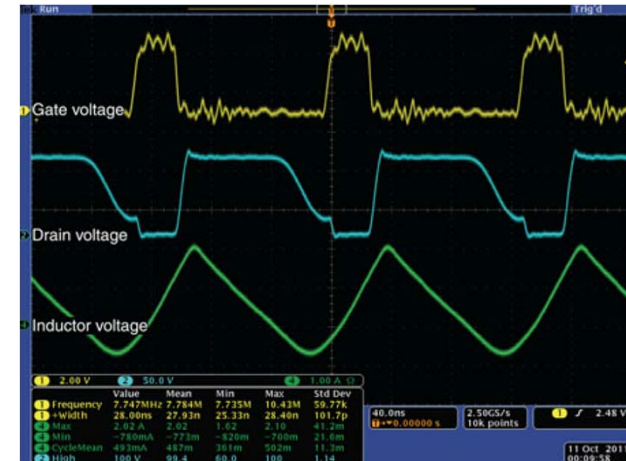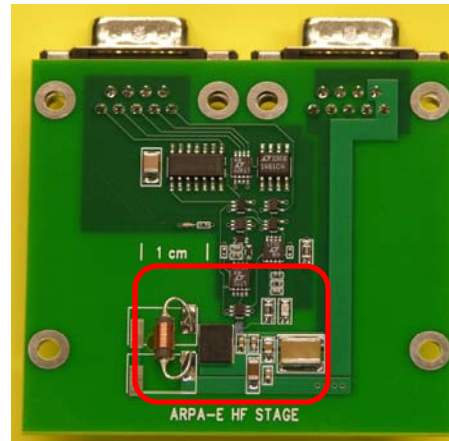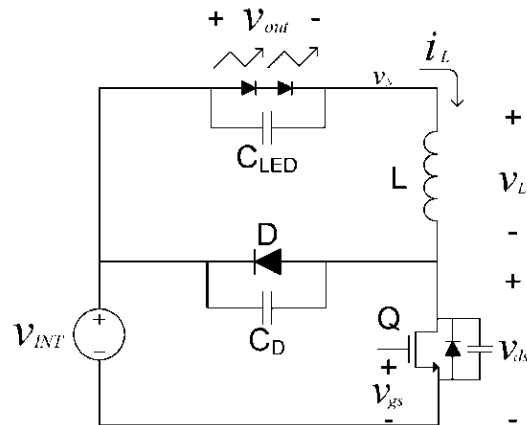

Discrete Prototype $V_{in}=100\text{ V}$, $V_{out}=35\text{ V}$, $f_{sw} \sim 7.8\text{ MHz}$

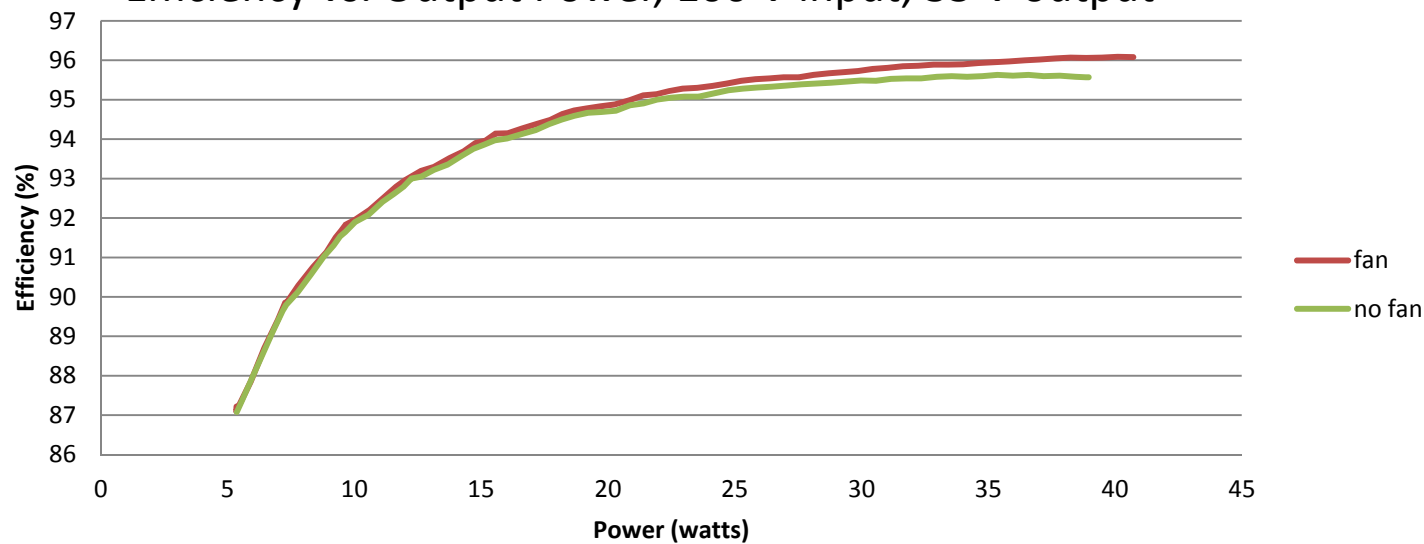
Efficiency vs. Output Power, 100 V input, 35 V output





- **Use a “stacked” circuit architecture to enable processing of high input voltage with lower-voltage blocks**
 - Enables scaling of individual circuit blocks to higher frequencies
 - Utilize “resonant-transition inverted buck” conversion to process energy at high frequency

- **Buffer line-frequency energy at relatively high voltage with large voltage swing to minimize buffer capacitor size**
 - Can use film or ceramic capacitors, eliminating electrolytic capacitors while maintaining high power density
 - This is important because energy buffering depends upon line frequency, and not upon switching frequency

HF AC-DC Architecture

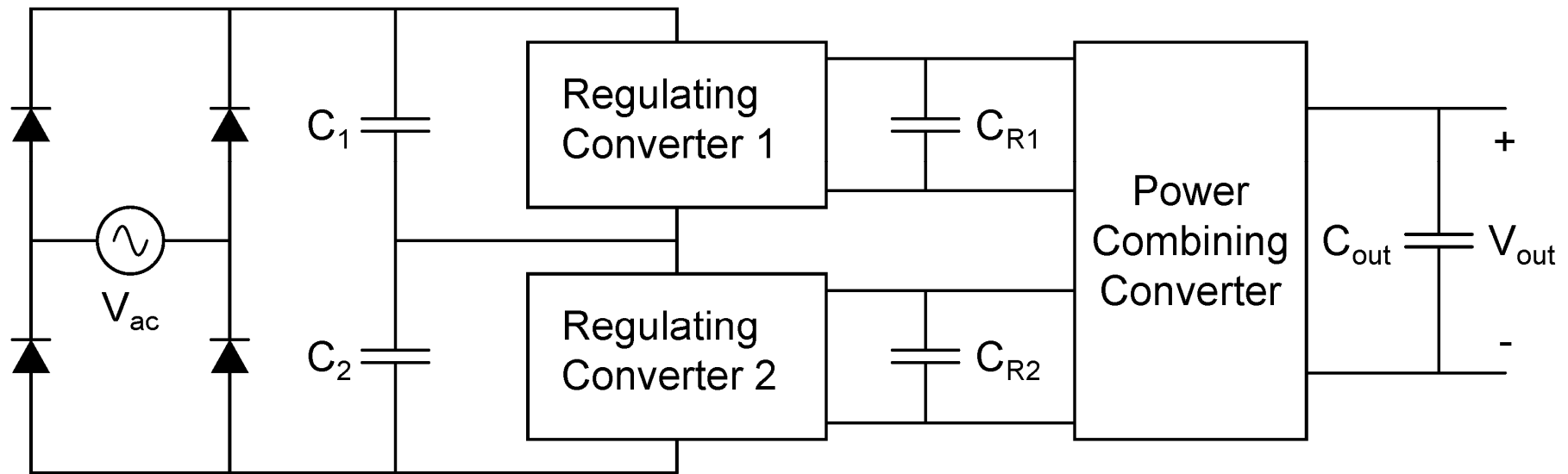



- **Two stacked “regulating” converters operating at HF**
 - Generate regulated voltages across C_{R1} , C_{R2}
- **Second stage combines power (but doesn’t need to regulate)**
- **Stacking is also used for energy buffering**
 - Capacitor C_2 (large) buffers twice-line-frequency energy (with high voltage fluctuation over the ac line cycle)
 - Capacitor C_1 (small) enables capacitor stack voltage to track line voltage

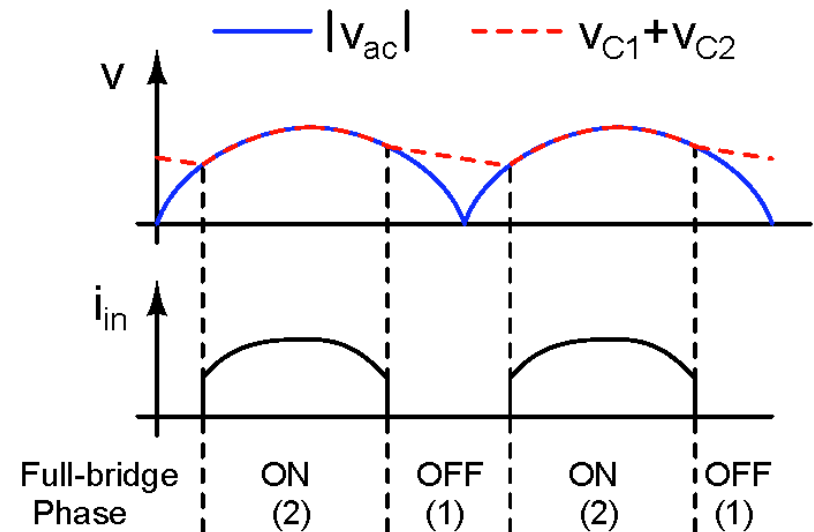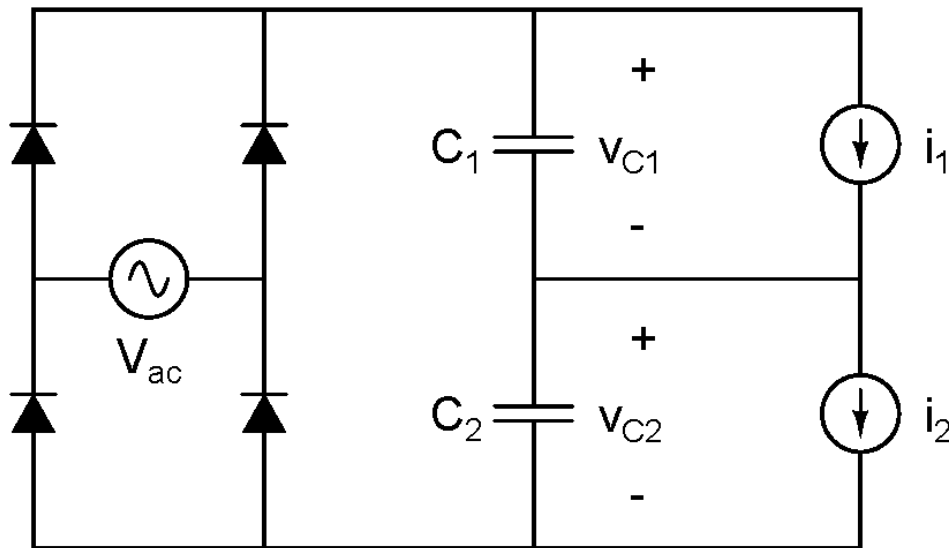

Control buck power stage currents i_1 , i_2 to:

- Provide desired (constant) total output power
- Draw net input current providing high power factor
 - Buffer twice-line-frequency energy on C_2
 - Follow a desired waveform over a limited fraction of the line cycle
 - “clipped sine” wave is optimal for highest power factor

Stacked Converter Model Simulation

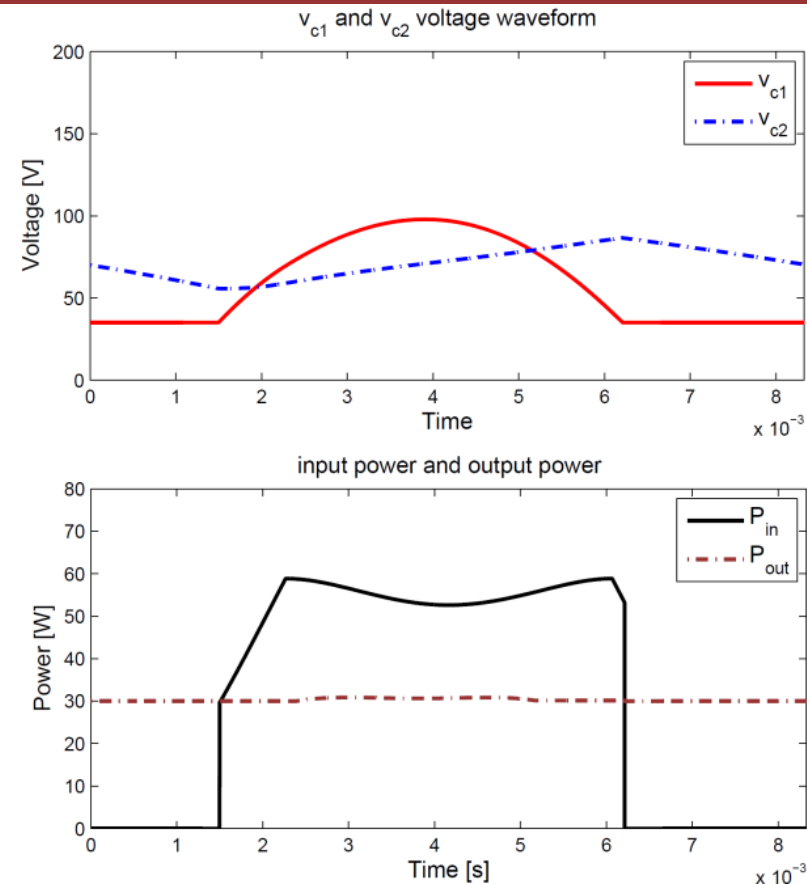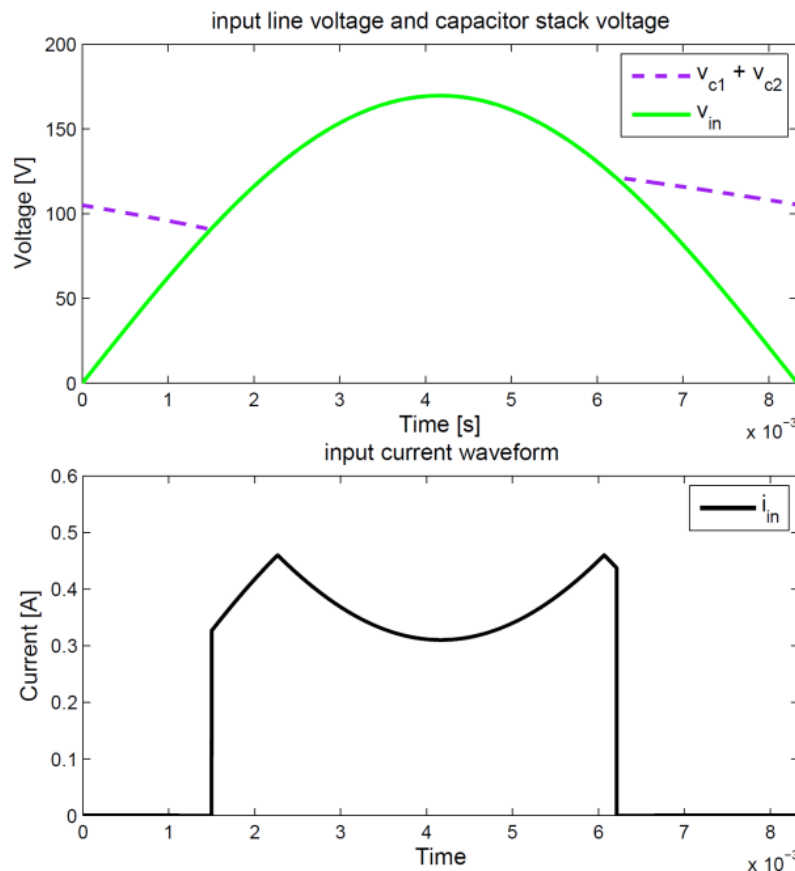


■ Example current and voltage waveforms

□ "Clipped-sine with inverted peak" flattens peak power draw while keeping high power factor

■ Constant output power supplied to load


□ Energy buffered on C_2 with large "triangular" voltage swing

Prototype Converter

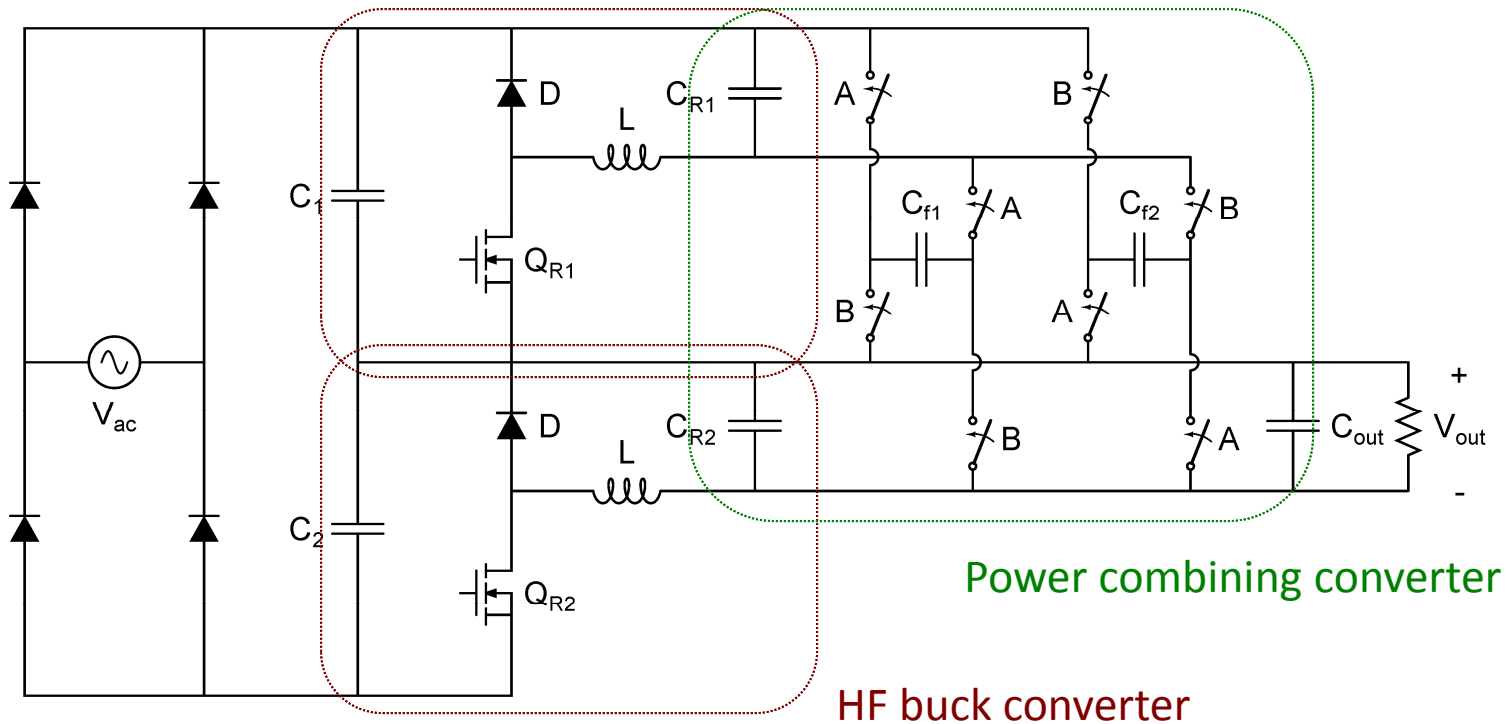


- Two stacked HF buck converters modulate input power across the ac line cycle, causing desired input current waveform and providing energy buffering in C_2
- SC circuit combines the power from converters to supply the load




SC Power Combining Converter

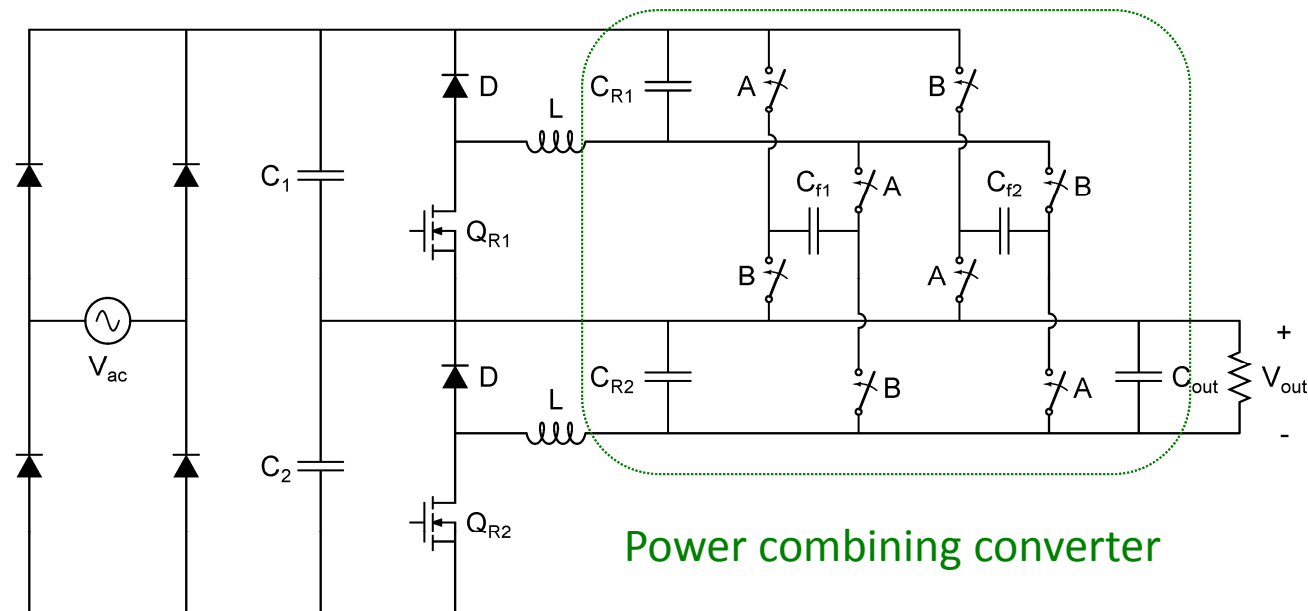

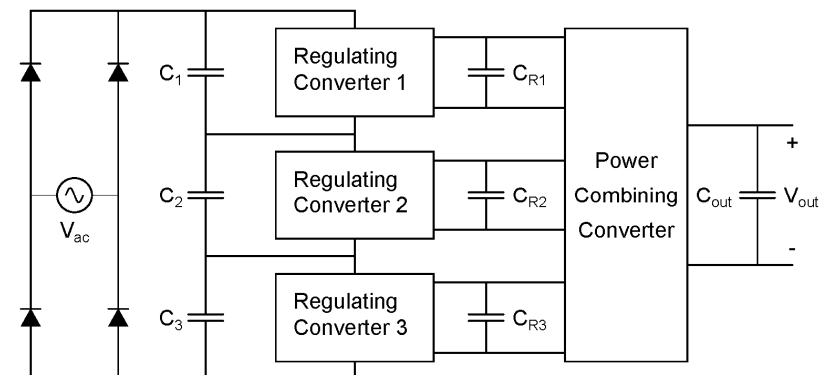- Interleaved switched capacitor charge transfer circuit
- Delivers power from C_{r1} to C_{r2} (output port)
- Operates at $\sim 30\text{kHz}$ with 50% duty ratio
 - High efficiency operation
- May be expanded:
 - Isolated power combining converters are also possible
 - Universal-input power converters




Prototype Converter (Gen 2)

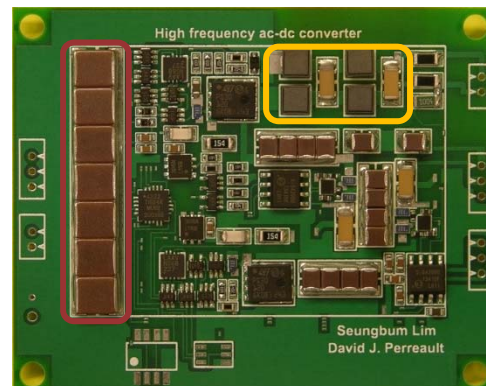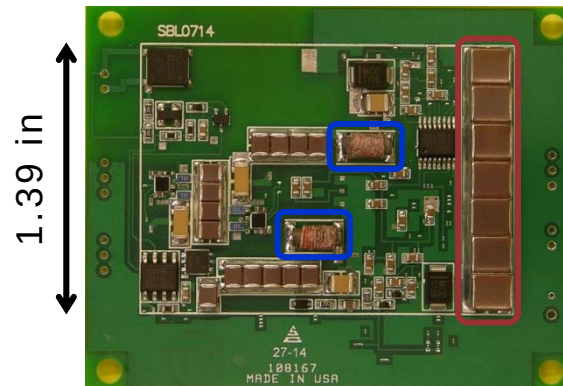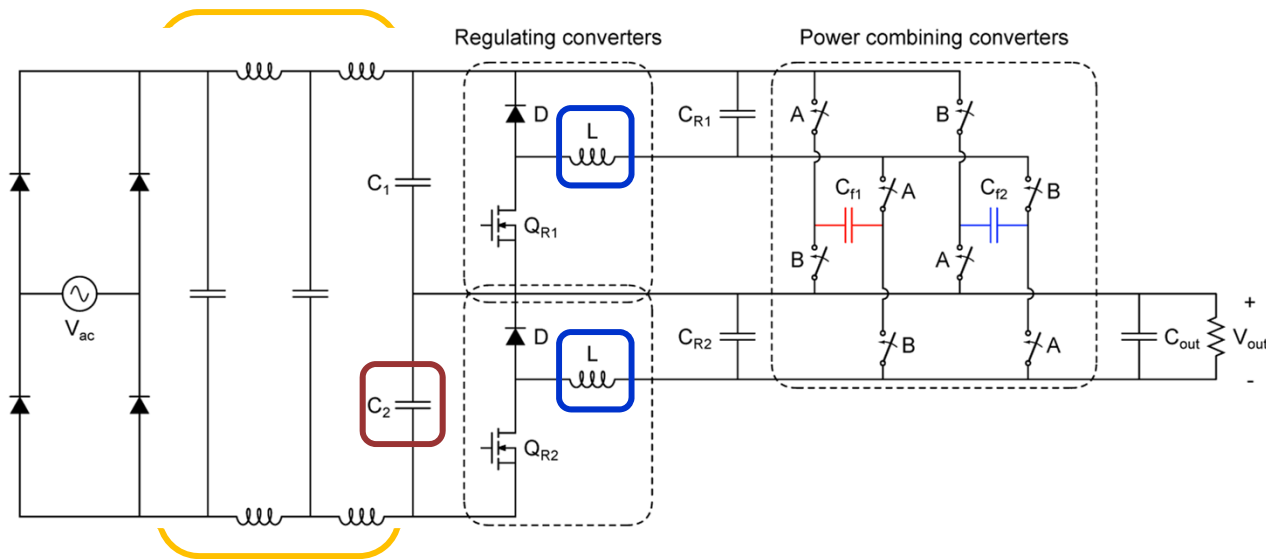

- Buffer Capacitors
- EMI Filter
- Inductors


- 120 Vac input, 35 V dc output, >30 W rating
- Switching frequency ~ 5-10 MHz (varies across operation)
- No electrolytic capacitors!

Prototype Converter Details

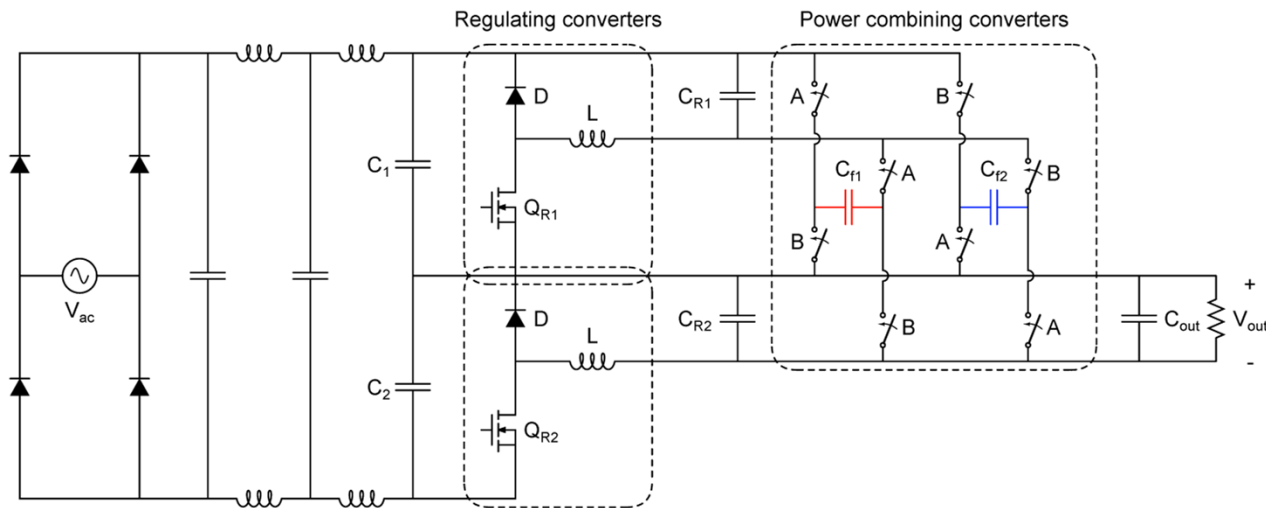


- **Buffer Capacitor: 14 x 15 uF (X7R 100V, Ceramic TDK)**
- **EMI filter:**
 - ❑ 4 x 47 uH inductors (1008PS-473KL, coilcraft)
 - ❑ 2 x 10 nF capacitors (200V, X7R ceramic, Kemet)
- **Regulating converters**
 - ❑ Inductor: 10 turn Litz wire on Micrometals P68-106 core (800 nH)
 - ❑ Switch: GaN HEMT transistor (EPC 2012, 200V 3A, EPC)
 - ❑ Diode: Schotky diode (STPS30120, 120V 30 A, ST)
- **SC circuit**
 - ❑ Switch: GaN HEMT transistor (EPC 2012, 200V 3A, EPC)

Experimental Results

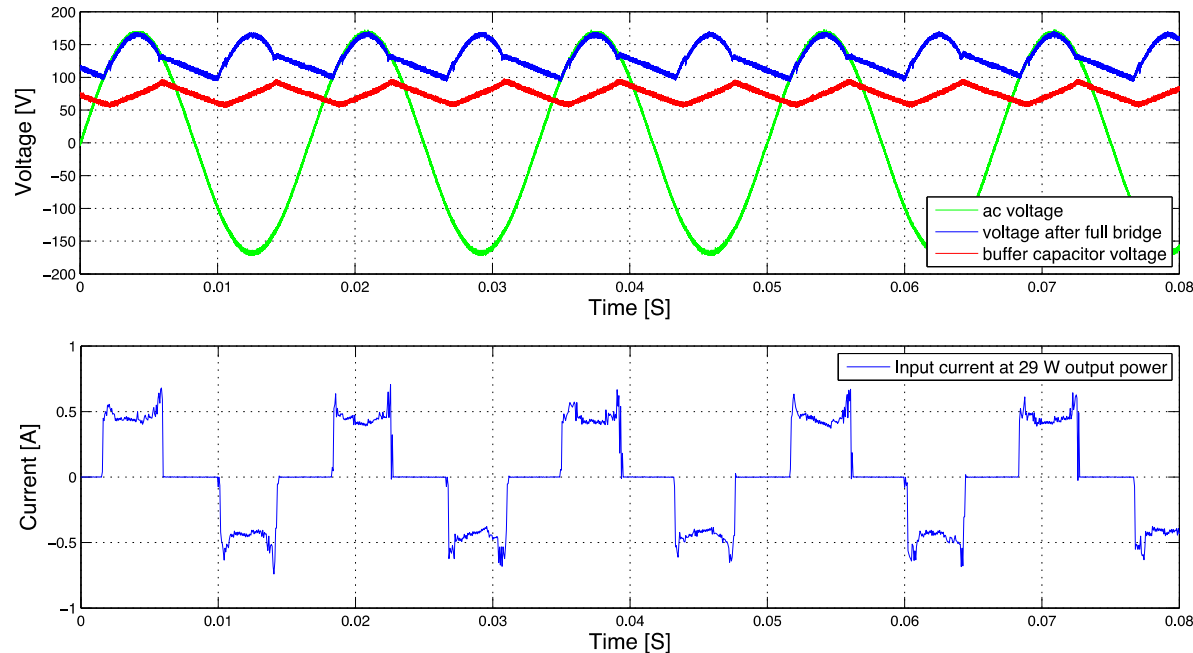


- **Design successfully demonstrates proposed approach**
 - Operation matches models
- **High power factor ~0.88 (higher appears possible)**
 - $15\mu\text{F} \times 14 = 210\text{ }\mu\text{F}$ MLCC ac energy buffer capacitor (works as ~50 μF at 70V): eliminates electrolytic capacitors at modest size
- **Efficiency ~92%**

Performance Across Output Power


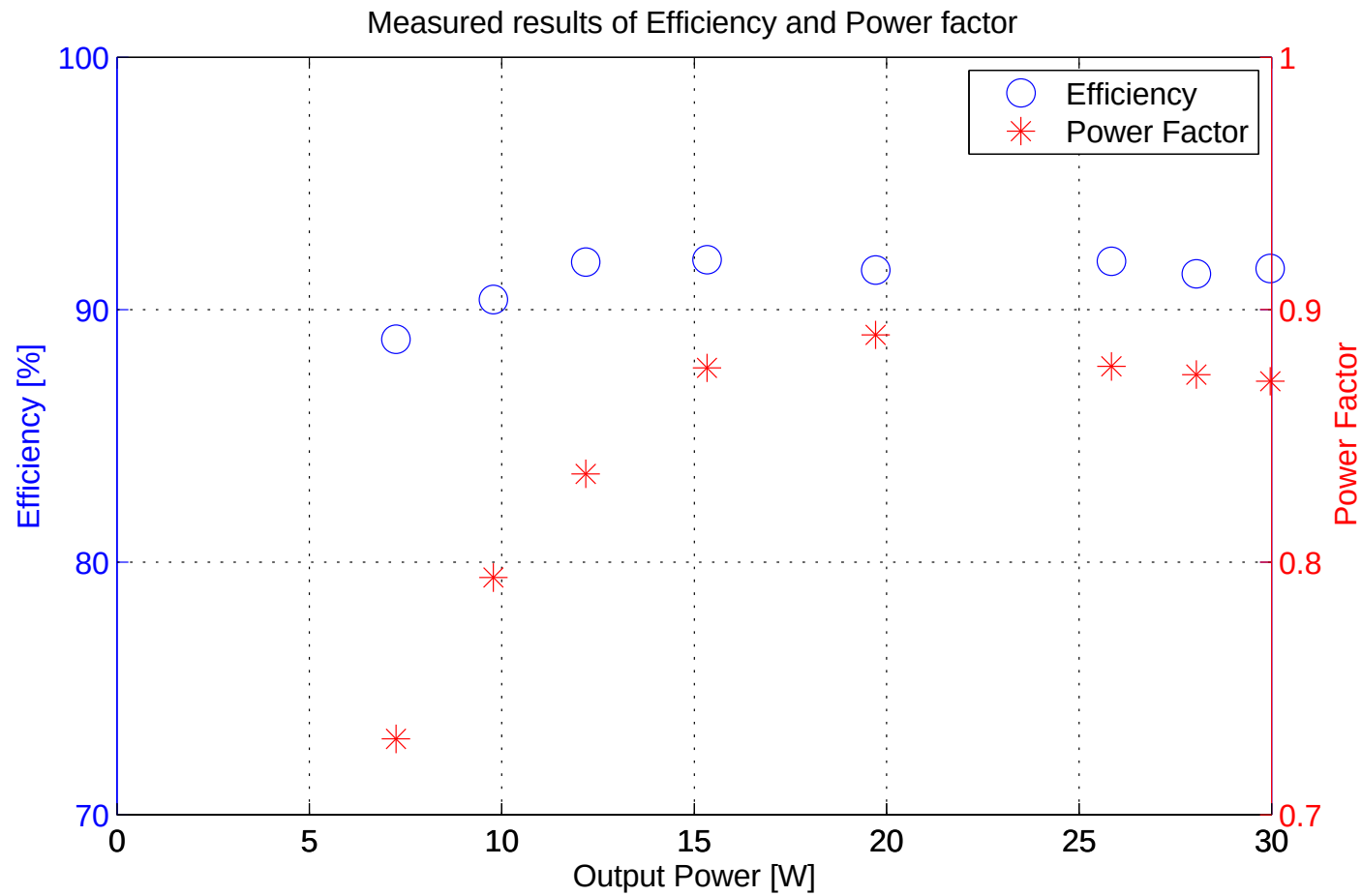


EMI Performance

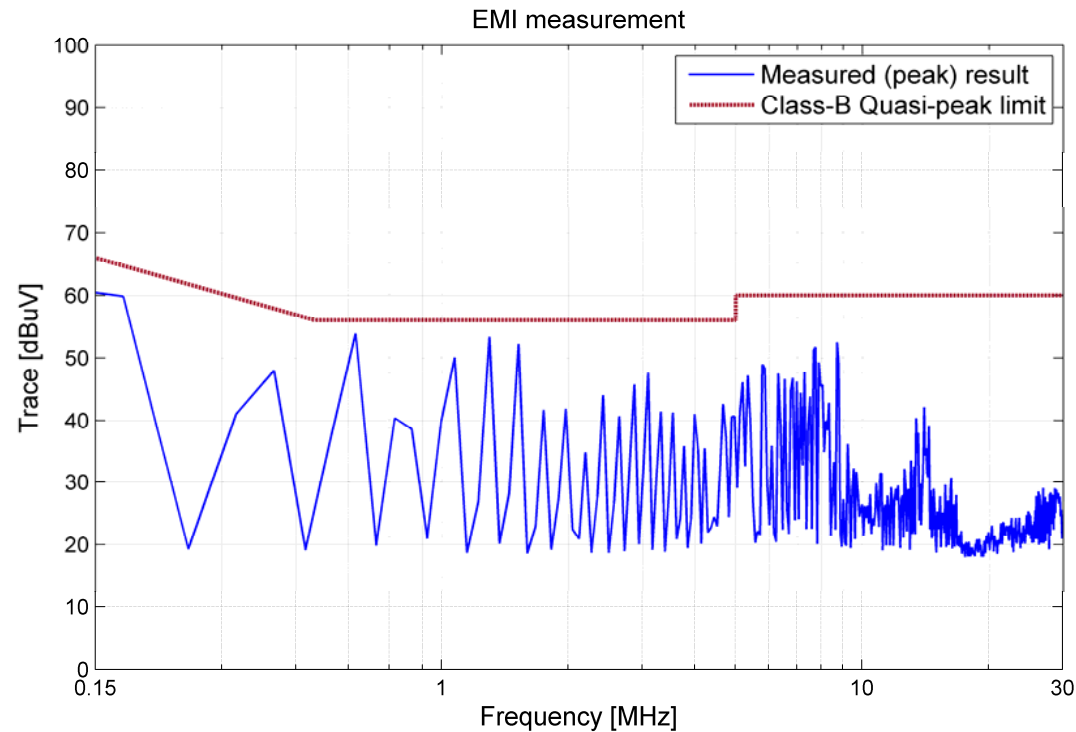

- **Meets FCC Class B EMI requirements with a small filter**
 - ❑ EMI filter not optimized
- **Measured 'peak' spectrum passes 'quasi-peak' limit**
 - ❑ (Quasi-peak response is always less than or equal to peak response)

Prototype Power Density

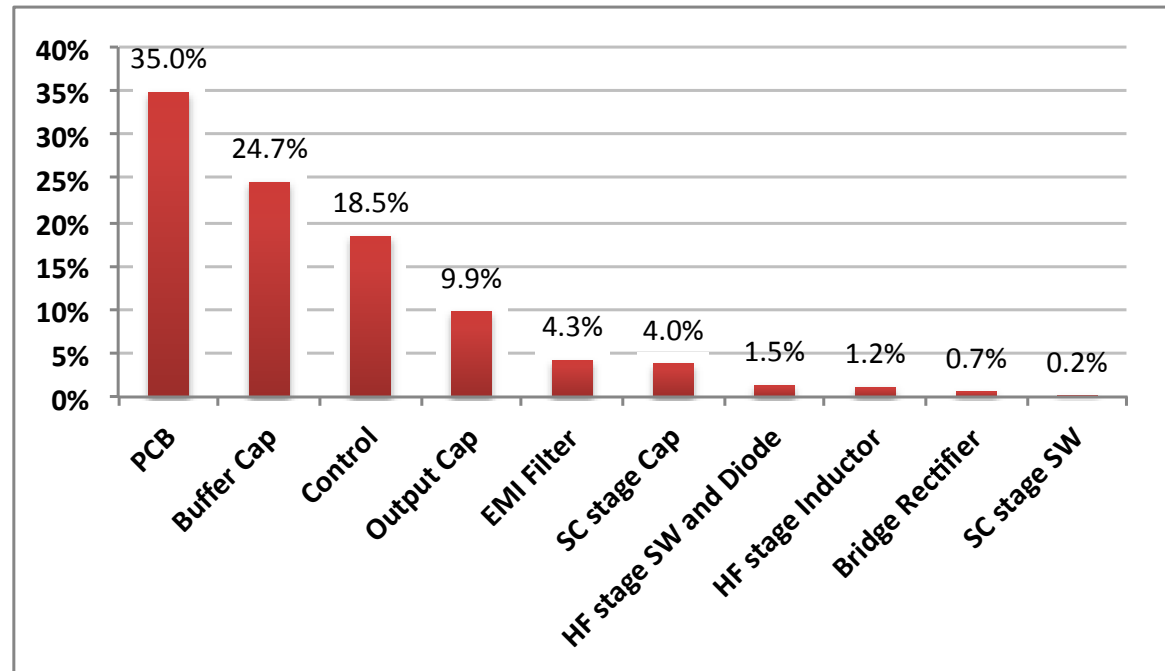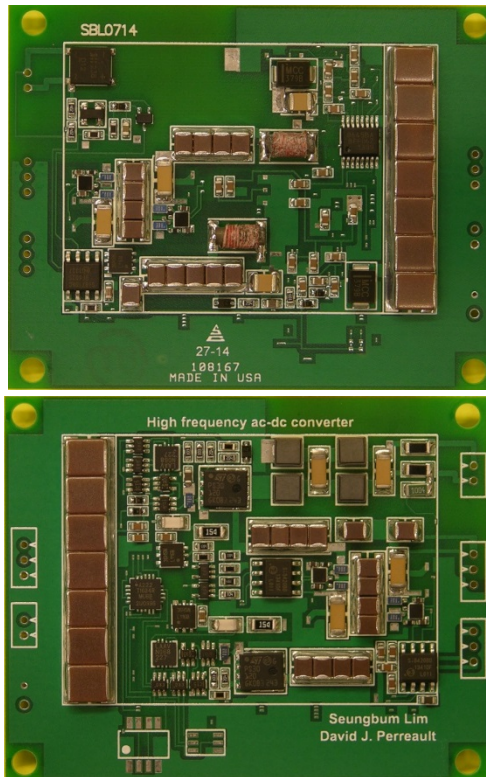

- **> 50 W/in³ “box” power density**
 - Displacement power density: 130 W/in³
 - Logic / controls, pcb volume and layout can be further optimized and integrated
- **~10X power density improvement over commercial designs (for a ~100x frequency increase)**

- **Greatly increased switching frequencies offer potential for substantial miniaturization**
 - For grid interface, must still manage twice-line-frequency energy buffering
- **Appropriate system design methods enable operation at HF and VHF frequencies (3-300 MHz)**
 - At grid interface voltages one must overcome both loss and parasitic limits to achieve high frequency operation
- **To push up frequencies at high V_{in} , moderate power:**
 - Use “stacked” architectures to reduce subsystem voltages, Z_o
 - Utilize converter topologies with ZVS and low Z_o

Summary (2)

- **Feasibility and advantages of this approach has been demonstrated in a high-frequency (5-10 MHz) LED driver**
 - ❑ ~10 x power density for ~100 x frequency increase
 - ❑ High power factor (~0.88) without electrolytic capacitors
 - ❑ High efficiency (>90%)
 - ❑ EMI requirements can be met with small filters

	Typ. Commercial	Powerchip
Efficiency	64 - 85 %	92 %
Switching Frequency	57 - 104 kHz	5-10 MHz
Power Factor	0.73-0.93	0.88
Power Density	< 5 W/in ³	> 50 W/in ³



Acknowledgements



■ ARPA-E & Texas Instruments

■ ARPA-E ADEPT PowerChip team members




■ Co-authors of this work

□ Seungbum Lim







□ David Otten

HF Inverted Buck Converter Control

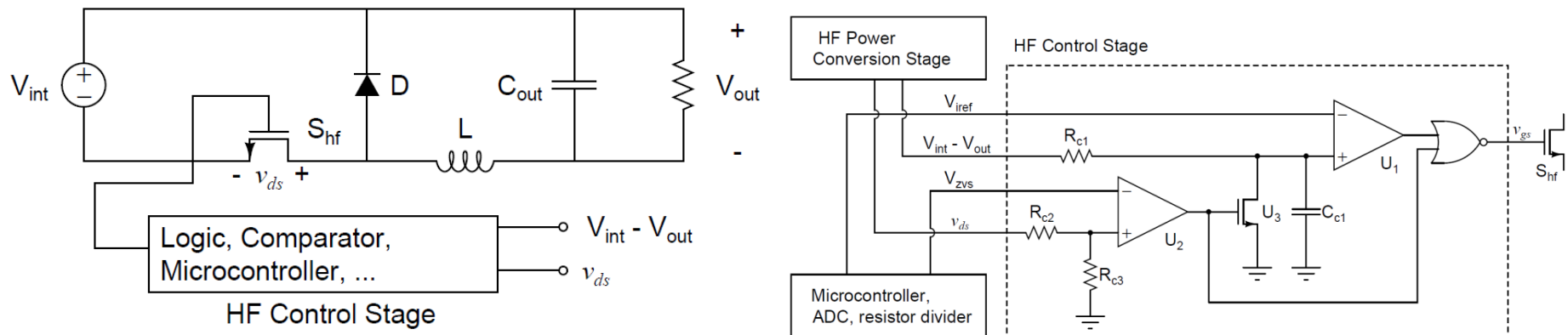

- peak inductor current is controlled by changing switch on-time
 - Enables continuous modulation of power at high frequency
- turn on at ZVS / near ZVS voltage

Stacked Converter Model Simulation

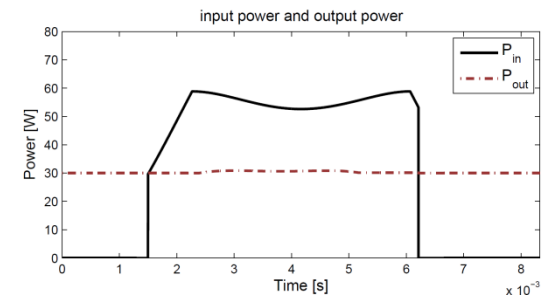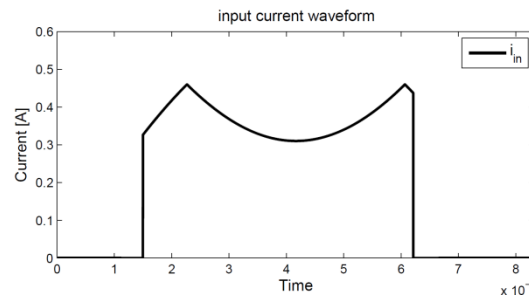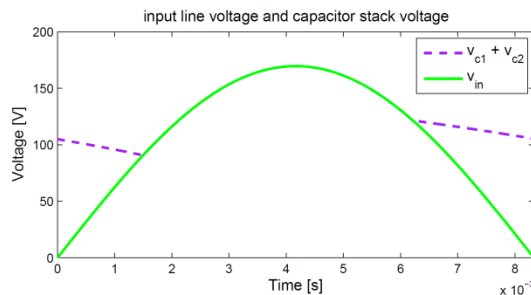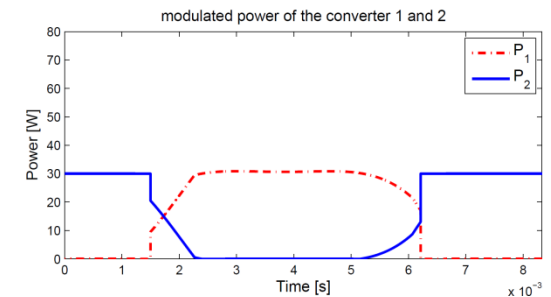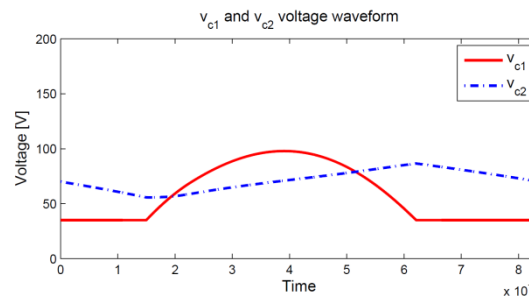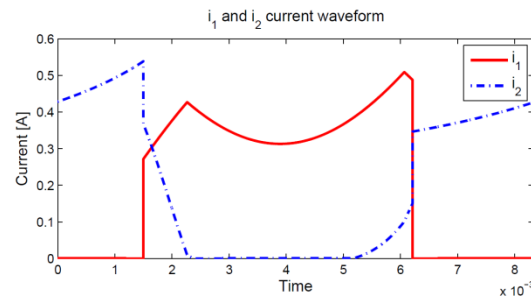

- Example current and voltage waveforms
- For desired input power, calculate i_1 and i_2 currents over the ac line cycle (command for the individual dc-dc conversion blocks)
- Constant output power supplied to load

■ FCC part 15 subpart B Conducted limits

Class B

Frequency of emission [MHz]	Conducted limit (dBuV)	
	Quasi-peak	Average
0.15 – 0.5	66 to 56	56 to 46
0.5 – 5	56	46
5 – 30	60	50

Class A

Frequency of emission [MHz]	Conducted limit (dBuV)	
	Quasi-peak	Average
0.15 – 0.5	79	66
0.5 – 30	73	60