



Converter Topologies for Large Conversion Ratios: A Story from SI, SC to Hybrid Architectures




Hanh-Phuc Le

<https://www.colorado.edu/ipower3es>

hanhphuc@colorado.edu

Hanh-Phuc Le

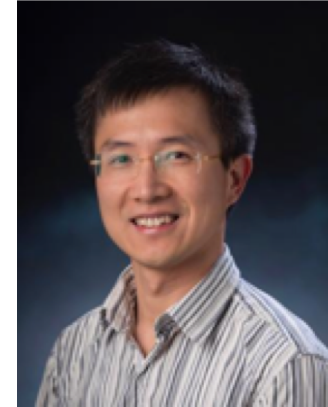
Assistant Professor, University of Colorado Boulder








- **Ph.D.** **UC Berkeley** **2013**
- **M.S.** **KAIST, Korea** **2006**
- **B.S.** **HUST, Hanoi, Vietnam** **2003**

- **Prior experience:**

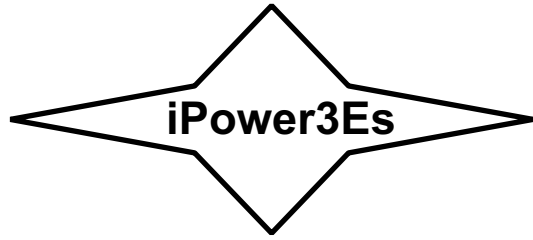- Lion Semi., San Francisco, CA 2012 – 2015 (shipping millions to large smart phone makers)
- Rambus, Sunnyvale, CA 2012
- Intel, Beaverton, OR 2009
- Oracle, Santa Clara, CA 2008
- JDA Tech., Korea 2004 – 2007
- VAST, Vietnam 2002 – 2004



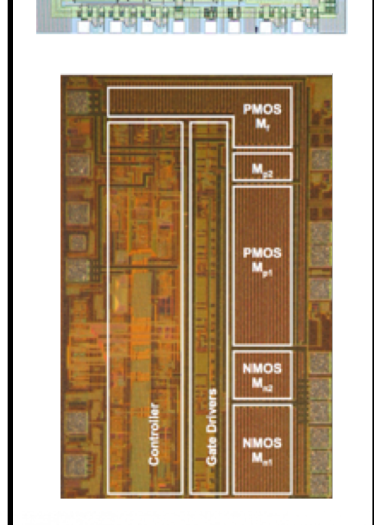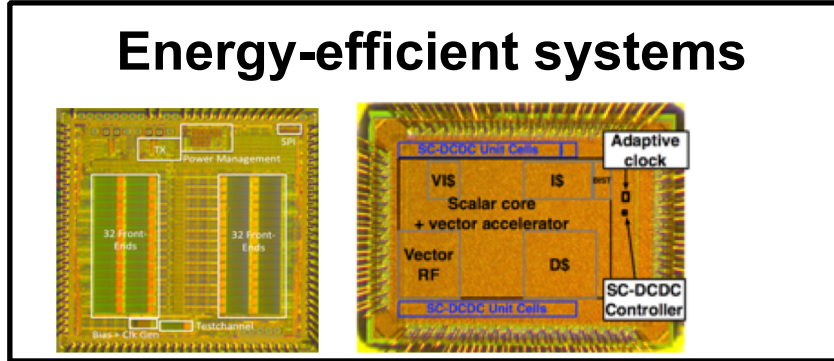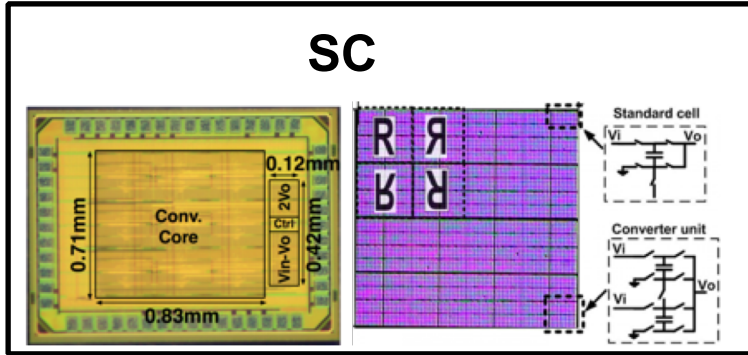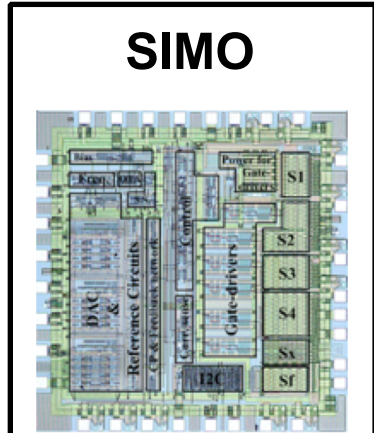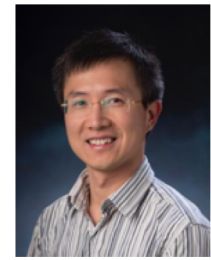Hanh-Phuc Le iPower3Es Group, CoPEC University of Colorado, Boulder



Smart-Cable (Hybrid) Converters


1 @ APEC '17, 2 @ COMPEL '18, 1 @ ISSCC '19

Hybrid, High-voltage

2 @ ECCE '18, 3 @ APEC '19




The Need for Advanced DC-DC Converter

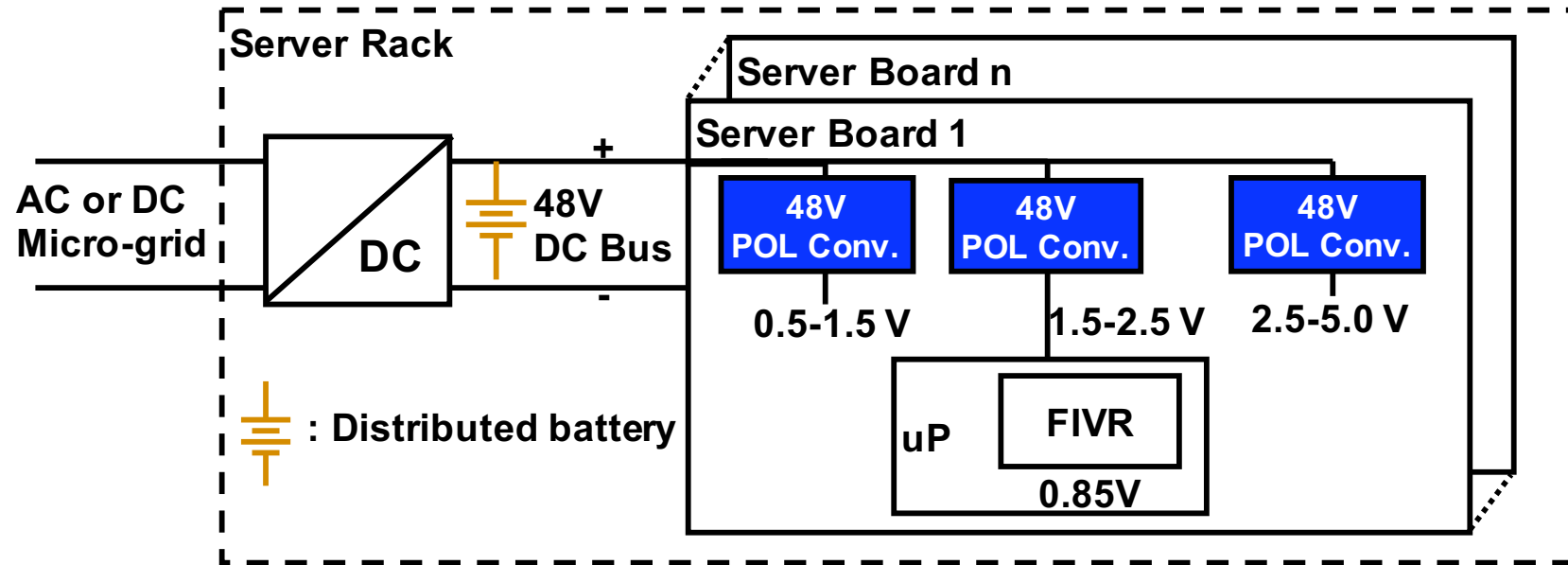




- **Global data traffic for data centers increases exponentially:**
 - 2 EB (2013) → 20 EB (2018) → 100 EB (2023)
 - ~73 billion kWh (2020), or ~\$7.3 billion cost of electricity in the U.S. alone
- **~15% power consumption lost over conversion stages and delivery.**

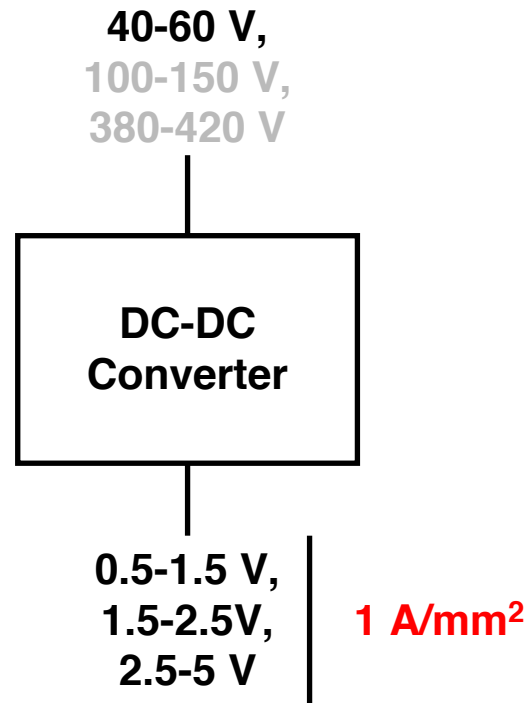Key Requirements for the “Magical” Converter(s)



- **Large conversion ratios, e.g. 48-to-1**
- **High input voltage, >40V**
- **Large current density, 1 A/mm²**
- **High efficiency, >95%**
- **Wide regulation range (wide input/output voltages)**
- **Scalable for both larger and smaller current**
 - Granular power supply (miniaturized converter unit)
- **Reliable**
 - More integration
- **Low cost**
 - More integration and miniaturization

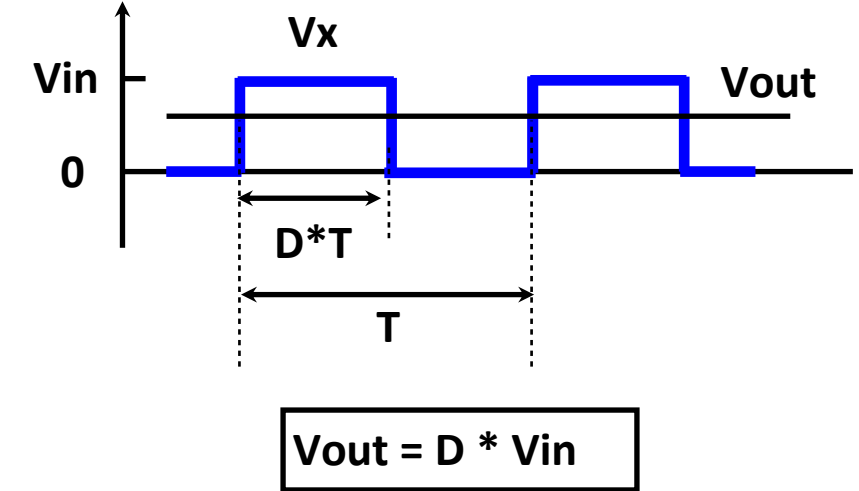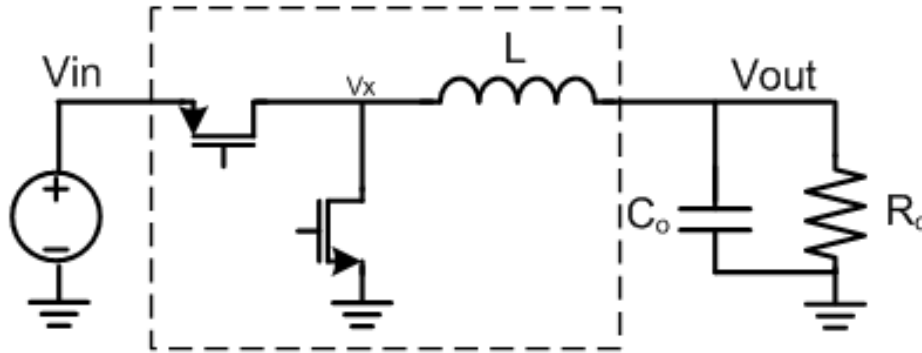
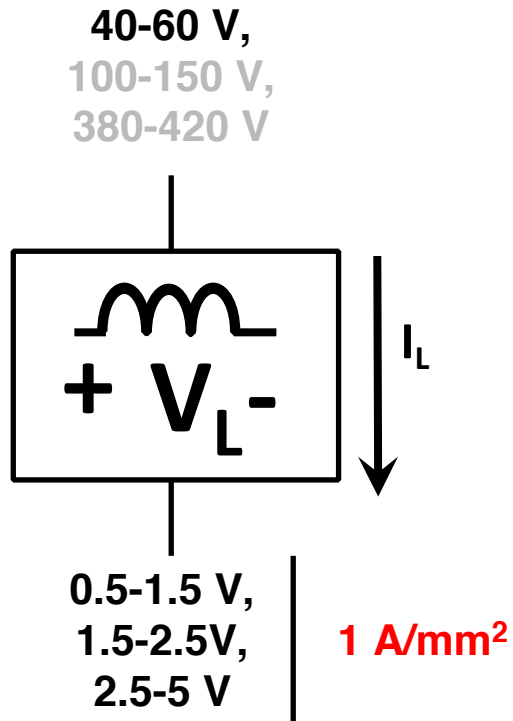
Converter Magic 1 – Switched Inductor (Buck)




- Transfer charge in form of current in inductor
- High efficiency for fine regulation
- **Require switches with large breakdown → high $R_{ds,ON}$**
- **Difficult/expensive integrated inductor**
- **Not easy to scale**

Converter Magic 2 – Switched Capacitor (SC)

40-60 V,
100-150 V,
380-420 V

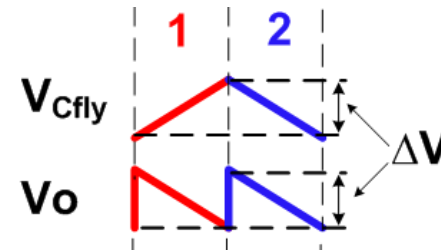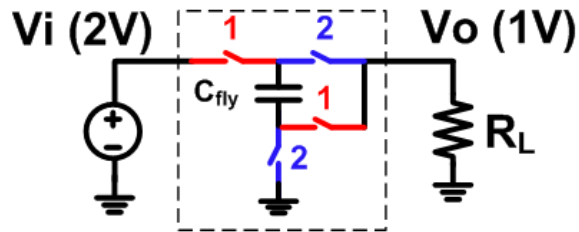


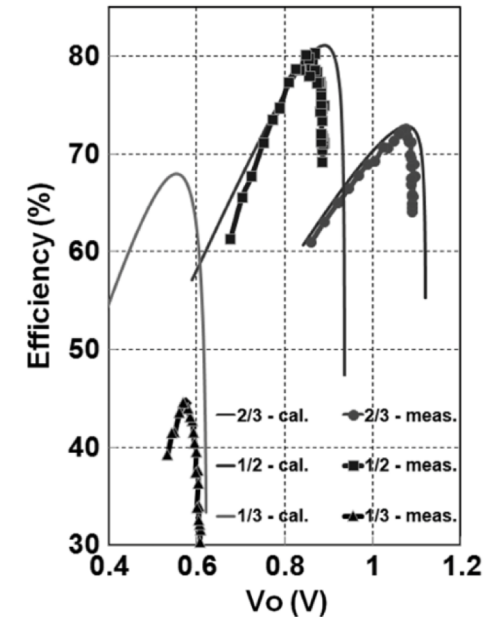- Transfer charge in form of cap. voltage ripple
- No bulky magnetic → can be integrated and scalable
- Integrated capacitors are readily available
 - MOS, MIM, MOM, deep-trench capacitors
- Small and inexpensive
 - Trend to use more capacitors to reduce stress on inductors
- **Problem in fine regulation efficiency**



Ref: Le, et al., ISSCC 2010

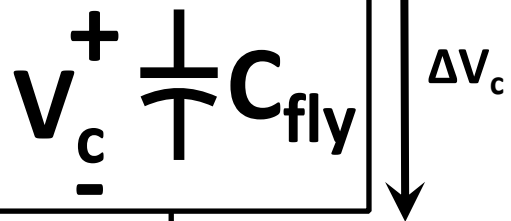- **~80% efficiency @ 0.9 A/mm²**
- **Linear efficiency degradation**
 - **hard charging**




0.5-1.5 V,
1.5-2.5V,
2.5-5 V

1 A/mm²


• Products: TI, Intel, Dialog, Lion Semiconductor, etc

Converter Magic 3 – Hybrid Architecture


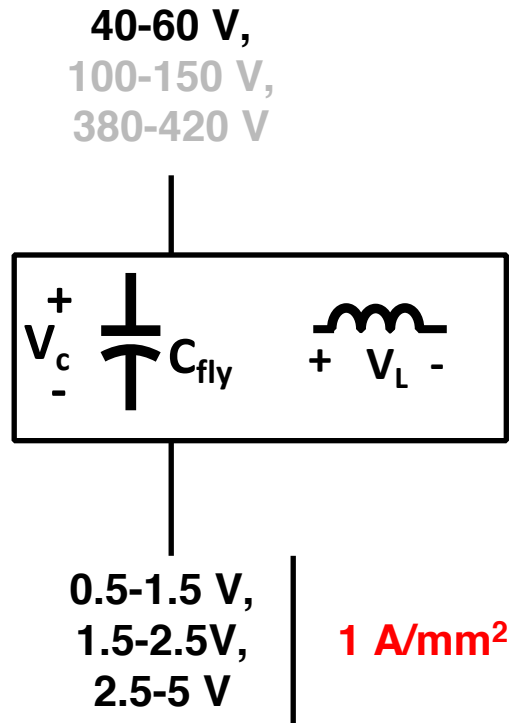


- **SC stage blocks large portion of V_{in}**
 - Only need to handle small voltage ripple
- **Flying inductor blocks a fraction of voltage**
 - Support fine regulation
- **Efficient use of both passive components**
 - Can support large conversion ratios


Hybrid Converter Architecture – Overview

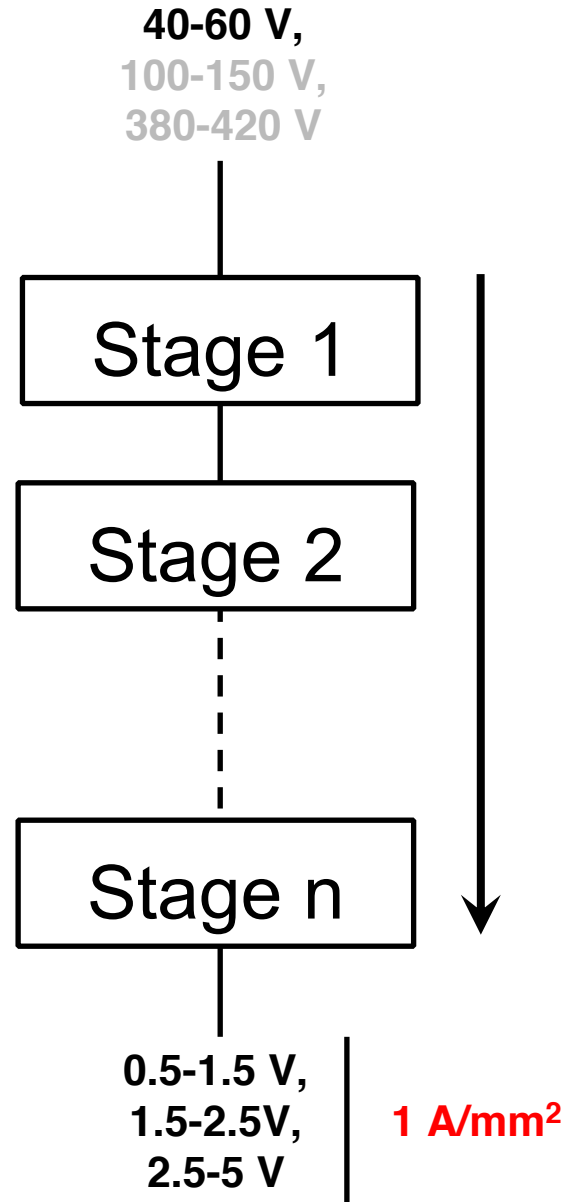

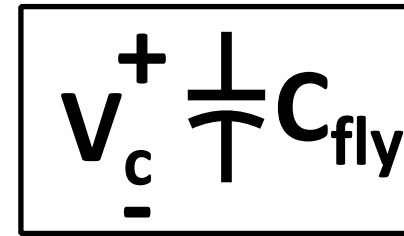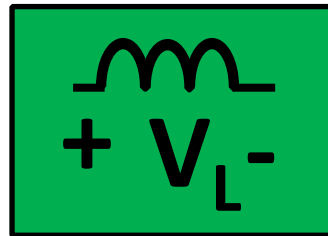- **Key challenge:**
 - Efficient conversion with large ratios
 - Fine voltage regulation
- **Want to have multiple stages**
 - Use both inductors and capacitor stages
 - Capacitor: block the voltage
 - Inductor: soft-charge capacitors, can be smaller and more integrated




Hybrid Converter Architecture – Overview

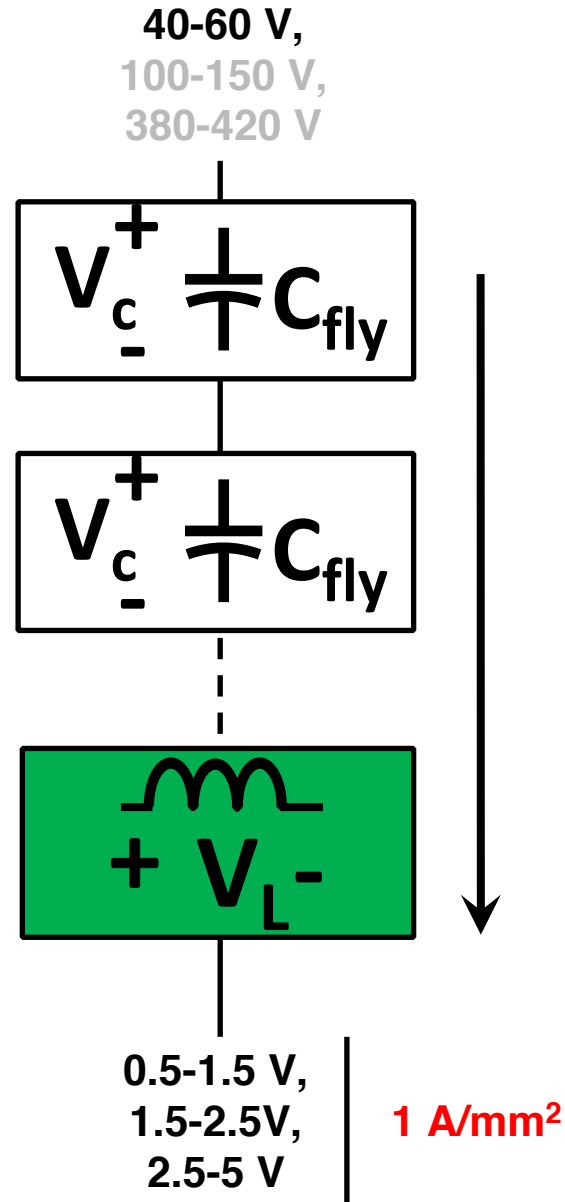

- **Key challenge:**
 - Efficient conversion with large ratios
 - Fine voltage regulation
- **Want to have multiple stages**
 - Use both inductors and capacitor stages
 - Capacitor: block the voltage
 - Inductor: soft-charge capacitors, can be smaller and more integrated
- **Option:**
 - Inductors at the output: convenient but inductor carry output currents


Hybrid Converter Architecture – Overview

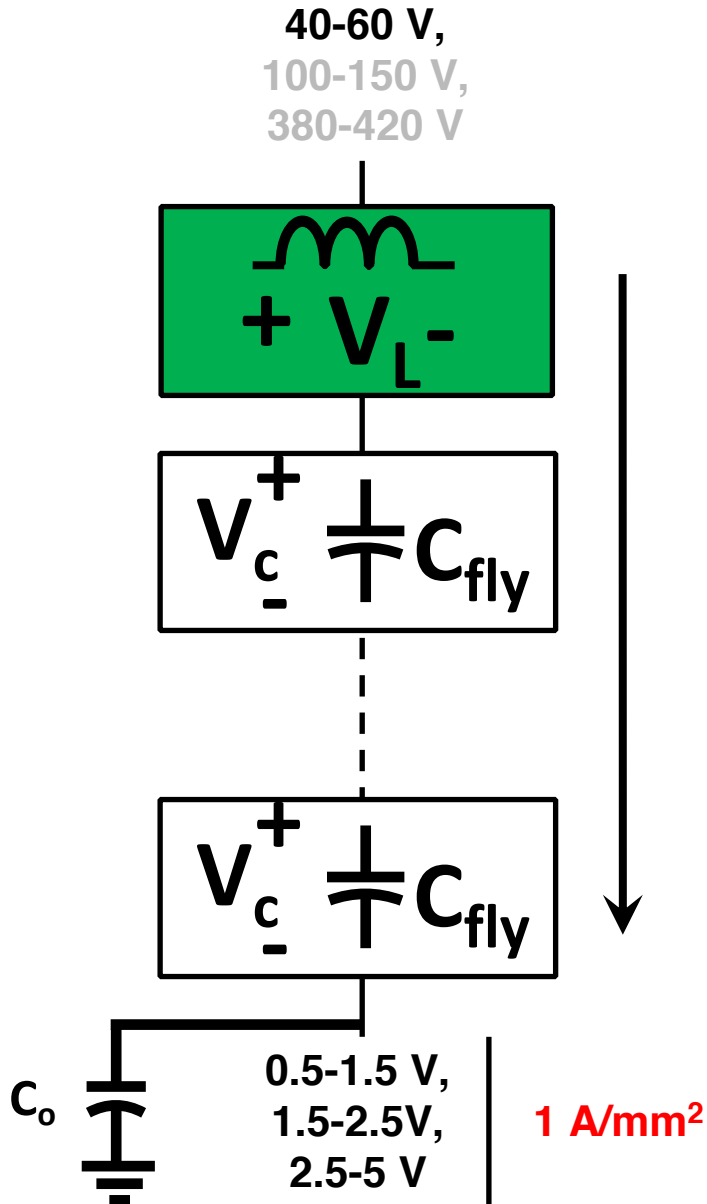

- **Key challenge:**
 - Efficient conversion with large ratios
 - Fine voltage regulation
- **Want to have multiple stages**
 - Use both inductors and capacitor stages
 - Capacitor: block the voltage
 - Inductor: soft-charge capacitors, can be smaller and more integrated
- **Option:**
 - Inductors at the output: convenient but inductor carry output currents
 - Inductors at the input: inductor only handles input current, but capacitor could hard charge with output capacitor

Hybrid Converter Architecture – Overview

40-60 V,
100-150 V,
380-420 V

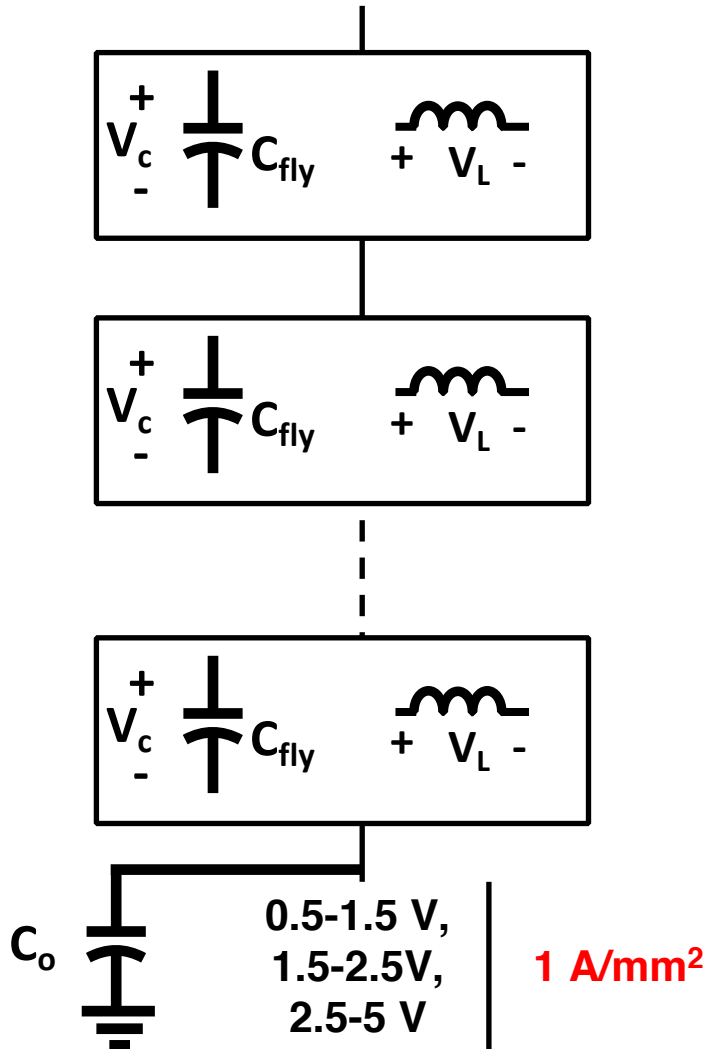

- **Key challenge:**
 - Efficient conversion with large ratios
 - Fine voltage regulation
- **Want to have multiple stages**
 - Use both inductors and capacitor stages
 - Capacitor: block the voltage
 - Inductor: soft-charge capacitors, can be smaller and more integrated
- **Option:**
 - Inductors at the output: convenient but inductor carry output currents
 - Inductors at the input: inductor only handles input current, but capacitor could hard charge with output capacitor
 - Resonant operation with both inductor and capacitors

Key: the stages need to work together!

Hybrid Converter – Inductor First (S-Hybrid)


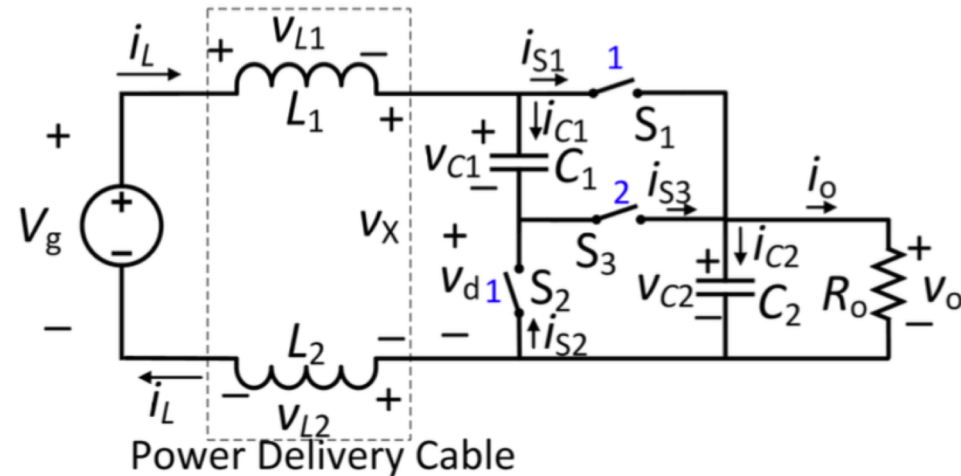
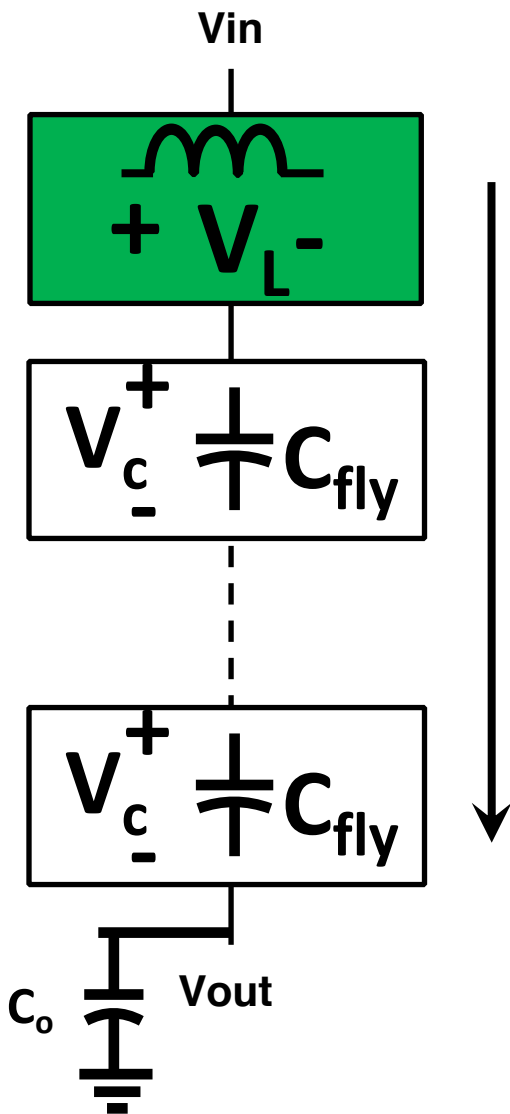
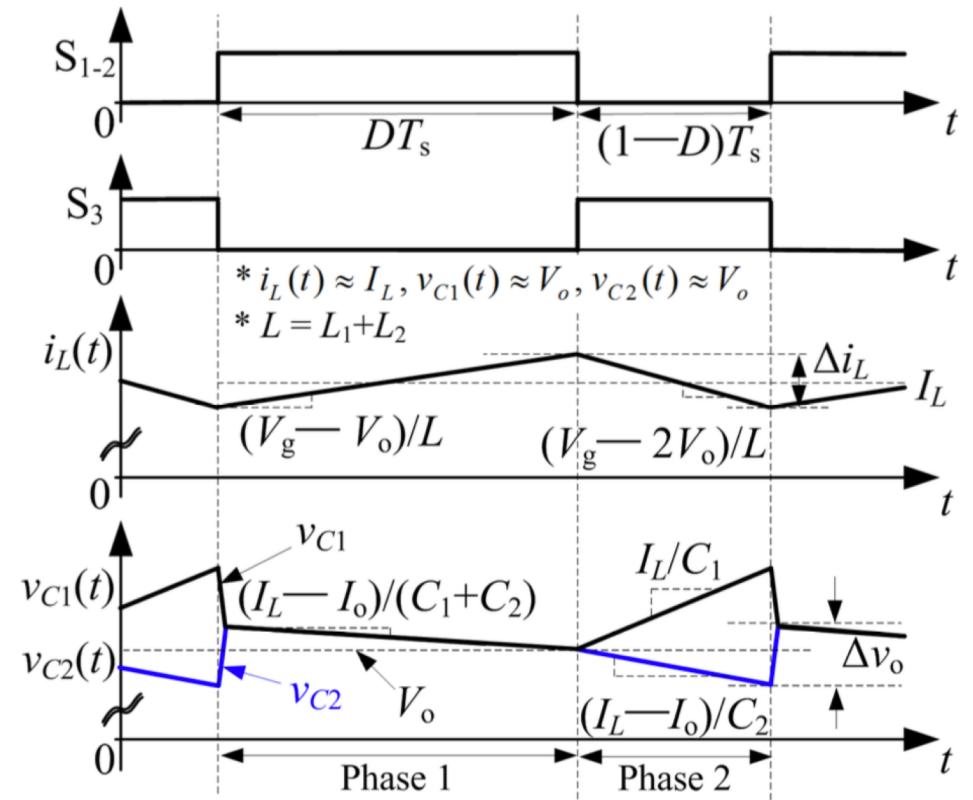
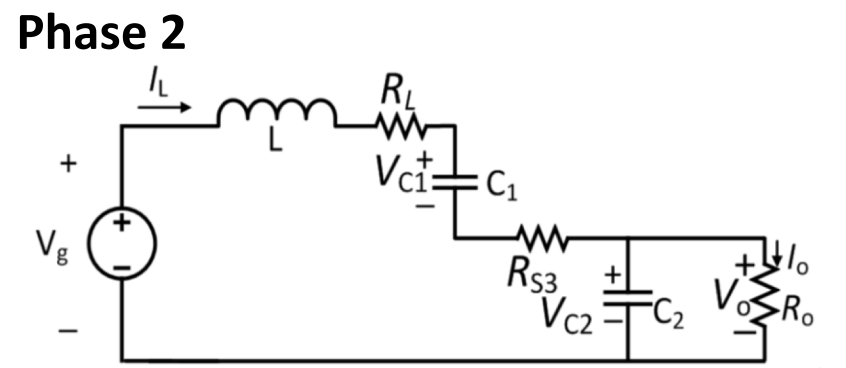
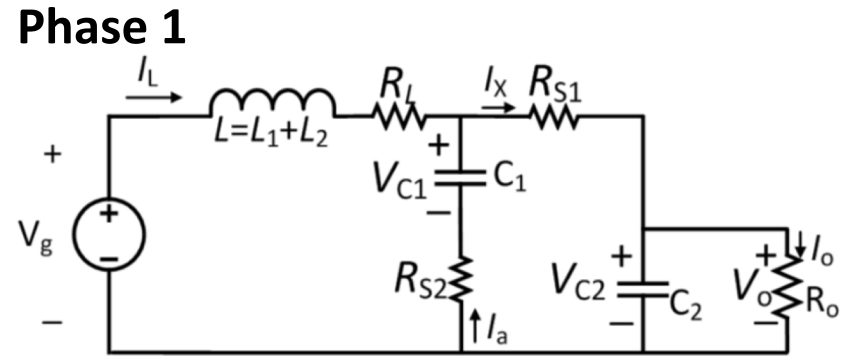


Fig. 3. Schematic of the S-Hybrid step-down converter.

- Ref: G-S. Seo and H-P. Le @ APEC & COMPEL 2017
- Inductor at the input
 - Step-down operation with synchronous SC network
 - Application-aware and environment-aware design:
 - Battery charger application: use USB cable for inductors



S-Hybrid Converter Operation

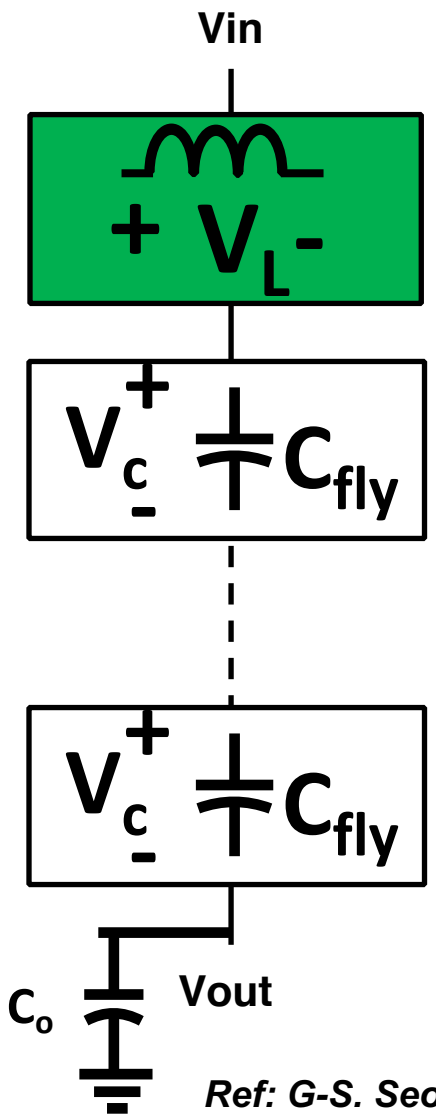

- Soft charging in Phase 2
- But still hard charging in Phase 1


Ref: G-S. Seo and H-P. Le @ APEC & COMPEL 2017

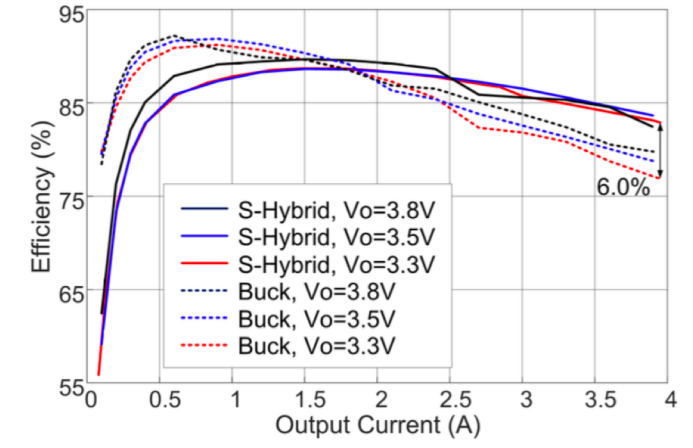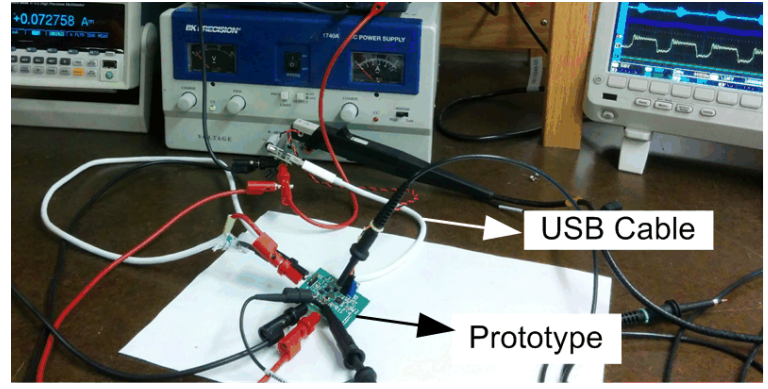Hybrid Converter – Inductor-First Designs



- **S-Hybrid topology @ APEC & COMPEL 2017**
 - Improve 6% efficiency (31.6% loss reduction) at 15 W power for USB charger

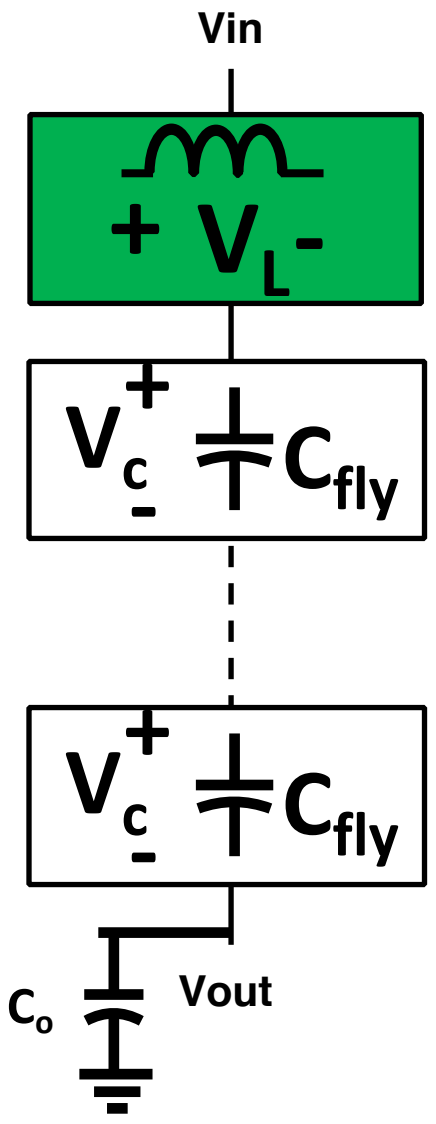**Covered unpublished materials
(To be presented at ISSCC 2019)**






- **Superior integrated version with 9V input.**
 - Proved operations and performance
 - Simultaneous data communication over the cable





(ISSCC 2019)

Hybrid Converter – Capacitor First (DIHC Family)

40-60 V,
100-150 V,
380-420 V

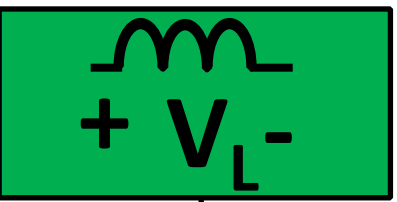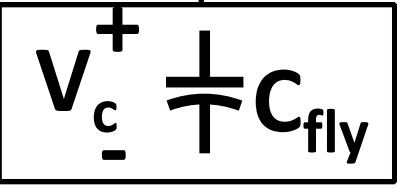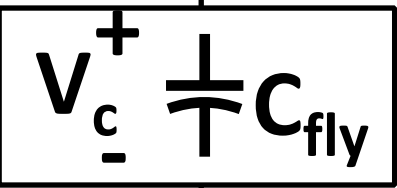


0.5-1.5 V,
1.5-2.5V,
2.5-5 V

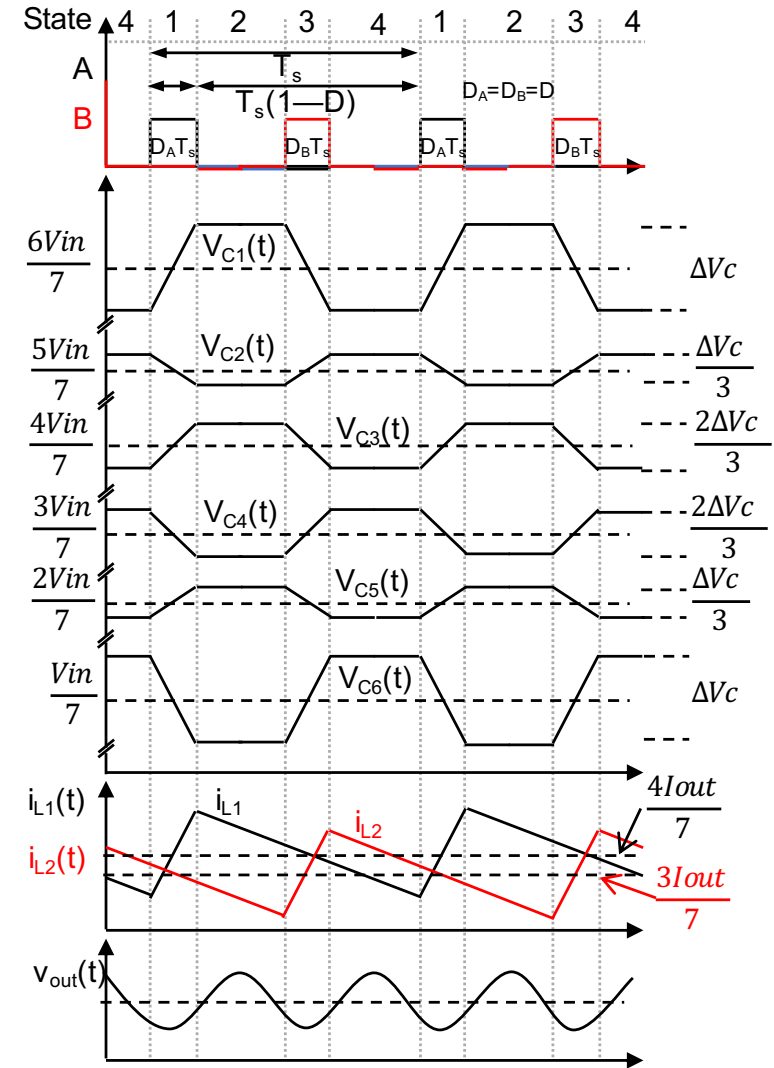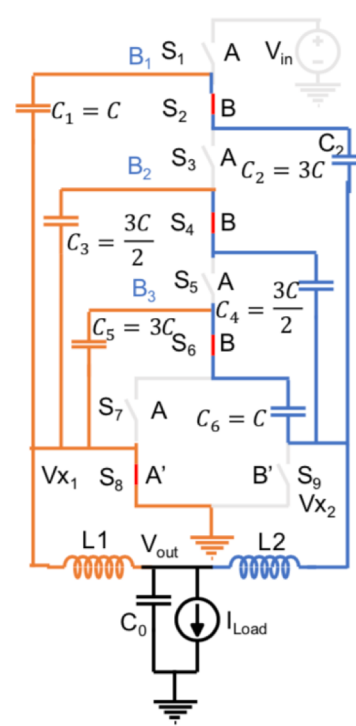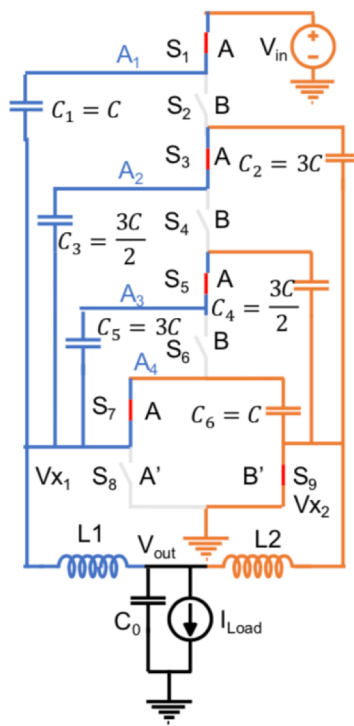
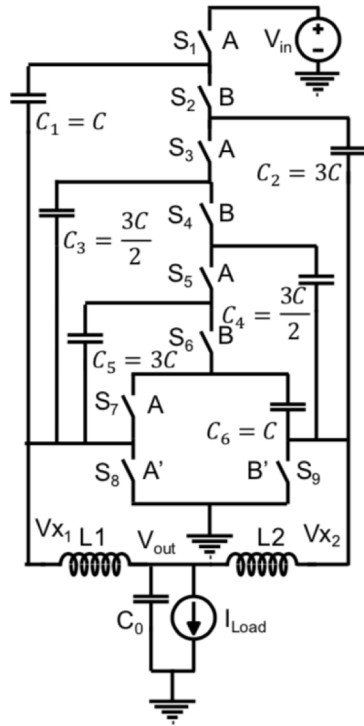


- **Dual inductors hybrid converter:**
 - One charges and one discharges the SC network
- Ref: R. Das, T. Xie, G-S. Seo, and H-P. Le @ ECCE 2018 (2 papers), **APEC 2019 (3 papers)**



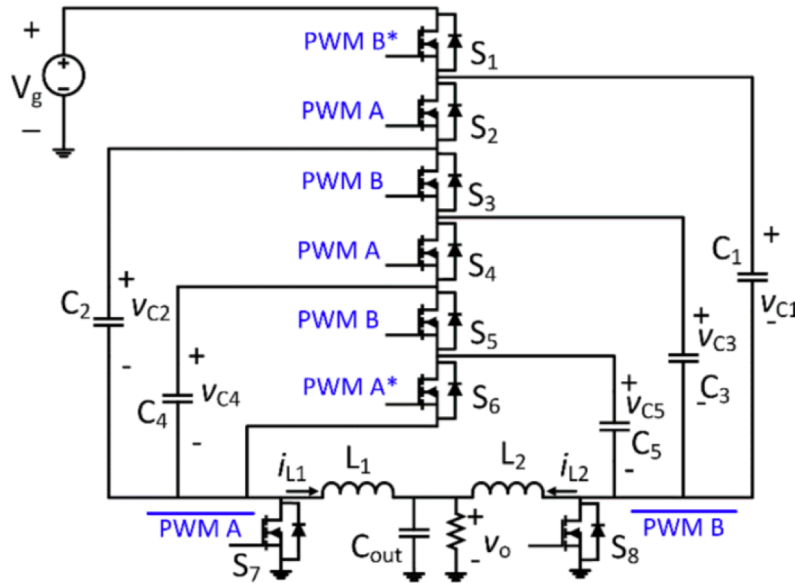
iP1 - DIHC 1 (Even-Level) – Data Center VRM



- **48V to 1.8V (nominal)**
 - 40-54V to 1-2V
- **>95% peak efficiency**
- **Split phase control to avoid hard charging**
- **Ref: G-S. Seo, R. Das, H-P. Le @ ECCE 2018**

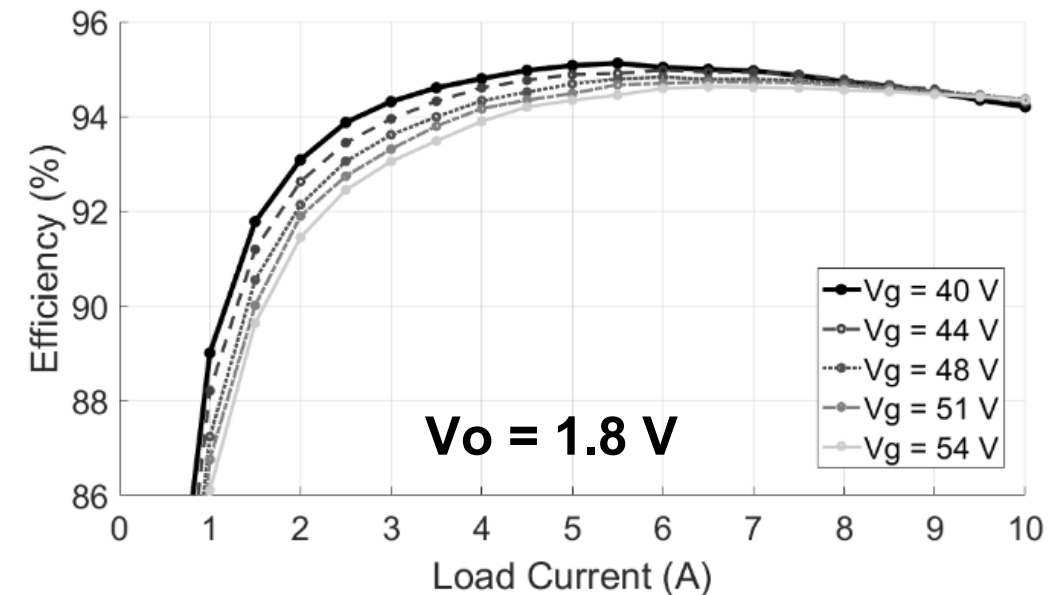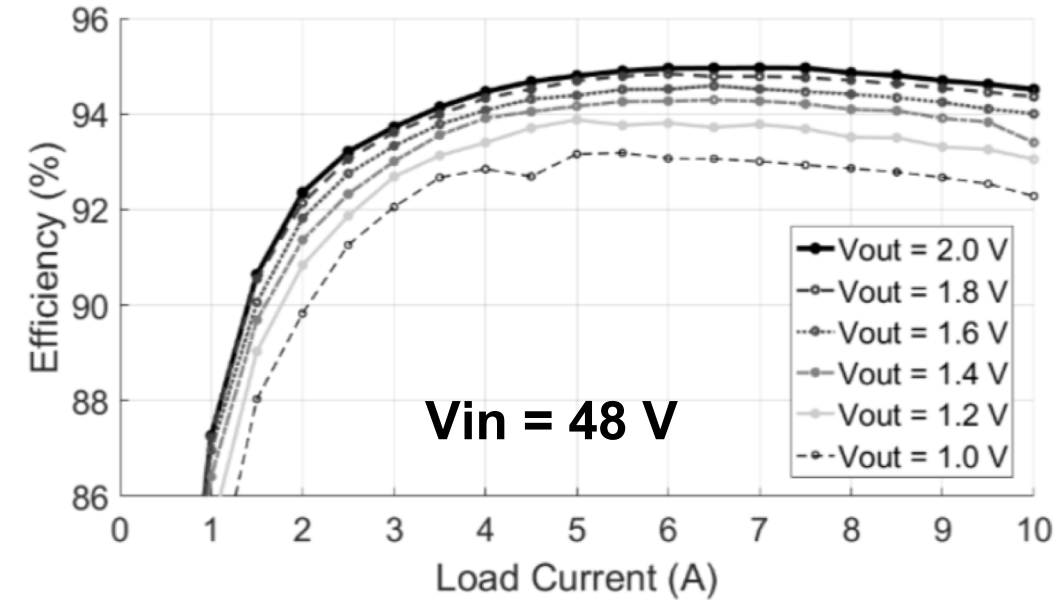

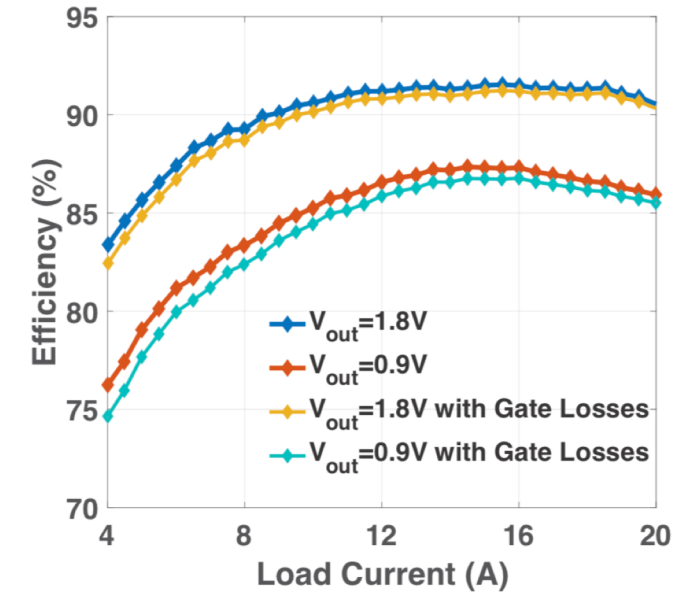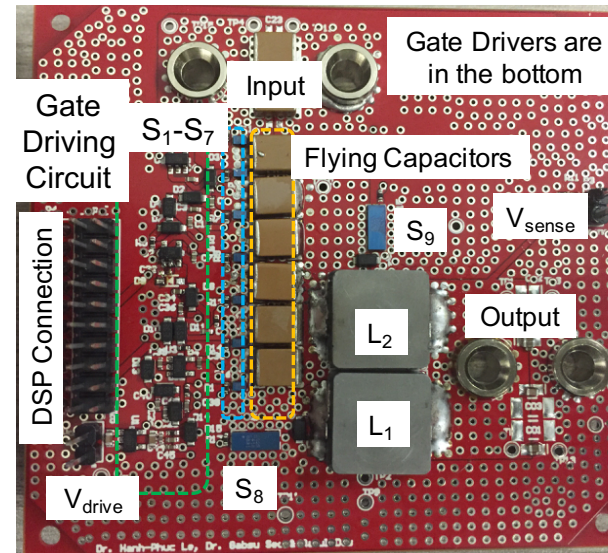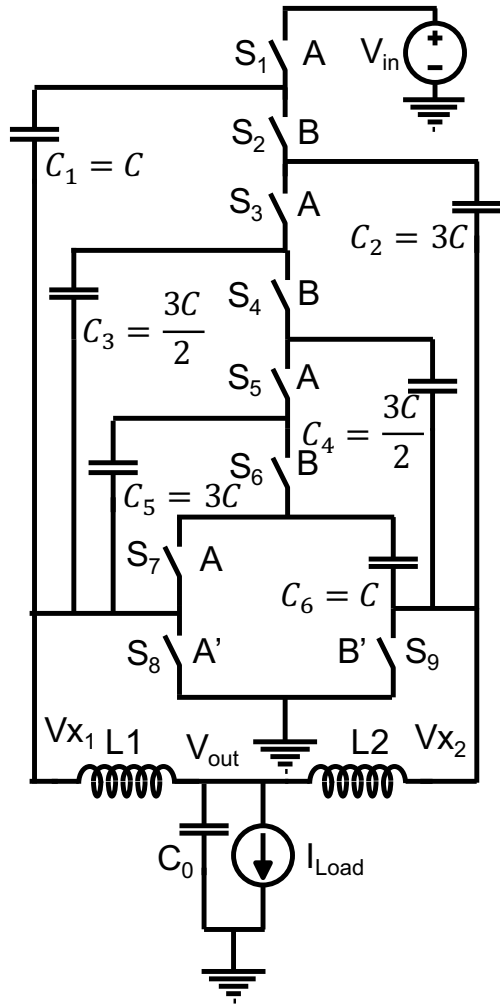iP2 - DIHC 2 (Odd-level) – Capacitor First, Extreme Conversion



- **Extreme conversion ratios:**
 - 87.3% from 120V to 0.9V (130:1) at 15A load
 - 91.5% from 120V to 1.8V at 15A load (66.7:1)
- **Ref: R. Das, G-S. Seo, and H-P. Le @ ECCE 2018**

iP3 - Multiphase Dual Inductor Hybrid Converter (MPDIHC)

- 2 inductors,
- 5 capacitors,
- 6 phases

- Individual charging and discharging phase for capacitors
 - Completely remove hard charging
 - But high side switches need to handle full inductor currents.

- **92.1%, 48V-to-1.8V @4A**

**Covered unpublished materials
(To be presented at APEC 2019)**

iP4 - Multi-Phase Multi-Inductor Hybrid Converter

**Covered unpublished materials
(To be presented at APEC 2019)**

- **3 inductors, 5 capacitors, 6 levels, 3 charging phases**
- **80-W 95%-Efficient 48V-to-1V/2V**

**Covered
unpublished
materials**

iP5 - Dual-Phase Multi-Inductor Hybrid Converter



**Covered unpublished materials
(To be presented at APEC 2019)**

- **4 inductors, 3 capacitors,
4 levels, 2 charging
phases**
- **90W, 92%, 48V-to-1.6V**

Covered unpublished materials

What's Next?


- More advanced hybrid converter topologies will come!
- They will cover large conversion ratios.
- They can support cover “impossibly” large current density.
- Multiple stages
 - But these stages have to **work together synchronously as one** for efficiency.
- Inductors and capacitors will be integrated!
- Power switches (GaN or more advanced MOS) will be more integrated!
- The whole converter will be **integrated ...**
 - ... as everything else has been!

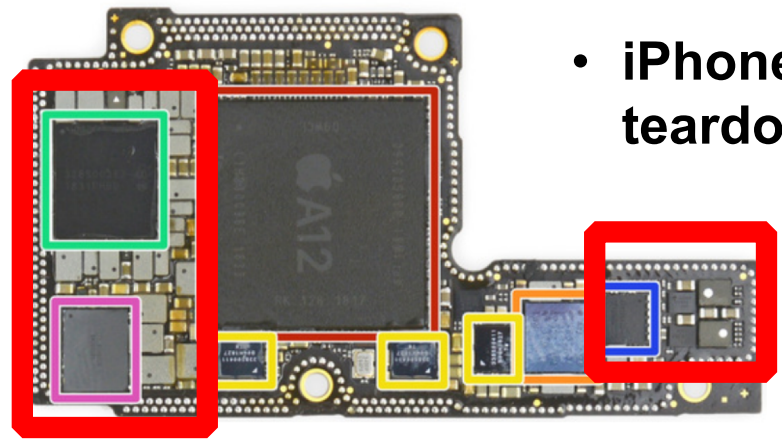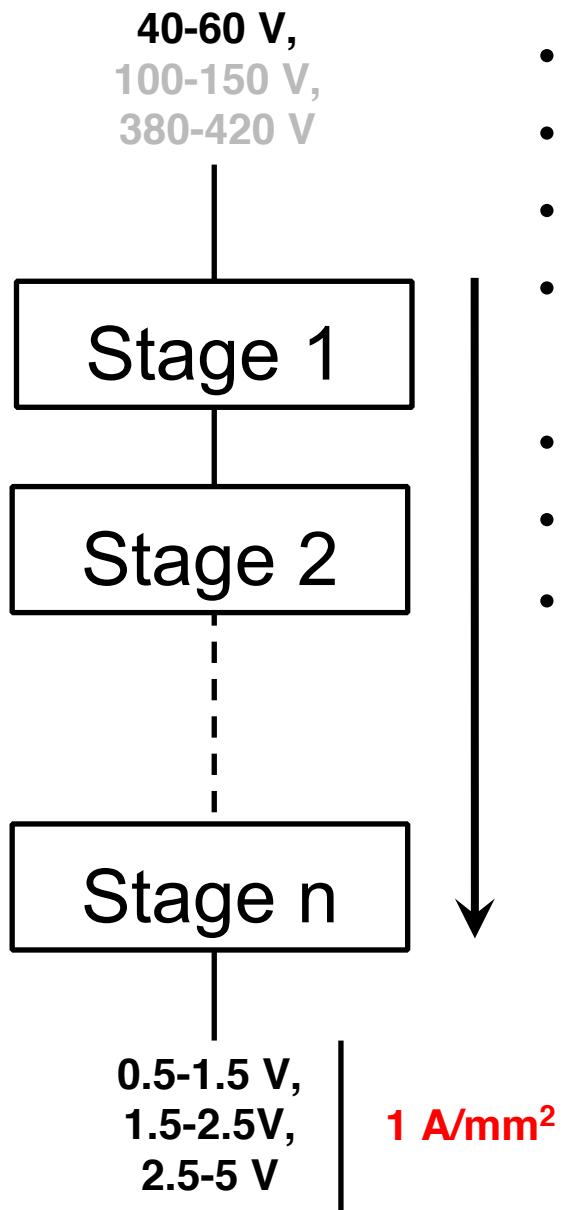

• iPhone XS
teardown

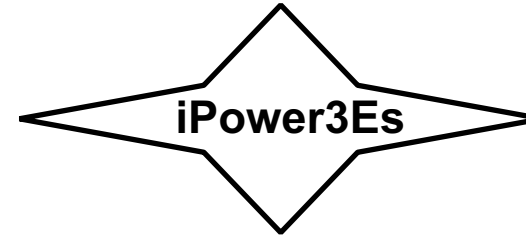• 4 unpublished papers was included in this talk!





Thank you!

Hanh-Phuc Le

<https://www.colorado.edu/ipower3es>
hanhphuc@colorado.edu