

*Greetings from  
Georgia Tech*

---

# Integrated Voltage Regulators for Computing Applications


*Madhavan Swaminathan*

*John Pippin Chair in Microsystems Packaging & Electromagnetics*

*School of Electrical & Computer Engg.*

*School of Materials Science & Engg.*

 *Director, 3D Systems Packaging Research Center (PRC)*




# Outline



- ☐ Overview
- ☐ Low & High Voltage Converters
- ☐ Integrated Magnetics
- ☐ Summary




# Data Centers & Energy

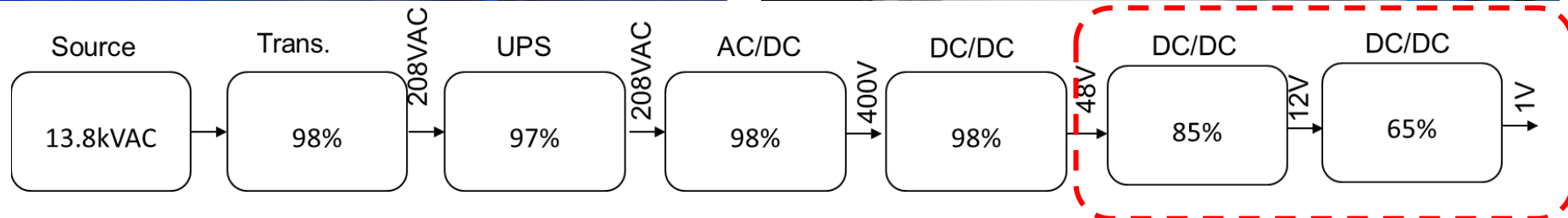



- ❑ Data Centers consume 70 billion KWh today in USA
- ❑ For every 2W drawn from the grid only 1W is used by the Data Center
- ❑ 20% improvement in efficiency can translate to 20% reduction in energy consumption

Source: Dept. of Energy, USA
 
# Efficient Power Delivery in Microsystems



Single Stage Conversion

  


- ❑ Bring the converter (power source) in close proximity to SOC
  - Significantly reduce Cu losses due to shorter current paths
- ❑ Need: High Efficiency, Highly Integrated, Highly Miniaturized, High Conversion Ratio, Single Stage Converters
- ❑ Low energy circuits

# Voltage Regulation and Integration




Buck Converter

 

Business as usual

Advantages: Reasonable signal and power

 
Integration: Low; Solution: Non-disruptive



New technology: SIP with embedded C & L, Buck Converter to SOC on board

Advantages: Slow/fast operation, Medium efficiency, Good Signal and Power Integrity,

 
Integration: Medium; Solution: Non-disruptive



New technology: SIP with embedded C & L, Buck Converter, SOC in package

Advantages: High Performance, High Efficiency, Modular, Excellent Signal and Power Integrity, Cost effective, Thermal Mgmt.

 Integration: Very High; Solution: Disruptive



Intel FIVR

New technology: SOC with on-chip integrated IVR, embedded C & L in package

Advantages: Very High Performance





Challenges: Non-modular, Non-scalable, Thermal Mgmt.

Integration: Ultra-High; Solution: Disruptive

# Integrated Voltage Regulators





IVR on package

    

- ❑ L and C values reduced by increasing switching frequency
- ❑ Provides an opportunity for embedding and miniaturization in package (Reasonable values for L and C)
- ❑ However, losses increase as switching speed increases
  - Transistor losses
  - Inductor losses (DC, eddy current, skin, hysteresis and proximity effect)
- ❑ But tradeoff possible between speed, component size and technology
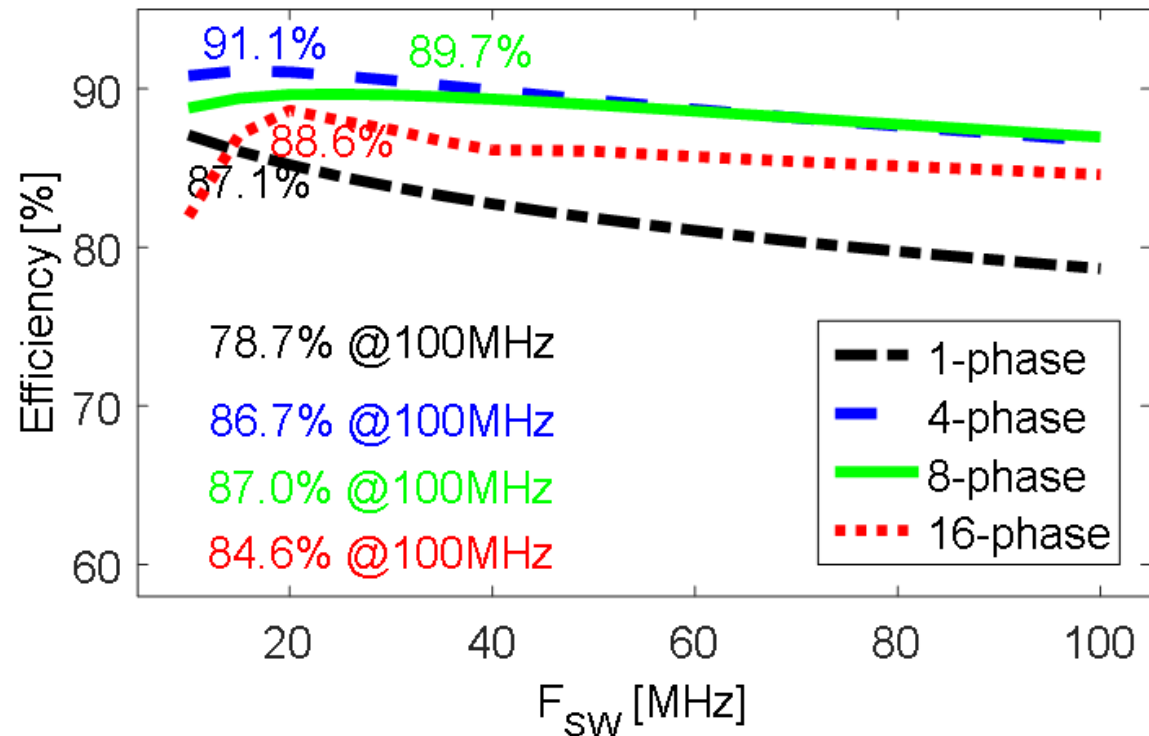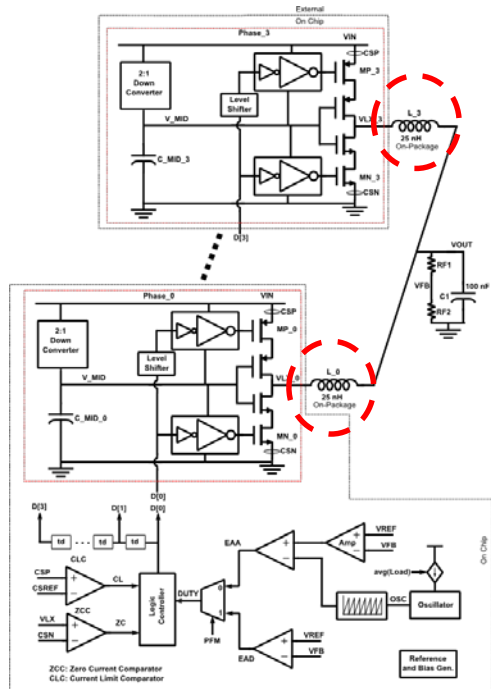
# Design Space Exploration through Chip-Package Co-Design: 1.7V/1V




- ❑ Tradeoff Analysis Critical
- ❑ Number of phases? (4 phases w/100nH total inductance)
- ❑ Maximum power efficiency 91% @ 20MHz
- ❑ Power efficiency improves by ~2% with transistor scaling



# Inductor Design Options


- Several inductor designs with magnetic material possible (published in literature)

 **Spiral inductor on or between magnetic material**




- Advantage:** simple structure / simple fabrication
- Disadvantage:** Inductances larger than a few nH require high permeability or large inductor area

 **Copper winding enclosed by a magnetic material**




- Advantage:** coupling between different inductor phases possible for DC field cancellation
- Disadvantage:** inductor uses single winding – high permeability required

 **“Solenoidal” inductor enclosing a magnetic core**



- Advantage:** higher number of windings – higher inductance for a given permeability
- Disadvantage:** “3D” structure – challenging fabrication

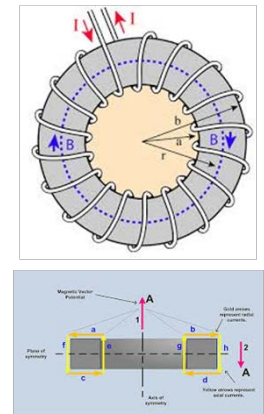**“Toroidal” inductor “Closed loop core**





- Advantage:** Higher inductance, Q & inductance density
- Disadvantage:** “3D” structure – challenging fabrication



# Inductor Design – An Example

- Final design: 4-phase design with 25nH inductance per phase
- Inductor properties as specified below:


	Optimized inductor design
L [nH]	24.8
$R_{DC}$ [m $\Omega$ ]	<b>14.7</b>
$R_{AC}$ [ $\Omega$ ]	2.26
C [pF]	1.9
Area [mm <sup>2</sup> ]	11.6
$L / L_{Aircore}$	3.1
Peak eff. 5V:1V	79.4%
Peak eff. 3V:1V	88.5%
Peak eff. 1.7V:1.05V	91.1%

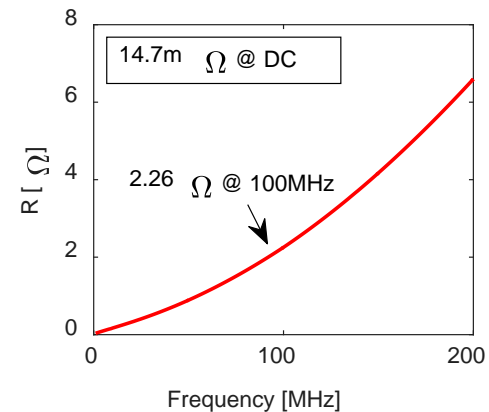 

# Power Losses


22 MHz

Magnetic Core Ind. (NiZn)

 Abs. loss (combined): **0.50 W**

■ FET RESISTIVE ■ FET SWITCHING  
■ INDUCTOR DC ■ INDUCTOR AC  
■ PDN ■ CAP ESR


Air Core Inductor

 Abs. loss (combined): **0.82 W**

■ FET RESISTIVE ■ FET SWITCHING  
■ INDUCTOR DC ■ INDUCTOR AC  
■ PDN ■ CAP ESR


100 MHz

Magnetic Core Ind. (NiZn)

 Abs. loss (combined): **0.74 W**

■ FET RESISTIVE ■ FET SWITCHING  
■ INDUCTOR DC ■ INDUCTOR AC  
■ PDN ■ CAP ESR

Air Core Inductor

 Abs. loss (combined): **1.04 W**

■ FET RESISTIVE ■ FET SWITCHING  
■ INDUCTOR DC ■ INDUCTOR AC  
■ PDN ■ CAP ESR

❑ 1.7/1V 5A Load Current (50% Load)

❑ 25nH inductance/phase

❑ 22MHz

- Ferrite Core: 47% FET; 28% Inductor (DC: 18% AC: 10%); 25% PDN
- Air Core: 29% FET; 56% Inductor (DC: 51% AC: 5%); 15% PDN


*Magnetic core increases inductance density and lowers DC resistance*

S. Mueller, Member, M.L. F. Bellaredj, A. K. Davis, P. A. Kohl, and M. Swaminathan, Design Exploration of Package-Embedded Inductors for High Efficiency Integrated Voltage Regulators", IEEE Trans. CPMT, Accepted, 2018.

## Impact of Heating on DC Loss


□ Impact of inductor heating on overall efficiency [6]:

### 5V:1V conversion

 

- 9% of overall loss related to resistance (“inductor DC” and “PDN”)
- **Inductor heating changes overall efficiency at 100 MHz from 70.5% to 70.2% (small)**


### 1.7V:1V conversion

 

- 17% of overall loss related to resistance (“inductor DC” and “PDN”)
- **Inductor heating changes overall efficiency at 100 MHz from 86.7% to 86.4% (small)**

[6] Modeling and Design of System-in-Package Integrated Voltage Regulator with Thermal Effects, S. Mueller, A. K. Davis, M. L. F. Bellaredj, A. Singh, K. Z. Ahmed, S. Mukhopadhyay, P. A. Kohl, M. Swaminathan, Y. Wang, J. Wong, S. Bharathi, Y. Mano, A. Beece, B. Fasano, H. Fathi Moghadam and D. Draper, To be presented at EPEPS, CA, Oct. 23-26, 2016

# Recent Work

 

Screen printed  
inductor on  
Organic Substrate

	[1]	[2]	[3]	[4]
Phases	4	Up to 16	8	8
Process node	130nm	22nm	45nm	45nm
Integration level	Package	Package	Silicon interposer	Die
Inductor type	Magnetic core	Air core	Magnetic core	Magnetic core
Inductance @100MHz	22.8nH	2.5nH	8nH	1.5nH
Peak eff. (1.7V:1V)	91.7%	90% (1.7:1.05)	82% (1.6:0.83)	84% (1.5:1.15)
Peak eff. (3V:1V)	89.6%	Not specified	Not specified	Not specified
Peak eff. (5V:1V)	81.3%	Not specified	Not specified	Not specified

[1] S. Mueller et al, *Design Exploration of Package-Embedded Inductors for High Efficiency Integrated Voltage Regulators*, IEEE Trans. CPMT, 2018.

[2] E. A. Burton et al., "FIVR - Fully integrated voltage regulators on 4th generation Intel(R) Core™ SoCs," in *2014 Twenty-Ninth Annual IEEE Applied Power Electronics Conference and Exposition (APEC)*, 2014.

[3] K. Tien et al., "An 82%-efficient multiphase voltage-regulator 3D interposer with on-chip magnetic inductors," in *2015 Symposium on VLSI Technology (VLSI Technology)*, 2015.

[4] H. K. Krishnamurthy et al., "20.1 A digitally controlled fully integrated voltage regulator with on-die solenoid inductor with planar magnetic core in 14nm tri-gate CMOS," in *2017 IEEE International Solid-State Circuits Conference (ISSCC)*, 2017.


Courtesy: PDES, GT & JUMP-SRC (ASCENT)




# Machine Learning for IVR Optimization



Overall SoP IVR Architecture

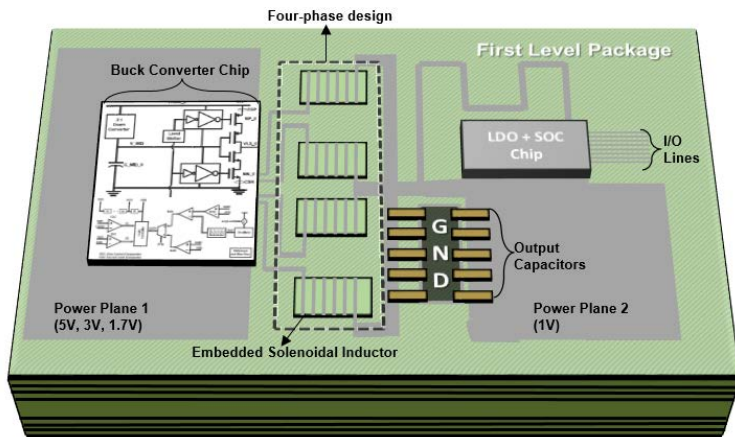

Embedded Solenoidal Inductor

 

Control Parameters

Parameter	Unit	Min	Max
Gap between windings	g	mil	2 20
Number of windings	N		3 13
Size of via	s <sub>v</sub>	μm	50 103
Copper Trace Width	w <sub>c</sub>	mil	2 20
Copper Thickness Bottom	t <sub>c,b</sub>	μm	35 170
Copper Thickness Top	t <sub>c,t</sub>	μm	35 170
Dielectric Thickness	t <sub>d</sub>	μm	50 650
Dielectric Width	w <sub>d</sub>	μm	50 350
Magnetic Core Thickness Ratio	t <sub>m</sub>		0.1 1
Magnetic Core Width offset	Δw <sub>m</sub>	mil	0 100

	Hand Tuned	Non-Linear	GP-UCB	IMGPO	TSBO
Inductor Area	11.3 mm <sup>2</sup> (+56.1%)	25.19 mm <sup>2</sup> (+79.6%)	5.18 mm <sup>2</sup> (%0.4)	6.64 mm <sup>2</sup> (%28.1)	5.16 mm <sup>2</sup>
Peak Efficiency	79.4%	78.6%	84.9%	84.4%	85.1%
CPU Time	N/A	>185 min (+72.9%)	117.33 min (+57.4 %)	115.6 min (+56.7 %)	50.1 min


**Hand Tuned:** S. Mueller *et al.*, "Design of High Efficiency Integrated Voltage Regulators with Embedded Magnetic Core Inductors," ECTC'16.

**Optimized:** H. M. Torun *et al.* "A Machine Learning based Global Optimization Algorithm and its Application to Integrated Systems". TVLSI '18

# Future Power Delivery Solutions

 
## HIGH VOLTAGE DC CONVERTER STATE OF THE ART

Integrated Si ▲ Integrated GaN ● Discrete GaN ■ Preliminary data with ZVS estimate





- ❑ GaN Converter: Up to 10x higher switching frequency at comparable efficiency
- ❑ Breakthrough in p-channel GaN FinFET with record on-current – a key enabler for GaN-CMOS
- ❑ Opportunity: GaN Buck Converters w/ Magnetics for 48V/1V Conversion
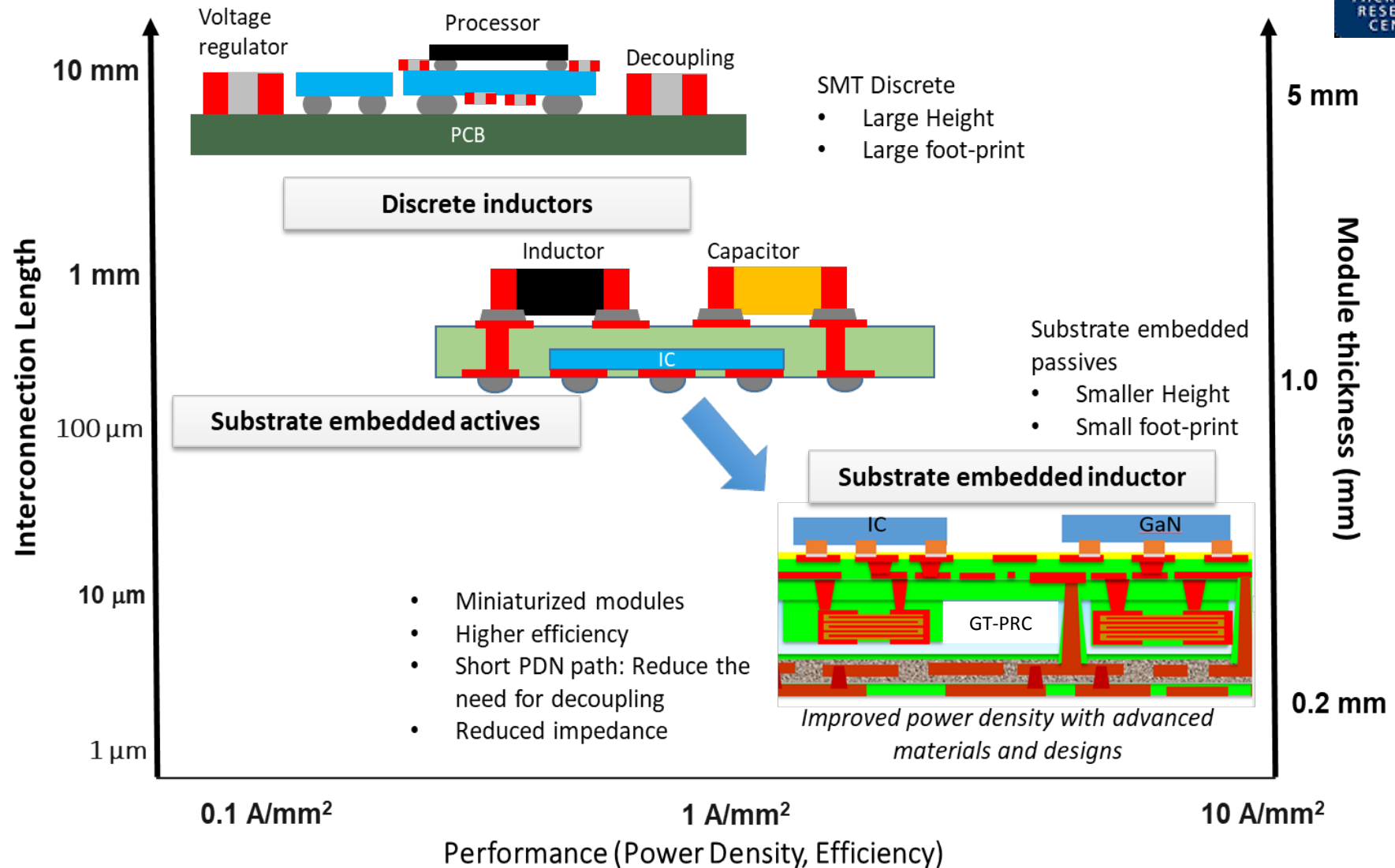
# Integrated Voltage Regulators (revisited)


 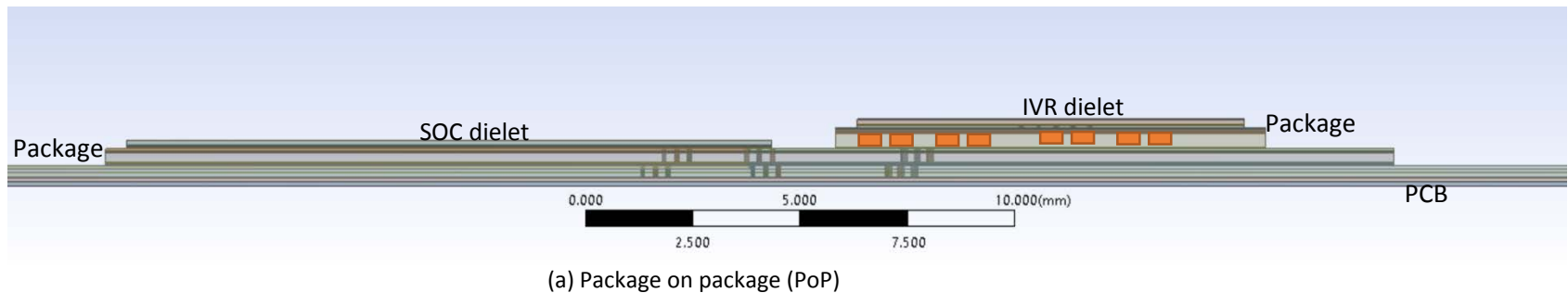
# Thermal Management

- ❑ Two heterogeneous architectures being explored
- ❑ Inductors embedded either in a package or in the substrate of the multi-chip package



	SOC (12mmx12mmx0.75mm)	IVR (10mmx10mmx0.75mm)	Embedded inductor (2mmx1mmx0.35mm)
TDP (W)	100	10	0.15




# Thermal Coupling and Joule Heating major issues


- ❑ Embedded inductors reach high temperatures in the range of 89-107°C
- ❑ Joule heating neglected here. Inductor temperature expected to increase

Configuration	Fan flow (CFM)	$T_{\text{ambient}}$ (°C)	$T_{\text{inductor}}$ (°C)	$T_{\text{cpu\_junction}}$ (°C)
Package on package	30	42	107	93.5
Multi-chip package	30	42	89.2	88.9

(a) Package on package

 

(b) Multi-chip package

 




## Summary

- ☐ Integrated Voltage Regulators (IVR) can lead to significant energy savings
- ☐ Requires integrated integrated magnetics and dielectrics
- ☐ Thermal management critical
- ☐ Heterogeneous Integration is the way forward (for various reasons)!

# Thank you

 

[www.prc.gatech.edu](http://www.prc.gatech.edu)  
[www.c3ps.gatech.edu](http://www.c3ps.gatech.edu)