

Miniaturizing Galvanically Isolated Power Supplies for Integration in Semiconductor Products

Presenter: Tim Merkin (tim@ti.com)

Kilby Labs, Dallas TX, Texas Instruments

Acknowledgements:


Orlando Lazaro (Kilby Labs, Dallas TX, Texas Instruments)

Giacomo Calabrese, Nicola Bertoni, Michael Lueders, Oliver Nachbaur (Kilby Labs, Freising Germany, Texas Instruments)


History of Integrated Isolation in ICs

"Transformer 20 may be integrated by manufacturing two parallel line segment conductors upon the integrated circuit semiconductor chip."


1977 – Patent transformer isolation

 

1968 – First patent on optical isolation

 

1978 – Thyristor load with photocoupler

 


1980 – Proliferation of optical isolated products


High Speed Optocouplers

Device	Description
6N135	Transistor Output
6N136	Transistor Output
HCPL-2502	Dual Channel Transistor Output
HCPL-2530	Dual Channel Transistor Output
HCPL-2531	Dual Channel Transistor Output
6N137	Optically Coupled Logic Gate
HCPL-2601	High Common Mode Rejection, Optically Coupled Logic Gate
HCPL-2602	Optically Coupled Line Receiver
HCPL-2630	Dual Channel Optically Coupled Gate


1986 – Invention of capacitive isolation

 


2000 – Magneto-resistive bridge

 


1997 – iCoupler for signal

 

Burr Brown capacitive ISO150

 


2007 – XFMR iso DC/DC + IO

 

2017 – XFMR air-core + IO



2016 – Silabs cap based power

 


Emergence of integrated power isolation

2021 – XFMR iso DC/DC




MID1W0505A

 


2019 – XFMR magcore




UCC12050 High-Density

 

2023 – Cap-based iso pwr

 


 2022 – XFMR (aircore) iso DC/DC and FET driver for SSR




Chip-scale Power Transfer Methods

 Definition: A “chip scale” isolated power supply fits within standard semiconductor packages and provides the energy to operate electrical circuits on the opposite side of a galvanic isolation barrier




Thermoelectric generators

 

- ✓ No EMI
- X Poor Efficiency
- X Very Intricate packaging
- X Hard to generate ΔT
- X Complicated CKTS


Cannot efficiency limits efficiency practically usually < 3%

$$\eta = 1 - \frac{T_{COLD}}{T_{HOT}}$$

 


P_available ~50W/mm² for ΔT = 10°C
[1] – Nature, CMOS integrated TEG

Optical energy transfer

 


 - ✓ No EMI
- X Poor Efficiency
- X Intricate packaging
- ✓ LEDs commonplace
- ✓ Simple CKTS
- X CTR degradation with age




[4] – Opto power transfer

Capacitive power transfer

 


 - X EMI non-negligible
- Δ Moderate Efficiency
- ✓ Simplest packaging
- ✓ Iso CAPs CMOS compatible




[3] – ICPT (isolated capacitive power transfer)

Transformer power transfer

 

 - X EMI non-negligible
- ✓ Best Efficiency
- Δ Moderate packaging
- ✓ Transformer on-silicon or in package, air-core and mag-core common






[2] – Integrated transformer


Less Power Typically < 100uW Typically < 100mW Typically < 2W More power

*Honorable mentioned: Piezoelectric. One day?

Capacitive power transfer: Basic idea

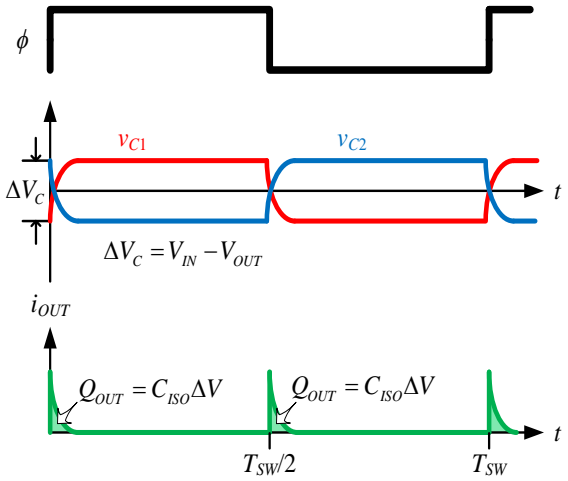  

Time-Averaged Model:

 

Principles


- Charge transfer occurs immediately after state transitions
- Capacitor voltages forced via DC voltages
- Charge $Q_{OUT} = C_{ISO} \Delta V_C$ delivered every half-cycle:

$$\langle i_{OUT} \rangle = \frac{Q_{OUT}}{T_{SW}/2} = 2 f_{SW} C_{ISO} (V_{IN} - V_{OUT})$$


Practical Considerations

- V_{OUT} voltage source can be replaced with a large C_{OUT} , ($C_{OUT} \gg C_{ISO}$)
- Capacitor voltages are compared half-cycle to half-cycle
 - With ΔC_{ISO} or $\Delta T/2 \rightarrow$ caps do not drift
- Synchronous rectifier can be replaced with diode bridge

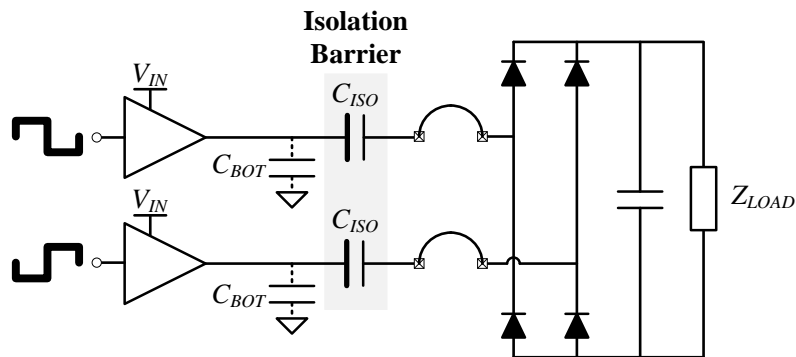Capacitive power transfer: Overcoming parasitics



 - Efficient capacitive power transfer is challenging when using integrated isolation capacitors, C_{ISO}
- On-Chip isolation caps ($\sim 5\text{kV}$ rated) have large bottom plate capacitance (As large as $C_{BOT} \approx 5C_{ISO}$)
- Consider an H-bridge inverter driver example:



- Maximum Power is Limited:

$$P_{(OUT)MAX} \sim C_{ISO} V_{IN}^2 f_{SW}$$

- Hard-Charging C_{BOT} is very lossy:


$$P_{DRV} \sim C_{BOT} V_{IN}^2 f_{SW} \approx 5C_{ISO} V_{IN}^2 f_{SW}$$

- Output power req. achieved by increasing C_{ISO} , V_{IN} , and/or f_{SW}

- P_{DRV} scales directly with $P_{OUT(MAX)}$
 η is constant as C_{ISO} , V_{IN} , or f_{SW} vary

Dealing with bottom plate parasitics

Resonant Drive

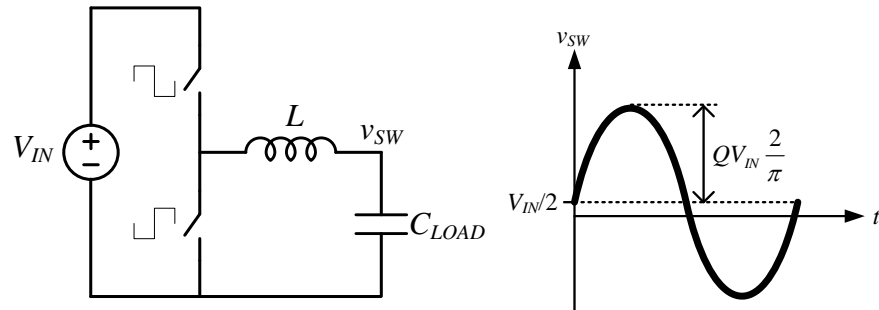


Boost drive voltage using resonance with series inductor

Pro: Driver losses are reduced by $Q \frac{4}{\pi}$

Con: On-Chip inductors exhibit poor Q (less than 5), until frequencies are $>200\text{MHz}$ and each coil can be large

Adiabatic Drive

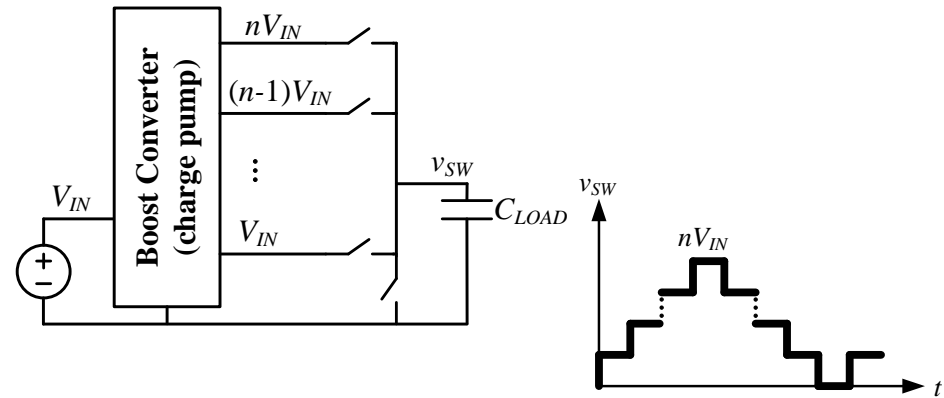


Boost drive voltage with multi-level charge-pump

Pro: Driver losses are reduced by n (# of levels - 1)

Con: Switches require bi-directional blocking, most switches still block high voltage and gate drive not straight-forward

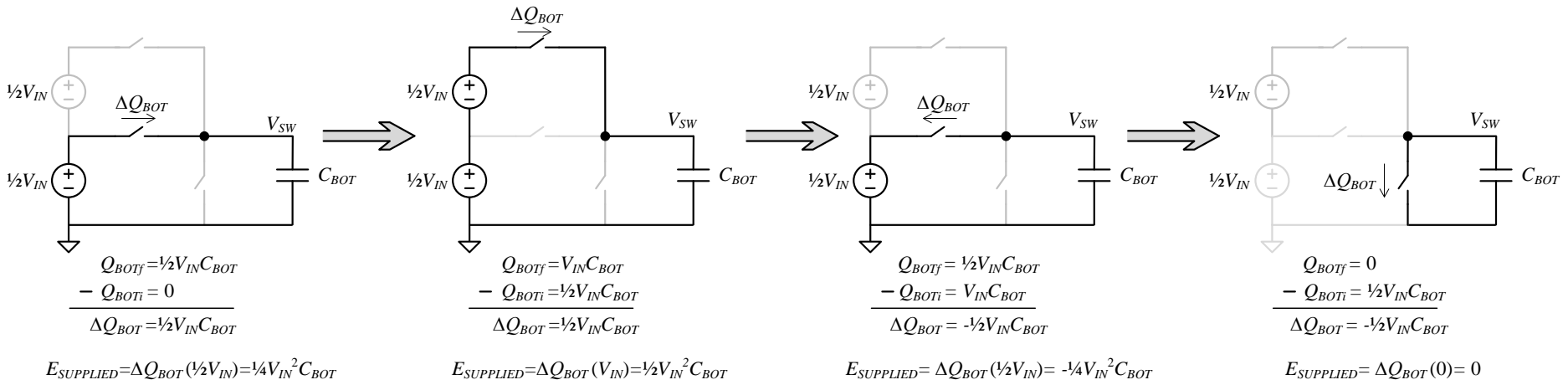Dealing with bottom plate: Adiabatic driving




- The total energy consumed to take V_{SW} to V_{IN} and back to ground is:
 $E_{SW} = C_{BOT}V_{IN}^2/2$ or in terms of power $\rightarrow P_{SW} = f_{SW}C_{BOT}V_{IN}^2/2$
 - This is **half of the power for the direct drive case!**


The more number of levels the more efficient we are!

$$P_{SW(n-level)} = \frac{P_{SW(direct-drive)}}{n-1}, \text{ where } n \text{ is the number of levels (3 in above)}$$


n-level Time-Averaged Model:

 

Cap power transfer: Linear model

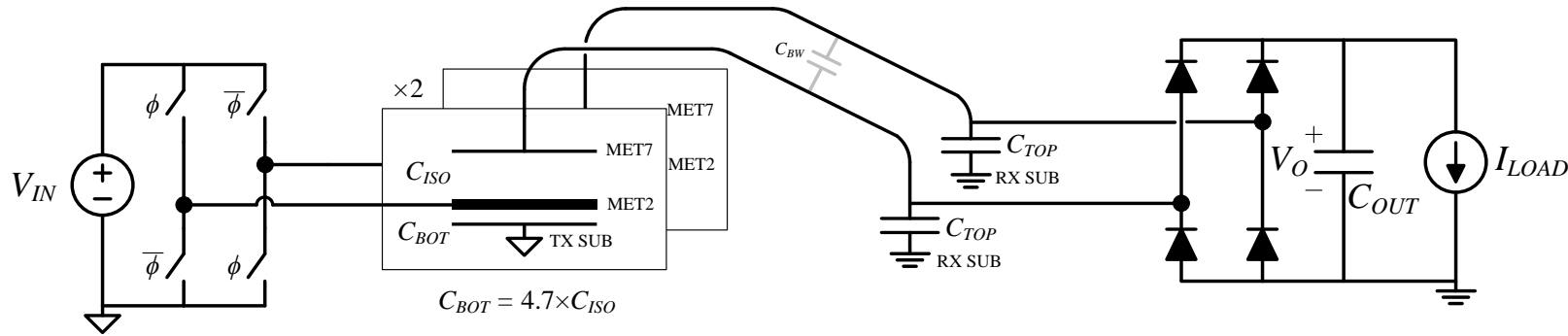

Simplified time-averaged model

 

$$R_{EQ_BOT} = \frac{n-1}{2f_{sw} C_{BOT}}$$

$$R_{EQ_TOP} = \frac{1}{2f_{sw} (C_{TOP} + 2C_{BW})}$$

$$R_{EQ_ISO} = \frac{1}{2f_{sw} C_{ISO}}$$



- Charging and discharging parasitic top and bottom plate capacitors consume current
 - Modeled with $R_{EQ(BOT)}$ and $R_{EQ(TOP)}$

$$V_{OUT} = V_{IN} \underbrace{\frac{C_{ISO}}{C_{ISO} + C_{TOP} + 2C_{BW}}}_{\text{cap divider}} - \underbrace{\frac{I_{LOAD}}{2f_{sw} (C_{ISO} + C_{TOP} + 2C_{BW})}}_{\text{load line}} - \underbrace{2V_D}_{\text{diode drops}}$$

- Increasing V_{OUT}
 - Increase $C_{ISO} \rightarrow$ Expensive + C_{BOT} losses ($C_{BOT} \propto C_{ISO}$)
 - Increase $f_{sw} \rightarrow$ C_{BOT} losses + divider limited + gate-drive
 - Reduce $I_{LOAD} \rightarrow$ Only so much one can do
 - Increase $V_{IN} \rightarrow$ C_{BOT} losses


Common-mode EMI

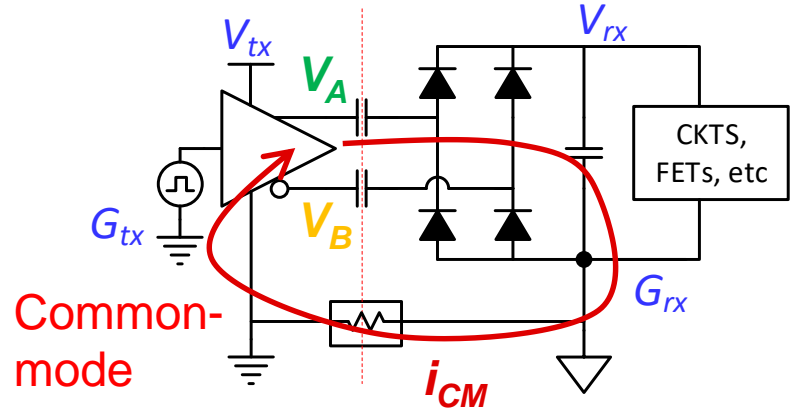 - Asymmetry results in common-mode current
 - Cap value mismatch
 - TX transient mismatch (delays and waveform shape)
 - Transformer based system also has similar issue (*C_{par}*)





Common-mode current loop

 Mismatch in delay between V_A and V_B causes common mode current injected across isolation barrier



Isolated Transformer Power transfer on-chip

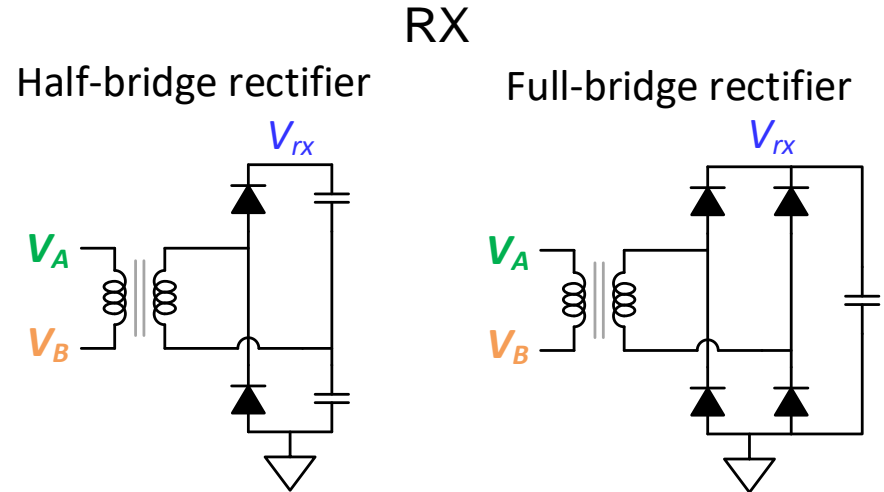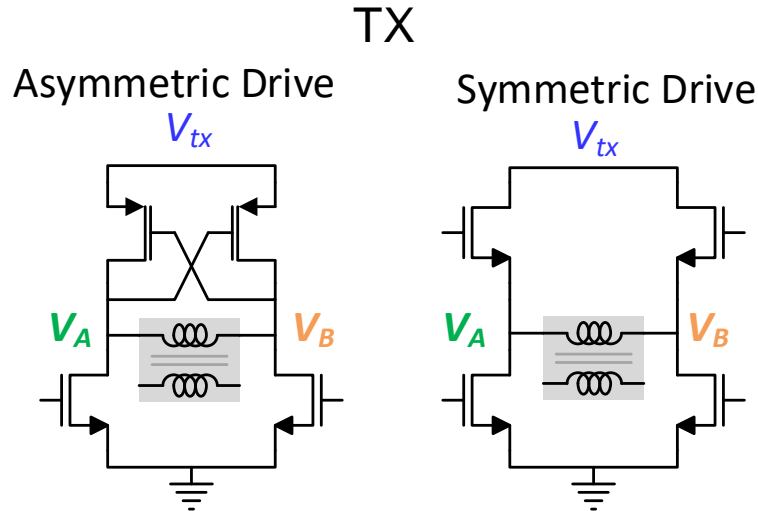
- Dual active bridge derived topologies most common
 - ZVS on TX driver can be achieved → Needed for efficiency
- Different TX and rectifier methods → Asymmetric and Symmetric
 - Symmetric better for EMI → more gate charge loss for TX




Can be passive or active “self-driven”
For active, non-self driven, expensive extra comms
channel needed. Sometimes worth it for higher power.

Isolated Transformer Power transfer on-chip

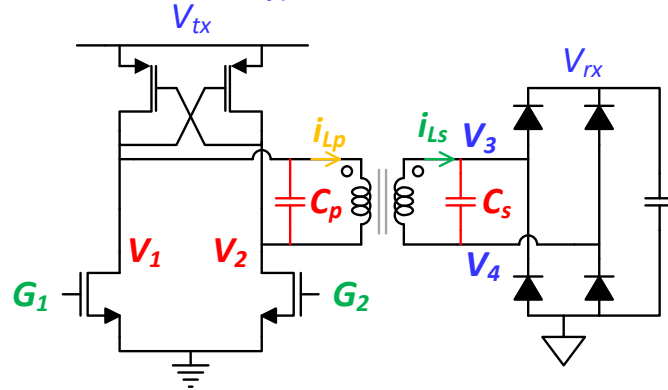Simple DAB derived topology (active on primary, passive rectification on secondary)




- Small package area \rightarrow Low achievable L, poor Q, k compared to a discrete component
- Need resonant operation on primary for efficiency
- Parasitics caps and transformer co-designed to operate in ZVS for a given drive Fsw and duty \rightarrow phase shift inherent, not directly controlled
- Regulation can be controlled by “bursting” or shunt regulation at secondary (poor efficiency)
- Must operate at very high frequency to keep transformers sizes small to fit on chip

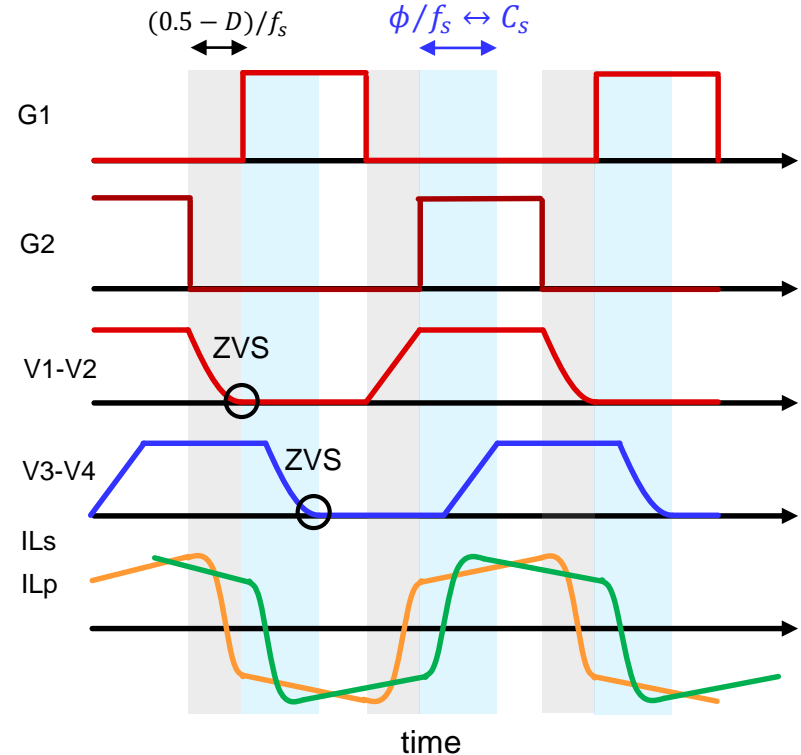

Common-mode clamping

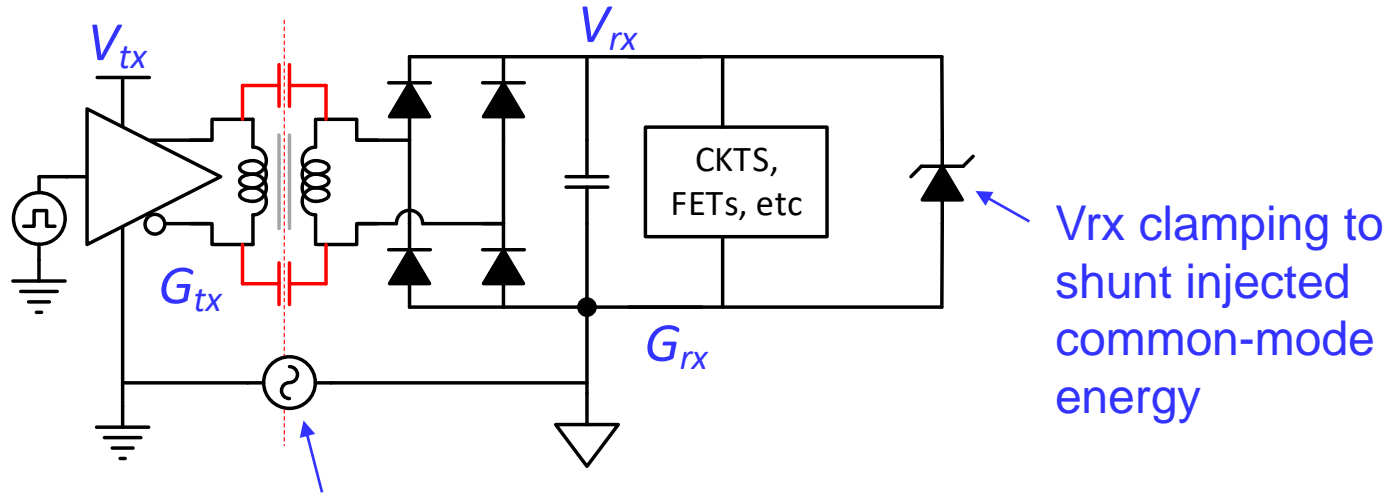- Common mode noise injection rectifies and can charge up on chip supply (need clamping and protection)



Common mode noise sources (incident RF, ground bounces in system, etc... inject current and charge V_{rx} → Need clamping

Summary

- Capacitor and transformer methods most common for on-chip isolated power supplies → Small size, compatible with CMOS and common packaging technologies
- EMI challenges arise due to asymmetries causing common mode injection → addressed by symmetry (both on TX and RX)
- Capacitor and transformer methods/circuits remarkably similar, for example, same passive rectifier can work for both
- Proliferation of commercially available on-chip isolated supplies (< 2W), expect trend to continue → Further improvements in total power, efficiency, cost, EMI
- ZVS, charge recycling, resonant drive, needed to make supplies as efficient as possible

References

- [1] – Gangyi Hu, Hal Edwards, Mark Lee, “Silicon integrated circuit thermoelectric generators with a high specific power generation capacity”, Nature Electronics, Vol. 2, July 2019.
- [2] – Yue Zhuo, et. al., “A 52% peak efficiency > 1-W Isolated Power Transfer System Using Fully Integrated Transformer with Magnetic Core”, IEEE JSSC, Vol. 54, No. 12, December 2019.
- [3] – Lei Chen, Joseph Sankman, Rajarshi Mukhopadhyay, Mark Morgan, Brian Ma, “A 50.7% Peak Efficiency Subharmonic Resonant Isolated Capacitive Power Transfer System with 62mW Output Power for Low-Power Industrial Sensor Interfaces”, ISSCC 2017
- [4] – ACPL-K30T, “Automotive Photovoltaic MOSFET Driver”, <https://docs.broadcom.com/doc/AV02-4500EN>