

Benefits and Constraints of SMPS Integration in Wireless Multi Media Terminals



D. Chesneau
F. Hasbani


November 24, 2008

Power SoC 08

200mm²

2/3

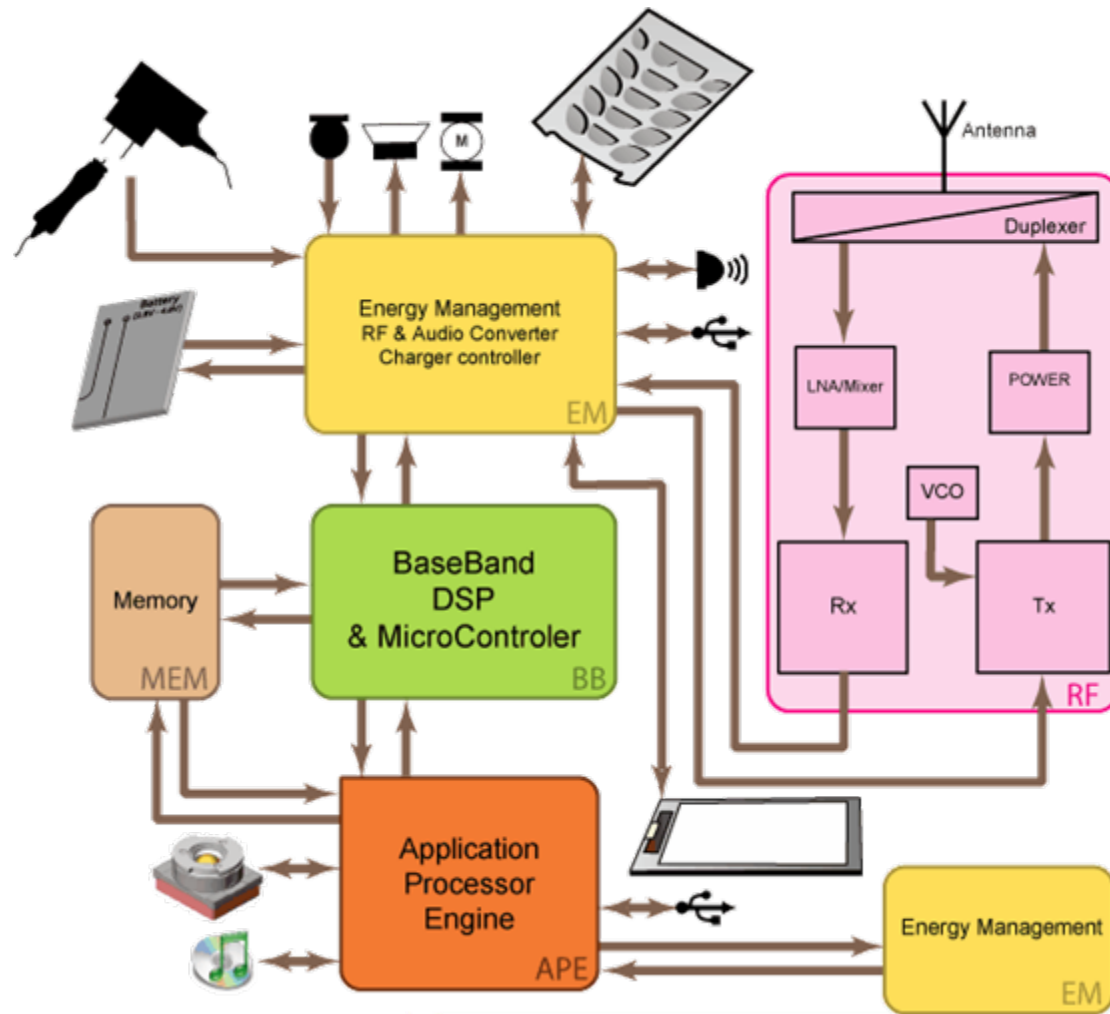Introduction: Mobile Terminal Typical Content



Introduction: The Problem

- ▣ More and more functions in mobile terminals
- ▣ Need massive integration
- ▣ Power consumption increases drastically
- ▣ But users still request large autonomy

- ▣ How to achieve
 - ▣ High Efficiency
 - ▣ Low Volume
 - ▣ Low Cost



Outline

Introduction

I

SMPS for Digital Base Band and Memories

- Requirements / Compatibility
- Constraints
- Possible Solutions

II

SMPS for Audio and Low Power RF functions


III

SMPS for RF Power Amplifier

Conclusion

I.0: Power Management Units Context

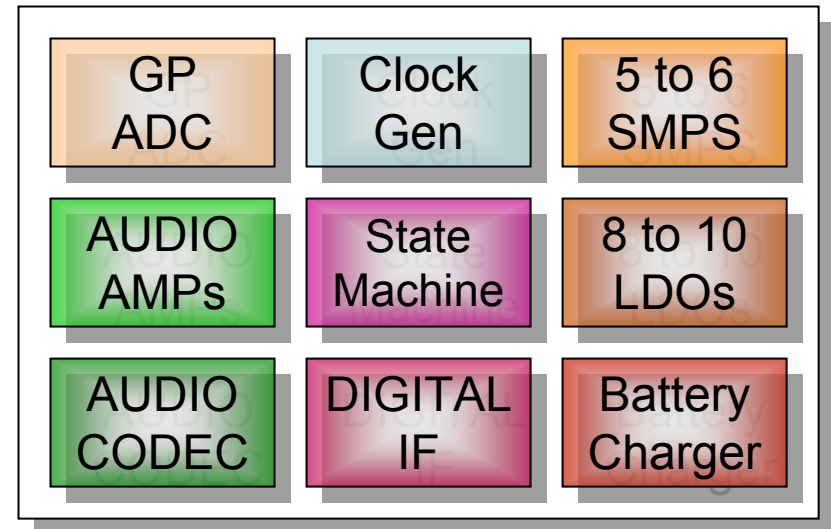- Companion chip of DBB
- Complex IC
- Many IOs (200 to 300)
- Low Cost CMOS (5V compliant)
- BGA package



I.1: SMPS for DBB Requirements

High Efficiency
Power Supply

$$\frac{MHz}{(mW \bullet mm^2)}$$

I.1: SMPS for DBB Requirements

High Efficiency Power Supply


■ At light and medium loads

- Low quiescent current
- Low switching losses
- Low AC losses in coil magnetic core

■ At heavy loads: Low ohmic losses


- In Power Transistors $\Rightarrow$ Low $R_{DS(on)}$
- In Package $\Rightarrow$ Low parasitic resistance
- In power coil $\Rightarrow$ Low DC resistance

I.1: SMPS for DBB Requirements

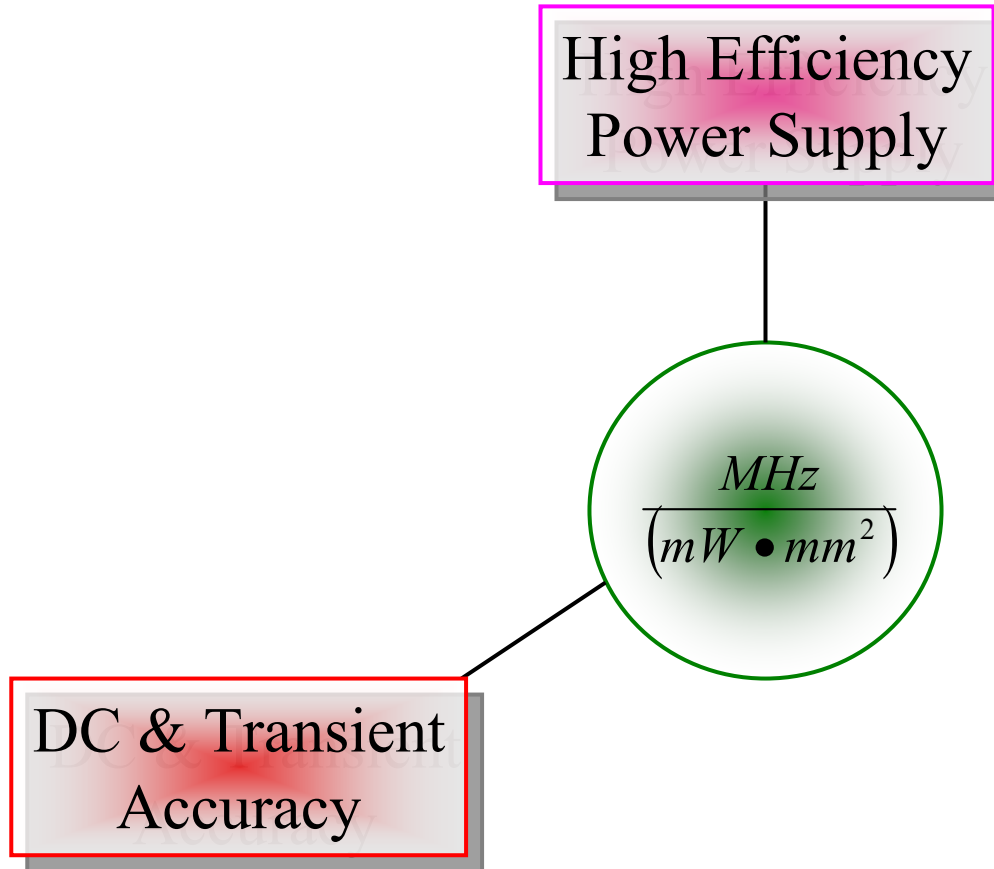


I.1: SMPS for DBB Requirements

DC & Transient Accuracy

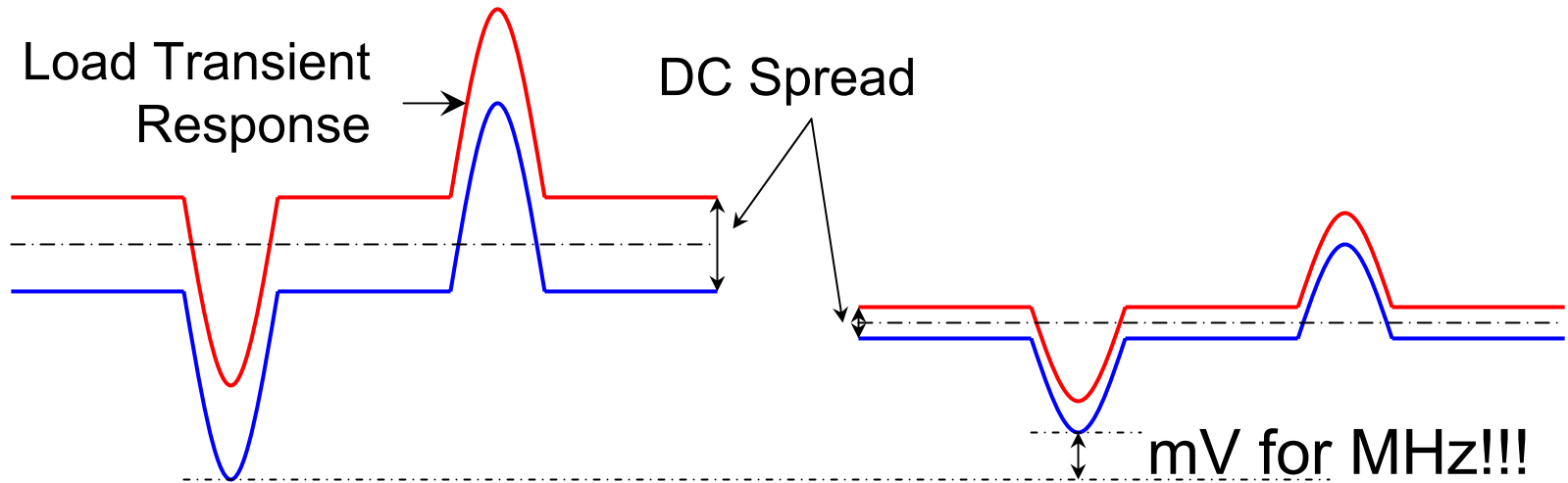



- Better DC & Transient accuracy helps to
 - Reduce static voltage & keep higher min voltage
 - Reduce buffering
 - Reduce silicon area
 - Reduce routing capacitance
 - Achieve more MHz for less mW and less area

I.1: SMPS for DBB Requirements

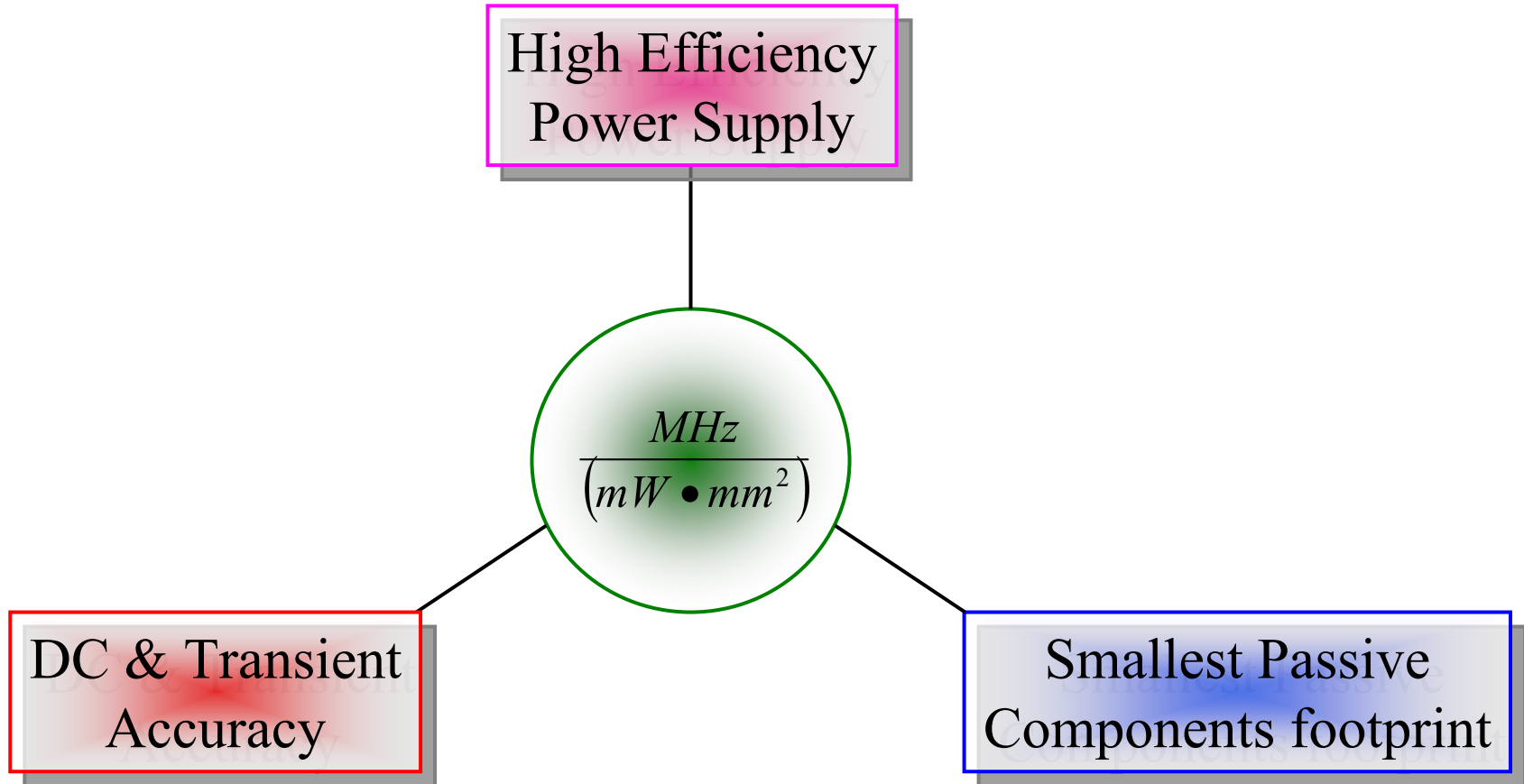


I.1: SMPS for DBB Requirements

Smallest Passive Components Footprint

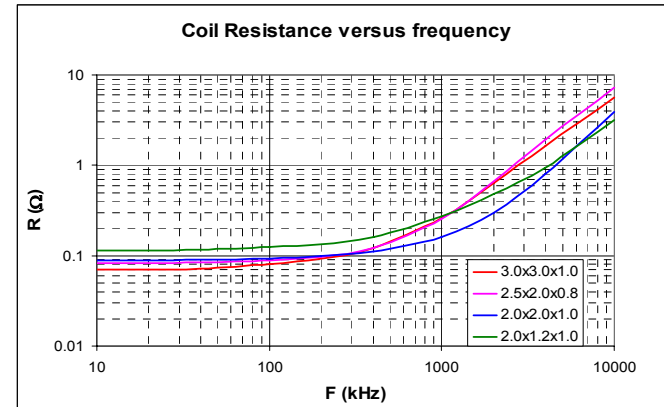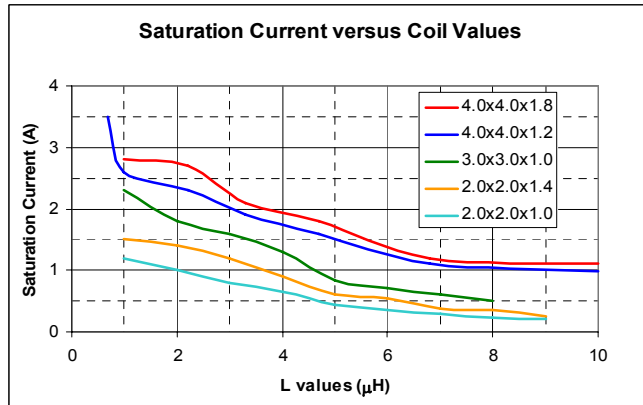

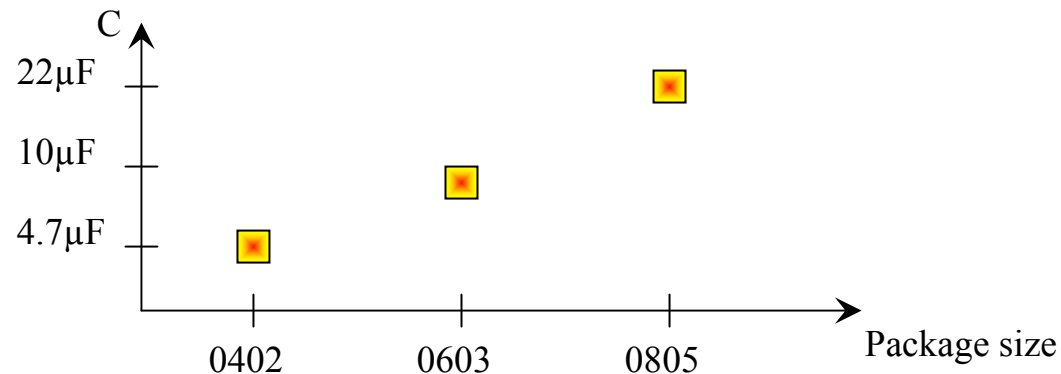
Must reduce L value and increase f ...but not too much!!!




Must reduce C value ...but not too much!!!

I.1: SMPS for DBB Requirements

Compatibility

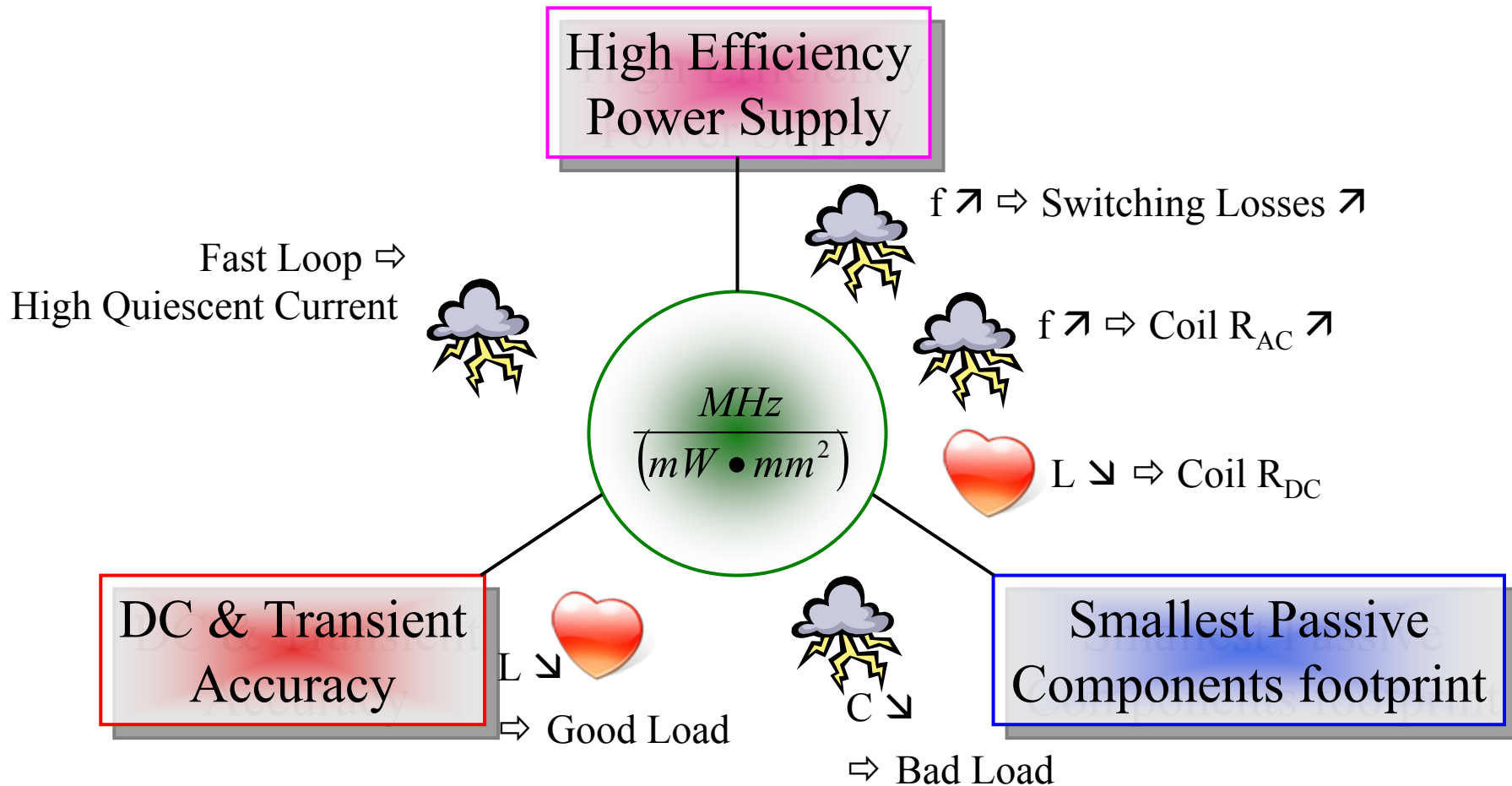

I.2: SMPS for DBB Constraints

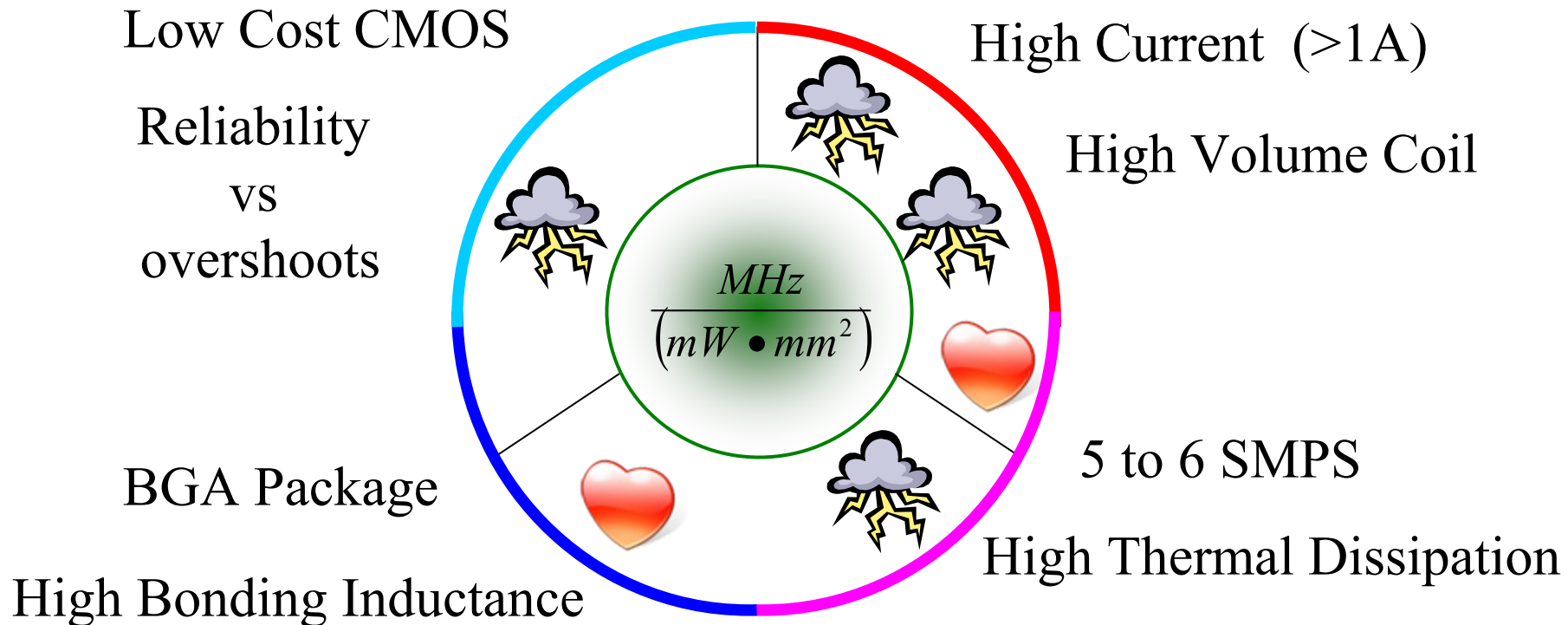

So What?

I.3: Possible integration solutions

- Select a low cost process
 - Select a package with low parasitic inductance
 - Select a mid range frequency and coil value
- And ...

- Keep External components outside...
- Or
- Split Power Management in 2, 3,... power modules
 - 2/3 Coil
 - 4/6 Capacitors

Outline

Introduction

I SMPS for Digital Base Band and Memories

II SMPS for Audio and Low Power RF functions

- Requirements / Compatibility
- Constraints
- Possible Solutions

III SMPS for RF Power Amplifier

Conclusion

II.0: Audio & Low Power RF Context

Audio functions

-  Inside PMUs

or

-  In stand alone ASSP

 -  < 50 IOS BGA or WLCSP

-  Low cost CMOS (0.13 μ m – 5V Compliant)


Low Power RF functions

-  In dedicated RF chips

-  0.65 μ m CMOS process

-  WLCSP

I.1: Audio and Low Power RF Requirements

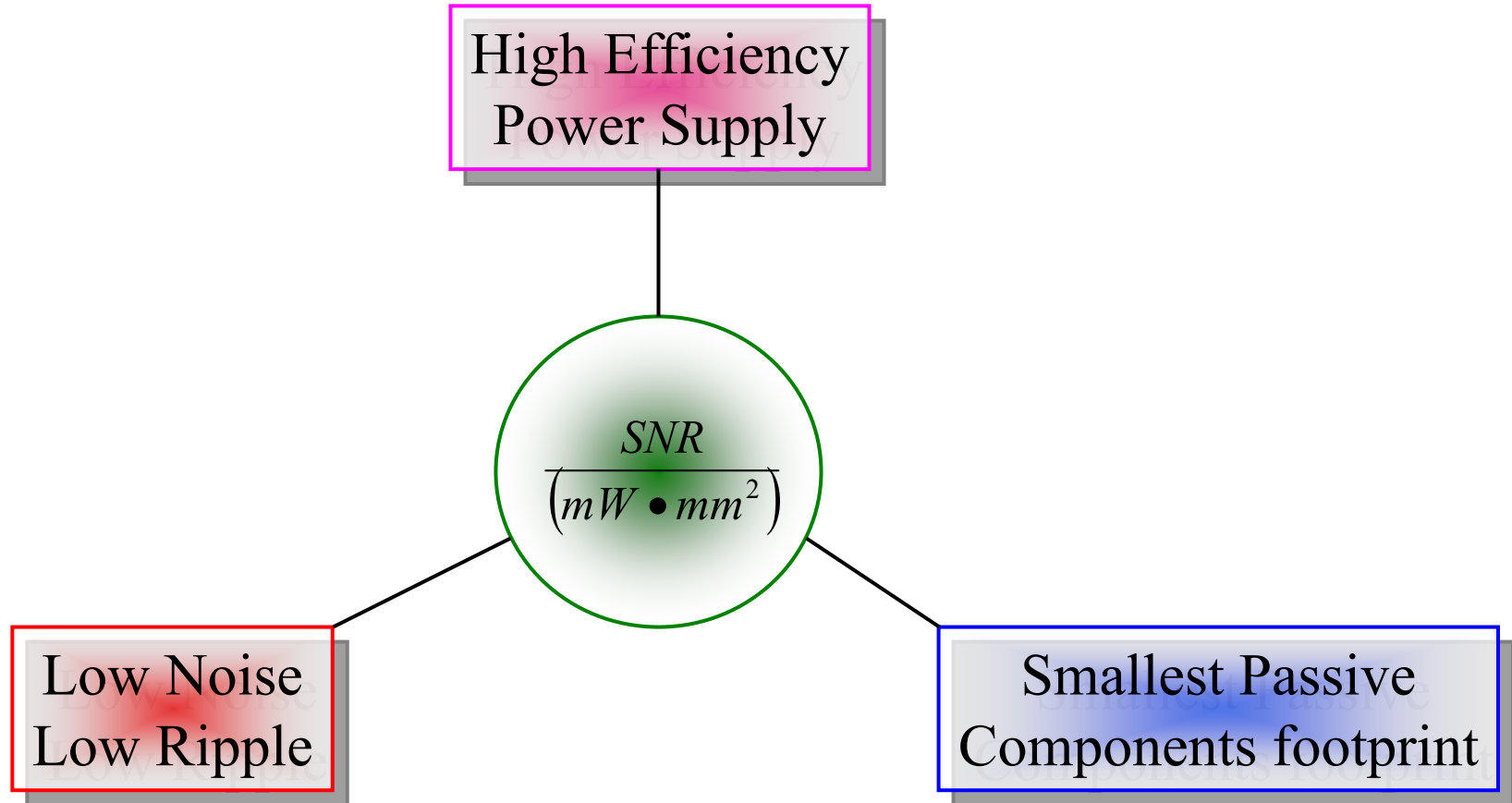

I.1: Audio and Low Power RF Requirements

Low Noise / Low Ripple


Low Noise

-  Fixed frequency
-  Compatible with Audio or RF constraints


Low Ripple

-  Relatively high coil value
-  Relatively high capacitor value
-  Medium Switching frequency

I.1: Audio and Low Power RF Requirements Compatibility

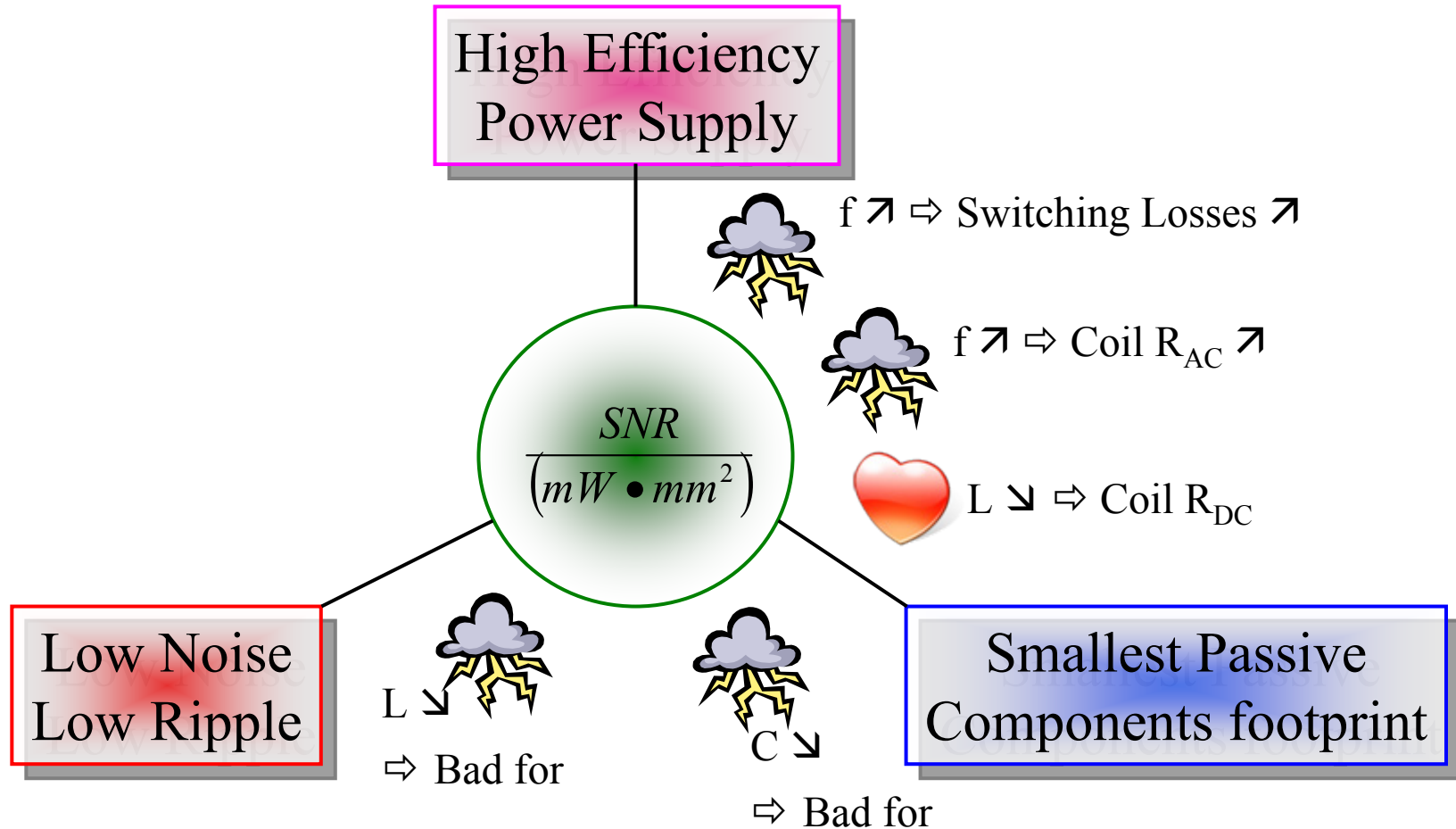

II.2: SMPS for Audio and Low Power Constraints

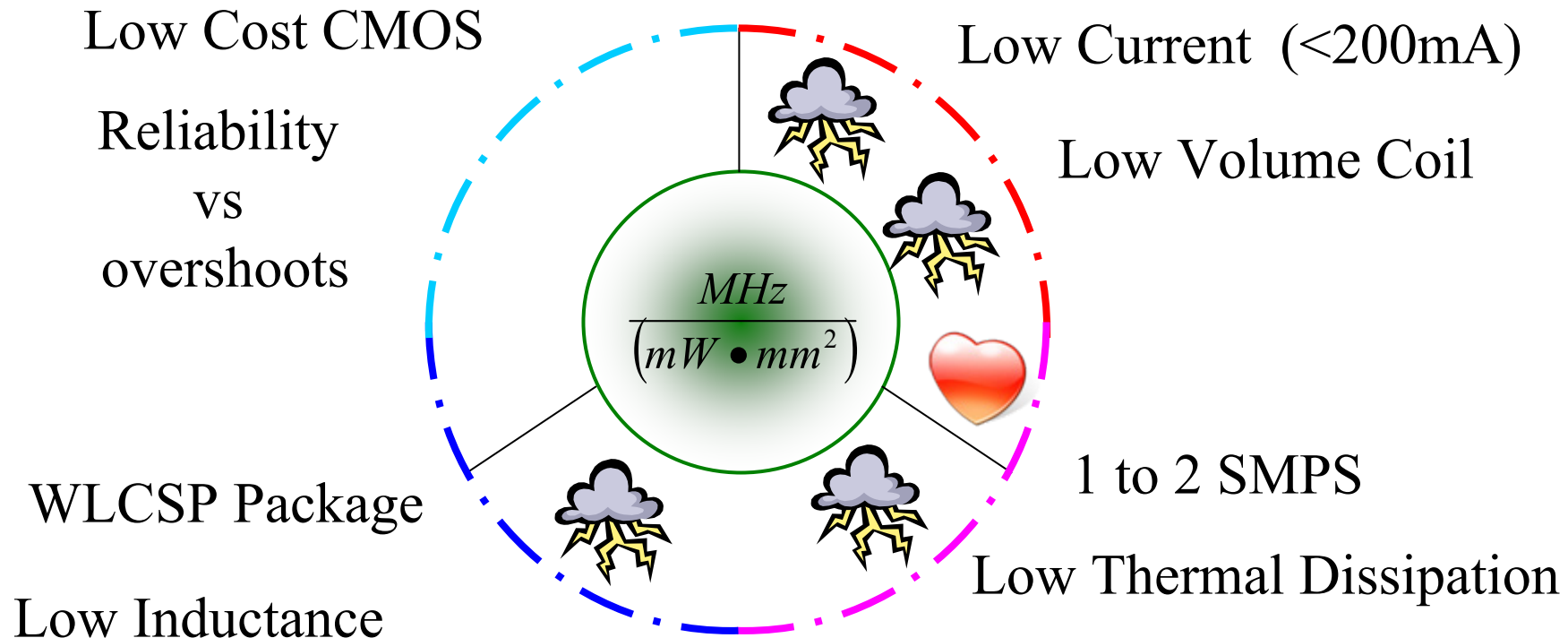

II.3: Possible integration solutions

- Low current requirement
 - OK for coil volume
 - OK for WLCSP
 - OK for medium frequency

- Possibility to build modules with
 - Stand alone ASSP
 - May be also with PMUs (1 coil)

Outline

Introduction

I SMPS for Digital Base Band and Memories



II SMPS for Audio and Low Power RF functions

III SMPS for RF Power Amplifier

- Requirements / Compatibility
- Constraints
- Possible Solutions

Conclusion

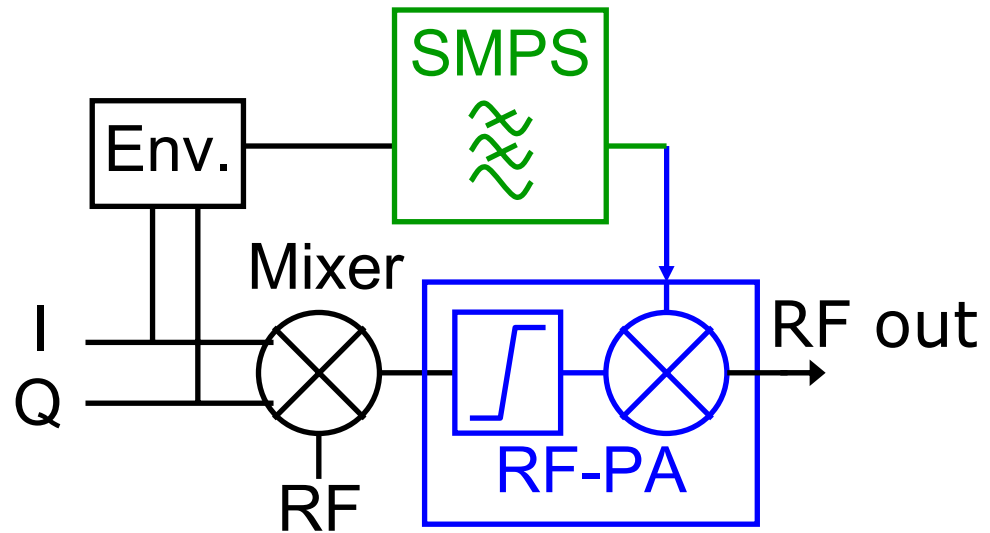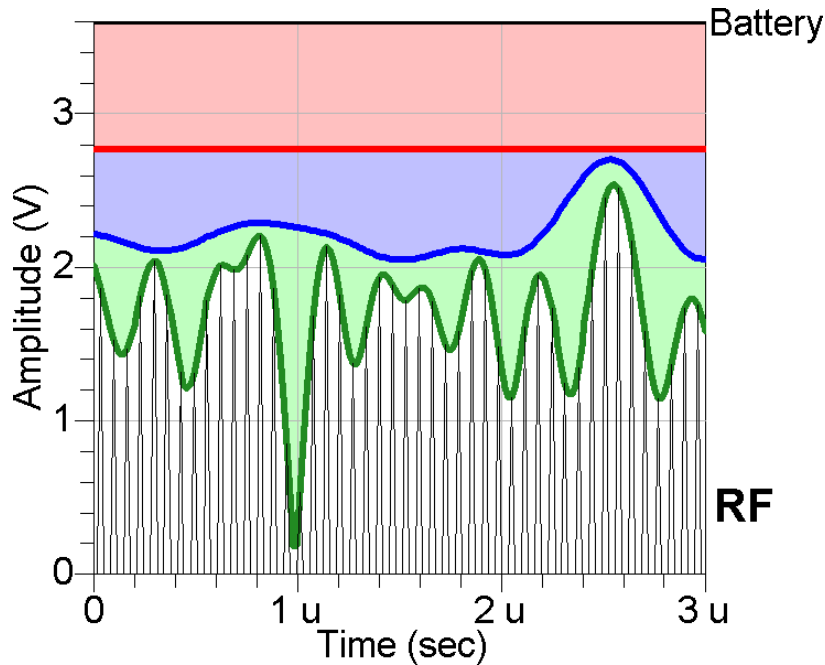Power supply of an Envelope Reconstruction RF PA




EER

- The PA operates in saturation
- The SMPS provides the envelope signal
- The full RF signal reconstructs at the output

SMPS in the signal path


From Analog ...	... to SMPS specification
Signal AC BW	Switching frequency
Large signal rate	Output filter cutoff freq.
Linearity	large BW close loop control
Spurious & Noise	Fixed freq, output filter mask
Stability	Load modeling
Low Z_{out} over full BW	Low Z_{in} over full BW

SMPS accuracy : WCDMA envelope tracking

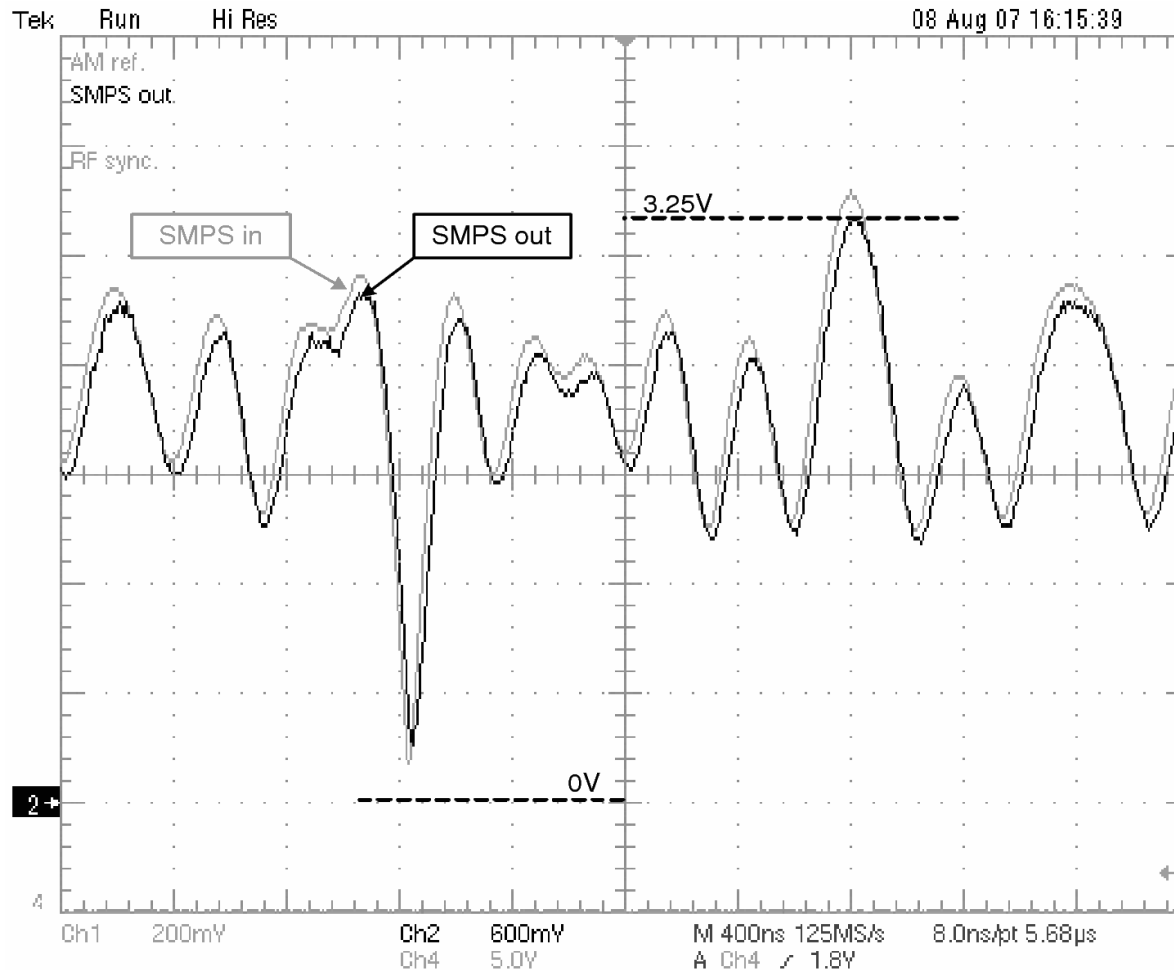

Symbol rate : 3.84MHz
Peak output power : 2.2W
V battery : 3.6V
PAPR : 3.5dB

Spurs filtering

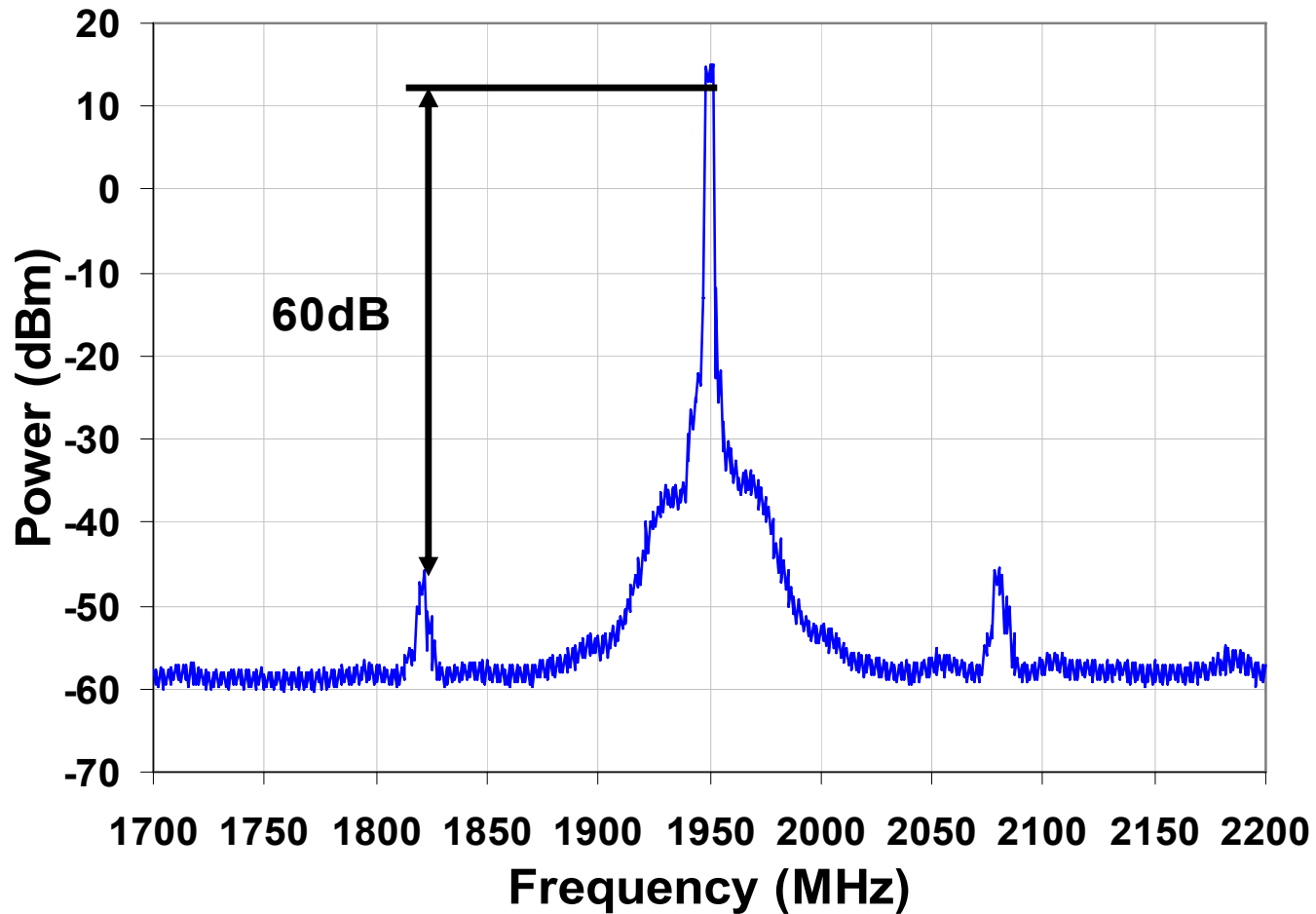

Convergent technology requirements

RF PA


-  driver stage : high-voltage bipolar (high Gm)
-  output stage : NLDEMOS (gain @ large I, high voltage tolerance, no thermal runaway, efficiency)

SMPS

-  Power switches : NLDEMOS (low R_{on} , low C_{gate})
-  Controller : bipolar (high Gm)

 Integration on a single chip!

Implementation example in ST BiCMOS 0.25

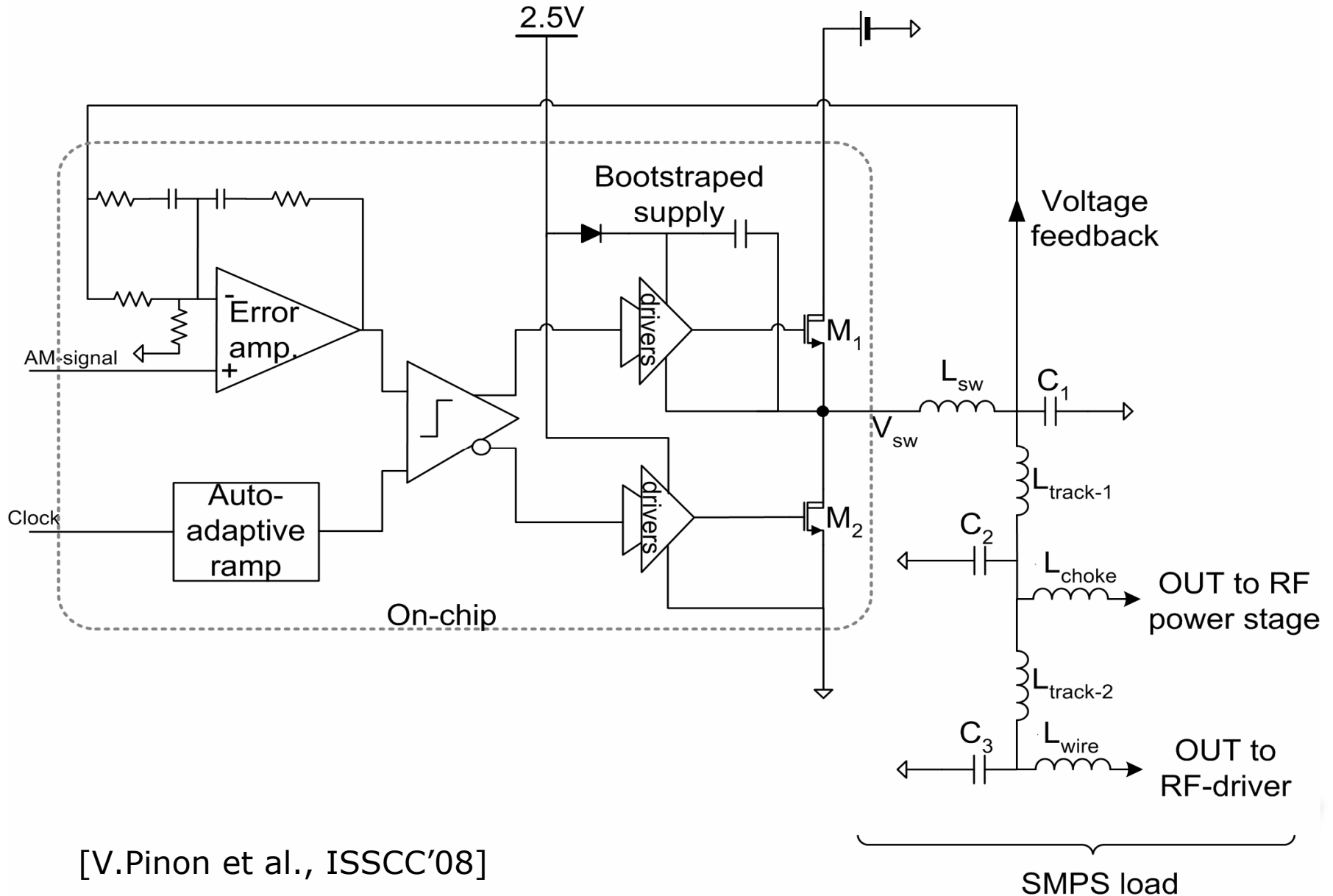


SMPS test results

Max Out power @ 3.6V battery	2W
Peak efficiency @ 3.6V battery	83% @2W
AC BW	15MHz
Fs	130MHz
Area (with pads)	0.5 mm ²


1.95GHz WCDMA EER chip test results

Chip efficiency	46% @ 27dBm RF out power
ACLR 1/2	-39/-47dBc
Peak switching noise	-60dBc
Battery range	2.9V – 4.3V
Chip area	1.1mm ²

Measured efficiencies vs. output power

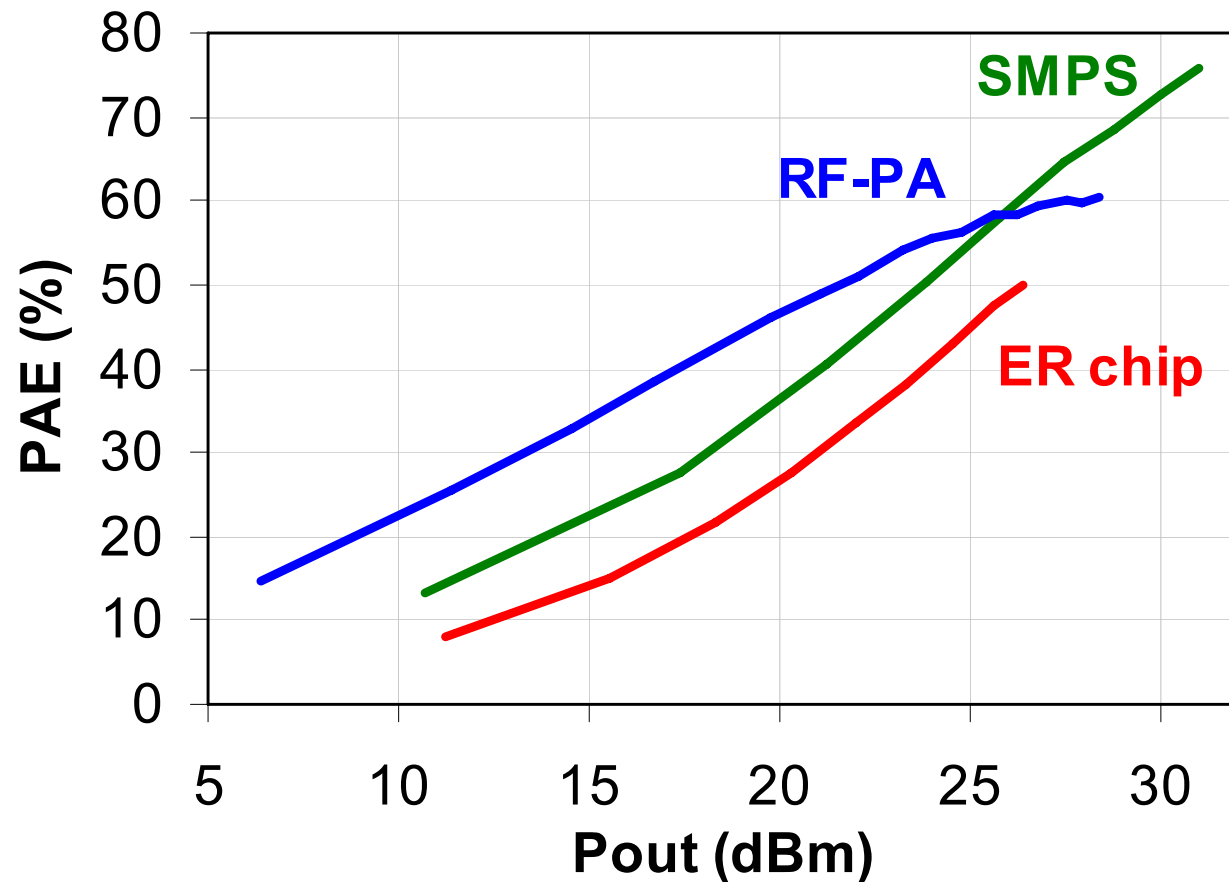

ST BiCMOS 0.25 die

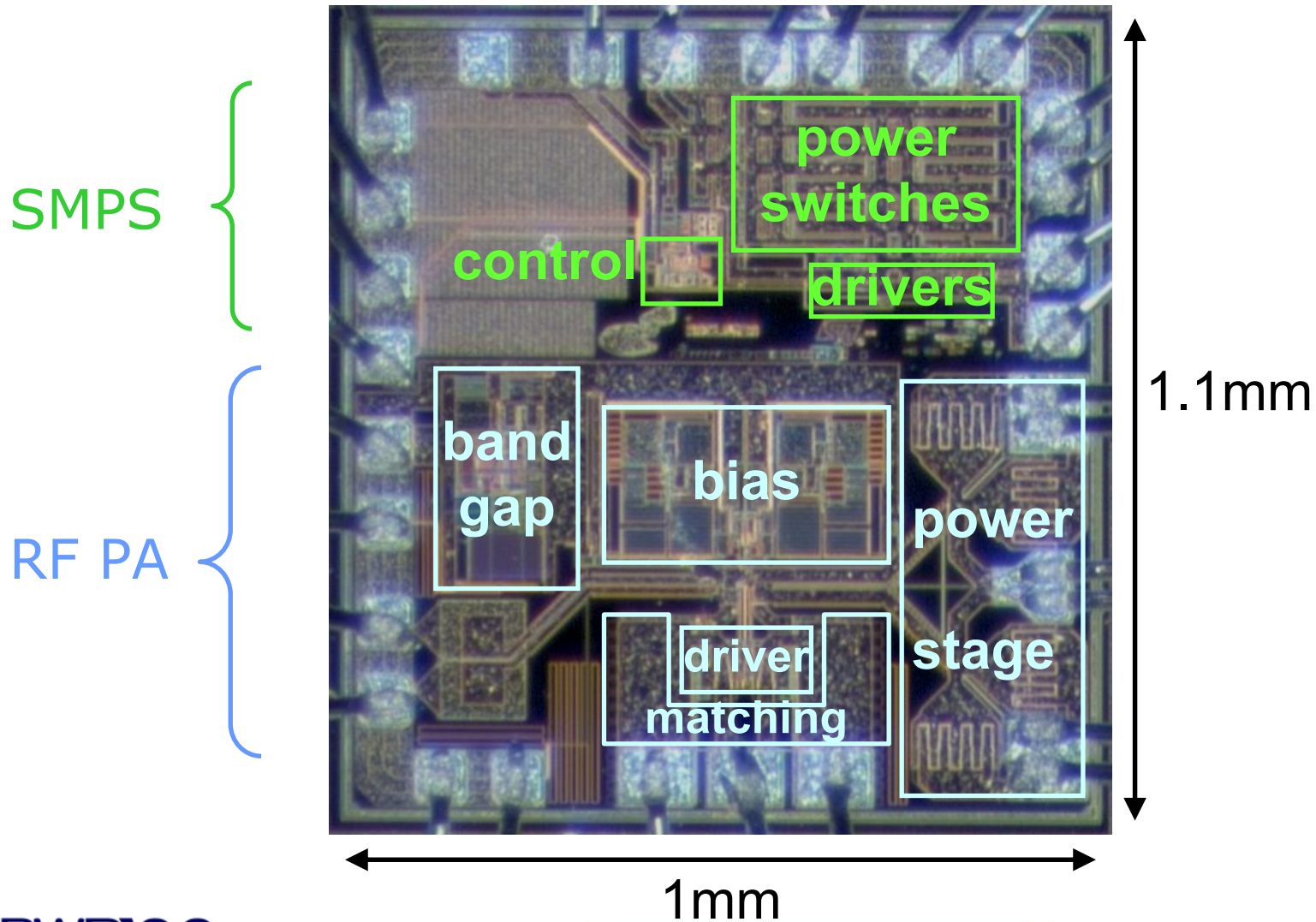

Outline

Introduction

I SMPS for Digital Base Band and Memories

II SMPS for Audio and Low Power RF functions

III SMPS for RF Power Amplifier

Conclusion

Conclusion

■ For DBB:

■ Integration in PMUs is difficult

■ High number of coils (5 to 6)

■ High current / High Power dissipation

■ Process and Package versus high frequency

■ Possible solution with new partitioning

■ Solve passive components congestion

■ Solve power dissipation issue

■ Is it cost competitive ? (multiple packages)

■ Analog solution still the most cost effective?

Conclusion

■ For Audio and Low Power RF:

■ Good Candidates for integration

■ Can be outside of PMUs

■ Less Ios than PMUs = WLCSP

■ 1 to 2 coils required

■ Medium current (200mA)

■ Do not require very high frequency

■ Mixed mode architecture for time to market

Conclusion

For RF PA

A real need for high frequency SMPS

-  Saves a lot of power in a EER system

-  Saves coil area on PCB...


-  ... and goes towards full integration

SMPS + PA common integration

-  SMPS and RF PA technology requirements are totally compatible

-  Gives a new degree of freedom for platform partitioning

Saturation Current versus Coil Values

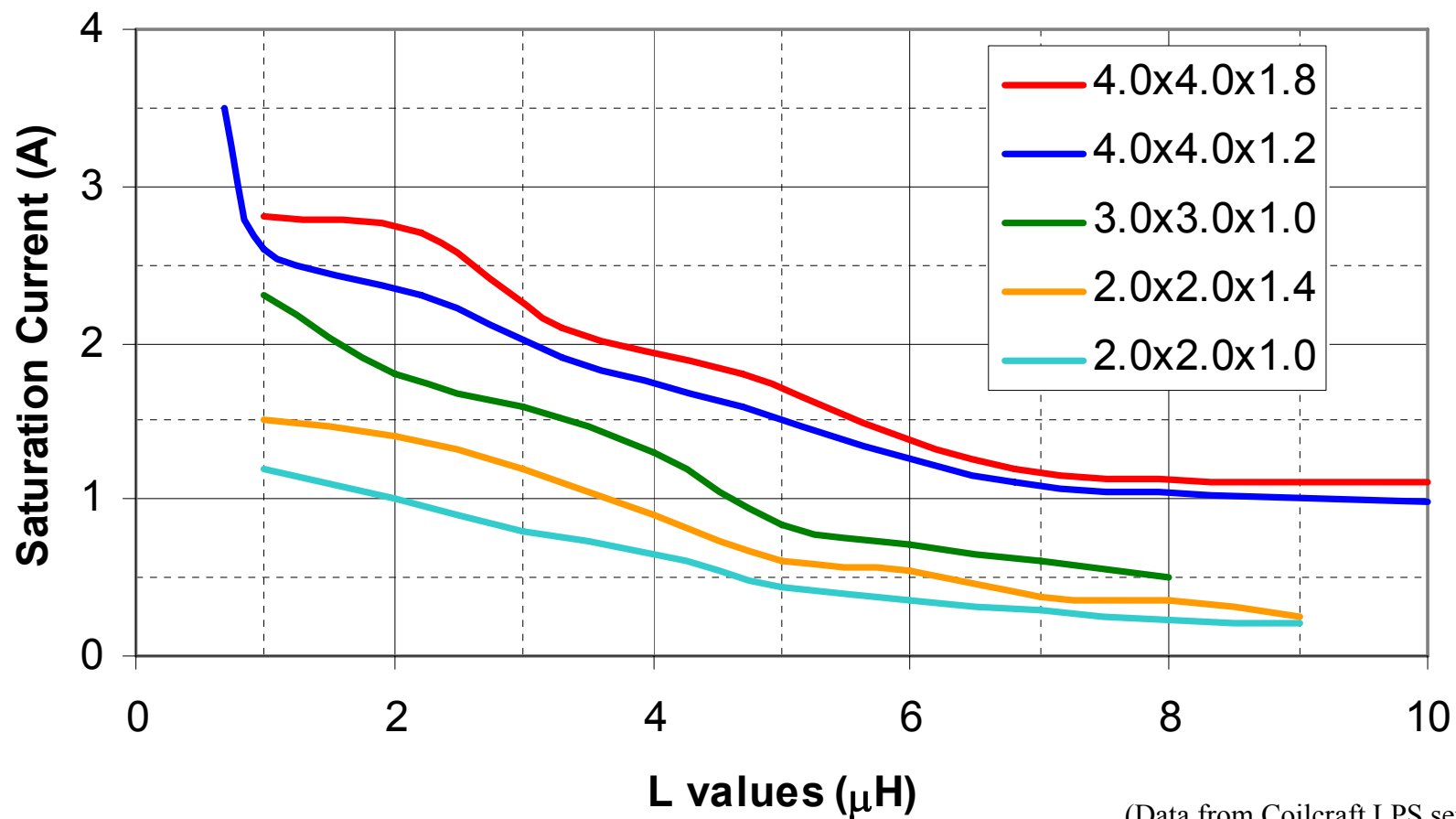

Coil Resistance versus frequency

