

# Efficient on-chip power conversion for energy harvesting and low-power mobile applications


*October 6, 2014*

Patrick Mercier

**Energy-Efficient Microsystems Group**


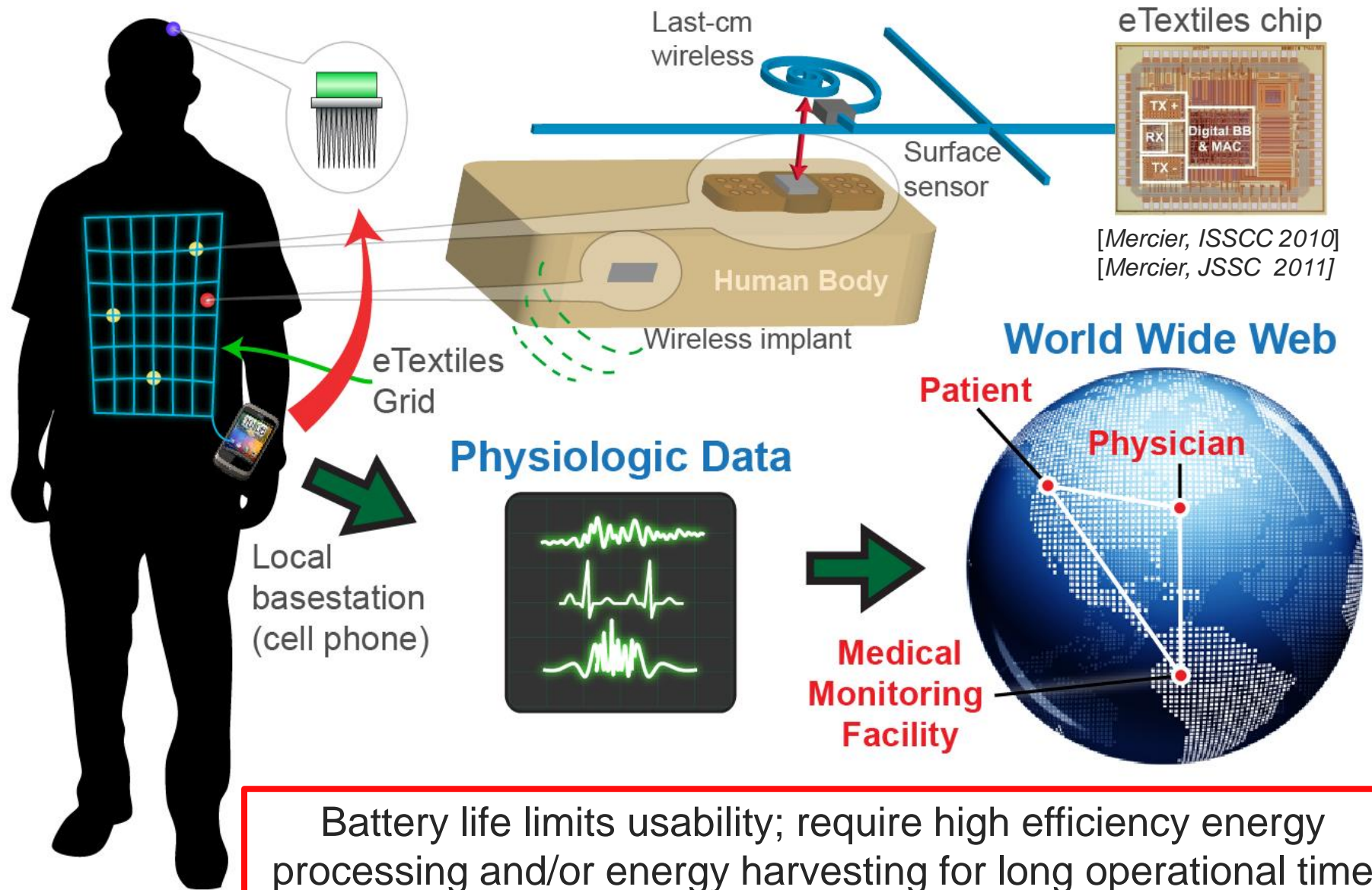
# Application example 1: wearable devices





# Application example 2: fine-grain power management

- POWER8, IBM

*A fully-integrated distributed and high  $\eta$  regulator enables larger savings*

ISSCC'14

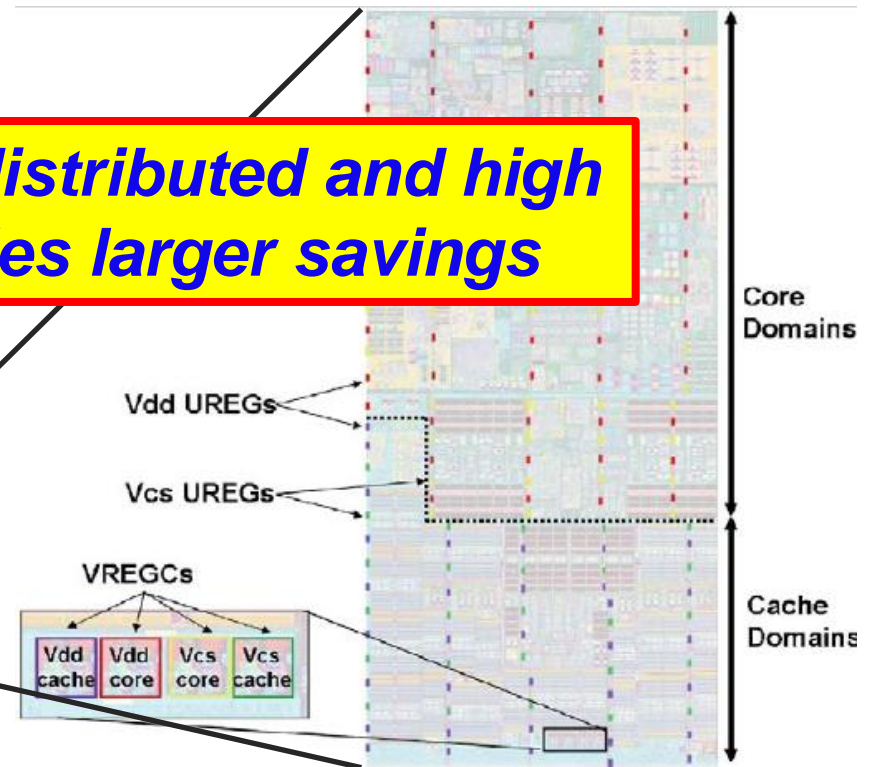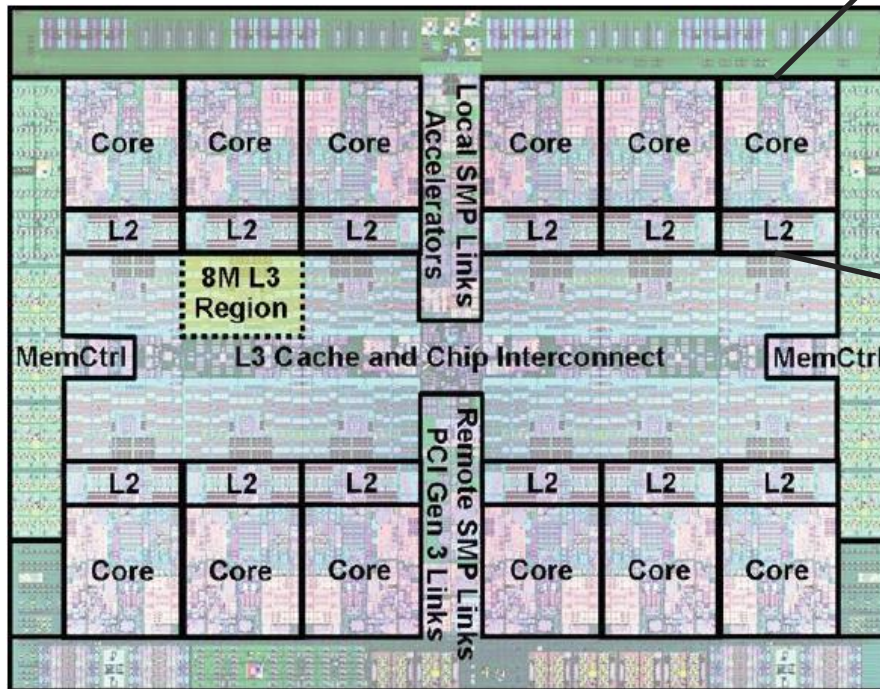

- 48 DVFS domains, each with ~64  $\mu$ Regulators
- ~1.5x power savings even with LDOs ( $\eta > 61\%$ )

# The key challenge...

...in both applications is achieving  
**high power conversion efficiency**  
in **very small sizes**

# Talk outline

---

- Energy harvesting from the human body
- Switched-capacitor converters: principal challenges
- New switched capacitor topologies that achieve high efficiency over large voltage ranges:
  - Recursive binary
  - Recursive ternary
- Conclusions

# Harvesting energy from the human body



Leg motion ( $\sim 10\text{W}$ )  
(Bionic Power)



Heel strike ( $\sim 1\text{W}$ )  
(MIT)




Thermoelectric ( $\sim 100\mu\text{W}$ )  
(MIT)




**External**


**Implantable**

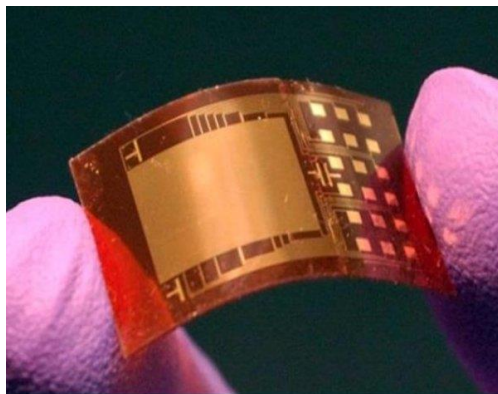

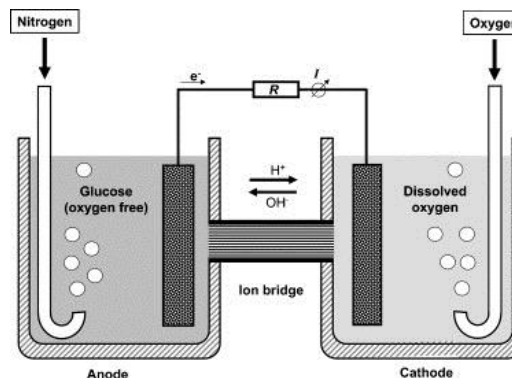Nanogenerator ( $\sim 1\text{mW}$ )  
(Georgia Tech)




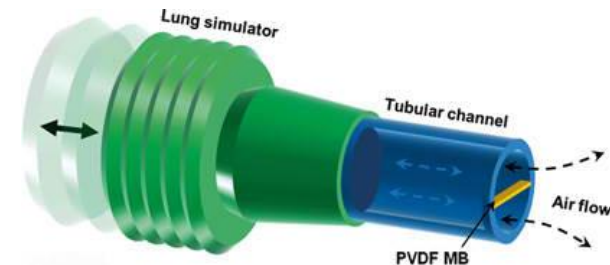Glucose fuel cell ( $\sim 10\mu\text{W}$ )  
(U. Freiburg)



Respiration ( $\sim 100\text{nW}$ )  
(U. Wisconsin-Madison)

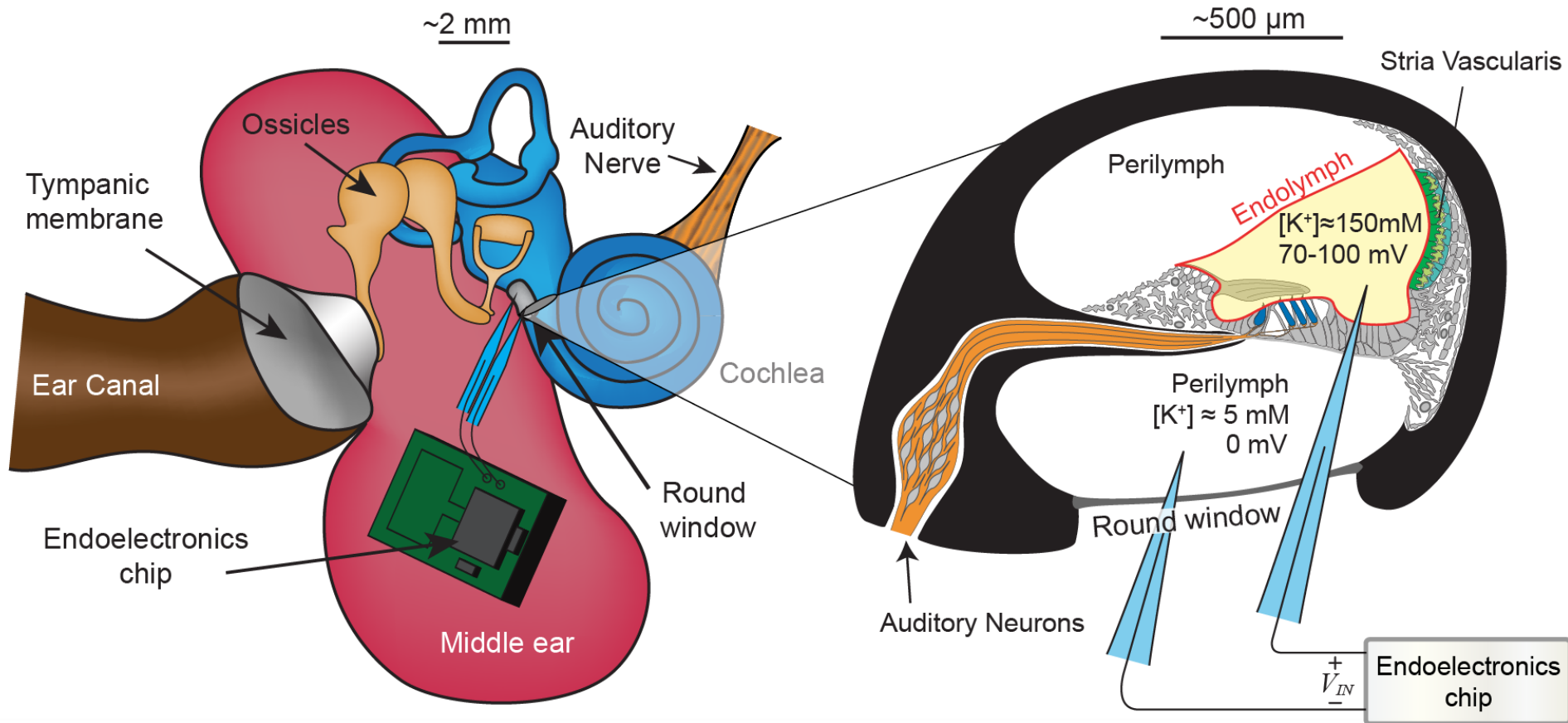
# A (new) energy harvesting source: the endocochlear potential




**Challenge:** anatomically-miniaturized electrodes limit extractable power to  $\sim 2\text{ nW}$

# Yes we can!

## Chip implementation details:

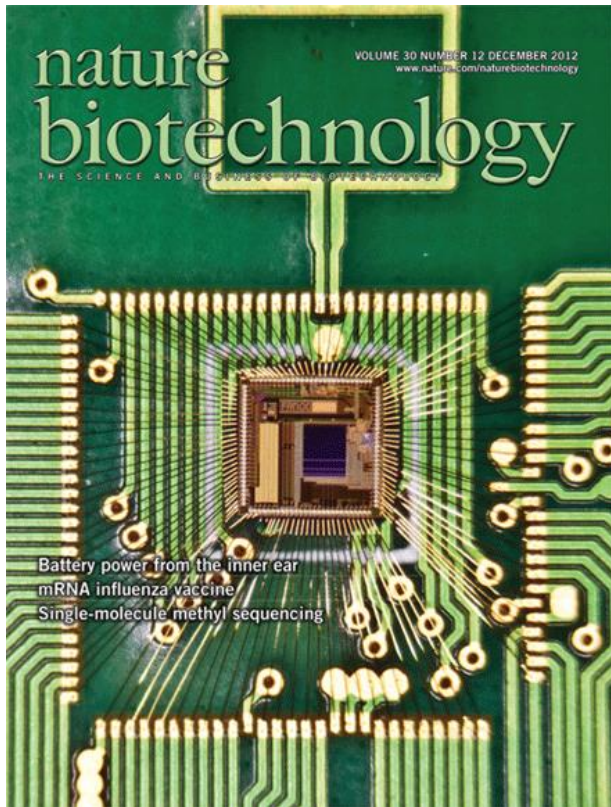


Technology	0.18 $\mu\text{m}$ CMOS
Supply	0.8 - 1.1 V
Charge-pump	1.4 - 2.2 V
Radio data rate	0.1 - 10 Mbps

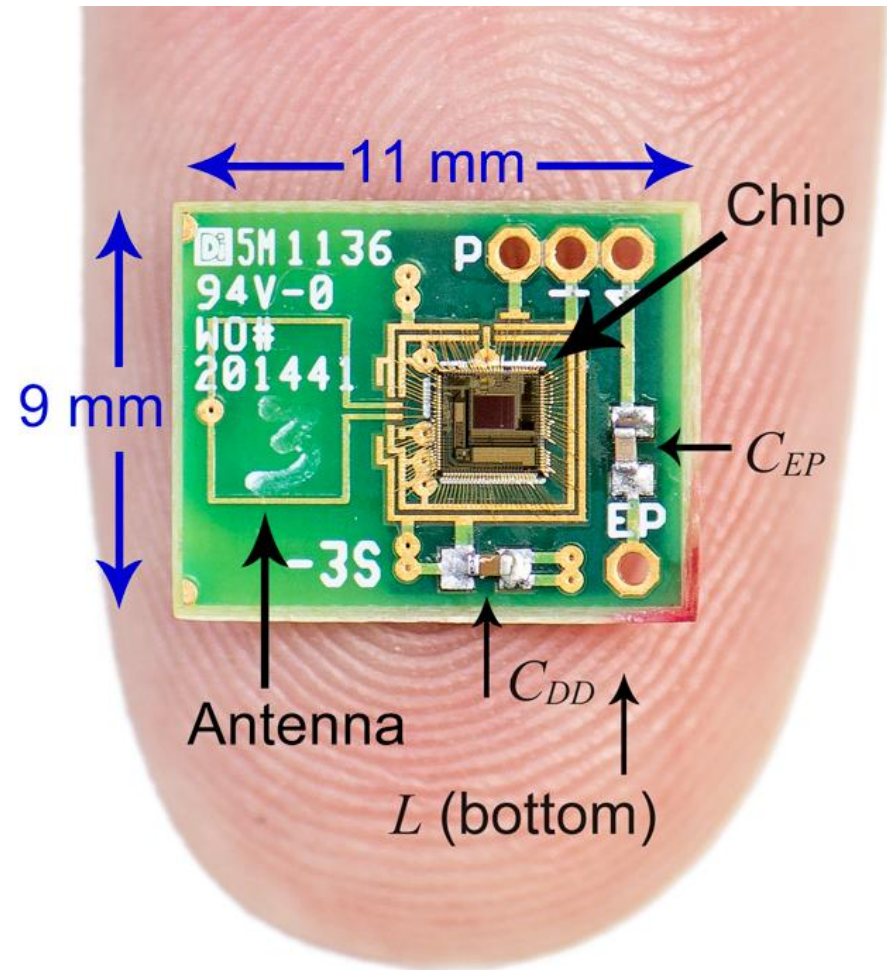

Chip-on board small enough to fit in the human mastoid cavity


[Mercier et al., *Nature Biotechnology*, Dec. 2012]
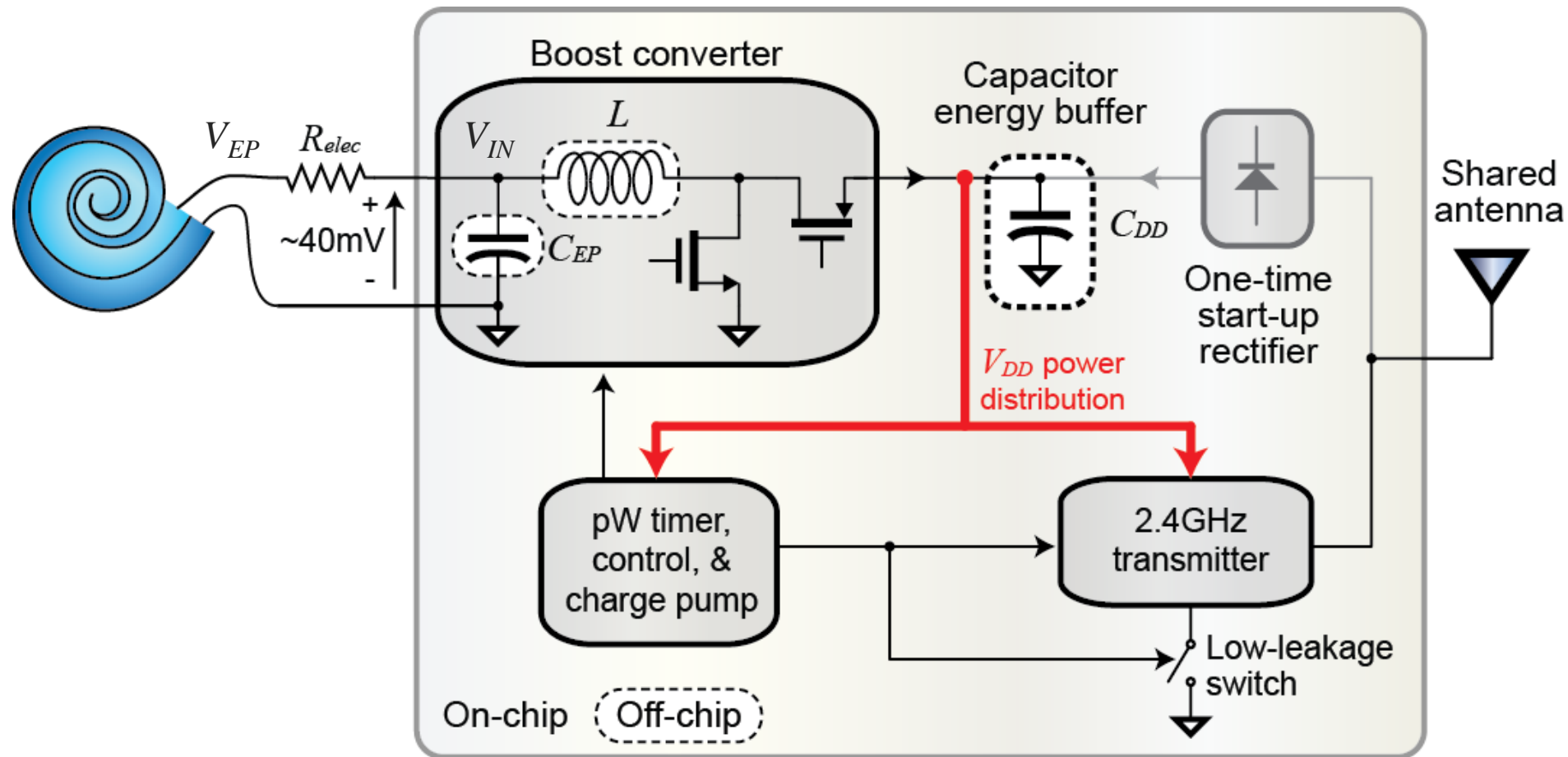
# Endoelectronics chip: EP harvester architecture



Acknowledgements: Saurav Bandyopadhyay, Anantha Chandrakasan, Konstantina Stankovic, Andrew Lysaght

# We can extract net positive power!

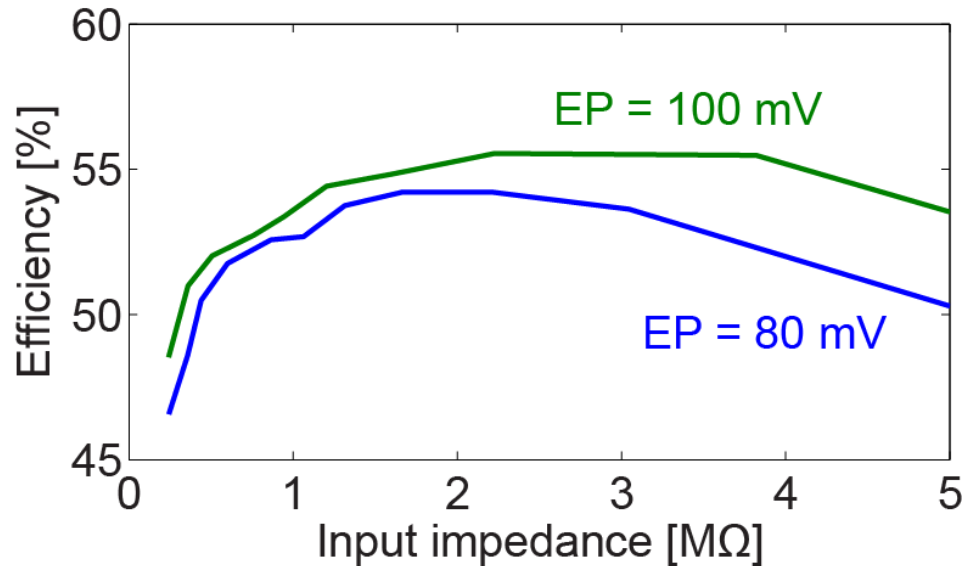

Efficiency of power train  
(@  $R_{elec} = 1 \text{ M}\Omega$ )



Available input power  
(1.6 – 2.5 nW)




## Block power consumption

12.5 Hz timer	350 pW
Control + drivers	100 pW
Charge-pump	70 pW
<b>Total:</b>	<b>520 pW</b>


**First boost converter  
at this power level**
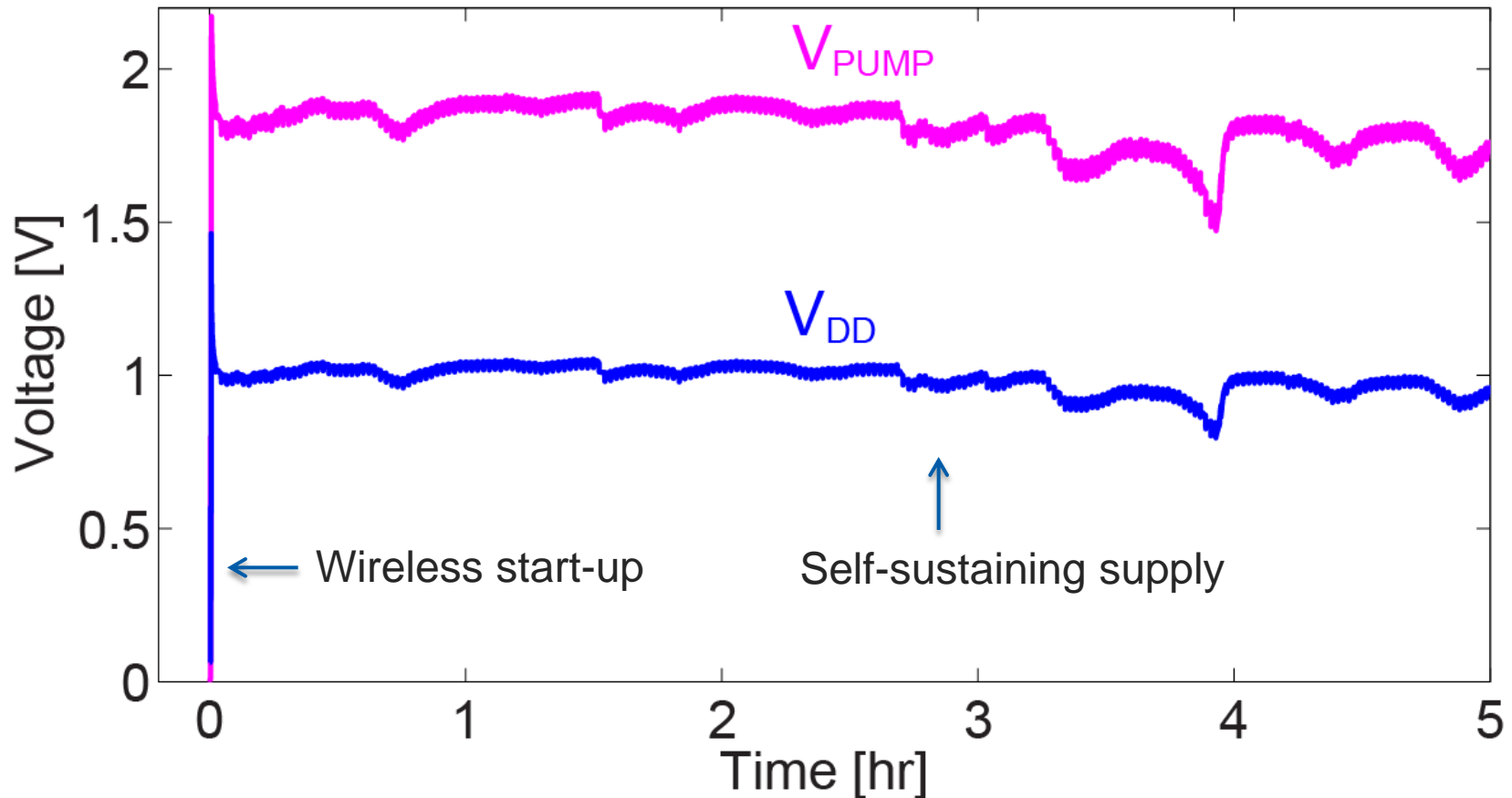
# Clinical guinea pig experiments - results



**First demonstration of an electronic system sustaining itself from a mammalian electrochemical potential!**

# Size constraints

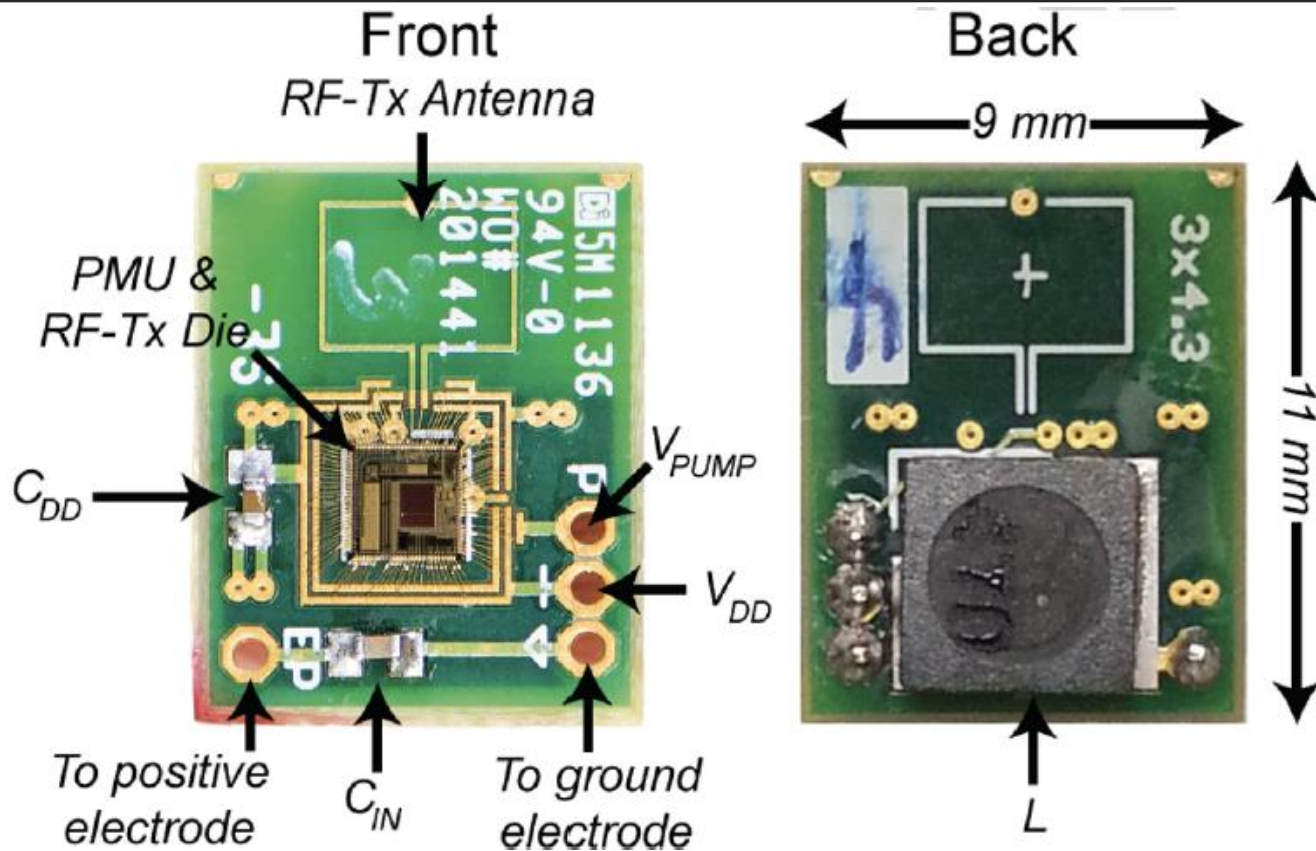

- The inductor is larger than the chip, and we are dealing with nanowatts!
  - Ultimately limits implant size
- Difficult to integrate in multi-output applications

# Talk outline

---

- Energy harvesting from the human body
- Switched-capacitor converters: principal challenges
- New switched capacitor topologies that achieve high efficiency over large voltage ranges:
  - Recursive binary
  - Recursive ternary
- Conclusions

# Switched-capacitor DC-DC converter: inherent size advantage



## Power inductor:

- 7x higher BOM cost
- 8x larger footprint
- Difficult to integrate on-chip




## Capacitor:

- Higher inherent power and energy density
- Easily integrated on-chip (e.g., MIM, MOSCAP, deep-trench)


# SC problem in DC-DC conversion

**Continuous DC  
conversion  
ratio**

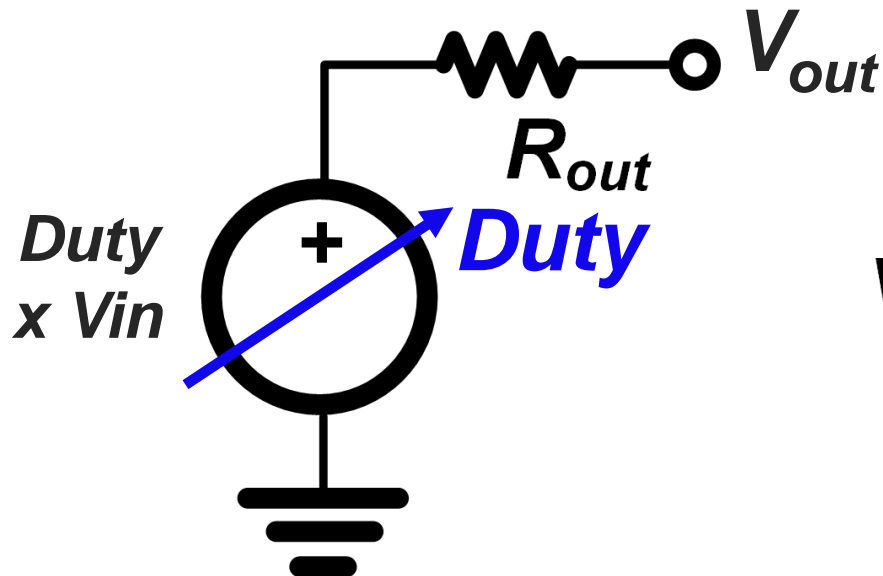

**Switched Inductor**


**Fixed DC  
conversion  
ratio**

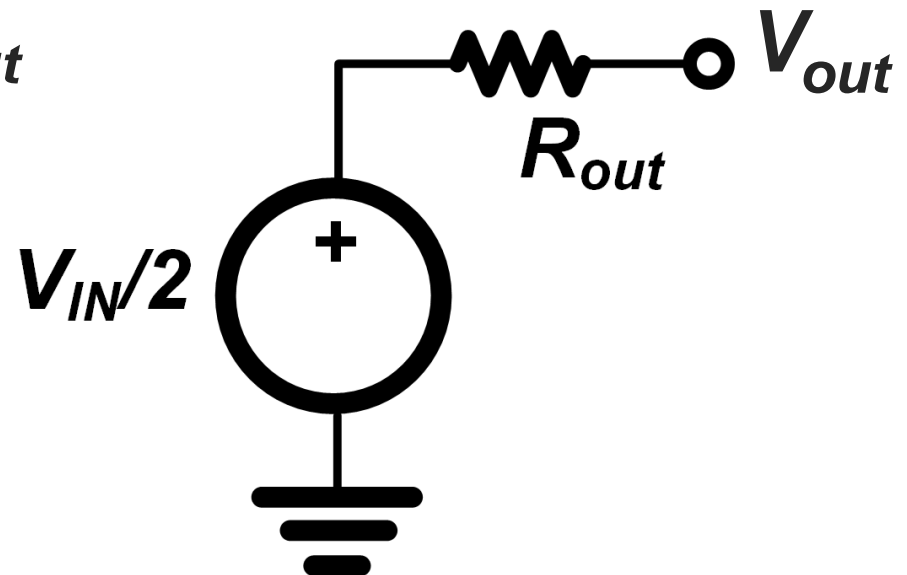

**Switched Capacitor**

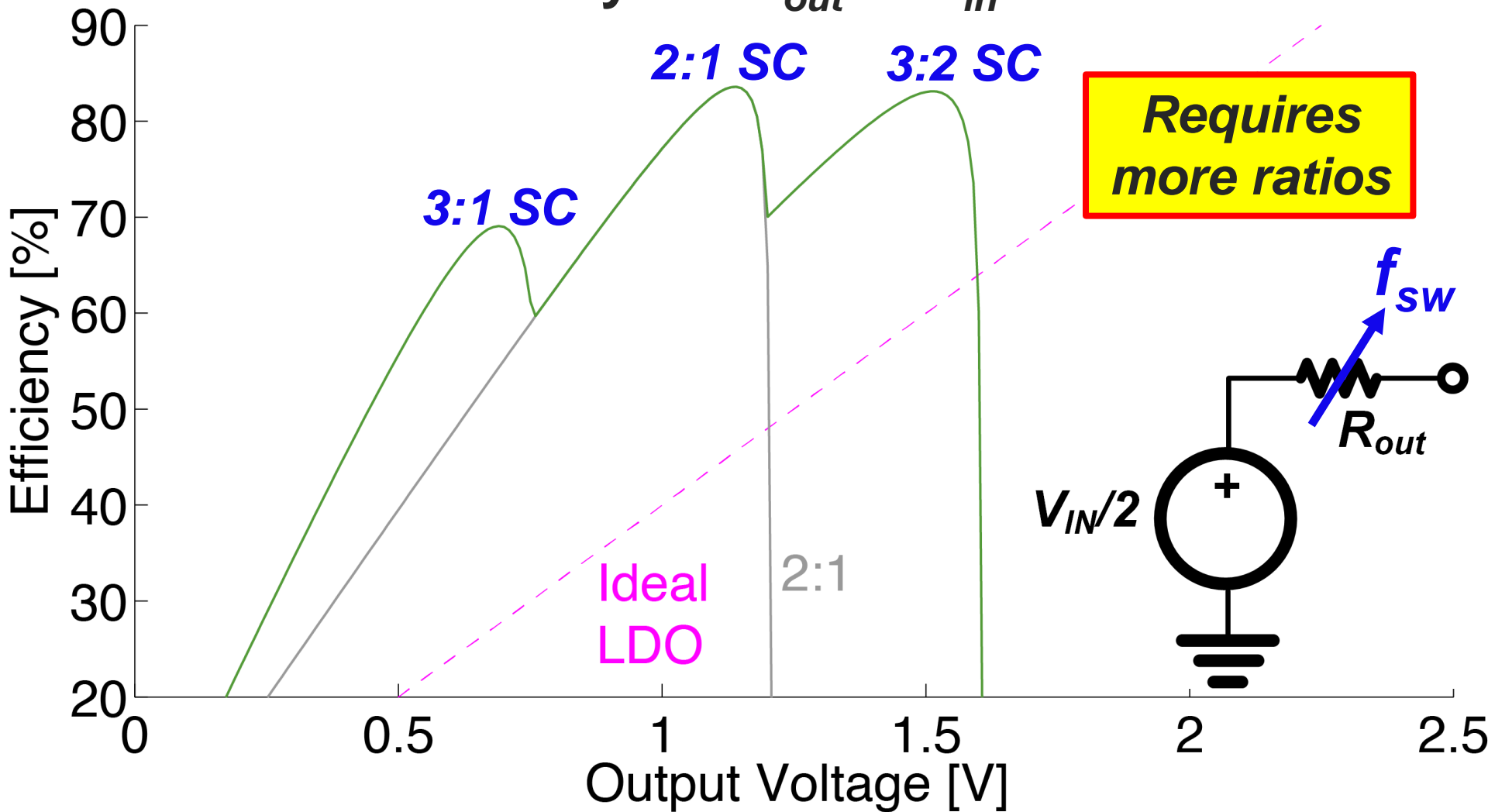
# SC Efficiency

Efficiency vs.  $V_{out}$  at  $V_{in} = 2.5V$


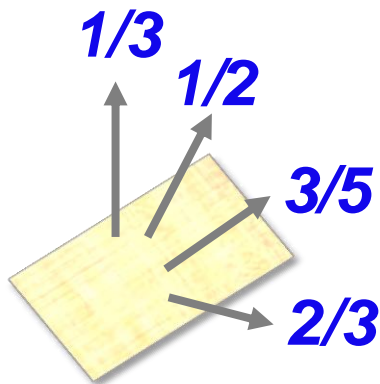
# Higher Number of Ratios Challenge with Conventional SC Topologies

**GOAL:** would like to re-use available capacitance for all ratios *to limit size*



## **PROBLEM:**

- No. Of caps and switches increases exponentially
- Each ratio requires a unique **arrangement**, which is difficult to re-use among other ratios

**More ratios requires  
a *Modular topology***


# Talk outline

---


- Energy harvesting from the human body
- Switched-capacitor converters: principal challenges
- New switched capacitor topologies that achieve high efficiency over large voltage ranges:
  - Recursive binary
  - Recursive ternary
- Conclusions

# Solution part 1: modular reconfiguration


## Cells Stacked

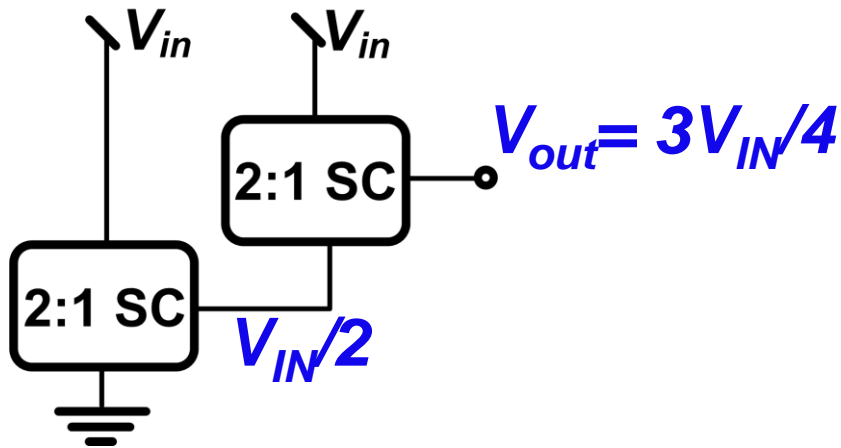

## Cells cascaded

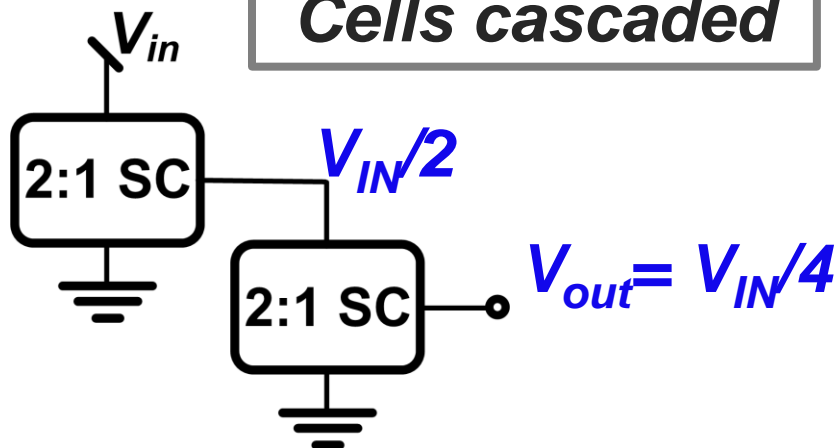
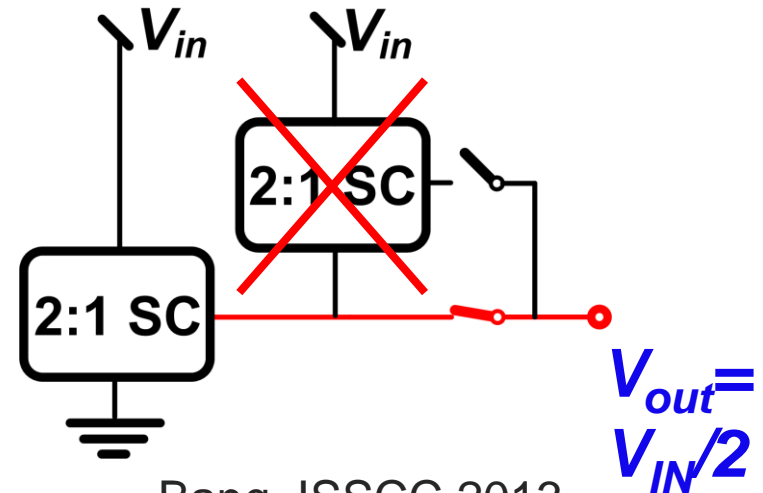
## Route $V_{out}$ from 1<sup>st</sup> cell for 1/2




Bang, ISSCC 2013


**PROBLEM:** Wastes the capacitance of the 2<sup>nd</sup> cell  $\rightarrow$  lower  $\eta$

# Solution part 2: recursive reconfiguration


## Cells Stacked

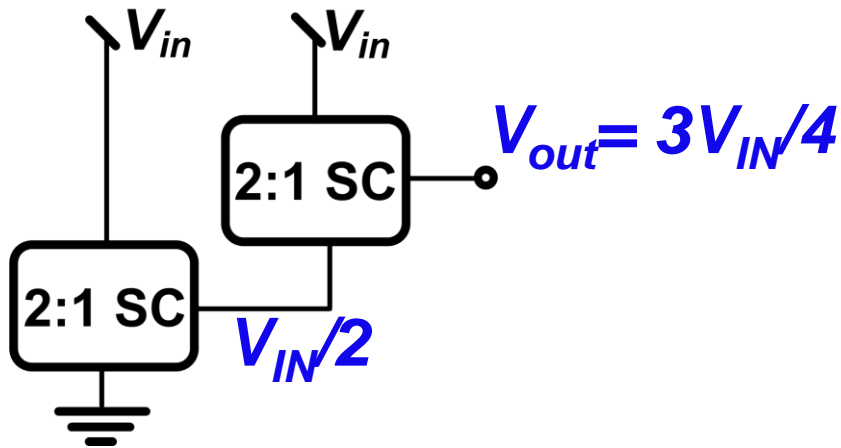

## Cells cascaded

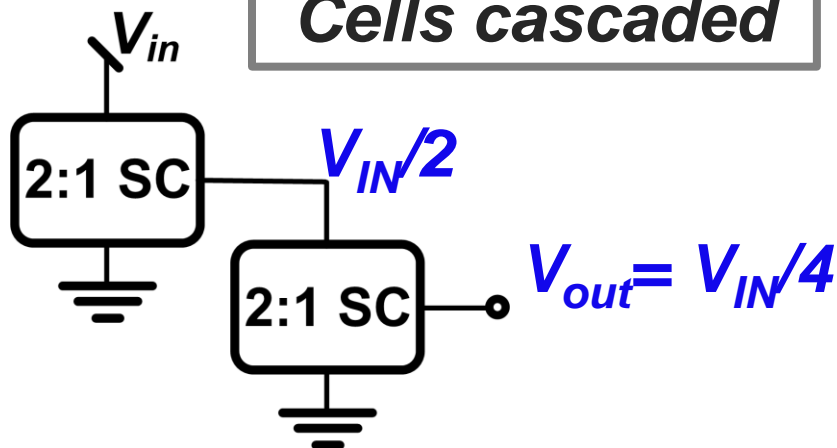


## Cells in parallel for 1/2

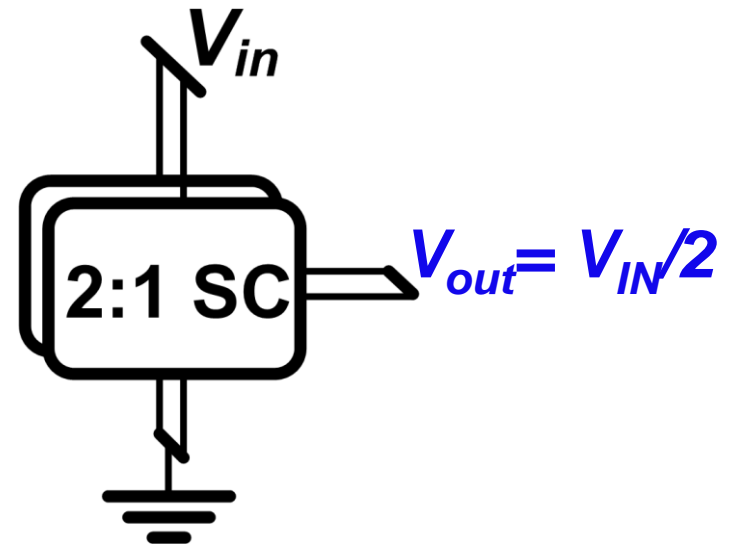

**Recursive Inter-cell  
Connection:** 100% of caps  
used amongst all ratios

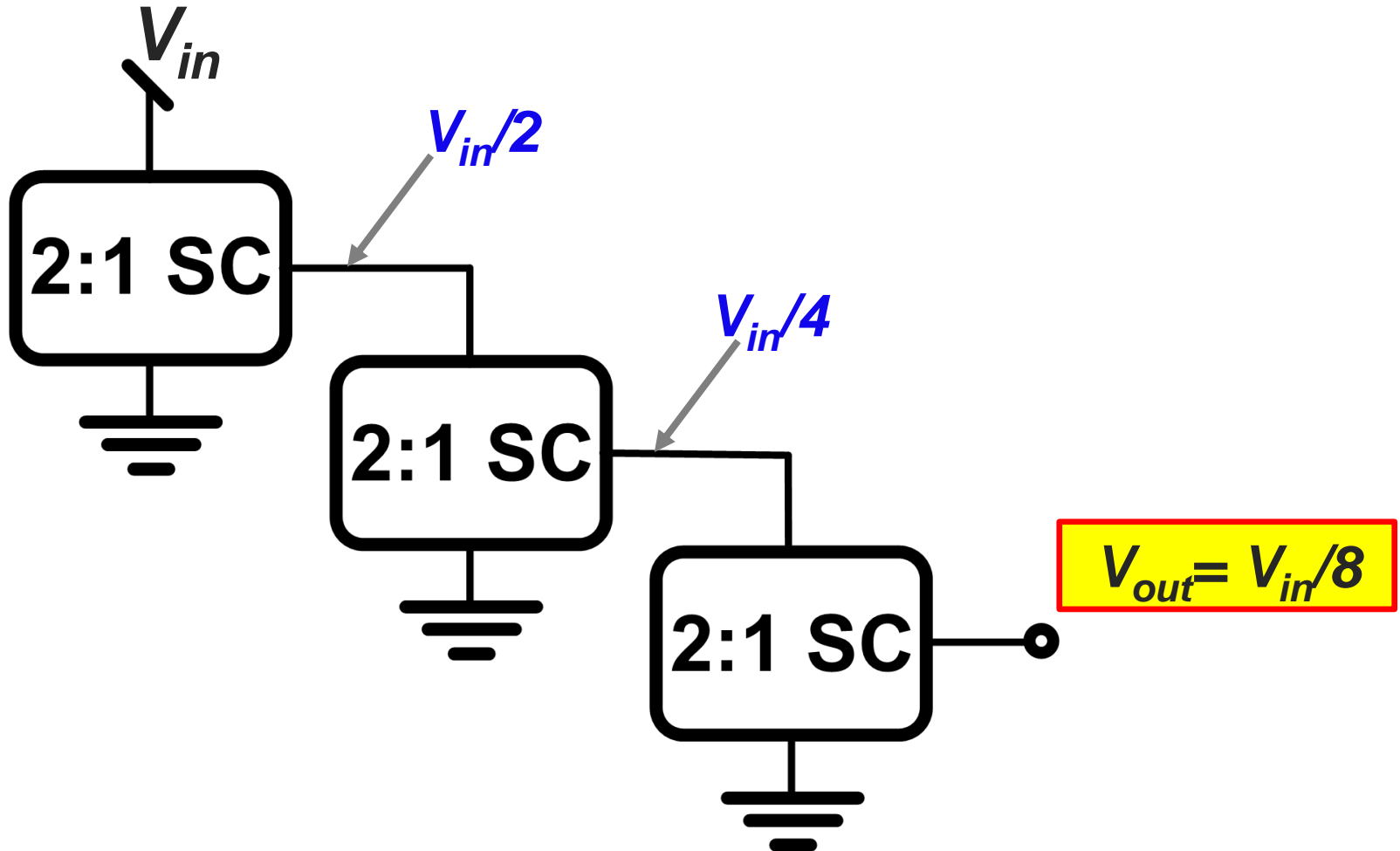
# Recursive 3-bit SC

- Adding a third 2:1 SC cell: resolution =  $V_{in}/2^3$




# Recursive 3-bit SC

- Realizing 3/8 ratio

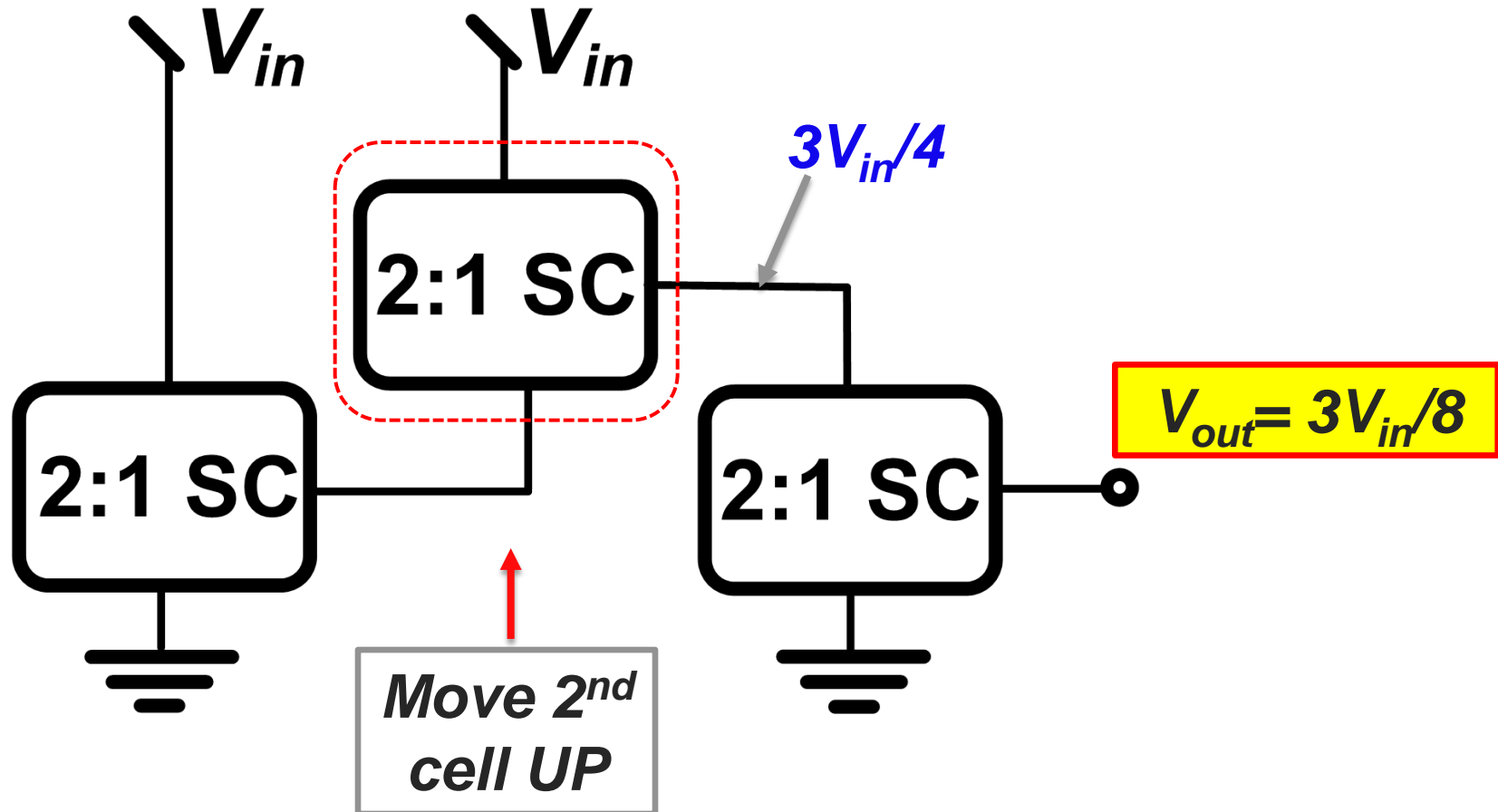

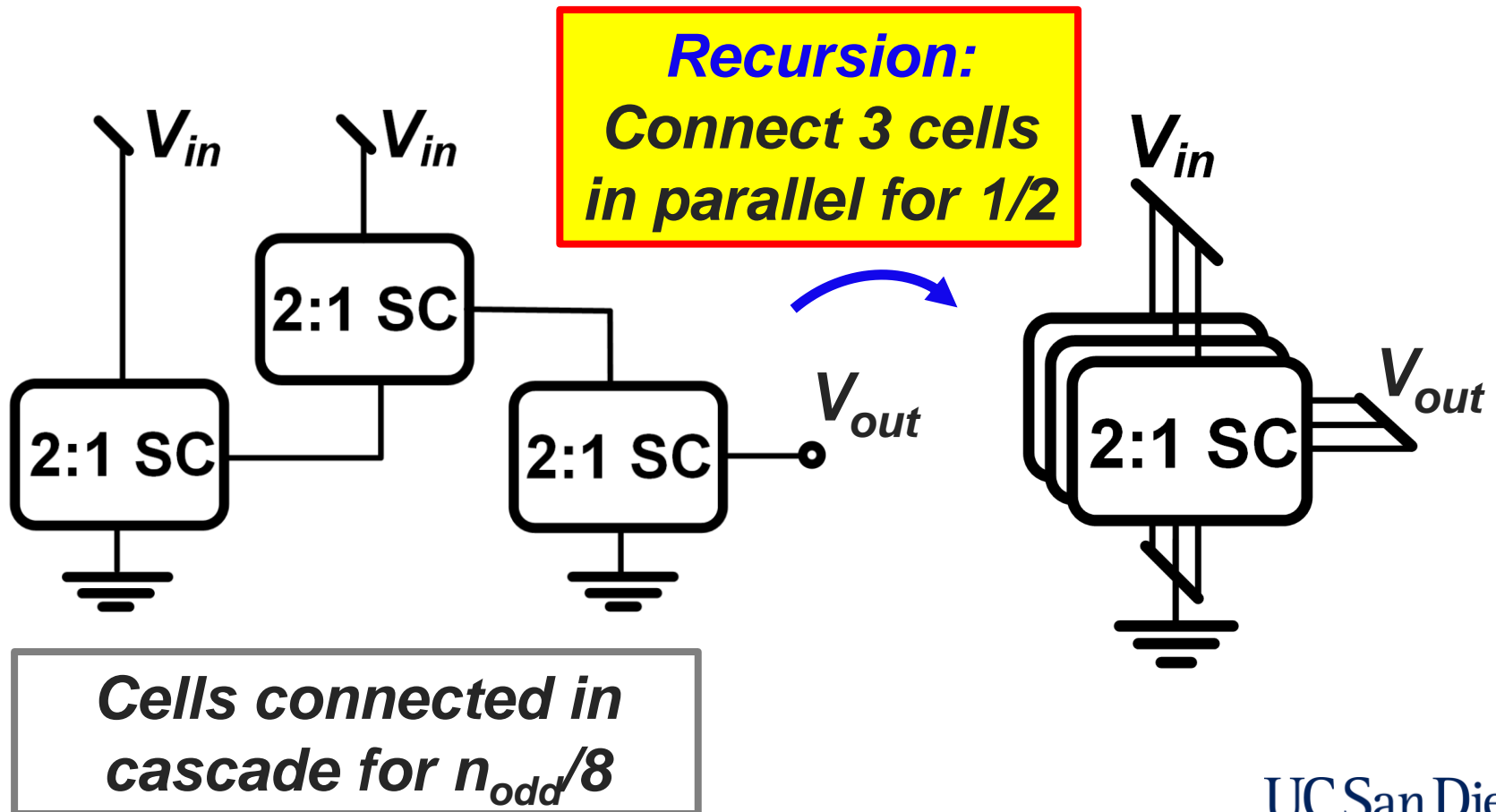
# Recursive 3-bit SC: 1/2 Realization

- Now  $1/8$ ,  $3/8$ ,  $5/8$ ,  $7/8$  are realized, how to achieve  $1/2$  using 3 cells?


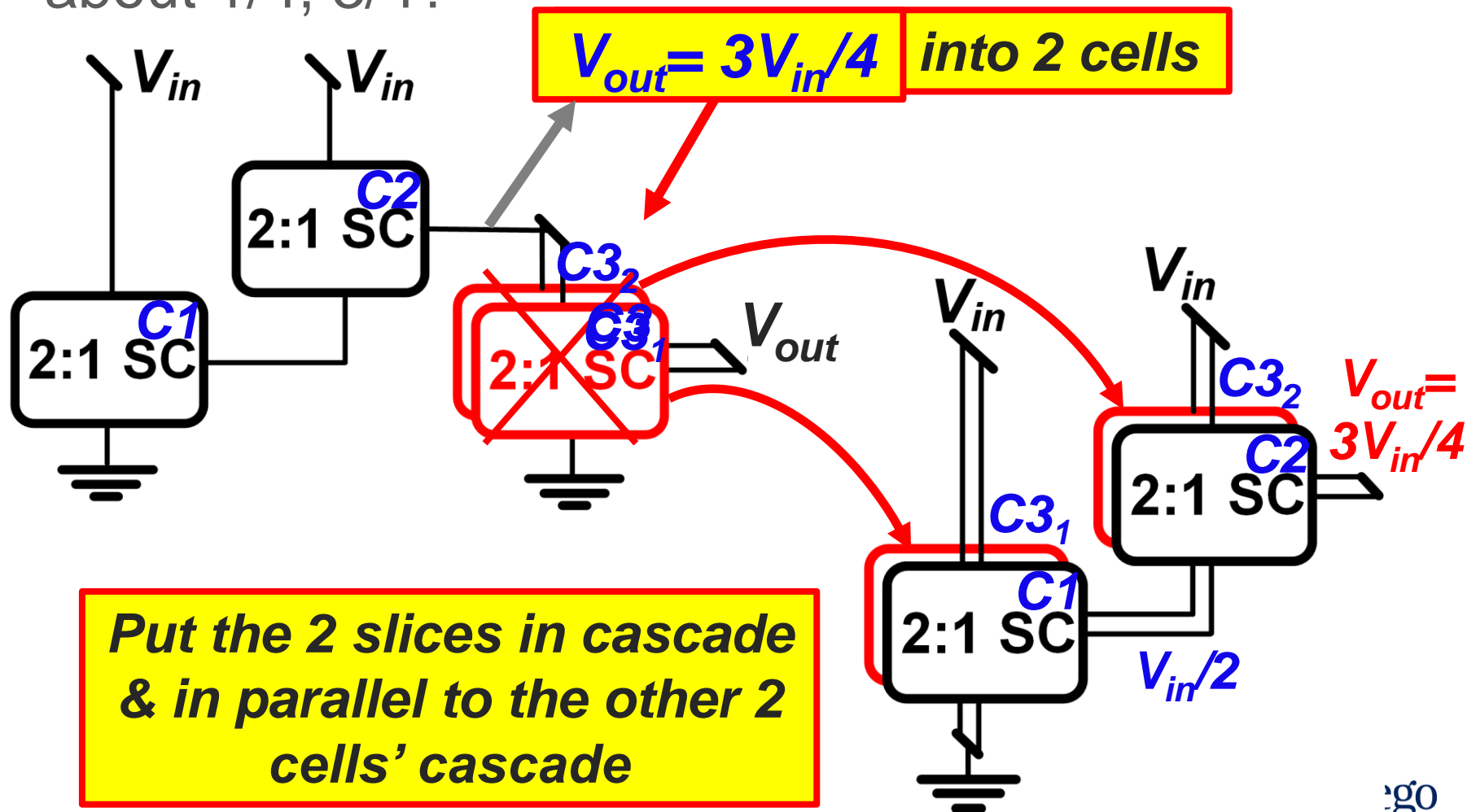
# Recursive 3-bit SC: 1/4, 3/4 Realization

- Now  $1/8$ ,  $3/8$ ,  $5/8$ ,  $7/8$ , and  $1/2$  are realized, what about  $1/4$ ,  $3/4$ ?




# Recursive 4-bit SC

- A 4-bit Recursive SC topology is implemented
  - *Balance between complexity and flat  $\eta$*


***Realizing 15-ratio, of high  $\eta$  by:***

- ***Recursive inter-cell connection for 100% cap utilization***
- ***Maximizing  $V_{in}$  & GND connections***
- ***Binary relative sizing***
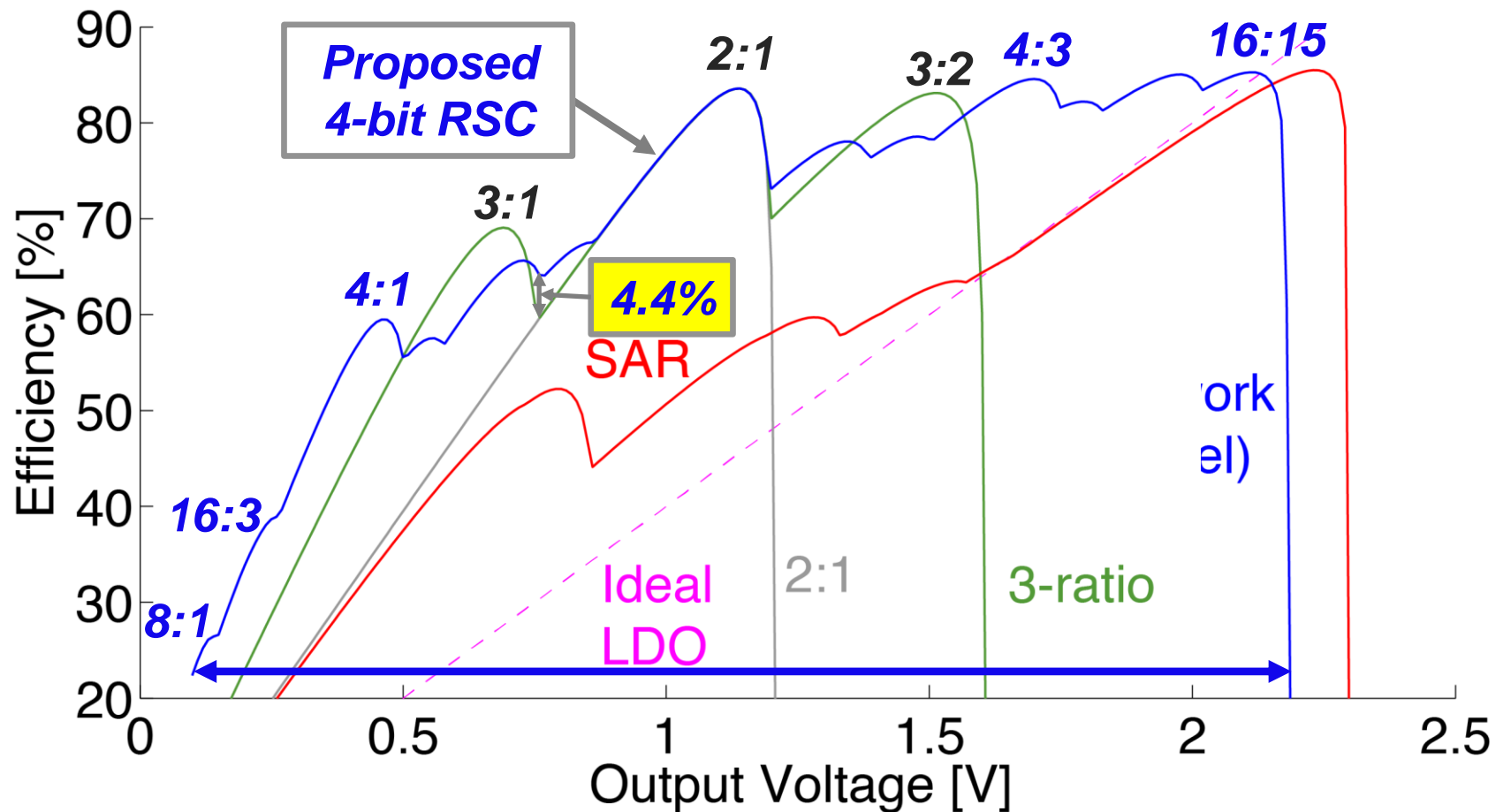
# 4-bit Recursive SC Efficiency vs. $V_{out}$


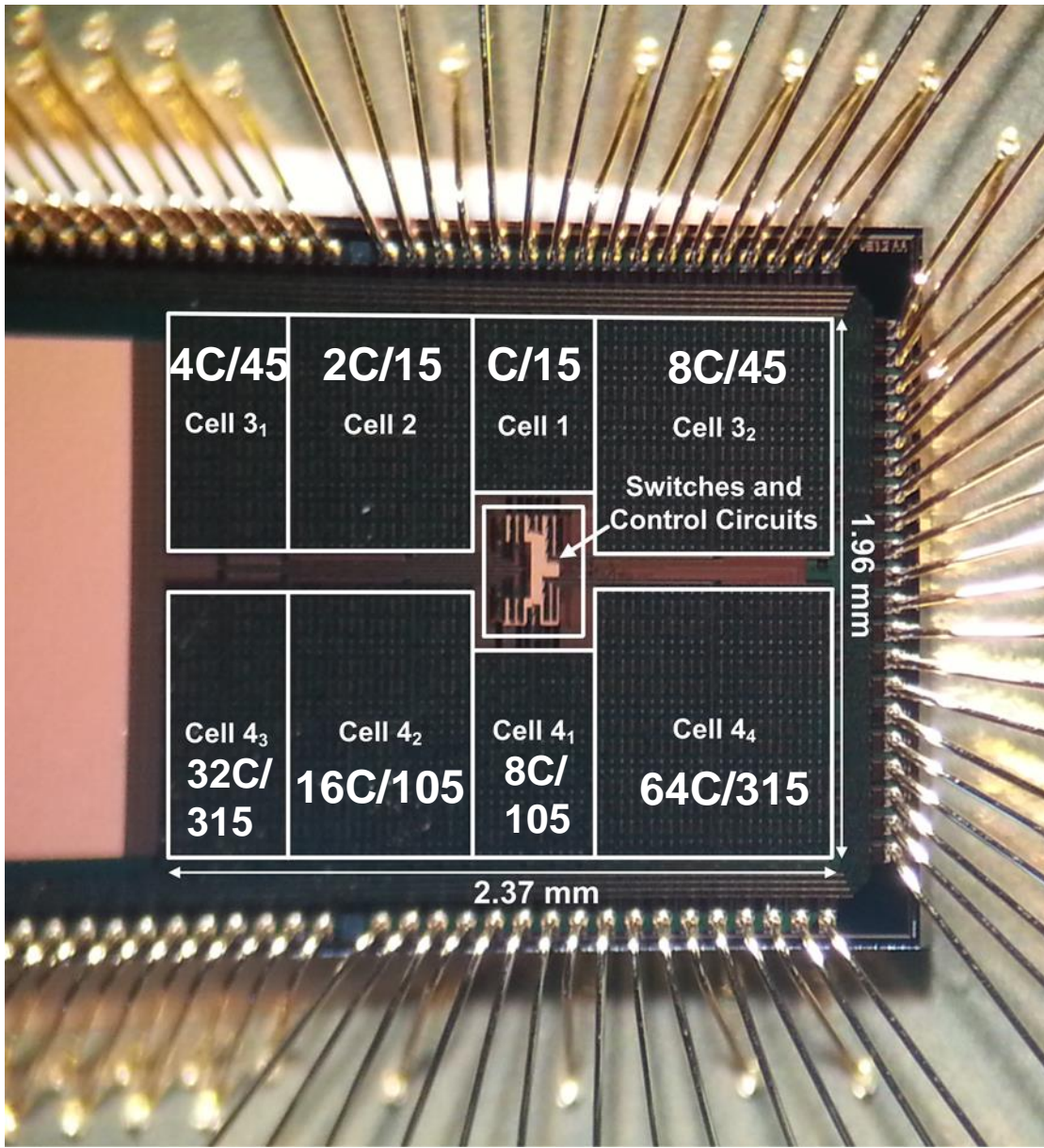
# Fully Integrated Recursive 4-bit SC Prototype




***0.25 $\mu$ m 2.5V  
bulk CMOS  
MIM  $\sim 0.9$  fF/ $\mu$ m<sup>2</sup>***

➤ **8 2:1 cells are used to enable recursion**

➤ **Cells are binary weighted for optimal relative sizing**

[Salem & Mercier,  
ISSCC 2014]

# Measured Efficiency vs. $V_{out}$

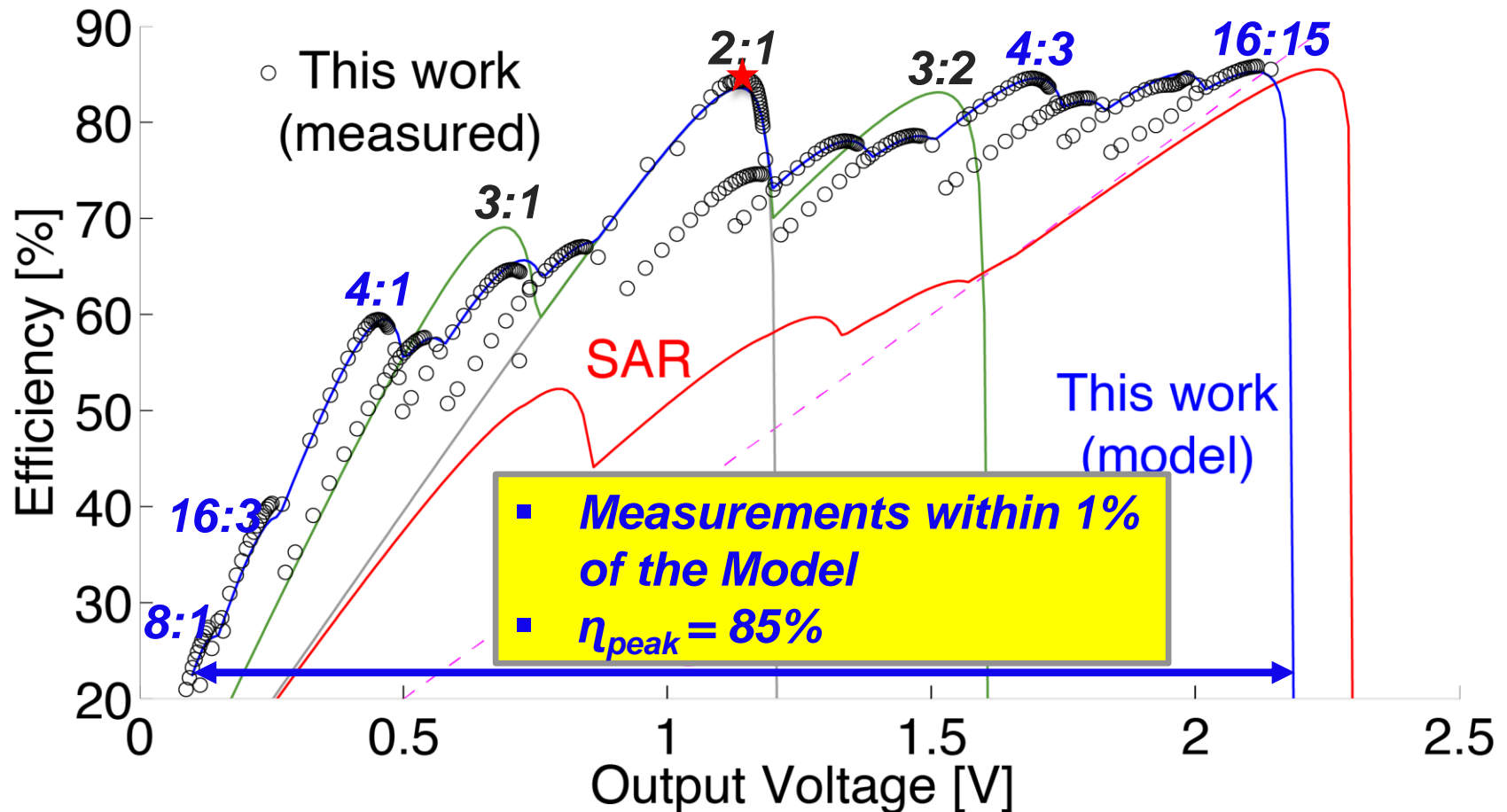


**For same silicon area: widest operating range, highest average efficiency**

# Talk outline


---

- Energy harvesting from the human body
- Switched-capacitor converters: principal challenges
- New switched capacitor topologies that achieve high efficiency over large voltage ranges:
  - Recursive binary
  - Recursive ternary
- Conclusions

# A new topology: Recursive Ternary SC

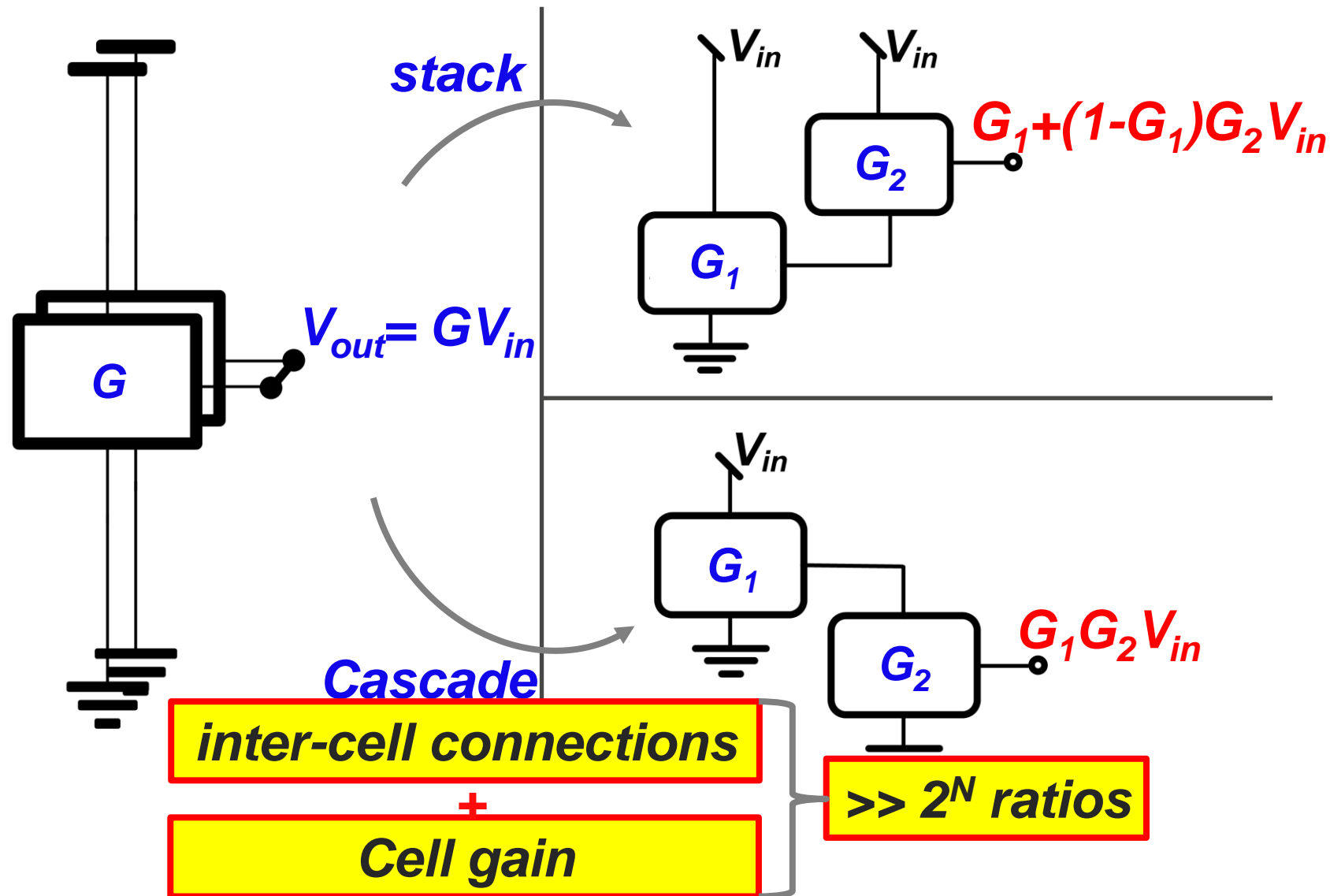


# Proposed Recursive Ternary SC

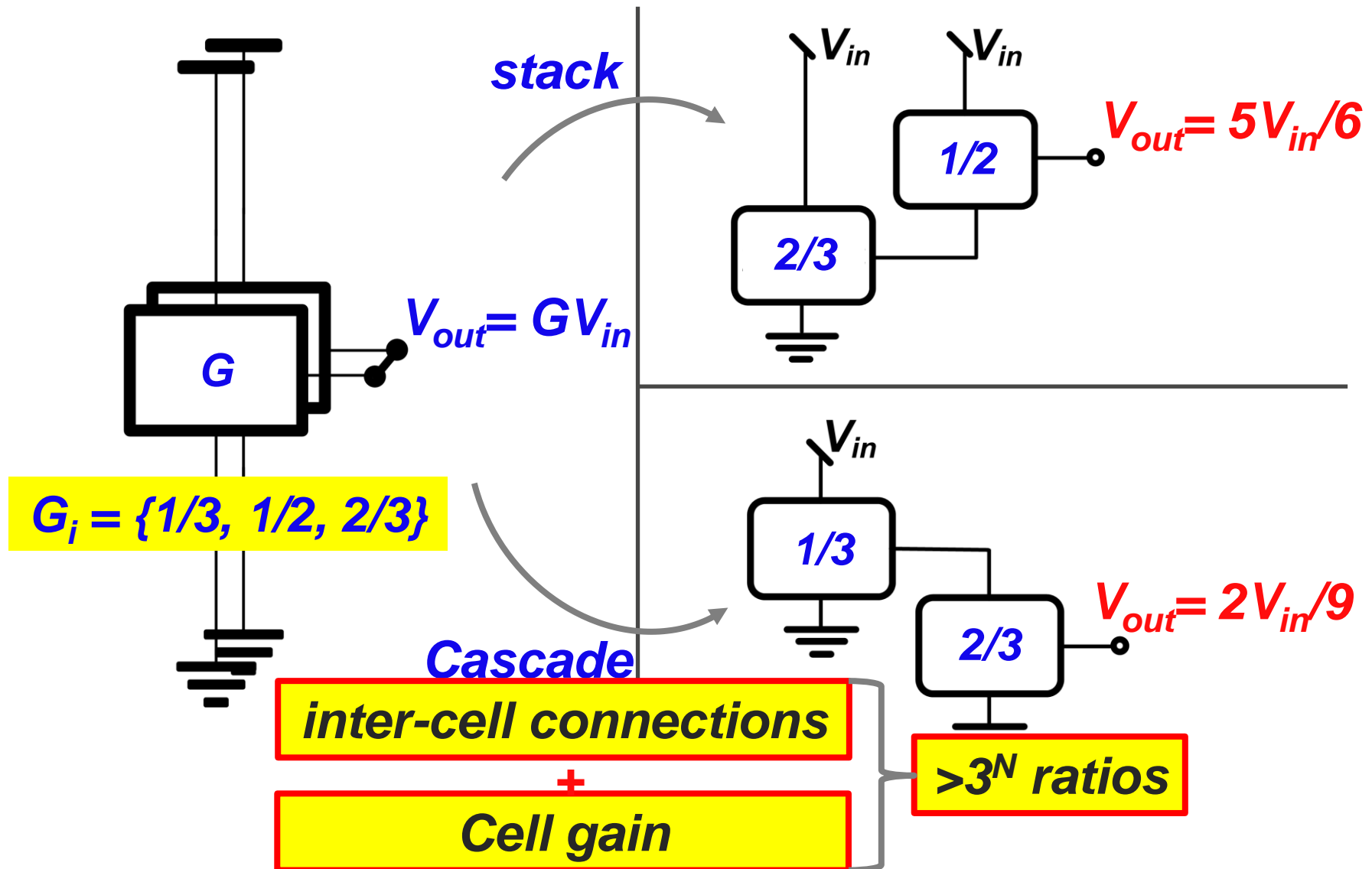

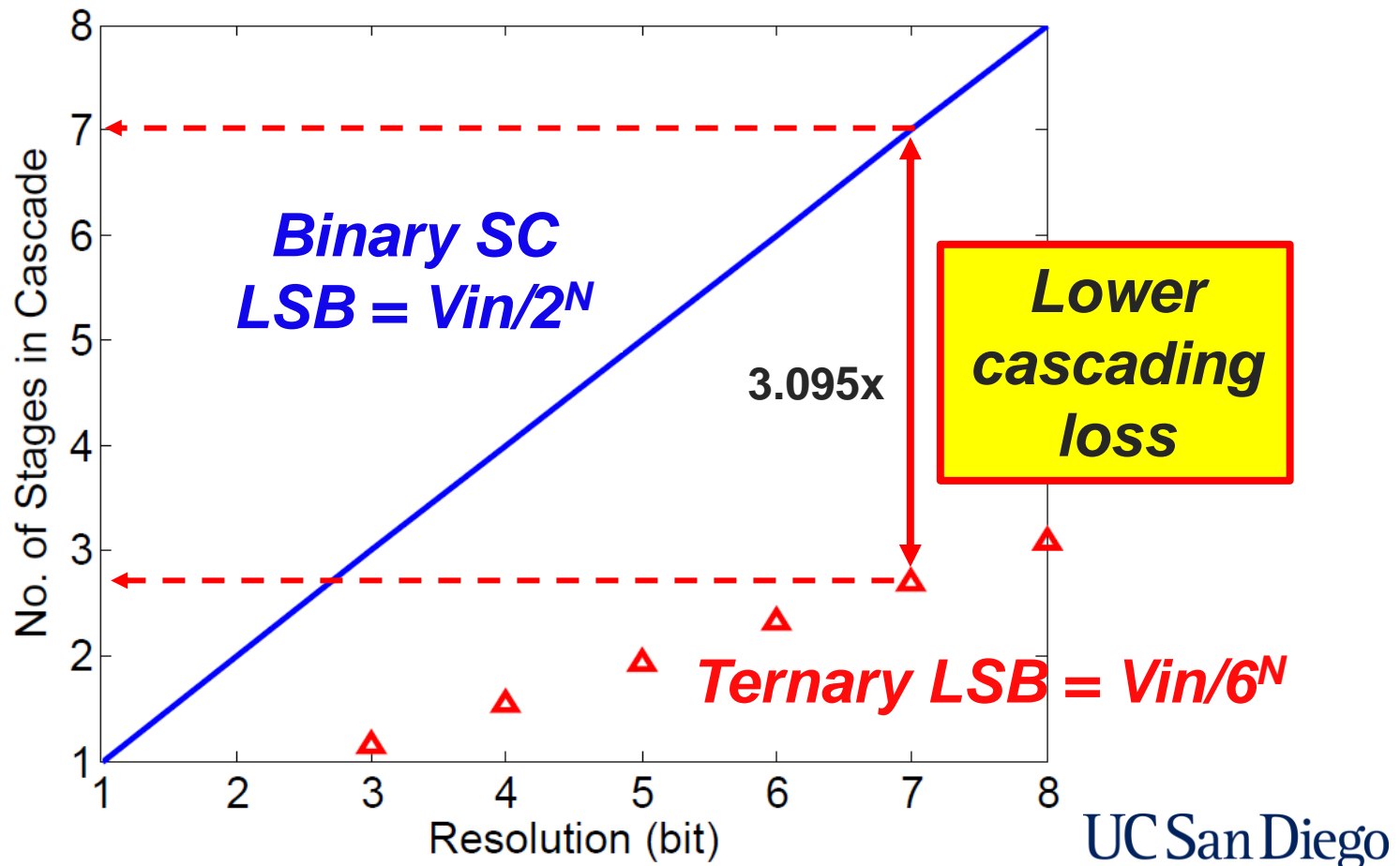
# Ternary SC: Minimum LSB

- Binary SC LSB  $\sim V_{in}/2^N$
- Ternary SC LSB  $\sim V_{in}/6^N$



# Ternary SC: What Ratios Result

- Binary conversion modes

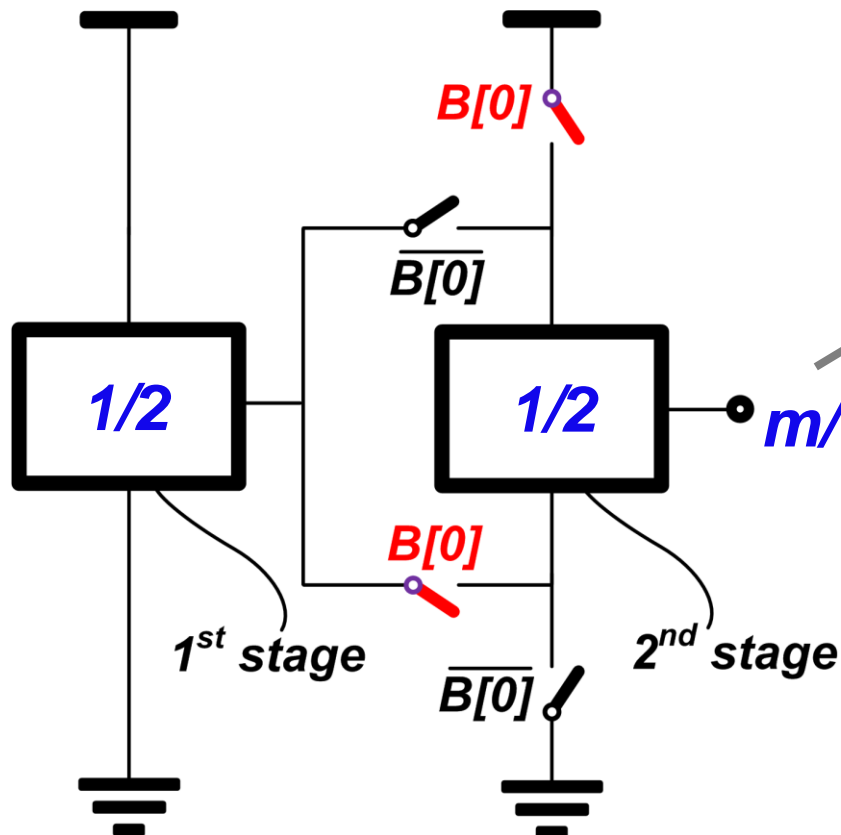

<i>G1</i>	<i>G2</i>	<i>Converter Ratio m/n</i>
$1/2$	$1/2$	$1/4 \quad 3/4$


$B[0]=0$

$B[0]=1$

*Can produce the same ratios as a Recursive Binary odd/ $2^2$*

# Ternary SC: What Ratios Result

- Ternary conversion modes

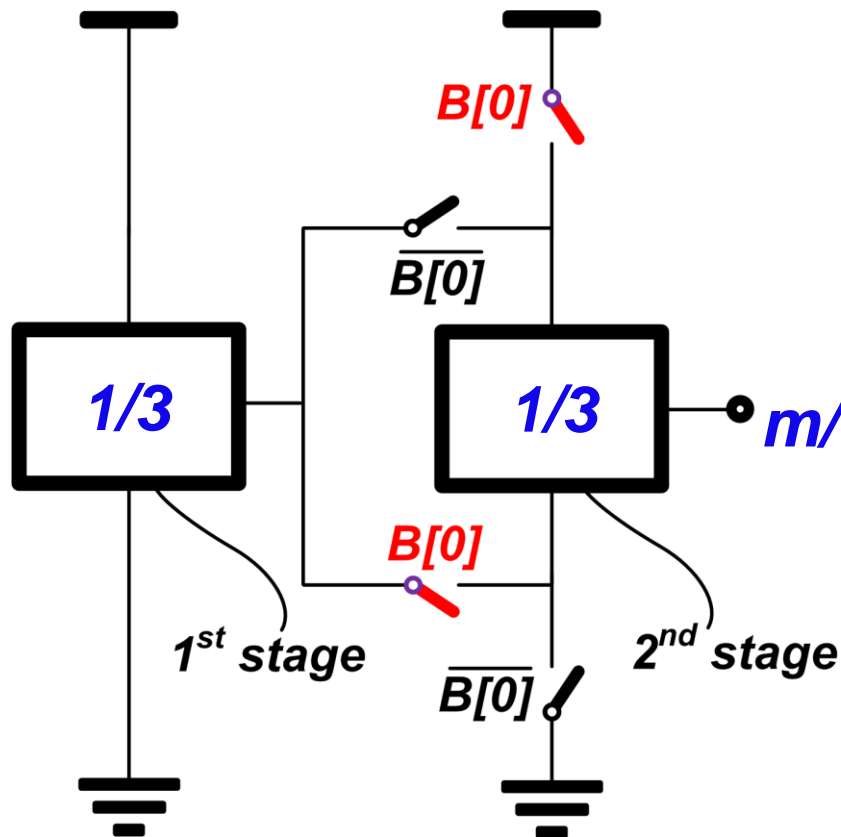

<i><b>G1</b></i>	<i><b>G2</b></i>	<i><b>Converter Ratio <math>m/n</math></b></i>
1/2	1/2	1/4 3/4
<b>1/3</b>	<b>1/3</b>	1/9 5/9


$B[0]=0$

$B[0]=1$

***Produces  
odd/ $3^2$  as  
odd/ $2^2$  for  $\frac{1}{2}$   
cell gain***


# Ternary SC: What Ratios Result

- Ternary conversion modes

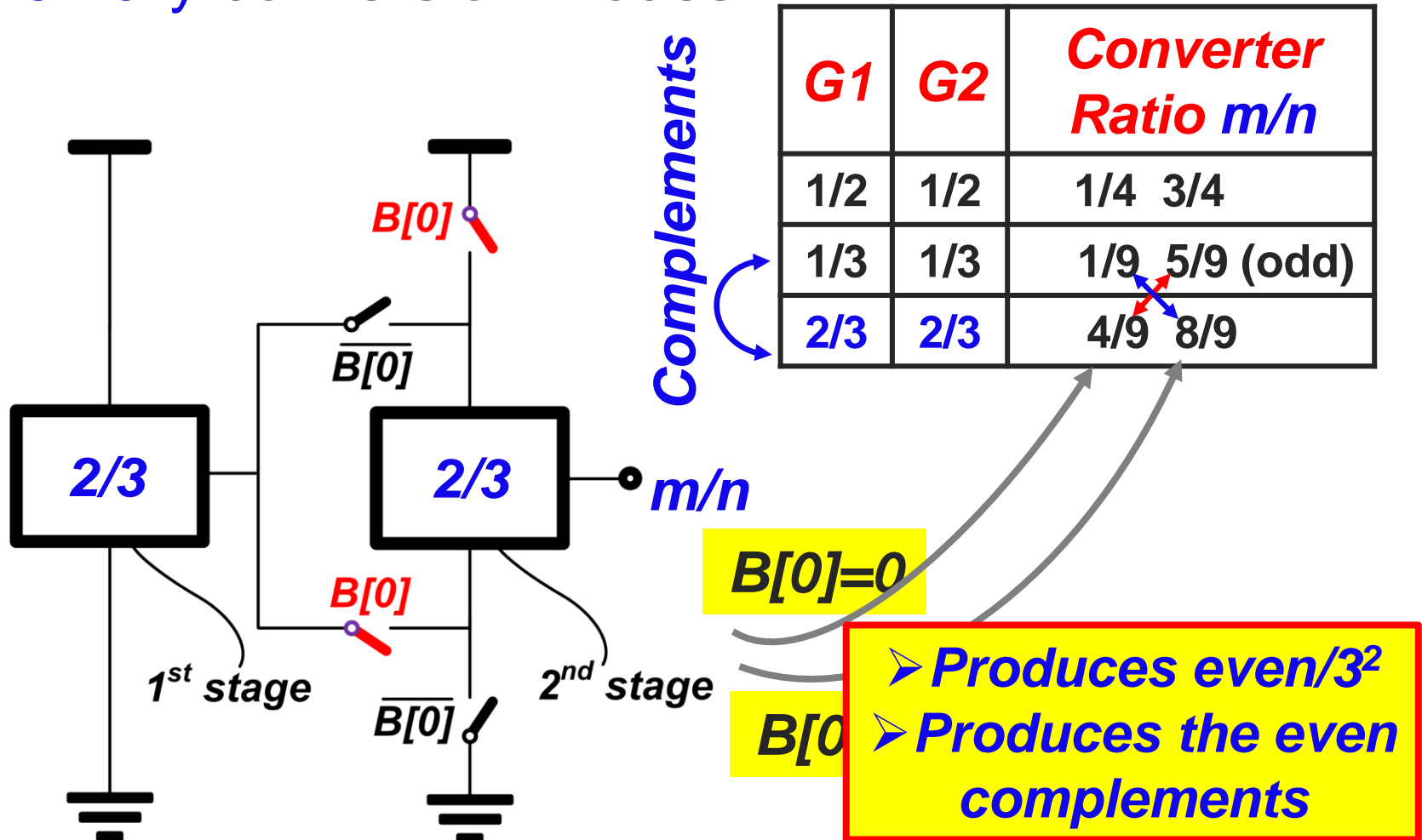

# Ternary SC: What Ratios Result

- Ternary conversion modes

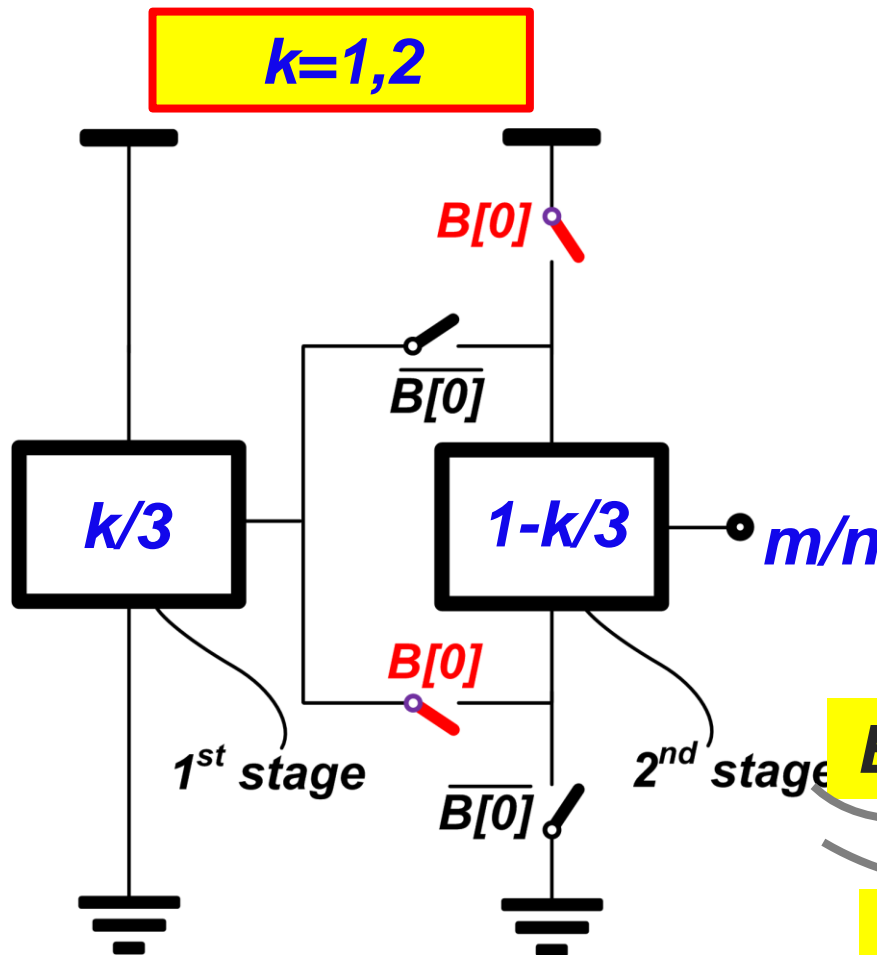

$G1$	$G2$	Converter Ratio $m/n$
1/2	1/2	1/4 3/4
1/3	1/3	1/9 5/9 (odd)
2/3	2/3	4/9 8/9 (even)
1/3	2/3	2/9 7/9
2/3	1/3	2/9 7/9


$B[0]=0$

$B[0]=1$

Produces complementary ratios

# Ternary SC: What Ratios Result

- Ternary conversion modes

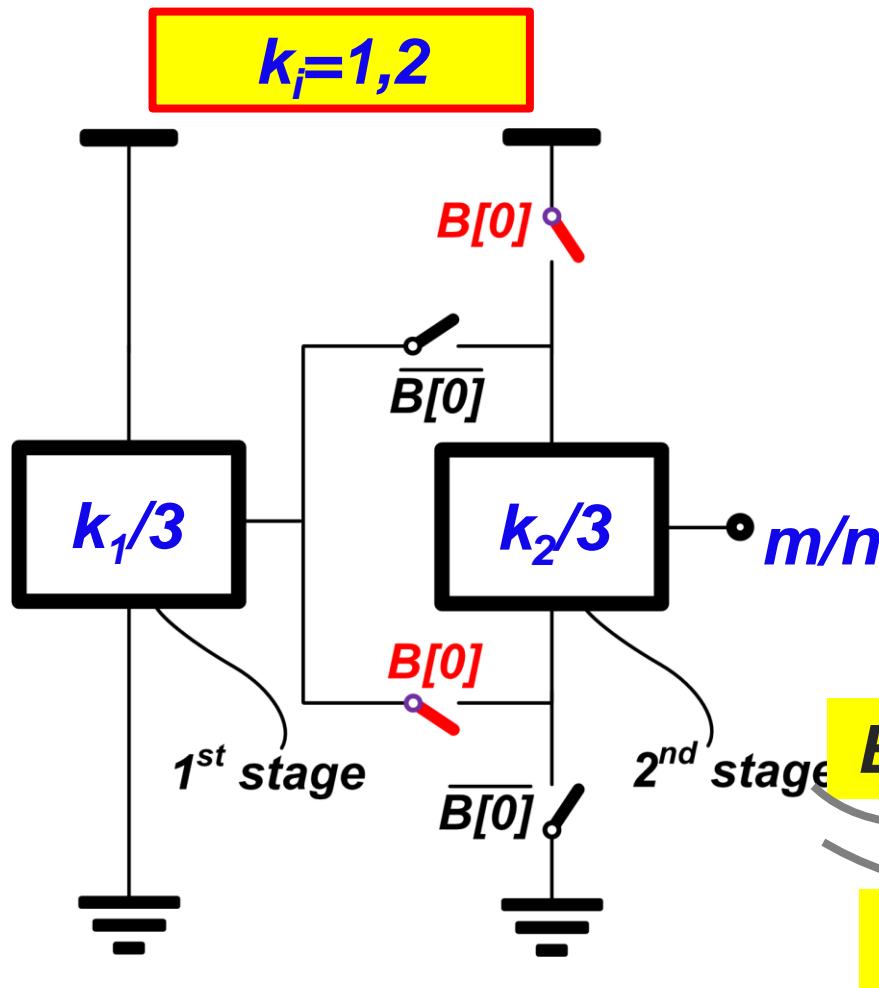

$G1$	$G2$	Converter Ratio $m/n$
1/2	1/2	1/4 3/4
1/3	1/3	1/9 5/9 (odd)
2/3	2/3	4/9 8/9 (even)
1/3	2/3	2/9 7/9 (complements)
2/3	1/3	2/9 7/9


Produces all  $m/3^2$  ratios except 3/9, 6/9 (i.e. 1/3, 2/3)

$B[0]=0$

$B[0]=1$

# Ternary SC: What Ratios Result

- Mixing conversion modes

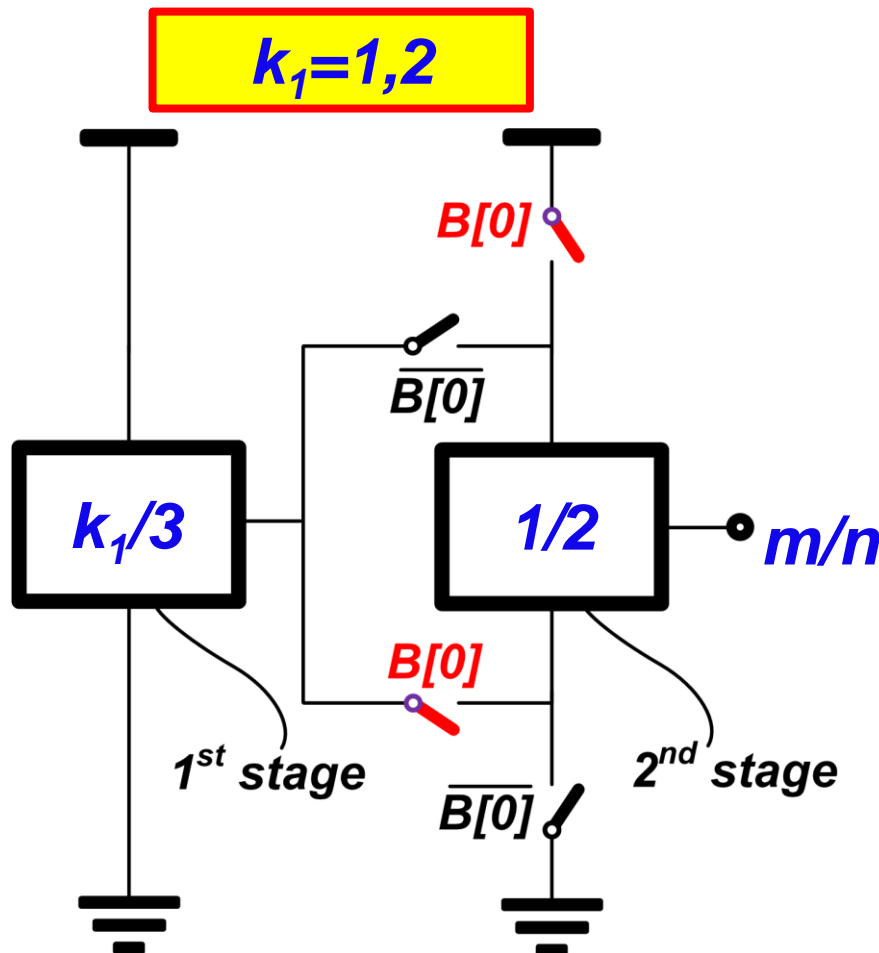

$G1$	$G2$	Converter Ratio $m/n$
1/2	1/2	1/4 3/4
1/3	1/3	1/9 5/9
2/3	2/3	4/9 8/9
1/3	2/3	2/9 7/9
2/3	1/3	2/9 7/9
1/3	1/2	1/6 6/9
2/3	1/2	3/9 5/6


$B[0]=0$

$B[0]=1$

UC San Diego

# Ternary SC: What Ratios Result

- Mixing conversion modes

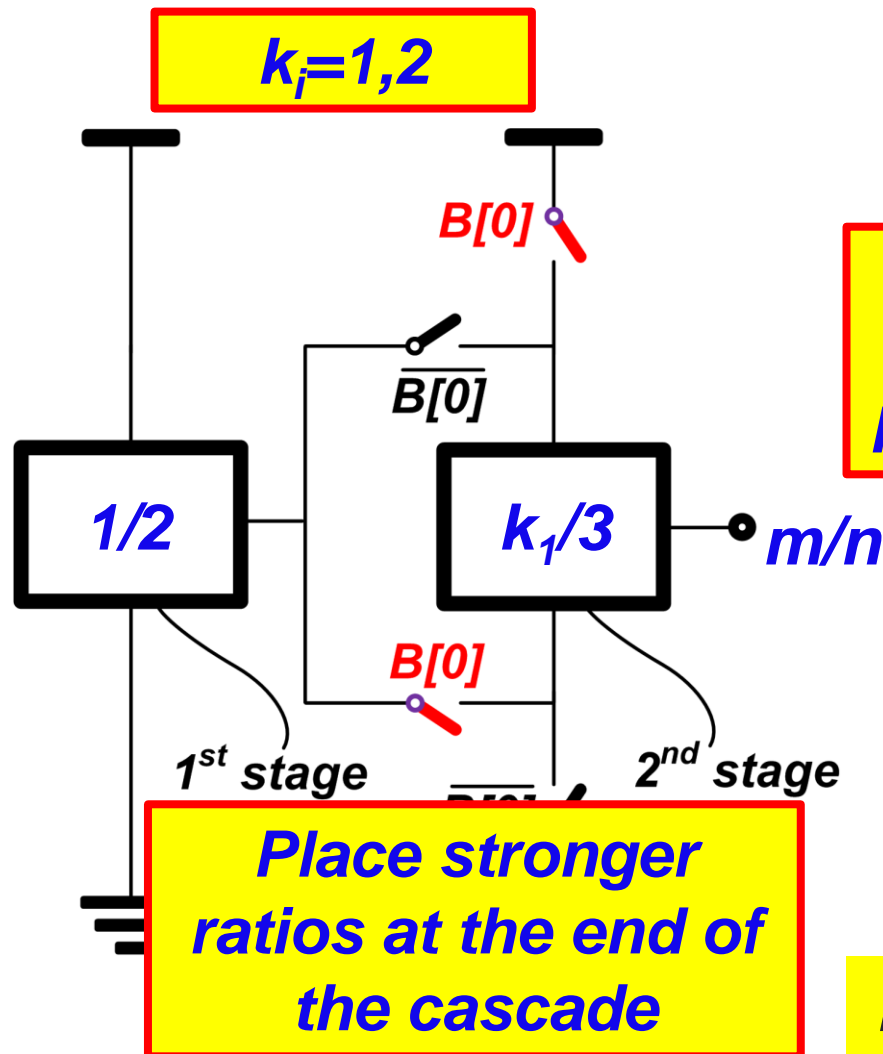

$G1$	$G2$	<b>Converter Ratio <math>m/n</math></b>	
$1/2$	$1/2$	$1/4$	$3/4$
$1/3$	$1/2$	$1/9$	$5/9$
$2/3$	$1/2$	$1/9$	$8/9$
$1/2$	$1/3$	$1/9$	$7/9$
$2/3$	$1/3$		
$1/3$	$1/2$	$1/6$	$6/9$
$2/3$	$1/2$	$3/9$	$5/6$
$1/2$	$1/3$	$1/6$	$6/9$
$1/2$	$2/3$	$3/9$	$5/6$

*Weak ratios, 1/3 handles larger currents*

*Higher loss*

$B[0]=0$


$B[0]=1$

iego

# Proposed Recursive Ternary SC

- Recursive Ternary incorporates the 3-Ratio Series-Parallel minimal charge sharing loss.

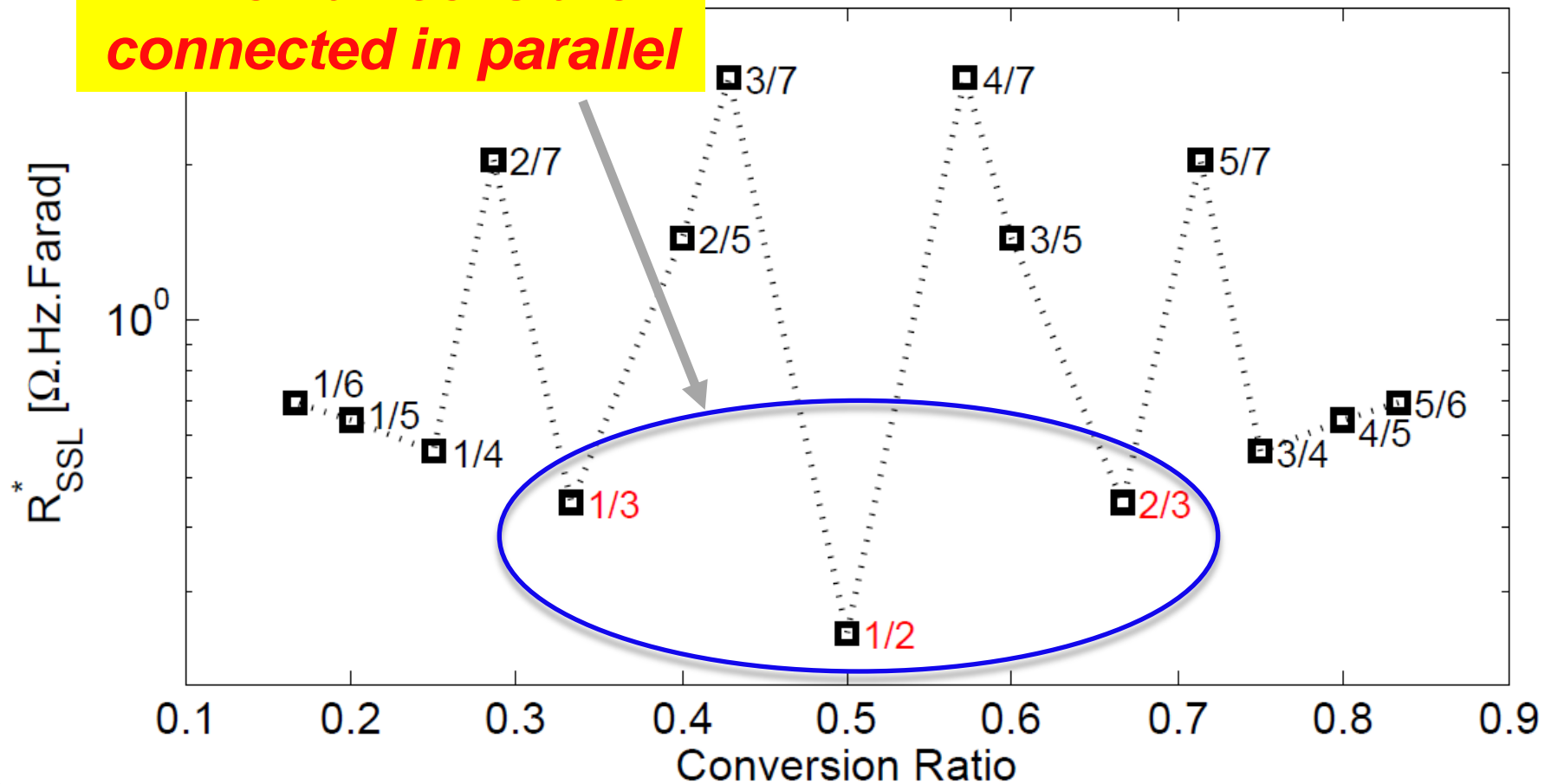
***When all cells are connected in parallel***




# Proposed Recursive Ternary SC

- Recursive Ternary *inherits* the superior performance of the 3-Ratio Series-Parallel topology

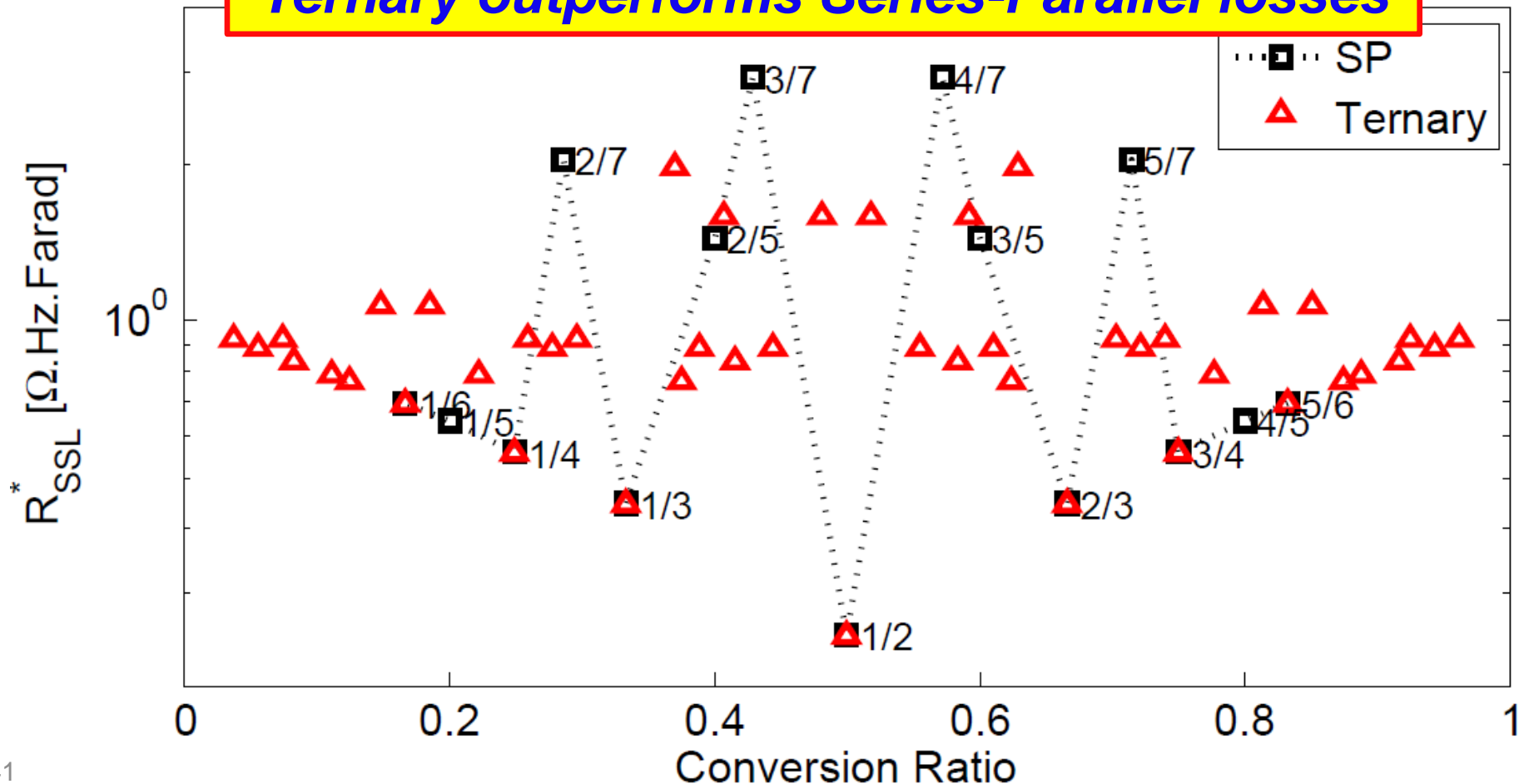***Ternary outperforms Series-Parallel losses***



# Recursive Ternary SC Prototype

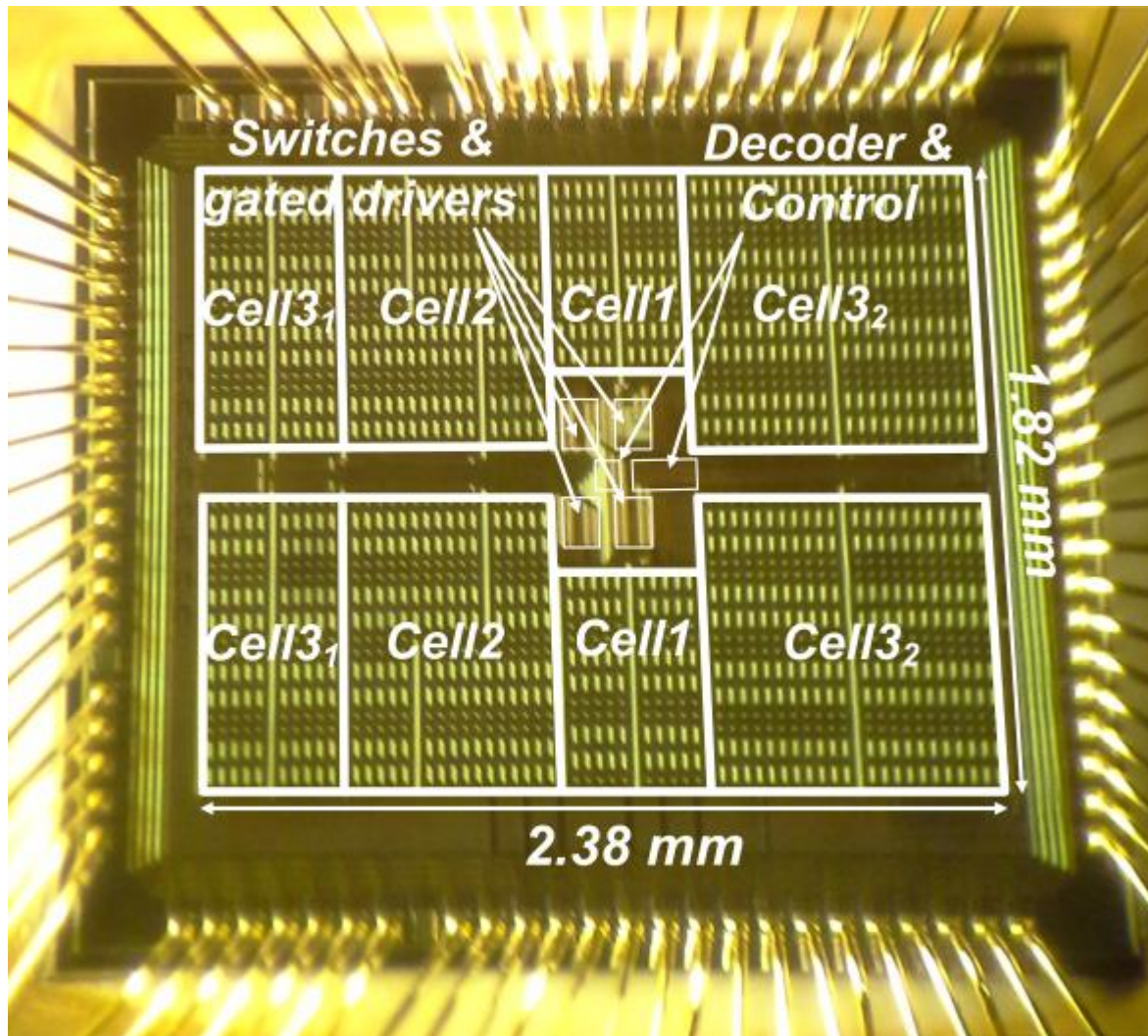


Tech.	0.25 $\mu$ m
Topology	3-stage RT
# of Ratios	45
Area	4.3mm <sup>2</sup>
Cap.	2.8nF

- *Cells are binary sized*
- *Bottom row is 0° phase*
- *Top is 180°*

[Salem & Mercier, CICC 2014]


# Measured Efficiency vs. $V_{out}$

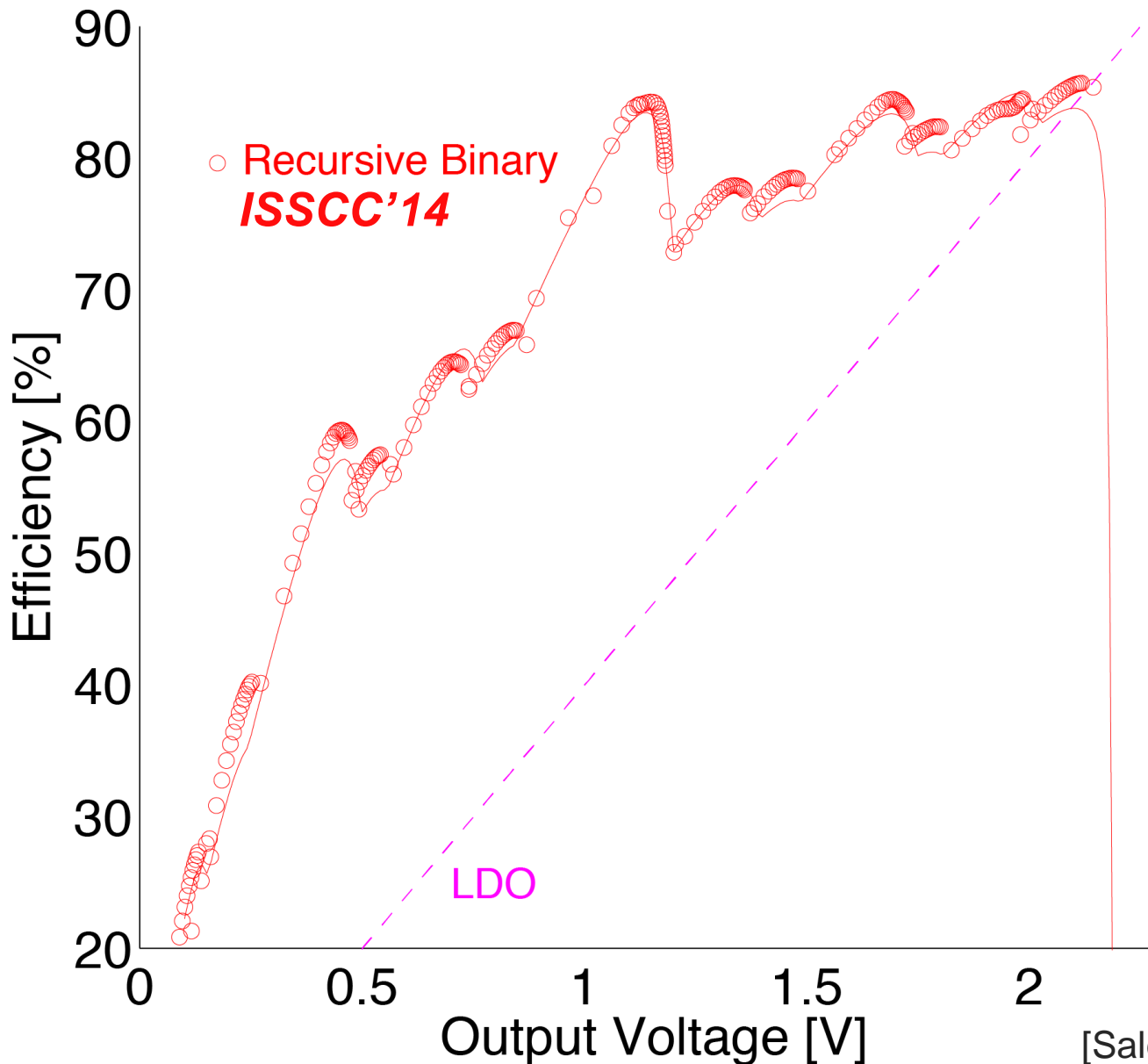

All topologies	
Tech	0.25μm
$I_L$	0.5mA/mm <sup>2</sup>
$V_{in}$	2.5V

*Recursive  
Binary  
large  $V_{out}$   
range*

# Measured Efficiency vs. $V_{out}$

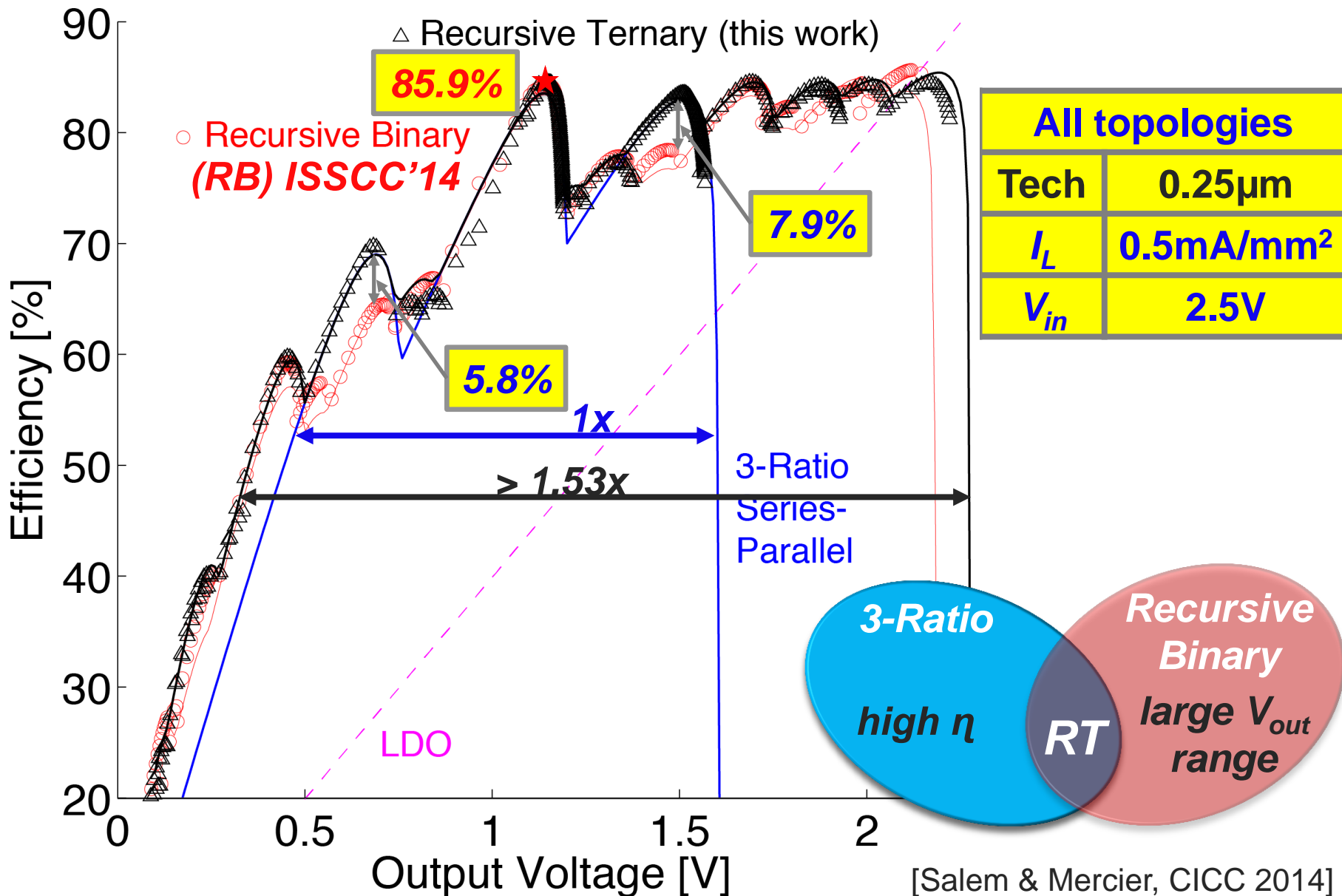

# Conclusions

- Miniaturized & efficient power converters are required for next-generation mobile and energy harvesting applications
- Switched-capacitors offer a route towards miniaturized efficiency
- New modular topologies are presented that achieve a **large # of conversion ratios while maintaining the performance benefits of simpler topologies**
  - Recursive binary implementation: 15-ratios, 85% peak efficiency, 0.2-2.2V range
  - Recursive ternary implementation: 45-ratios, 86% peak efficiency, 0.2-2.2V range
    - Combines the benefit of RB and 3-ratio SP for best-in-class efficiency

## **Acknowledgments:**

- *Energy harvesting*: Saurav Bandyopadhyay, Anantha Chandrakasan, Konstantina Stankovic, Andrew Lysaght (MIT/Harvard/MGH/MEEI), SRC IFC/C2S2
- *Switched capacitor DC-DC converters*: Loai Salem (UCSD)