

Monolithic Capacitive Power Converters Towards Higher Voltage Conversion Ratios



Hans Meyvaert
Aki Sarafianos
Nicolas Butzen
Michiel Steyaert

8 October 2014

micas



KATHOLIEKE UNIVERSITEIT
LEUVEN

Overview

- ***Introduction & Motivation***
- Capacitive AC-DC Step-Down Approach
- High Voltage Conversion Ratio DC-DC Approach
- Conclusions

Problem & Facts

Although **standby power** of individual mains connected appliances is low (<1 W), it represents a **significant fraction of global electricity consumption** due to the large amount of devices

Consumers:

- TV, VCR, Set-top, Stereo
- Computer
- Kitchen appliances
- External power supplies
- Ceiling fans

Consumption:

Annual Domestic Percentage

- France 2000: 7%
- UK 2004: 8%
- Other: up to 13%

Problem & Facts

Although **standby power** of individual mains connected appliances is low (<1 W), it represents a **significant fraction of global electricity consumption** due to the large amount of devices

Consequence:

- Emissions: International Energy Agency attributes 1% of 2007 global CO₂ emissions to vampire power
 - ↔ 3% CO₂ due global air traffic
 - CO₂ → Global warming
 - SO₂ → Acid rain
- Fire risk : Heat dissipation

Goal


- Provide low power from the mains with an **auxiliary power supply** enabling a **low loss standby power consumption**
 - Main power supply fully off
 - Low cost
 - Low volume
 - Low input power
 - Optimal power throughput

 **Large Voltage Conversion Ratio Required**

Bridging the voltage gap

1 ■ Series impedance

 - Resistor
 - Very lossy due to high voltage ratio
- Series capacitor
 - Lossless in ideal case
 - Large impedance as result of low mains frequency



2 ■ Direct mains connection

- Stacked voltage domains (high VCR / Extensive stacking)


Overview

- Introduction & Motivation
- ***Capacitive AC-DC Step-Down Approach***
- High Voltage Conversion Ratio DC-DC Approach
- Conclusions

A Capacitive AC-DC Step-Down Converter

■ Ideal model

 - $P_{out} = f(V_{out}, C_{in}, f_{mains}, V_{in})$
- f_{mains}, V_{in} fixed



$$V_{in}(t) = \sqrt{2}V_{in}\sin(2\pi f_{mains}t)$$

$$V_{C_{in}}(t) \approx (\sqrt{2}V_{in} - V_{out})\sin(2\pi f_{mains}t)$$

$$i_{C_{in}}(t) = C_{in} \frac{dV_{C_{in}}}{dt}$$

$$= C_{in}(\sqrt{2}V_{in} - V_{out})\cos(2\pi f_{mains}t)$$


$$2\pi f_{mains}$$

$$\langle |i_{C_{in}}| \rangle = 4f_{mains}C_{in}(\sqrt{2}V_{in} - V_{out})$$

$$P_{out} = \langle |i_{C_{in}}| \rangle V_{out}$$


Modeling result

 - $P_{\text{out}}(C_{\text{in}})$ linear
- $P_{\text{out}}(V_{\text{out}})$ linear
for low V_{DC}



Circuit implementation

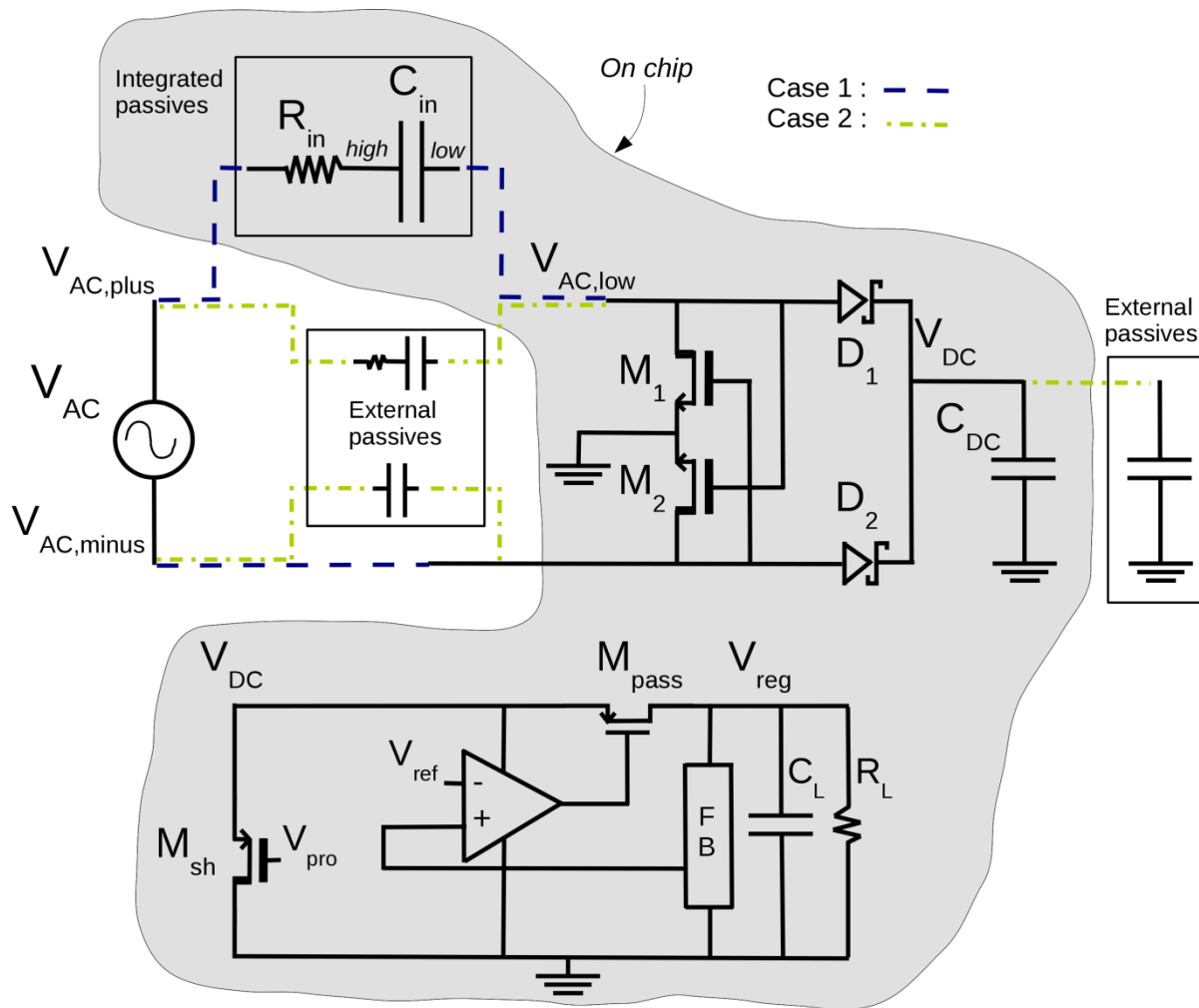- 2 cases: Fully integrated (μW 's), Highly Integrated (mW 's)




Chip implementation

■ Capacitor

- Metal-metal capacitor
- High voltage plate in top metal
- $4\mu\text{m}$ spacing
- 50 pF

■ Resistor

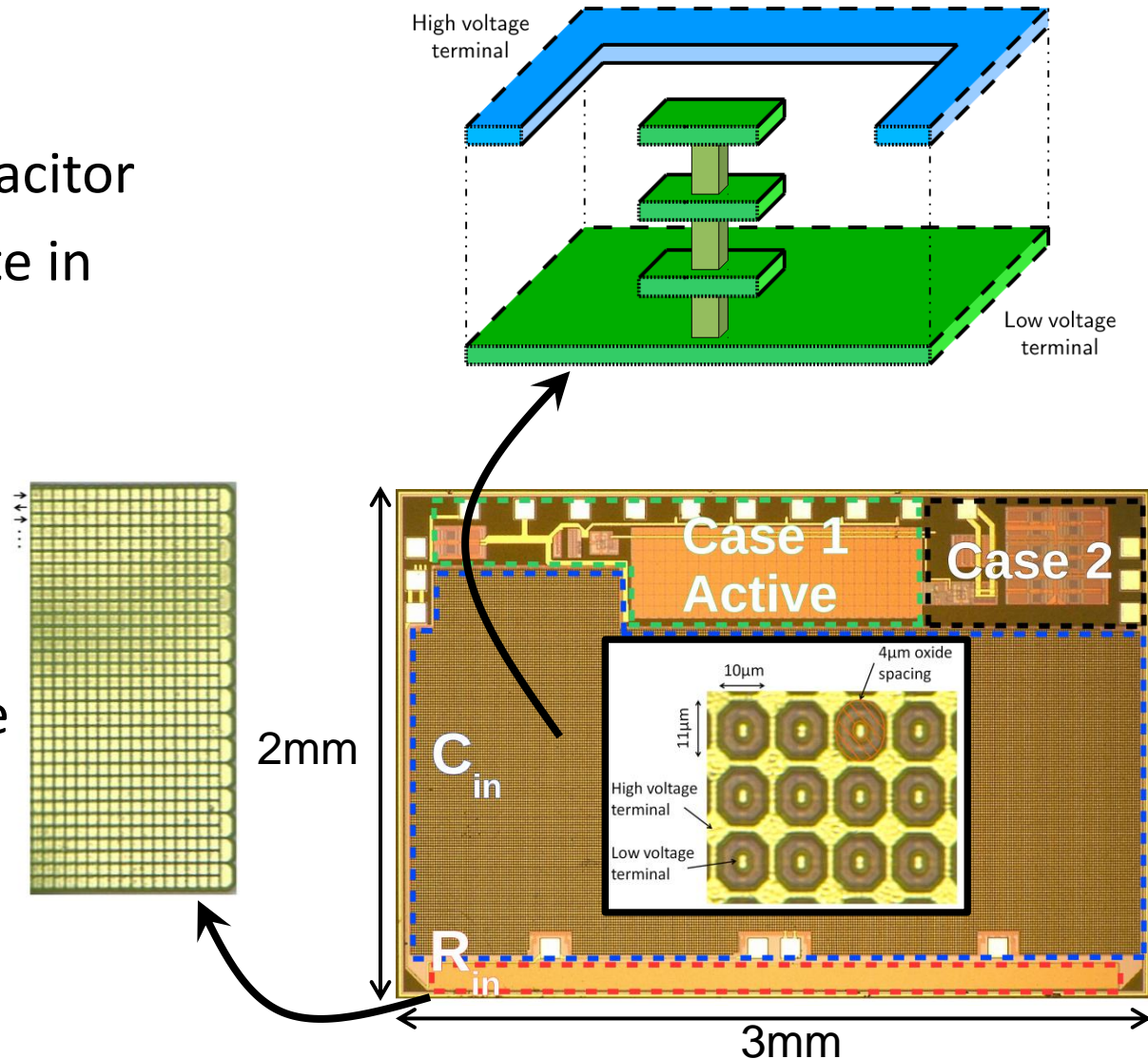- $6\mu\text{m}$ to substrate
- Top metals
- Vias
- $36\text{ k}\Omega$



Measurements



- Universal mains

- 85-265V_{rms}
- 50-60Hz

- C_{in}: 50pF

- US: 6.4 μW

- EU: 9.5 μW

 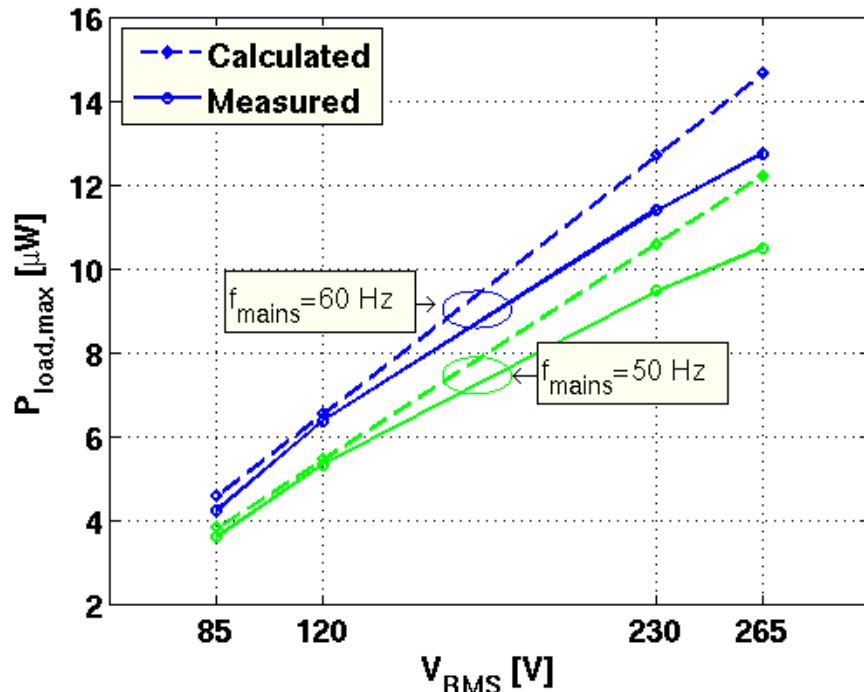

Measurements

- Universal mains



- 85-265V_{rms}

- 50-60Hz

- C_{in}: 2x 68nF

- US: 4.2 mW

- EU: 7 mW

 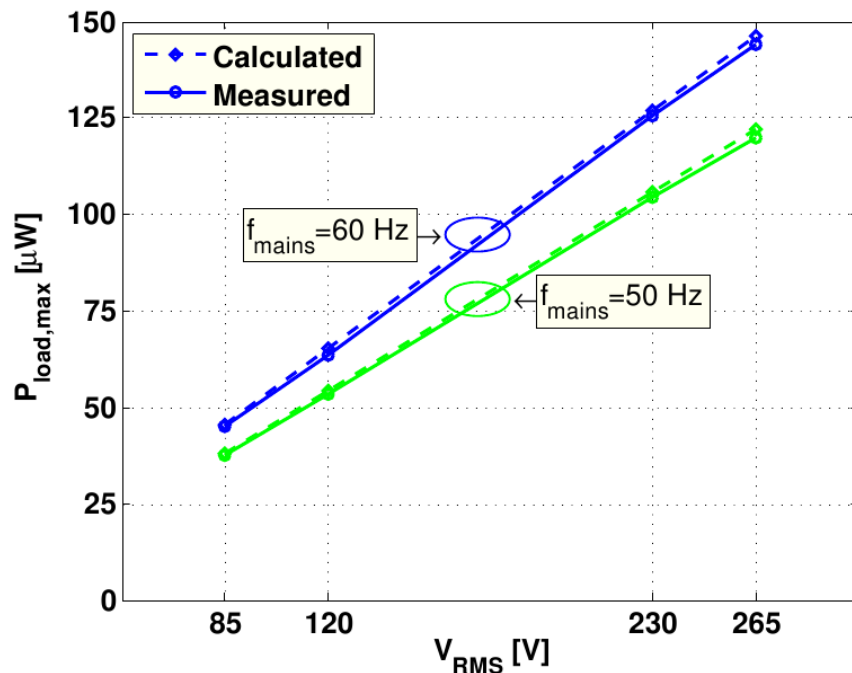

Measurements

Reference	[Tamez, Esscirc'10]	Case 1		Case 2 (2x68nF)	
Tech node	0.13μm	0.35μm			
V_{RMS}	120V	120V	230V	120V	230V
f_{mains}	60Hz	60Hz	50Hz	60Hz	50Hz
Power/area	0.43μW/mm ²	1.06μW/mm ²	1.58μW/mm ²	-	-
V_{reg}	4V	3.3V			
$t_{on,diode}$	48%	91%	93.5%	91%	93.5%
$P_{out,max}$	1.5μW	6.4μW	9.5μW	4.2mW	7mW

Overview

- Introduction & Motivation
- Capacitive AC-DC Step-Down Approach
- ***High Voltage Conversion Ratio DC-DC Approach***
- Conclusions

Concept & Goal

- *High voltage conversion ratio from a high input voltage with a monolithic IC*

Switched Capacitor approach?

➡ *Duty cycle 50%*

↔ *Inductive DC-DC converter : PWM*

✚ *Monolithic integration*

✚ *Voltage domain stacking/serialization*

➡ **Investigate SC DC-DC potential for Monolithic Very High VCR DC-DC**

Problem considerations

- What do we need to make a high VCR converter?
 - VCR is topology dependant
 - Min #capacitors set by Fibonacci Limit (Makowski)
 - Higher VCR requires more components
 - Switches & Capacitors
 - Voltage ratings set by topology
 - Control
 - Getting signals from start to finish throughout voltage domains

Problem considerations

- What do we have to make a high VCR converter?

- Switches

- Low voltage: GO1, GO2, (GO3)
- High voltage: DMOS

Impact

'high' f_{sw} Ok

'low' f_{sw} only

- Capacitors

- Low voltage: GOX cap, (MIM cap)
- High voltage: Fringe cap

'low' density

'very low' density



It will be impractical to use DMOS devices since low f_{sw} and very low density capacitors are not a good match

Problem considerations

- What do we need to pay attention to in a monolithic high VCR converter?
 - How does VCR influence component requirement?
 - Component rating
 - Component utilization
 - Parasitics related to components
 - Ex. parasitic capacitor coupling to substrate with $V_{c, \text{rated}}$

➡ Where are the loss contributions coming from?

CMOS considerations


- Where are the loss contributions coming from?

- Intrinsic losses

- R_{out} related

- Extrinsic losses

 
- R_{dyn} related
 - Parasitic capacitor coupling factor
 - Parasitic capacitor swing
 - $M_{sw} = \sum a_{c,i} V_{Cpar,swing,i}^2$




Investigated topologies

- Known to have efficient capacitor utilization


(a) Dickson Star 4:1

 


(c) Fibonacci 5:1

 


(d) Dickson Star Embedded Cascade 8:2:1

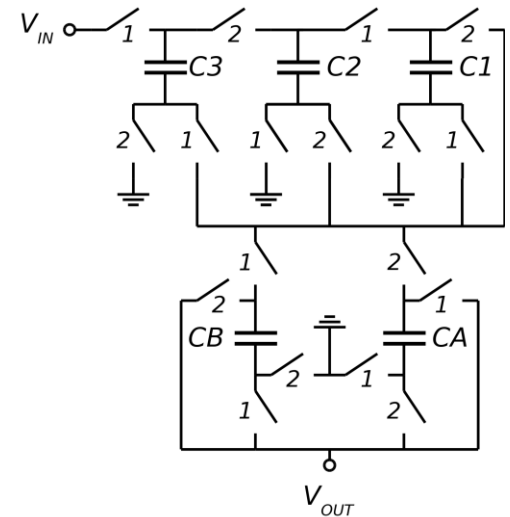

(b) Series parallel 4:1

 

(e) Doubler 4:1

 


Topology results


	Dickson Star	Series Parallel	Fibonacci	Dickson Star Embedded Cascade	Doubler
# columns = k k_c $V_{C,rated} [V_{out}]$ $V_{sw} [V_{out}]$	$k = N - 1$ $[\frac{1}{N} \dots \frac{1}{N}]$ $[1 \ 2 \ 3 \dots N-1]$ $[1 \dots 1]$	$k = N - 1$ $[\frac{1}{N} \dots \frac{1}{N}]$ $[1 \dots 1]$ $[1 \ 2 \ 3 \dots N-1]$	$Fib_{k+2} = N^a$ $[Fib_1 \dots Fib_k]$ $[Fib_2 \dots Fib_{k+1}]$ $[Fib_1 \dots Fib_k]$	$k = \frac{N}{2} - 1^b$ $[\frac{1}{N} \dots \frac{1}{N} \ \frac{1}{4} \ \frac{1}{4}]^b$ $[2 \ 4 \ 6 \dots (\frac{N}{2} - 1) \ 1 \ 1]^b$ $[2 \dots 2 \ 1 \ 1]^b$	$k = 2\log_2(N) - 1$ $[\frac{1}{2} \ \frac{1}{2^2} \ \frac{1}{2^2} \ \frac{1}{2^3} \ \frac{1}{2^3} \dots \frac{1}{2^N} \ \frac{1}{2^N}]$ $[1 \ 2 \ 2 \ 4 \ 4 \dots \frac{N}{2} \ \frac{N}{2}]$ $[1 \ 2^1 \ 0 \ 2^2 \ 0 \dots 2^{\log_2(N)} \ 0]$
M_{sw}	$\frac{N-1}{N}$	$\frac{1}{N} \sum_{i=1}^{N-1} i^2$	$\frac{1}{N} \sum_{i=1}^k (Fib_i)^3$	$2.5 - \frac{4}{N}$	$\frac{1}{2} + \sum_{i=1}^{(\log_2 N)-1} 2^{i-1}$
$K_c = (\sum_{i=1}^N k_{c,i})^2$ $K_c, N = \infty$			$(\frac{N-1}{N})^2$ 1		$(\frac{1}{2} + \sum_{i=1}^{(\log_2 N)-1} 2^{-i})^2$ 2.25
$M_{sw}, N = 2$ $M_{sw}, N = 4$ $M_{sw}, N = 8$ $M_{sw}, N = 16$ $M_{sw}, N = 64$ $M_{sw}, N = \infty$	$\frac{1}{2}$ $\frac{3}{4}$ $\frac{7}{8}$ $\frac{15}{16}$ $\frac{63}{64}$ 1	$\frac{1}{2}$ 3.5 17.5 77.5 1333.5 ∞	$\frac{1}{2}$ — 4.62 — $N = 55 - 89$ 220.6 – 578 ∞	$\frac{1}{2}$ 1.5 2 2.25 2.375 2.5	$\frac{1}{2}$ 1.5 3.5 7.5 31.5 ∞
^a $Fib_1 = 1, Fib_2 = 1$ ^b $N > 2$ and N even and $\frac{N}{2}$ even					

Topology Simulations

 ■ Validation of Dickson Star: $\eta[\alpha]$, $\eta[\text{VCR}]$



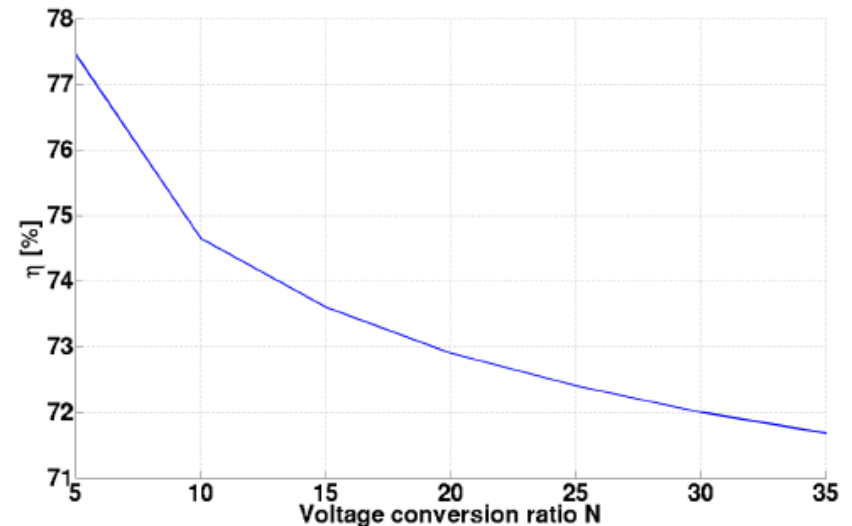
(a) Dickson Star topology with parasitic reduction at $\text{VCR}=11$, $f_{\text{sw}} = 10\text{MHz}$, $V_{\text{in}} = 41.7\text{V}$, $V_{\text{out}} = 3.3\text{V}$, $P_{\text{out}} = 40\text{mW}$, $C_{\text{tot}} = 2.9\text{nF}$



 (b) Evolution of the converter efficiency with rising voltage conversion ratio, $f_{\text{sw}} = 10\text{MHz}$, $\alpha_{\text{par}} = 3\%$, $V_{\text{out}} = 2.5\text{V}$, $P_{\text{out}} = 20\text{mW}$, $C_{\text{tot}}/V_{\text{in}} = 1.94\text{nF}/19\text{V}$ for $N=5$ to $2.86\text{nF}/100.5\text{V}$ for $N=35$


Inclusion of practical C_{fly} voltage rating

- Variable VCR; $V_{out}=1.8$, $\gamma=0.88$, $f_{sw}=15\text{MHz}$, $P_{out}=20\text{mW}$




Inclusion of practical C_{fly} voltage rating

 - Variable VCR; $V_{\text{out}}=1.8$, $\gamma=0.88$, $f_{\text{sw}}=15\text{MHz}$, $P_{\text{out}}=20\text{mW}$



Inclusion of practical C_{fly} voltage rating

 - Variable VCR; $V_{out}=1.8$, $\gamma=0.88$, $f_{sw}=15\text{MHz}$, $P_{out}=20\text{mW}$



Overview

- Introduction & Motivation
- Capacitive AC-DC Step-Down Approach
- High Voltage Conversion Ratio DC-DC Approach
- ***Conclusions***

High VCR topology conclusion

- M_{sw} highly volatile over investigated topologies
 - Dickson Star clearly differentiates and outperforms
 - Highest possible capacitance utilization
 - Lowest possible M_{sw} metric (*converges!*)
 - Good match for CMOS implementation
- Embedded D* Cascade not better than D*
 - Even though it is a single stage conversion

*Decreasing η drop
with increasing VCR*

Conclusions

- **High VCR AND Monolithic integration**
 - α_{par} and $V_{\text{Cpar,swing}}$ have *large* impact on solution space
 - **Dickson Star** topology very *promising*:
 - Converging f_{ac}
 - Converging M_{sw}
 - Large **component count** *no issue*

Thank you!

QUESTIONS?