


Fully-Integrated Digital Average Current-Mode Control Voltage Regulator Module IC

Mor M. Peretz

The Center for Power Electronics and Mixed-Signal IC
Department of Electrical and Computer Engineering
Ben-Gurion University of the Negev, *ISRAEL*

Emails: morp@ee.bgu.ac.il

 Website: <http://www.ee.bgu.ac.il/~pemic>




Contributors

Mr. Eli Abramov, PEMIC - BGU

Mr. Timur Vekslender , PEMIC - BGU




IC division of Vishay Ltd. (Siliconix)

 


Controllers for VRMs and PoLs

Control Objectives

 - Regulate the output voltage
- Obtain zero or small steady-state (DC) error
- Fast recovery from input and load changes
- Reasonable overshoot



 


Analog Controllers

+++

Still in the lead

- ✓ Accurate and efficient
- ✓ Fast response – wide bandwidth
- ✓ High (continuous) resolution
- ✓ Lower costs (<3A – All analog)

 - × Labor intensive
- × Tailored compensation
- × Pin count
- × Limited flexibility/scalability
- × Communication and interface
Big D + Big A



Digital Controllers

+++


- ✓ Comparable or better dynamics
- ✓ Reduced size of overall solution
- ✓ Scalable and flexible
- ✓ Auto-tuning - No compensation
- ✓ Plug-and-play
- ✓ Lower pin count
- ✓ Efficiency optimization

- × Different design
- × Power hungry

What do we really trade for a digital controller


- Mimicking analog controller operation by a digital one
- Conventional ADCs are too expensive
- High-res PWM is power hungry
- Do we 'settle' for voltage-mode

How "lean" can we go?

 

**WRONG
WAY**

 Protection, power management, etc. are still in...




Digital Architecture Bottom up

Create an attractive alternative to analog control

- Hardware redesign
 - Focus on the benefits of digital electronics
 - Specifically targeted to power management
 - Avoid sensitive analog units
 - Standard-cell digital design (no custom design)
- Standardize the design flow
 - Reduce labor efforts
 - Easier testing
 - Faster development

 *One step ahead:
Entire controller created
through code*




Digital Process

Synchronous

- ✓ Reliable
- ✓ Well-defined behavior
- ✓ Sequential or parallel
- × Power hungry (HS clk)
- × Synchronization hardware (e.g., clock tree)


Asynchronous

 - ✓ Low power
- ✓ Ultrafast
- ✓ Area saving
- × Different design method



Objective

 - Develop a compact All-digital controller architecture for VRM or PoL
- Entire hardware described through HDL
 - All standard digital design flow
 - No analog part
- Integrated switches (12V nominal input)
 - Minimize analog labor (drive)



Compensation type

Voltage-mode

$$D[n] = D[n-1] + av_{err}[n] - bv_{err}[n-1] - cv_{err}[n-2]$$

$$D[n] = D[n-1] + a * v_{err}[n] - b * v_{err}[n-1] - c * v_{err}[n-2]$$

3 multiplications + accumulator

Current-mode

$$d[n] = d[n-1] + k \left[i_{err}[n] - \left(1 - \frac{T_s}{t}\right) i_{err}[n-1] \right]$$

Single multiplication


Buck IC Conceptual diagram

Core controller


- Single-multiplier PI comp.
- Shared hardware
- 6-bit window ADC
- 12-bit HR-DPWM

Periphery

- SPI
- Programmable deadtime

 


Control flow

 


$$v_c[n] = v_c[n-1] + a v_{err}[n] - b v_{err}[n-1]$$
 
$$a = k_p \quad , \quad b = k_p (1 - T_S / T_i)$$




Current (inner) loop

 
$$d[n] = d[n-1] + k \left[i_{err}[n] - \left(1 - \frac{T_s}{t}\right) i_{err}[n-1] \right]$$



Voltage (outer) loop
 
$$v_e[n] = v_e[n-1] + k \left[v_{err}[n] - \left(1 - \frac{T_s}{t}\right) v_{err}[n-1] \right]$$




 


Timing sequence – key waveforms

- Ring-osc. generates mid-range frequency (10-20 MHz)
- Time-interleaved ADC
- Time scheduling PI operation

 Each unit is designed as an asynchronous block





Delay-Line ADC

 



- Voltage-controlled delay
- Key factor – custom design of the delay cell
 - Not suitable for standard-cell synthesis
 - Difficult scalability
 - More complex layout


Constant-supply DL ADC

  - 2-phase conversion: ATC + TDC
- ATC outside the buffer string
 - Realized by OS-timer
 - Digital gates
 - RC creates the analog link
 - No S&H




Window DL ADC

  

 


HR-DPWM HS clock

 - High power consumption
- High accuracy – very high clk freq




HR-DPWM Delay-Line



- Area demanding

 

- Segmented DL

 


HR-DPWM Segmented DL

  

- Low power consumption
- High accuracy


Gate driver

 - Extended drain - similar to LDMOS structure
- Enabling the use of high drain-to-source voltages
- Compatible with ESD scenario




HS drive level shifter Capacitive method

 
- Capacitive coupling level shifter
 - Short delay
- For higher shifting ratios ($>2V_{DD}$) – ladder configuration is essential



Level Shifter – current biased

 


Bias circuitry

 


$$I_{Bias} = \frac{V_{ref}}{R_{ref}}$$

“Lean” Level shifter

Biasing circuitry (Analog) removed

 

Fabricated IC

 

IC Block / Digital Core	0.18 μ m CMOS
Supply Voltage	5V
DPWM resolution	12-bits
DPWM nominal frequency	1.25MHz
DPWM Si area	0.03 mm ²
ADC resolution	6-bit
ADC conversion time	20nSec
ADC Si area	0.022 mm ²
PI calculation time	< 40nSec
PI Si area	0.034 mm ²
Effective controller Si area	0.16 mm ²
including Ring-Oscillator, Dead-Time and SPI	



Experimental results




Specifications

Value

Package	5x5 QFN - MLP
V_{in}	12V
Power-stage R_{on}	$\sim 160\text{m}\Omega$
Nominal V_{out}	1.5V
Nominal I_{out}	1.5A
Off-chip LC filter	2.2 μH , 50 μF
Switching frequency f_{sw}	1.25MHz (620KHz)
Peak efficiency	70% (76%)
***package limited	
Total chip Si area	4.4mm ²

  


 

Loading Transient

Loading transient 1.5A ->2.5A



$V_{in}=12V$, $V_{out}=1.3V$

 


Unloading Transient

Unloading transient 2.5A ->1A

$V_{in}=12V$, $V_{out}=1.3V$,

  


 

Acknowledgements



 This research is supported by the IC division of Vishay Ltd. (Siliconix)



Fully Integrated Digital ACM VRM IC

THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

Thank You !