



Faster, Higher, Monolithic – Efficient Energy Conversion with GaN


Bernhard Wicht

Leibniz University Hannover, Germany

PwrSoC Corridor Webinar Series 2020
International Workshop on Power-Supply-on-Chip
November 11, 2020

Introduction

Motivation

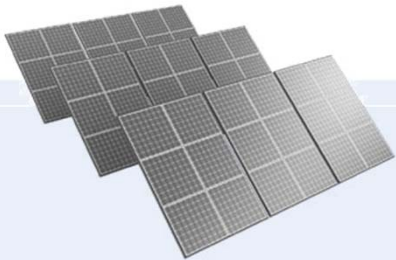

GRID



HOME APPLIANCES



INDUSTRIAL



ELECTRIC VEHICLES



DATA CENTERS



CONSUMER

Demands on Modules and Components


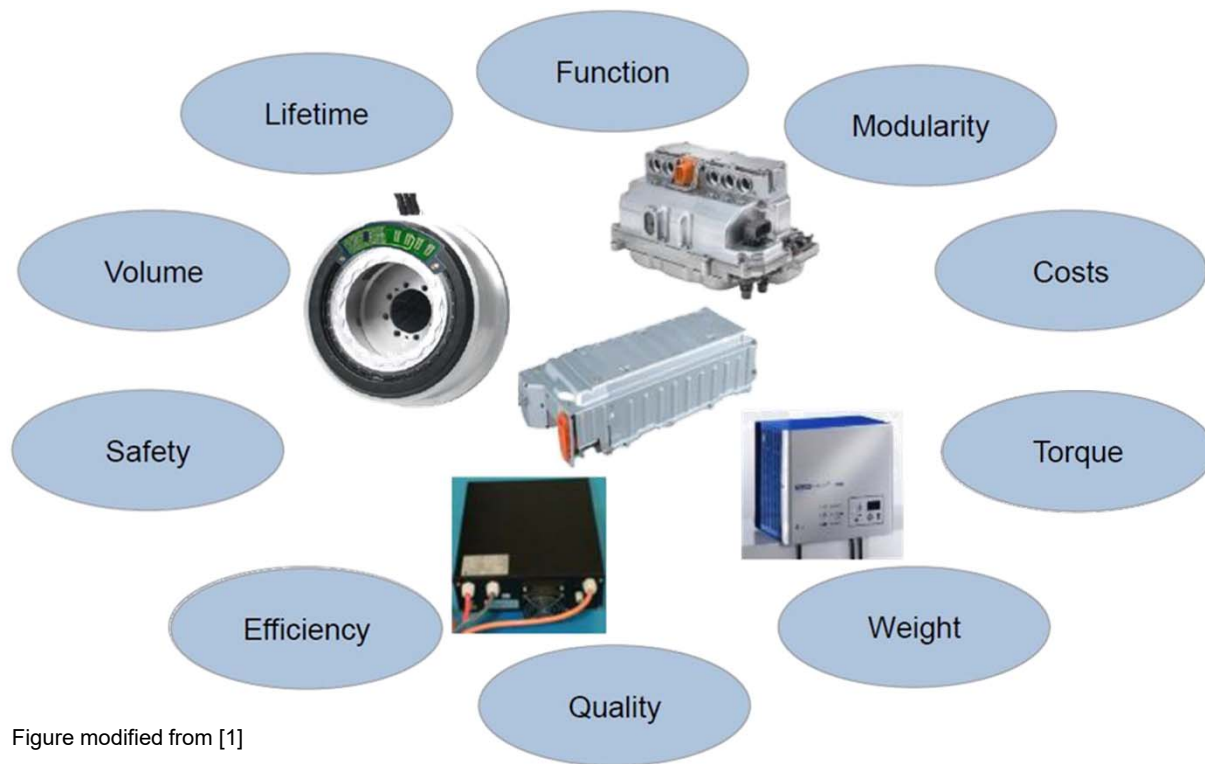


Figure modified from [1]

Success Factors

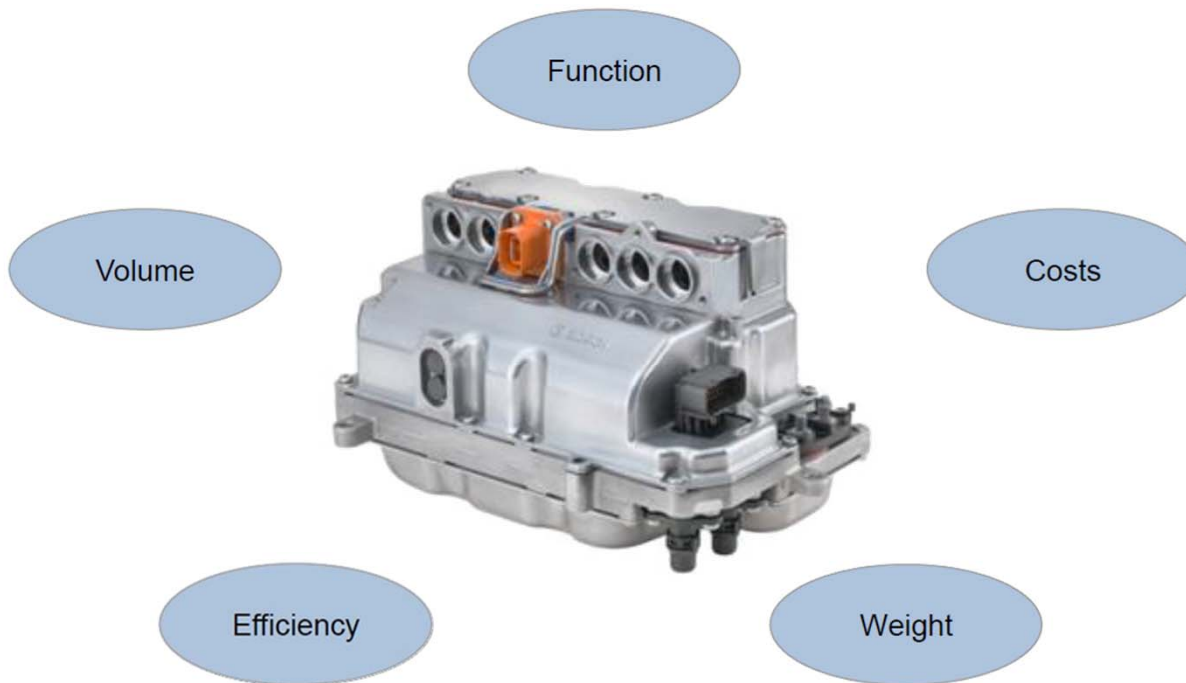→ Miniaturization, efficiency, reliability & controllability, cost



Success Factors

→ Miniaturization, efficiency, reliability & controllability, cost


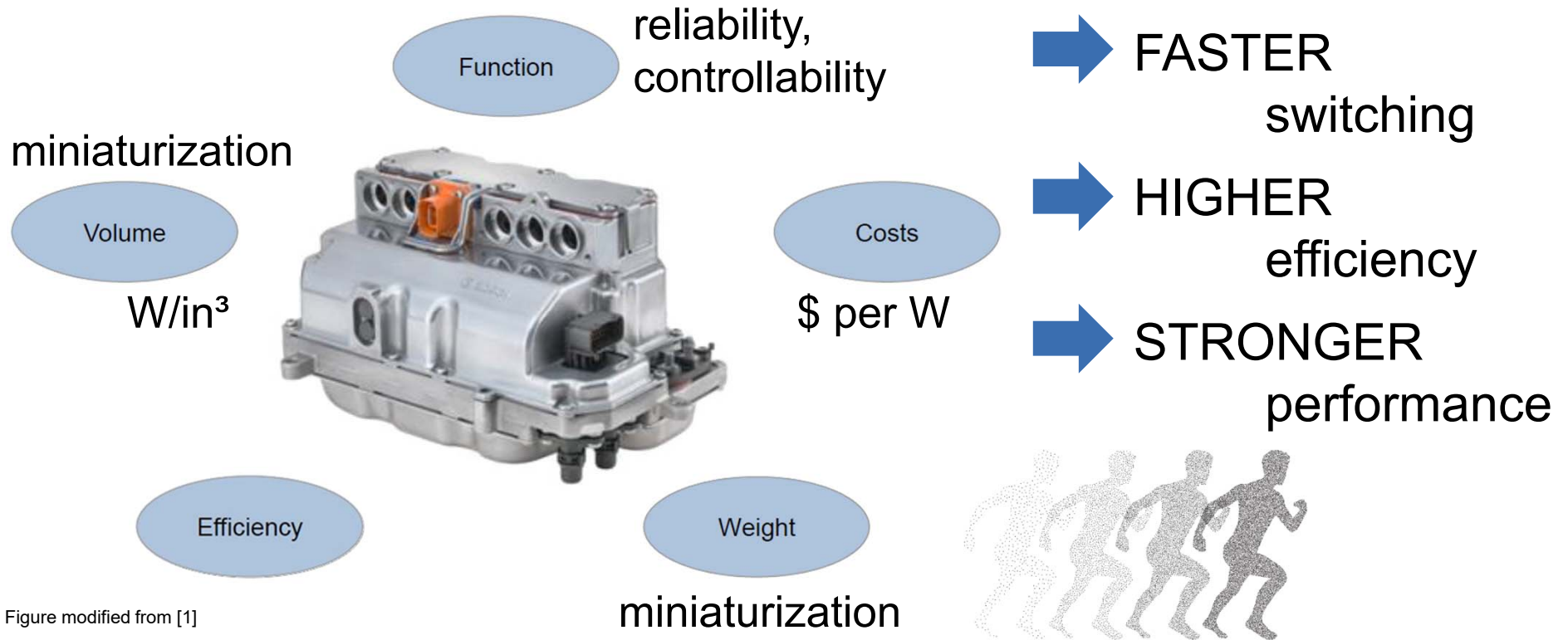



Figure modified from [1]

The E-Mode GaN Device

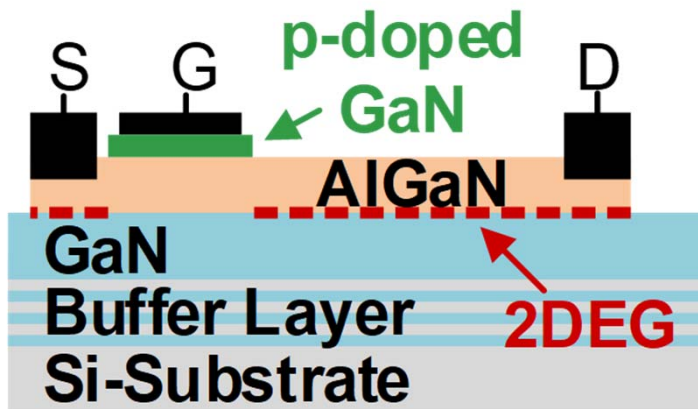

- Utilizes high electron mobility of GaN: Small chip area → lower parasitic capacitance → high speed, efficiency, miniaturization, lower system cost
- No junction → no body diode, zero reverse recovery charge Q_{RR}
- Lateral device: Simpler monolithic integration and packaging → GaN ICs

GaN for Power Electronics

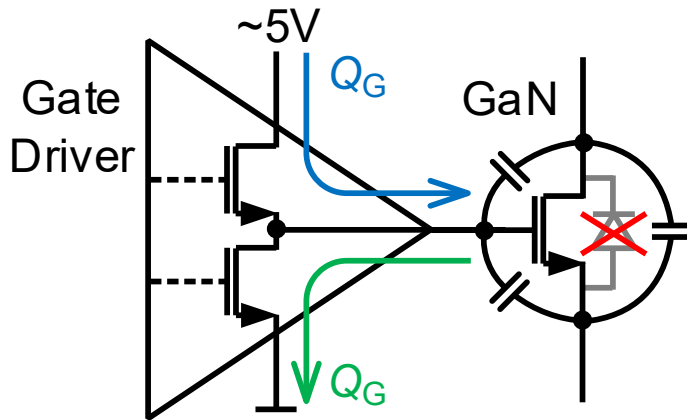

	Si CoolMOS C7 * (650V / 52mΩ / 33A)	GaN Transistor ** (650V / 55mΩ / 30A)
V_{GS}	15V	~5V
V_{th}	3.5V	1.6V
Q_G	64nC	5.8nC
Q_{RR}	10μF	0


>10x

Key parameters of GaN transistors:

- ~5V gate drive, low threshold voltage V_{th}
- >10x lower gate charge Q_G , zero reverse recovery charge Q_{RR}

*IPP65R065C7, **GS66508T

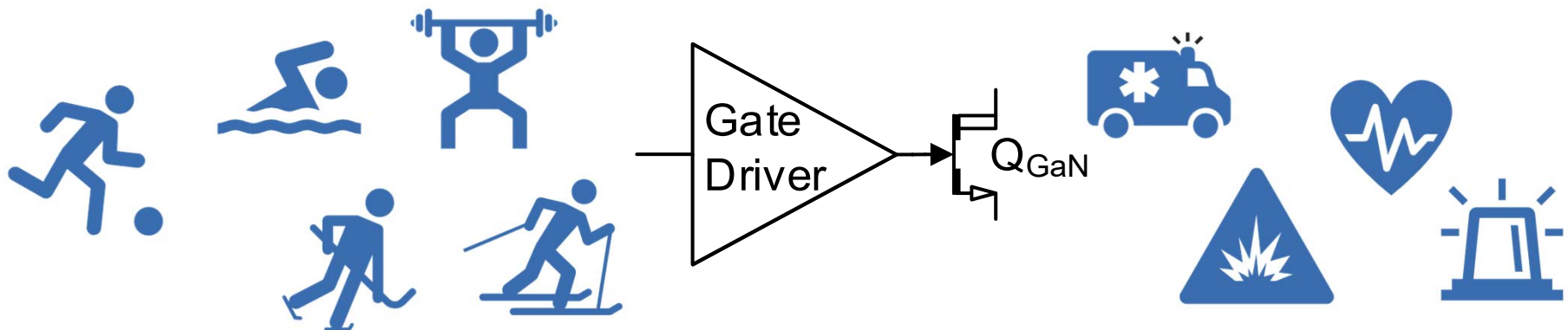GaN Driver Requirements: Faster, Higher, Stronger



FASTER switching:
Miniaturization



HIGHER efficiency:
Low switching losses,
high dV_{DS}/dt

STRONGER performance:
Reliability and save operation

- Save on- and off-state
- Low V_{GS} overshoot


Gate Driver – Turn-on Behavior

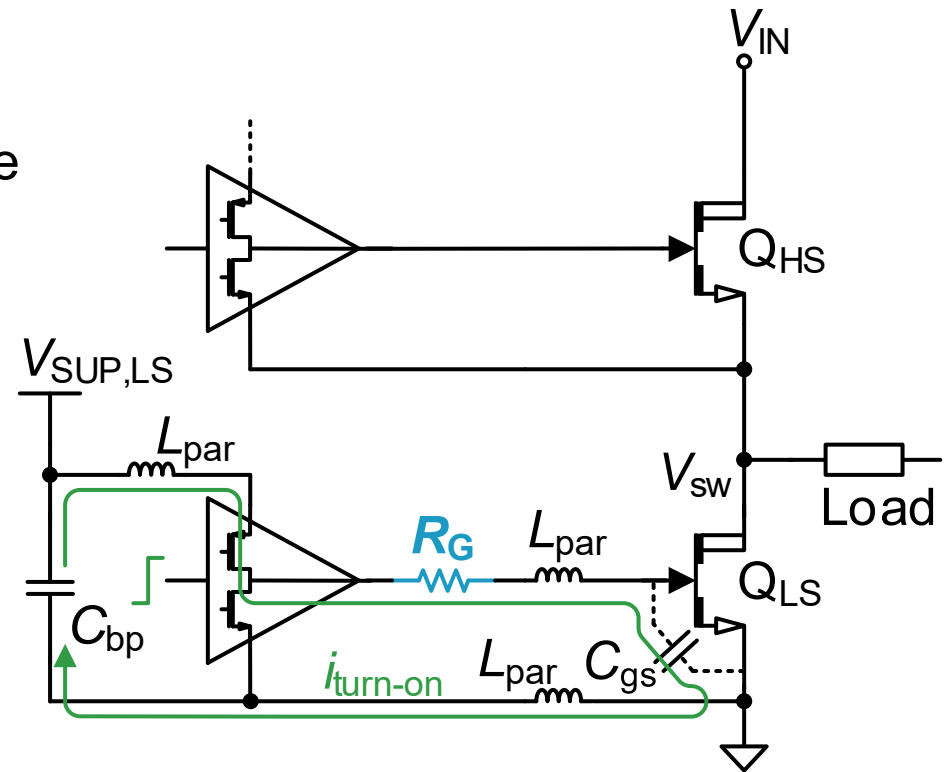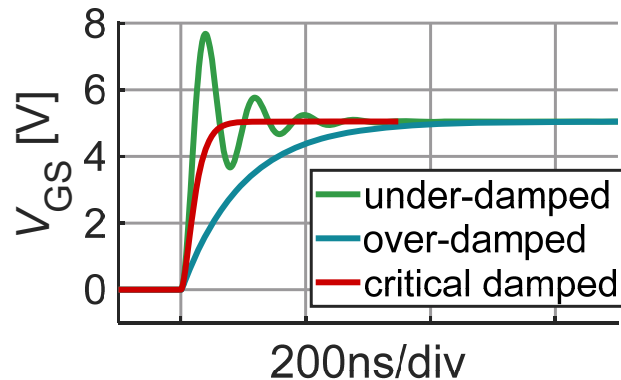- L_{par} , C_{bp} and C_{gs} form a resonant tank
→ V_{GS} overvoltage and ringing
- Gate resistor to prevent gate overvoltage
→ slows down the driver




Gate Driver – Save Off-State

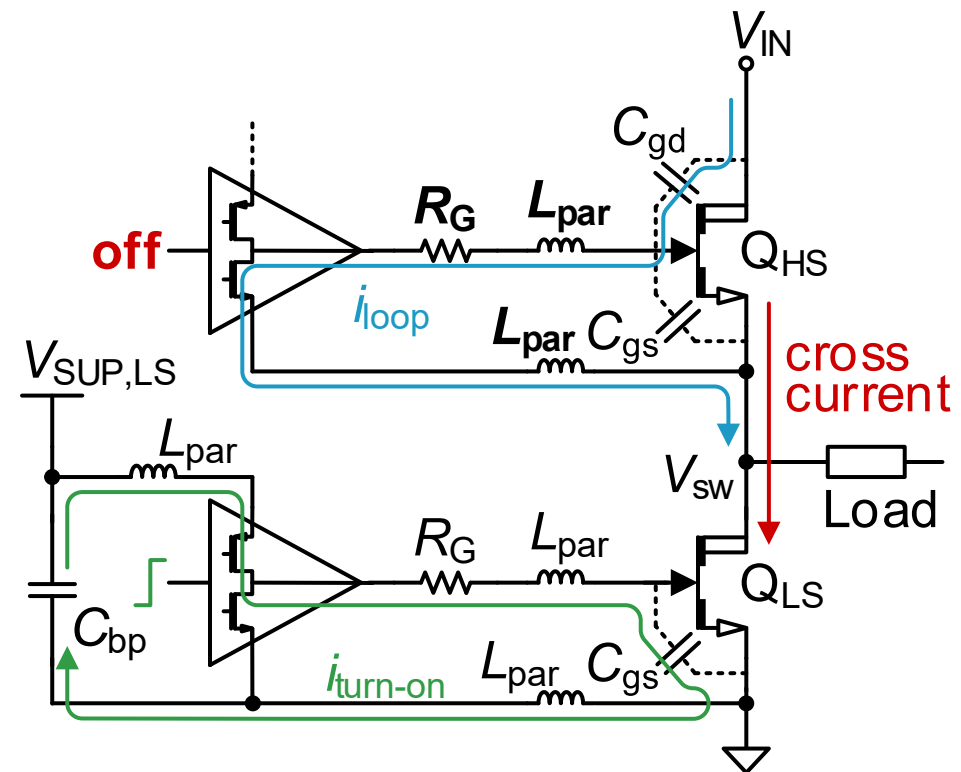- $dV_{DS}/dt \gg 100V/ns$ (GaN)
→ large current i_{loop} through C_{gd}
- R_G and L_{par} → risk for Q_{HS} to turn on
→ cross current
- Addressed by:
 - Bipolar gate drive ($V_{GS} < 0V$)
 - Larger C_{gs}
 - reduced efficiency and speed



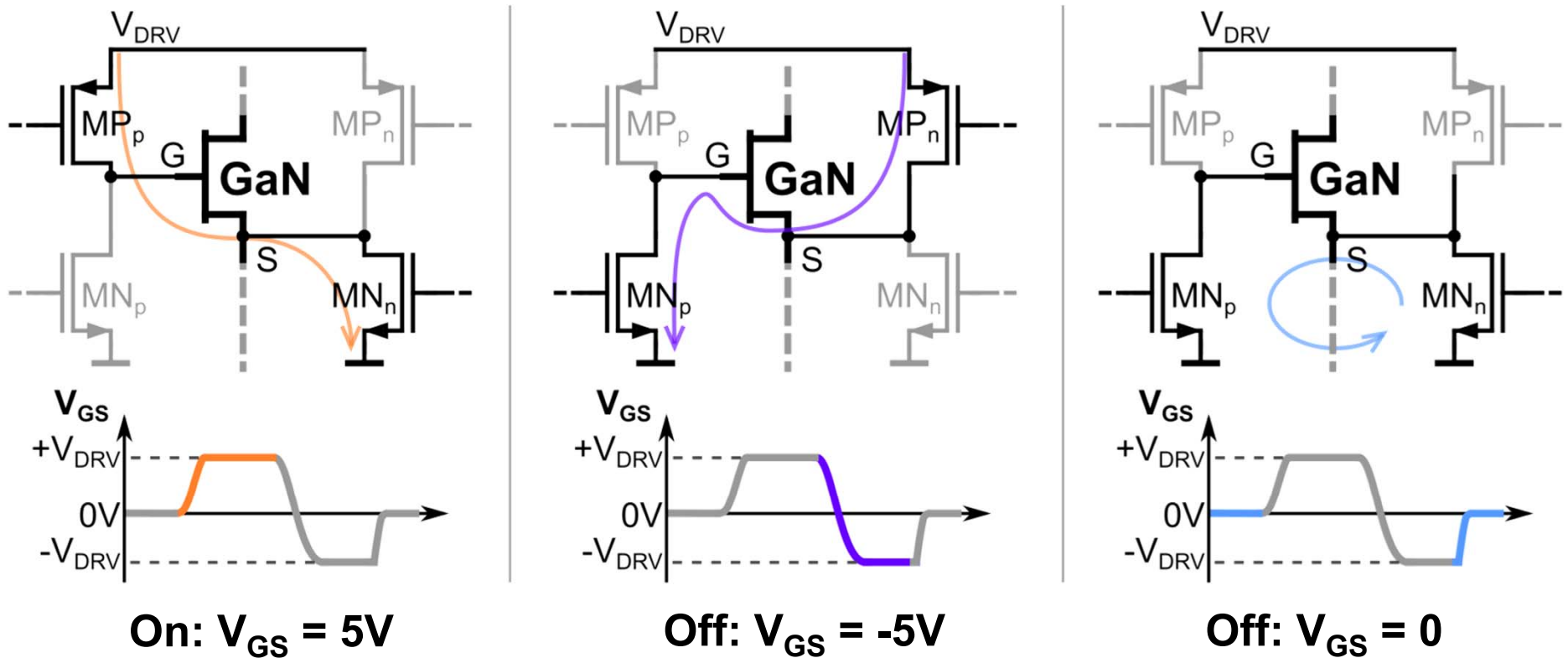Full-Bridge Gate Driver for Bipolar and Three-level Driving




IC level integration: 5V devices result in a compact (layout) and fast driver

High-Voltage Energy Storing (HVES)

Gate Drivers for GaN

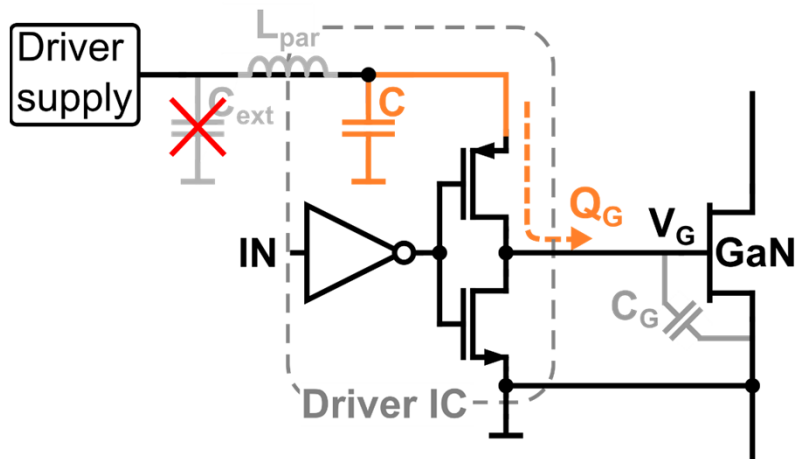Integration of the buffer capacitor \rightarrow fewer interconnections, smaller parasitics, smaller footprint, fast switching



$$Q_G = \Delta V_C \cdot C$$


Example:

$$Q_G = 10\text{nC}, \Delta V_C = 0.1\text{V} \rightarrow C \geq 100\text{nF}$$


\rightarrow How to integrate a capacitor of this size?

Gate Drivers for GaN: High Voltage Energy Storing (HVES)

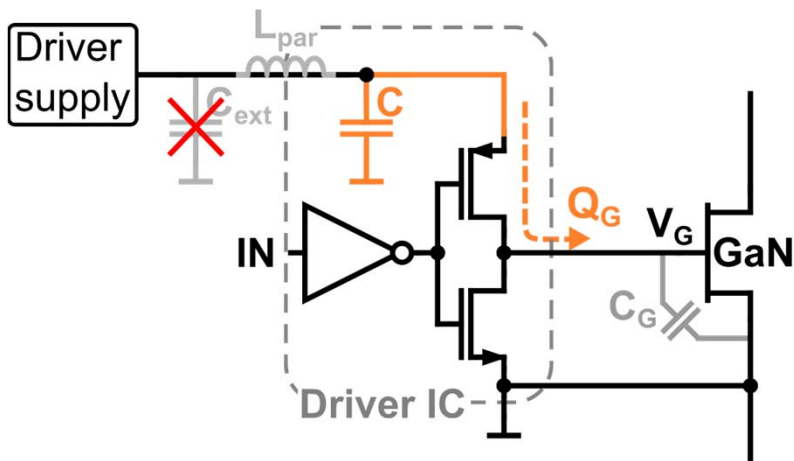Integration of the buffer capacitor → fewer interconnections, smaller parasitics, smaller footprint, fast switching



High-Voltage
Energy Storing
(HVES)

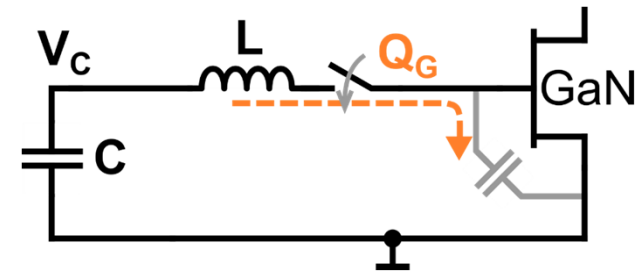

$$Q_G = \Delta V_c \cdot C$$

Seidel et al.,
ISSCC 2017, 2018 [2], [3]

HVES reduces cap size to reasonable values for on-chip integration:




>10x higher gate charge without any external components

Gate Driver with High Voltage Energy Storing (HVES)

- $V_{HV} = 15V$, $C_{HV} = 0.6nF$,
 $L_{int} = 14nH$
 → 11nC gate charge
 → fully integrated on IC
- C_{HV} dominates
 → faster turn-on:

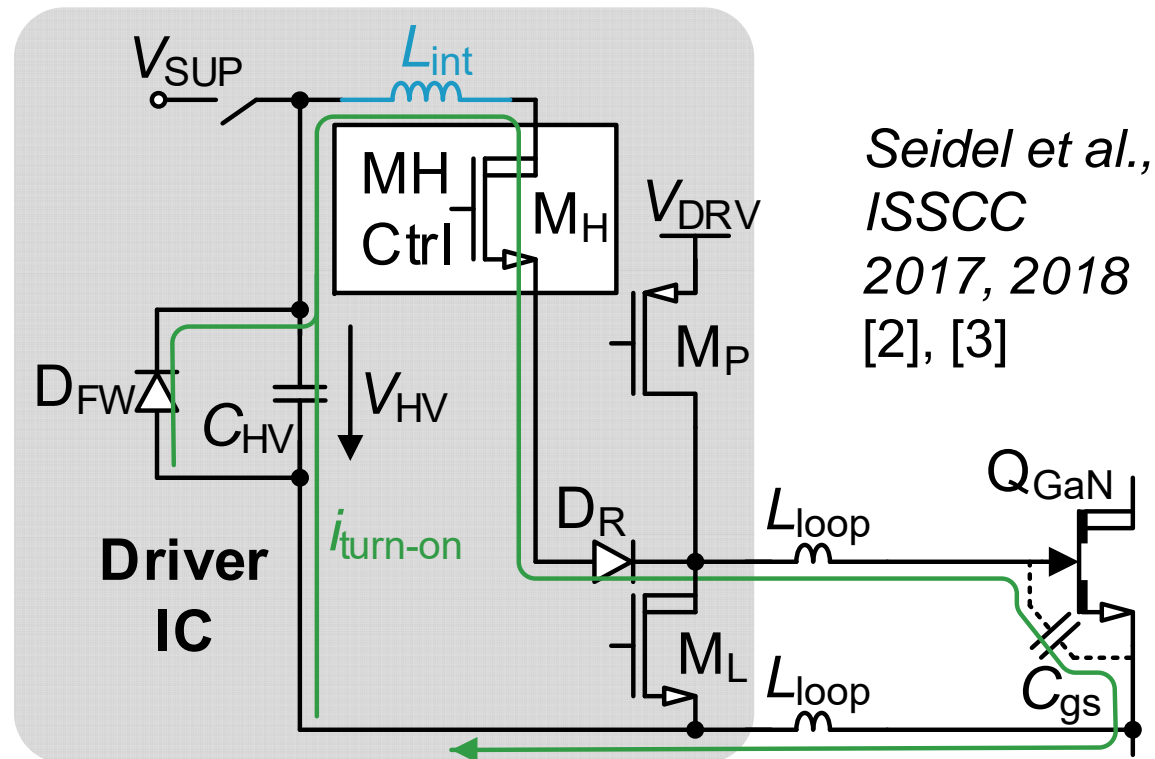
$$f_{res} \approx \frac{1}{2\pi \sqrt{L_{par} \cdot C_{HV}}}$$



*Seidel et al.,
ISSCC
2017, 2018
[2], [3]*


D_R : Block reverse current
 D_{FW} : Freewheeling

Gate Driver with HVES – Toplevel

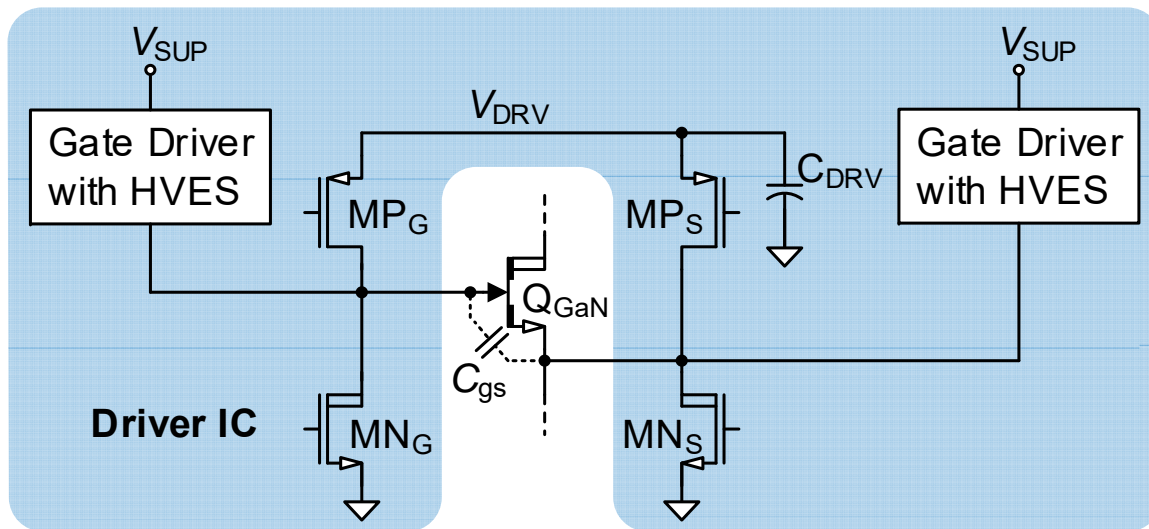

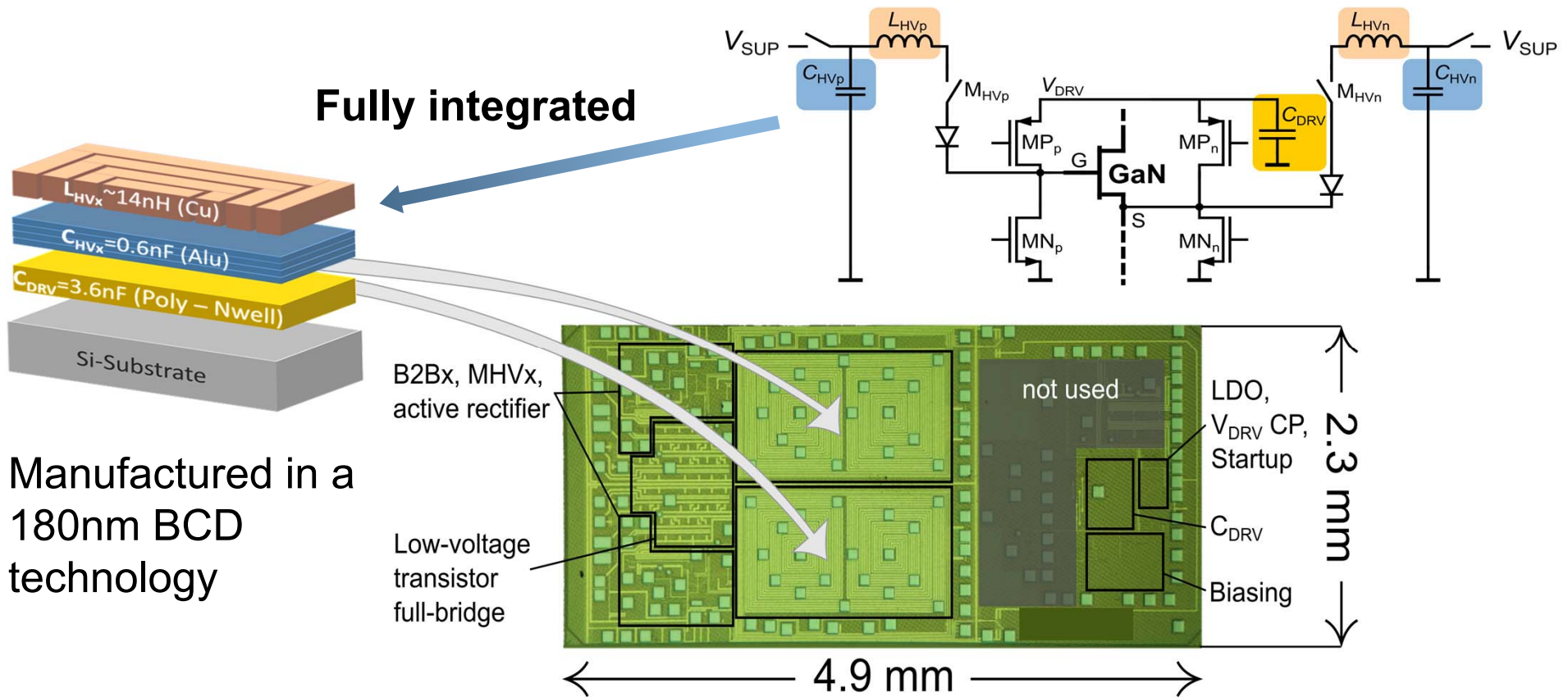
- Full-Bridge for bipolar and three-level driving and stable DC level
- HVES at gate and source for fast on / off transitions








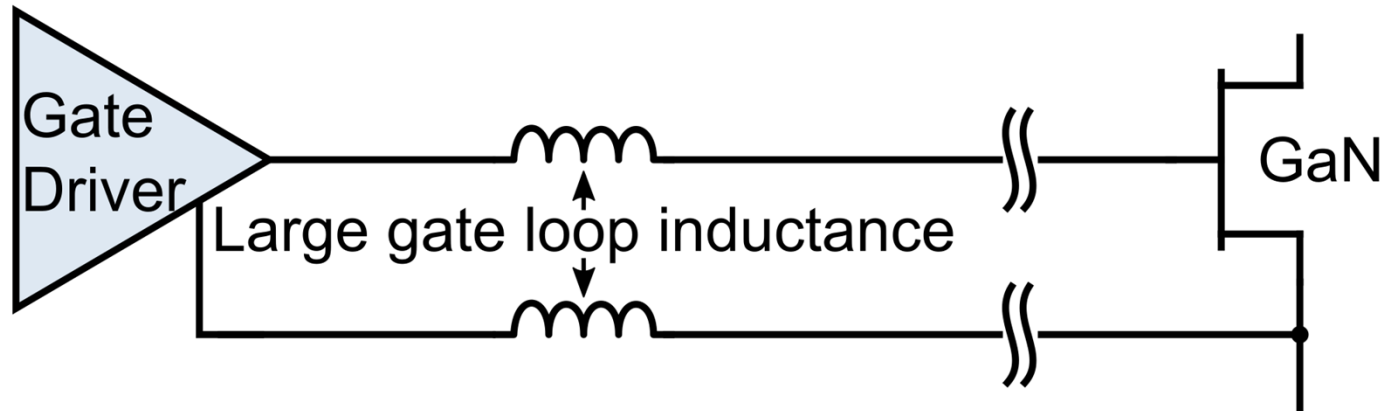
Gate Driver IC with High Voltage Energy Storing (HVES)



Large Gate Loops

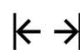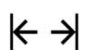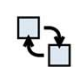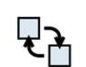
Flexible Driver Placement: Large Gate Loop





- | | | |
|--|--|--|
|  Lower temperature | |  High temperature |
|  Multi-layer PCB | |  High-current substrate |
|  Space restrictions | |  Optimized transistor and heat sink placement |
|  Modularity | |  Modularity |

Flexible Driver Placement: HVES Applied to Large Gate Loop

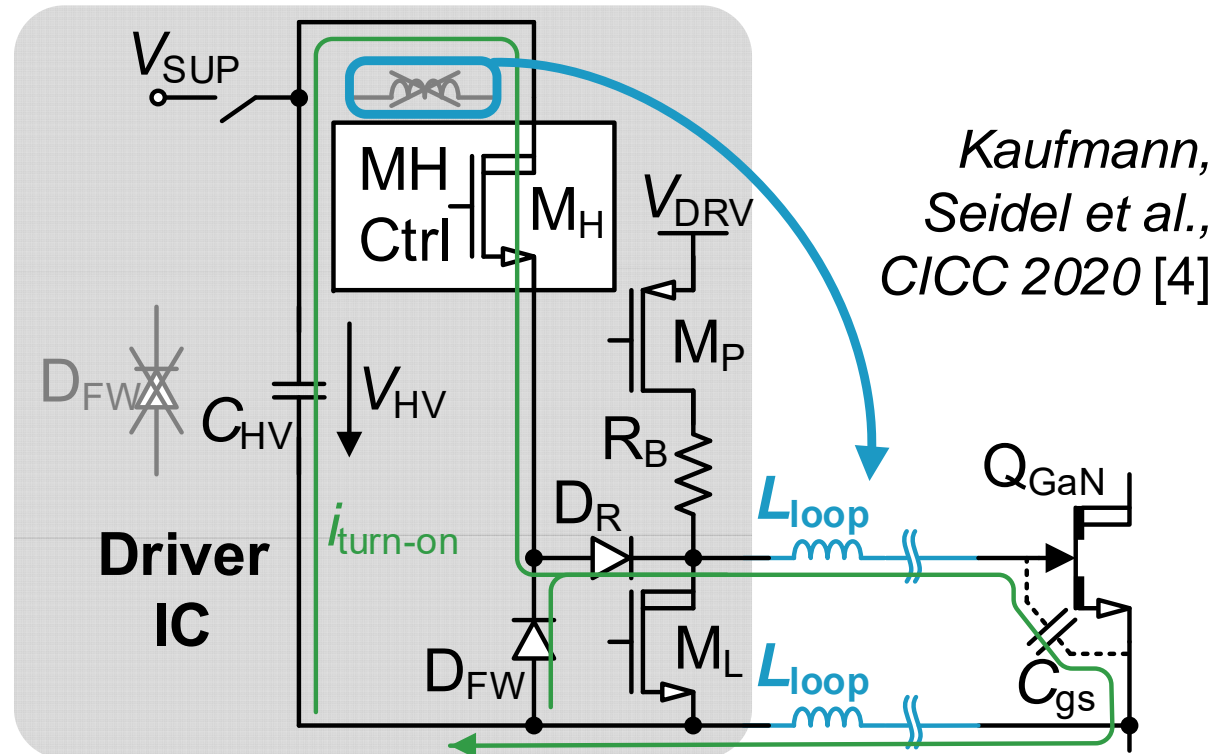- Loop inductance utilized for resonant gate driving
- Fully integrated solution with small C_{HV} in turn-on loop



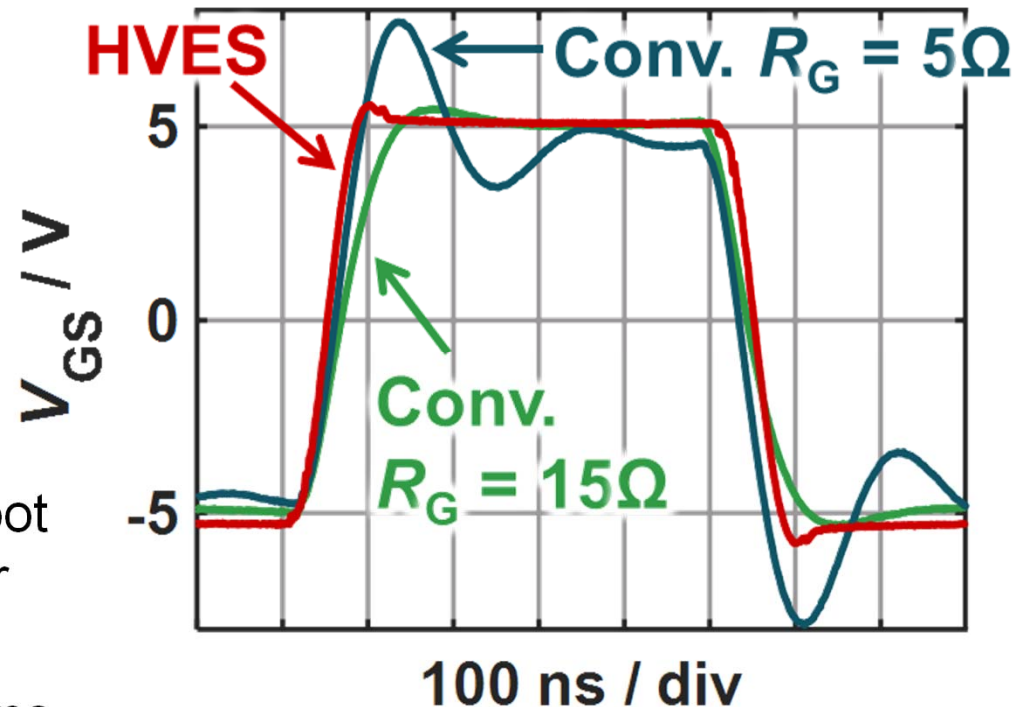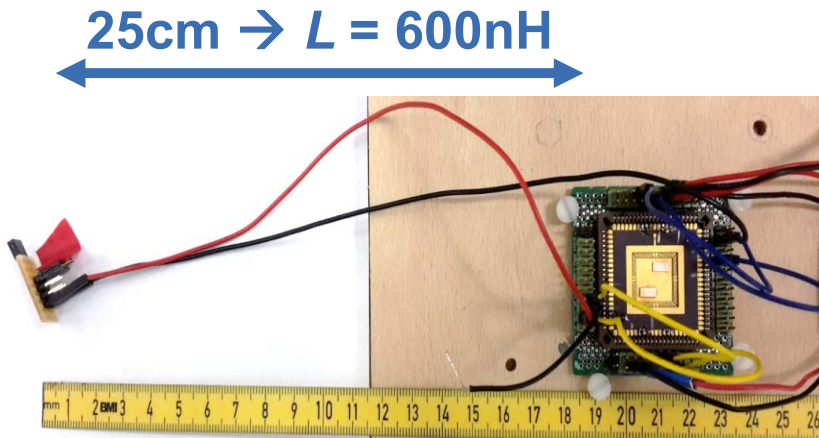
Gate Driver with HVES – Experimental Results



- HVES achieves 80% lower overshoot than conventional driver with similar rise time
- HVES achieves 45% shorter rise time than conventional driver with similar overshoot

*Kaufmann et al.,
CICC 2020 [4]*

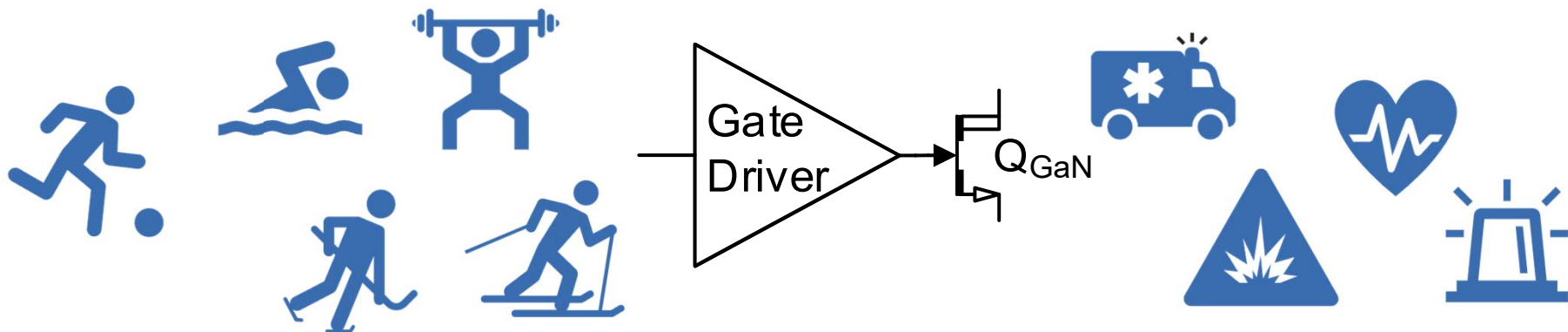Gate Driver with HVES: Faster, Higher, Stronger



Miniaturization:

- Integrated buffer caps
- Use of parasitic Loop

Low switching losses, high $dVDS/dt$:

- Fast switching due to small integrated high-voltage cap

Reliability and save operation:

- Bipolar / 3-Level gate drive for increased margin
- Low VGS overshoot with resonant driving

Monolithic GaN Integration

Monolithic GaN-ICs – Foundries / IDMs



intel®


EPISIL




Monolithic GaN-ICs – Foundries / IDMs and GaN Industry



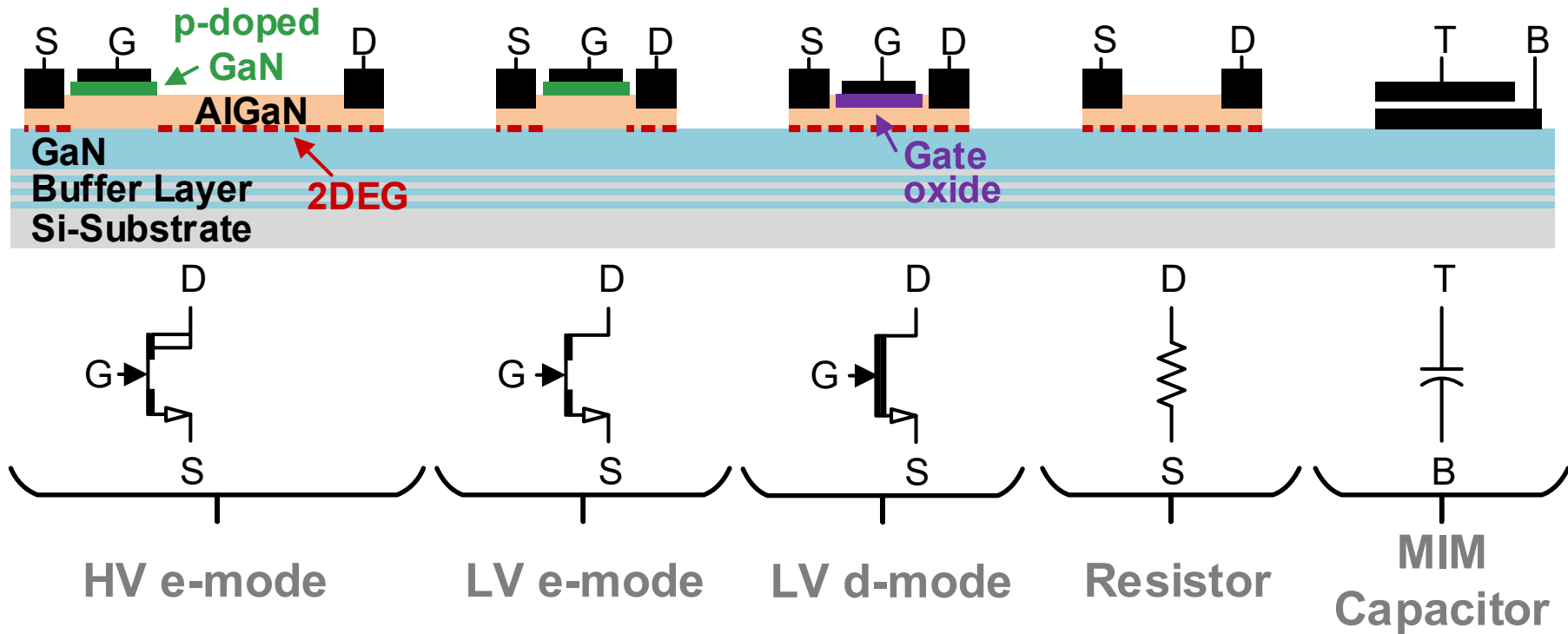Monolithic GaN Integration: Available Devices



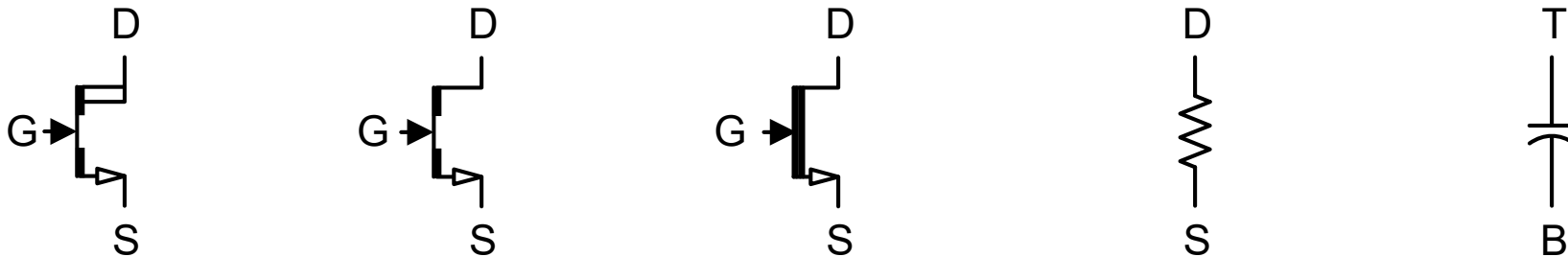Monolithic GaN Integration: Opportunities and Challenges




- Monolithic integration: Gate loop inductance $\rightarrow 0$
- Tracks PVT variations of the driving voltage for the integrated GaN power device

-
- Limited device types and options, no p-type
 - No diodes, neither designed nor parasitic
 - Immature technology with poor matching properties

To be addressed on system and circuit level \rightarrow *learning from the 1970ies*

Monolithic GaN Integration: System Partitioning


Gate driver and power transistor in GaN:

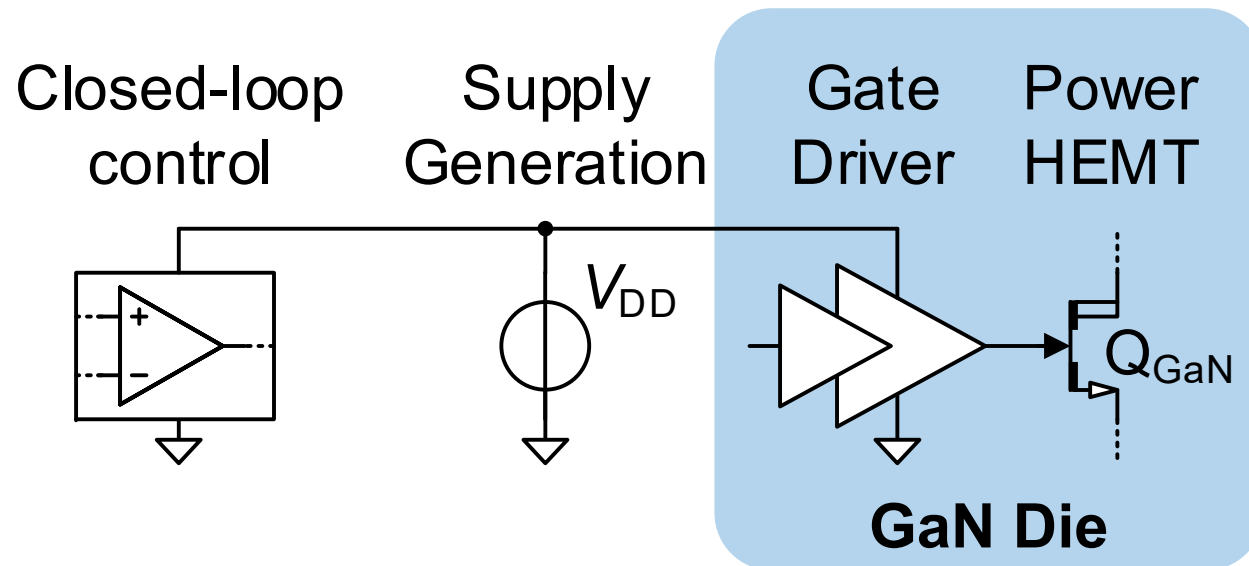

*Xue et al. (Navitas),
APEC2017 [5]*


Monolithic GaN Integration: System Partitioning

Full system in GaN:

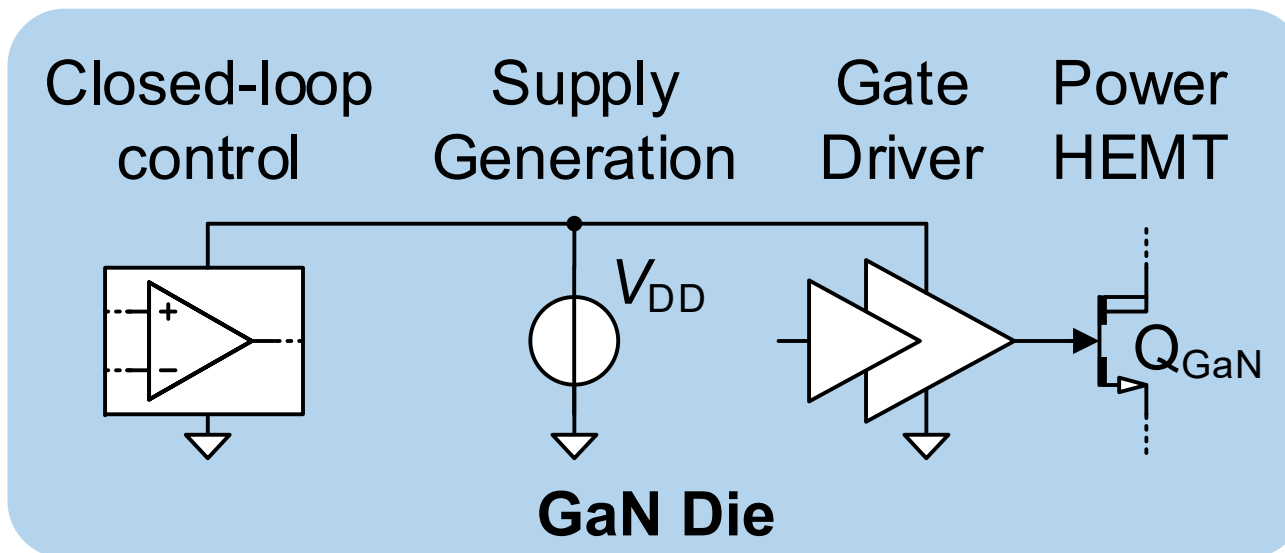


*Kaufmann et al.,
ISSCC 2020 [6], [7]*

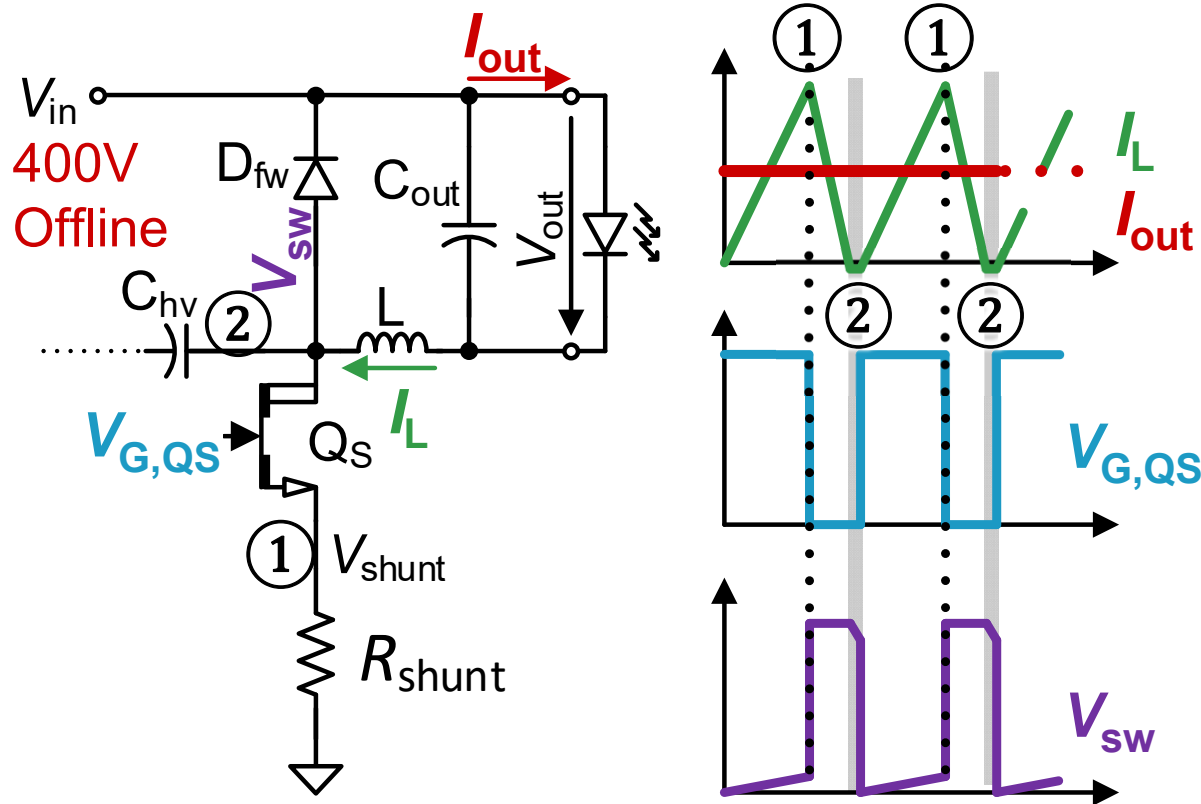Monolithic GaN Integration: 400V Offline Buck Converter




- Constant current output for LED load
- Hysteretic control:
 - ① Cycle-by-cycle peak current control
 - ② Boundary conduction mode
- Asynchronous rectifier

Monolithic GaN Offline Buck Converter

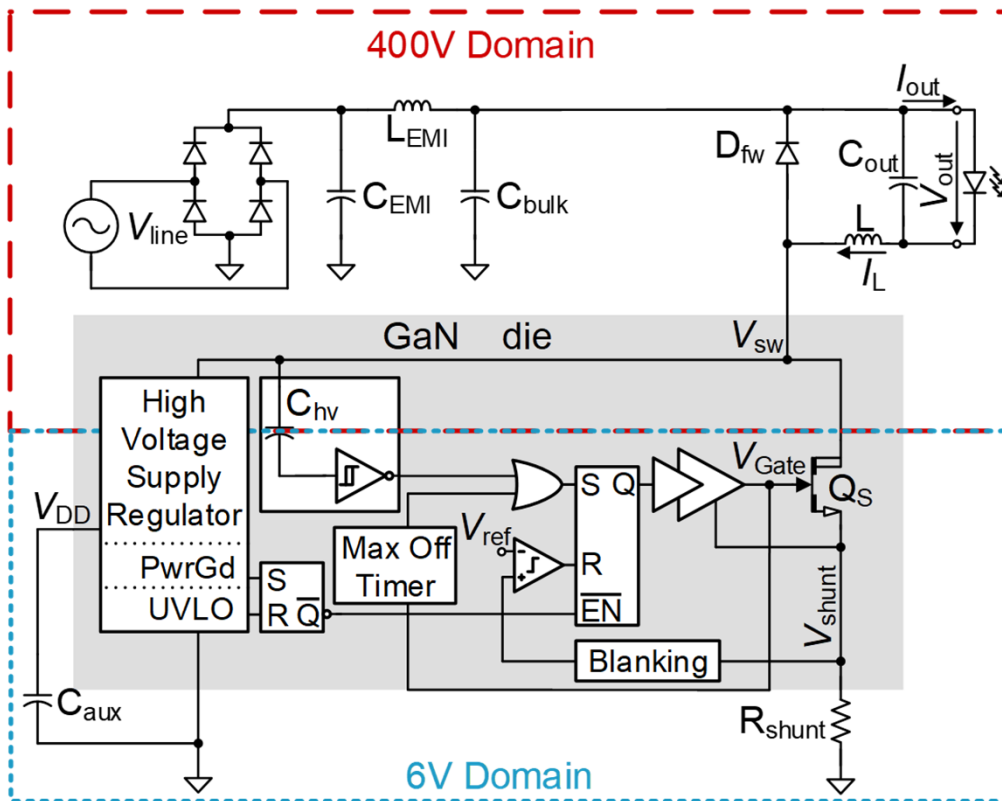


Monolithic GaN Offline Buck Converter

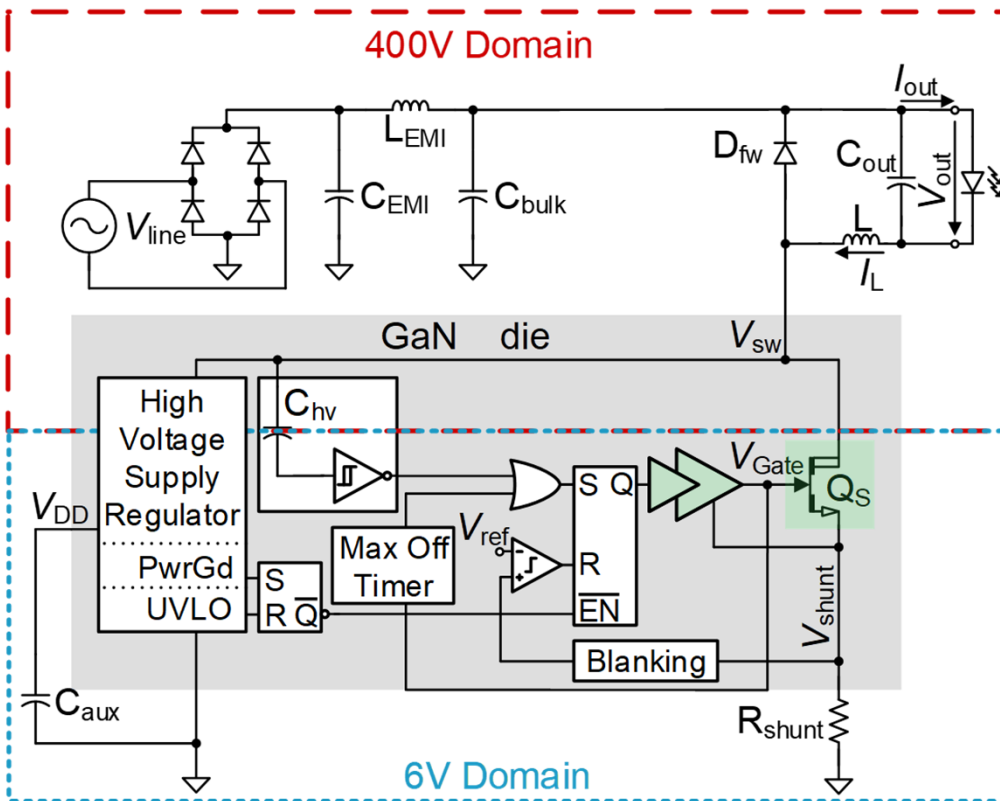


- Gate driver and high voltage power HEMT

Monolithic GaN Offline Buck Converter

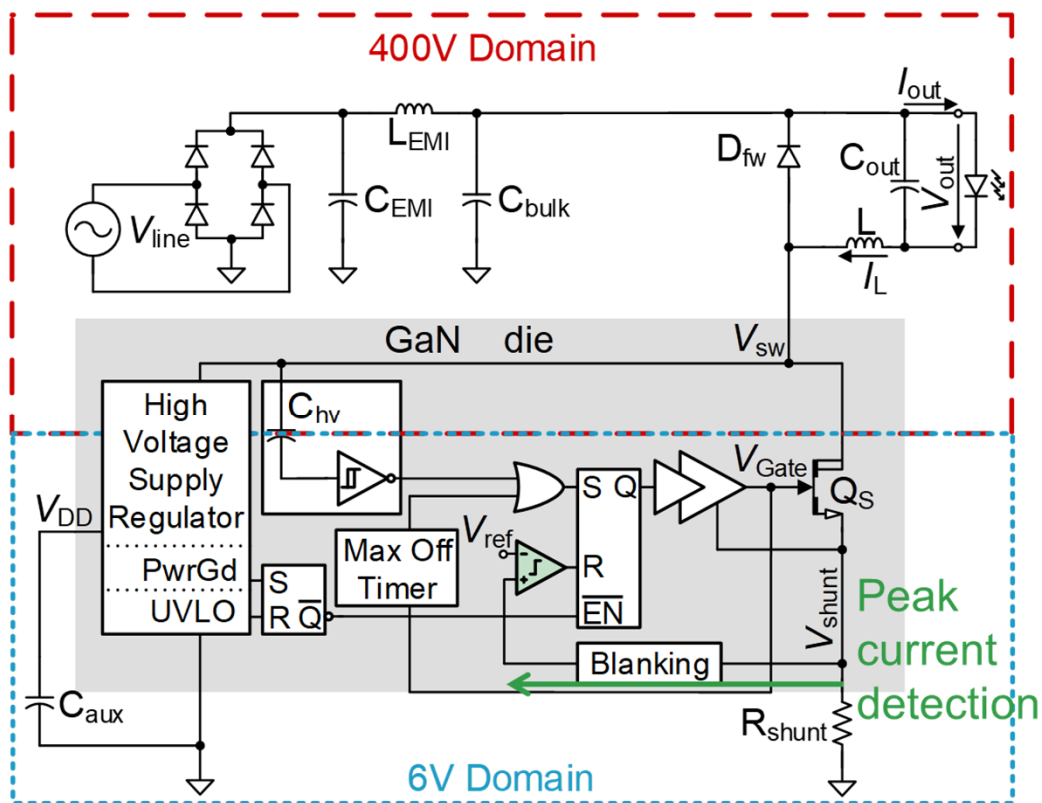


- Gate driver and high voltage power HEMT
- **Peak current comparator with autozeroing**

Monolithic GaN Offline Buck Converter

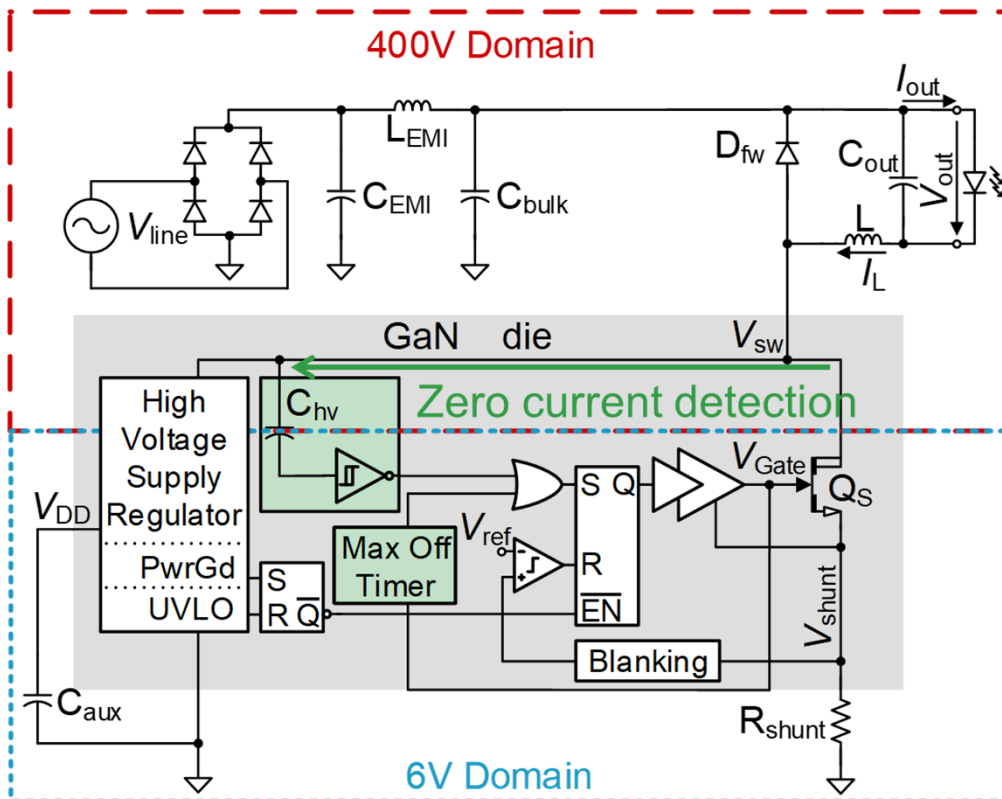


- Gate driver and high voltage power HEMT
- Peak current comparator with autozeroing
- **Zero current detection for boundary conduction mode**
- **Max off timer for startup**

Monolithic GaN Offline Buck Converter

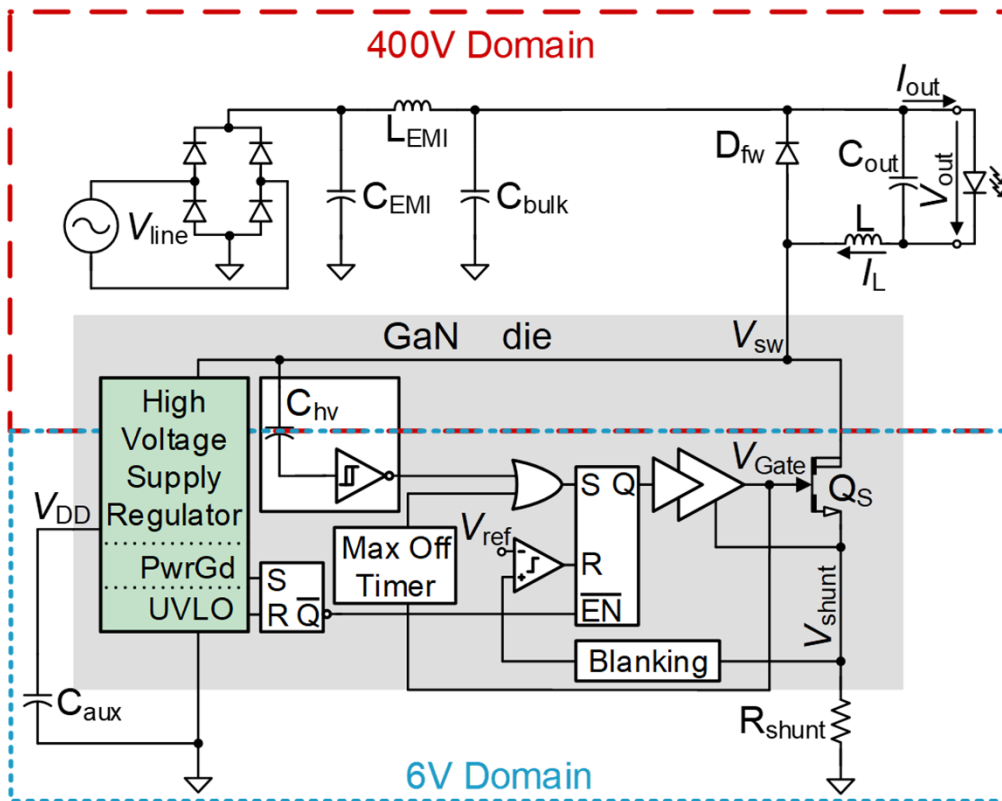


- Gate driver and high voltage power HEMT
- Peak current comparator with autozeroing
- Zero current detection for boundary conduction mode
- Max off timer for startup
- **HV supply regulator for self-biased offline operation**

Monolithic GaN Offline Buck Converter

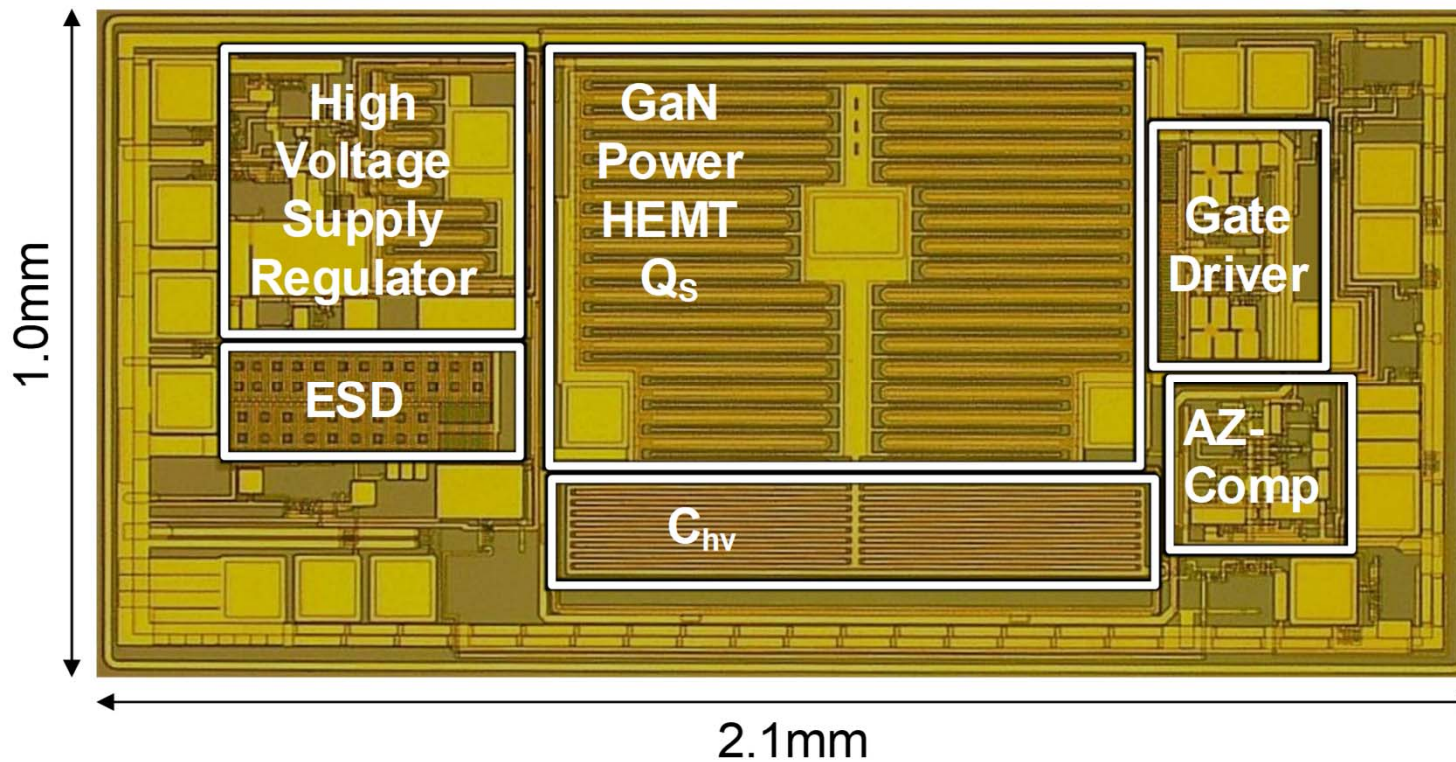

**650V
GaN-on-Si**

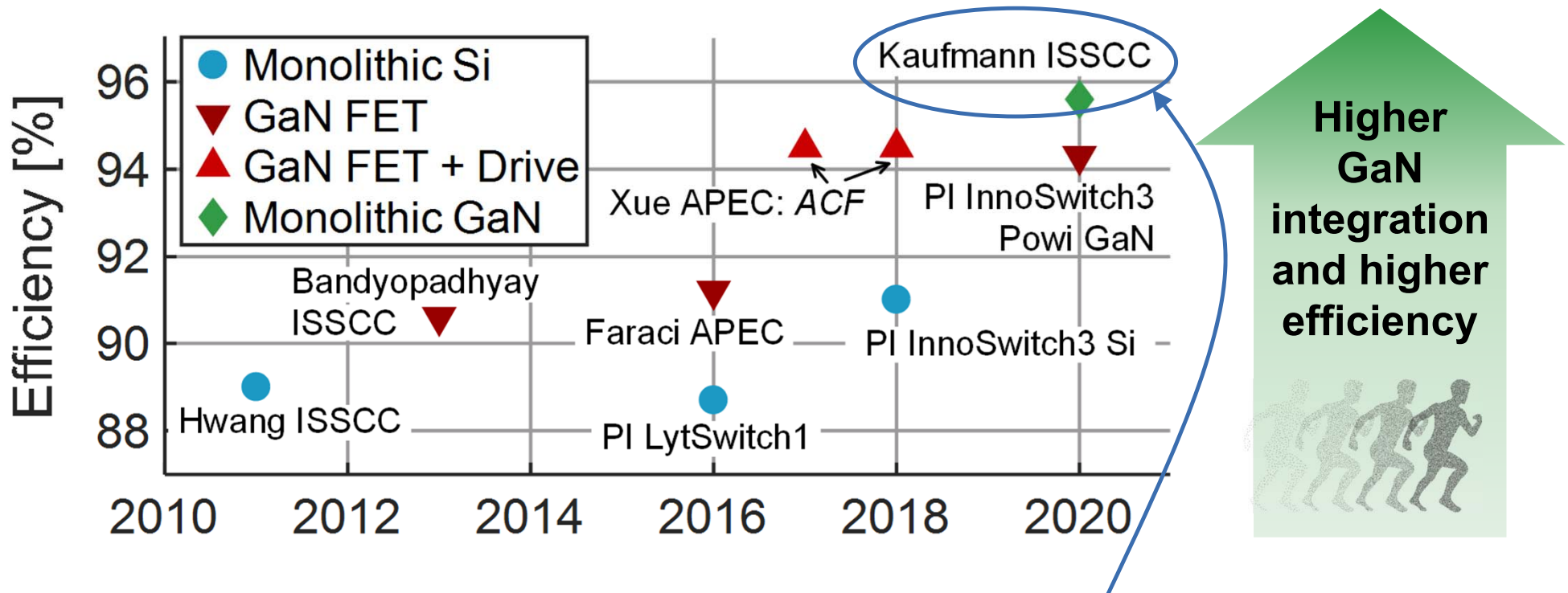10-50W Offline Converter Integration Trends



- 95.6% peak efficiency → highest achieved with fully integrated power stage
- Low component count and small passives → 44W/in³ power density

Conclusion

- GaN enables highly efficient and compact power conversion **BUT** gate driving is more challenging
- High-voltage energy storing (HVES) gate driver actively uses gate loop inductance for quick and robust resonant switching
- Monolithic integration with GaN eliminates gate loop parasitics and tracks PVT of the driving voltage for the GaN HV-HEMT

The presented GaN gate drivers and circuits show high levels of integration for compact and efficient high-voltage power supplies



References

- [1] Plikat, T. Leifert (VW), "Challenges for Power Devices in Electrified Drivetrains," ECPE Workshop Power Electronics for e-Mobility 2016
- [2] A. Seidel and B. Wicht, "25.3 A 1.3A gate driver for GaN with fully integrated gate charge buffer capacitor delivering 11nC enabled by high-voltage energy storing," ISSCC 2017
- [3] A. Seidel and B. Wicht, "A fully integrated three-level 11.6nC gate driver supporting GaN gate injection transistors," ISSCC 2018
- [4] M. Kaufmann, A. Seidel and B. Wicht, "Long, Short, Monolithic - The Gate Loop Challenge for GaN Drivers: Invited Paper," CICC 2020
- [5] L. Xue and J. Zhang, "Active clamp flyback using GaN power IC for power adapter applications," APEC 2017
- [6] M. Kaufmann, M. Lueders, C. Kaya and B. Wicht, "18.2 A Monolithic E-Mode GaN 15W 400V Offline Self-Supplied Hysteretic Buck Converter with 95.6% Efficiency," ISSCC 2020
- [7] M. Kaufmann and B. Wicht, "A Monolithic GaN-IC With Integrated Control Loop for 400-V Offline Buck Operation Achieving 95.6% Peak Efficiency," JSSC 2020 (early access)
- [8] J. T. Hwang, et al., "A simple LED lamp driver IC with intelligent power-factor correction," ISSCC 2011
- [9] "Single-Stage LED Driver IC with Combined PFC and Constant Current Output for Buck Topology," LysSwitch1 Family Datasheet, Power Integrations, Jul. 2016
- [10] "Reference Design Report for a 40 W Power Supply Using InnoSwitch 3-Pro INN3377C-H301 and Microchip's PIC16F18325 Microcontroller," Power Integrations, Aug. 2018
- [11] S. Bandyopadhyay, et al., "90.6% efficient 11MHz 22W LED driver using GaN FETs and burstmode controller with 0.96 power factor," ISSCC 2013
- [12] E. Faraci, et al., "High efficiency and power density GaN-based LED driver," APEC 2016
- [13] "DER-917, 60 W Power Supply Using InnoSwitch™3-CP PowiGaN™ INN3270C-H203," Power Integrations, Sep. 2020
- [14] L. Xue and J. Zhang, "Design considerations of highly-efficient active clamp flyback converter using GaN power ICs," APEC 2018