




Hybrid Converters for Mobile and IoT Applications

Patrick Mercier
University of California, San Diego



Power Management Research Focus Areas

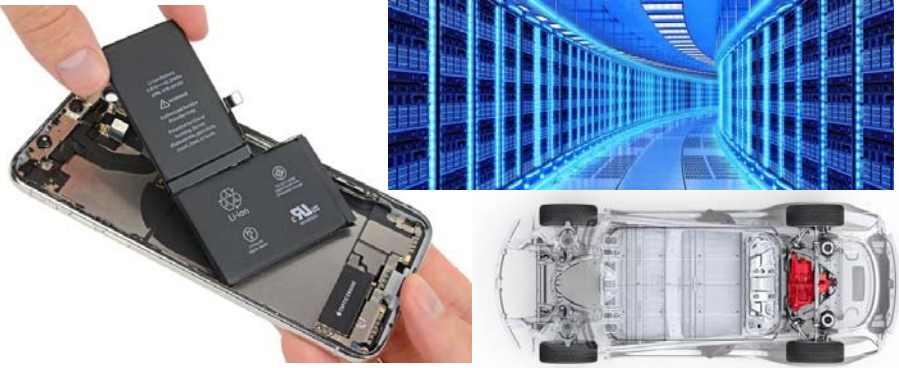
High Power Density Hybrid Converters:
Mobile phones, data centers, automotive



RF Power Amplifiers
5G, Wi-Fi 6, Long Range IoT



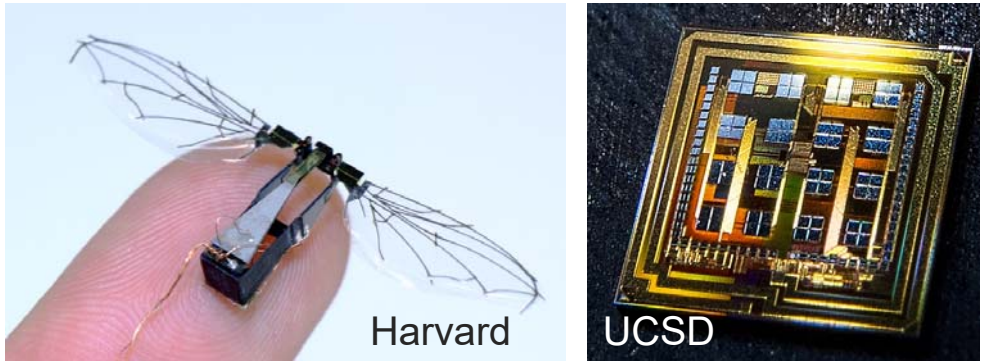Integrated High-Voltage Conversion
Microrobotics, Neural Implants



Harvard

UCSD


Wide Dynamic Current Range Converters
IoT, Wearables





Power Management Research Focus Areas

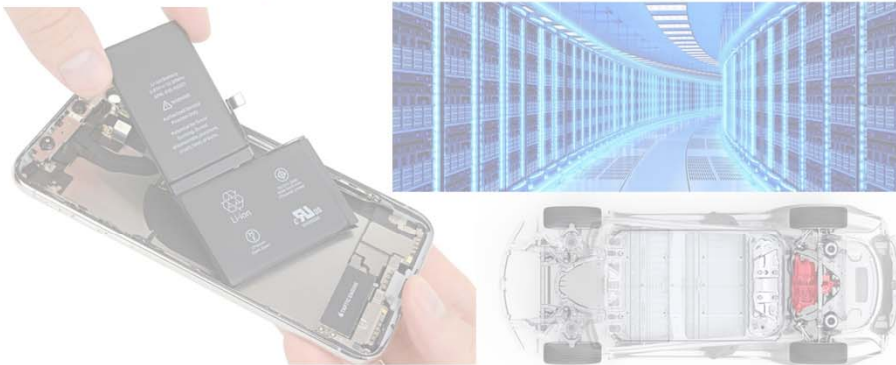
High Power Density Hybrid Converters:
Mobile phones, data centers, automotive



RF Power Amplifiers
5G, Wi-Fi 6, Long Range IoT



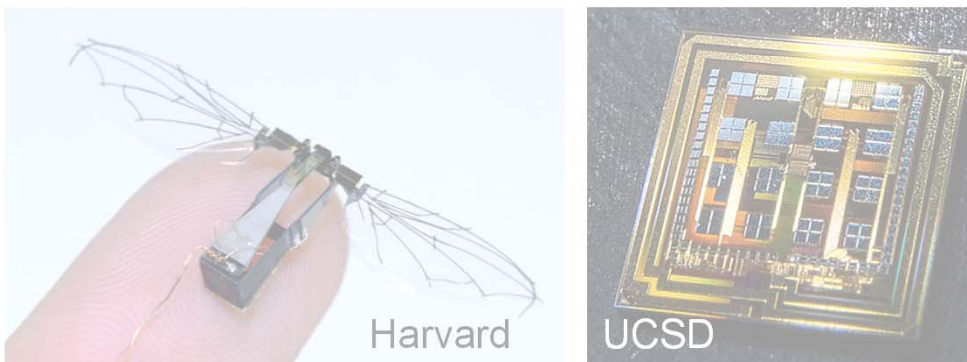Integrated High-Voltage Conversion
Microrobotics, Neural Implants



Wide Dynamic Current Range Converters
IoT, Wearables







Major limiter in IoT devices: battery size / battery life




Battery

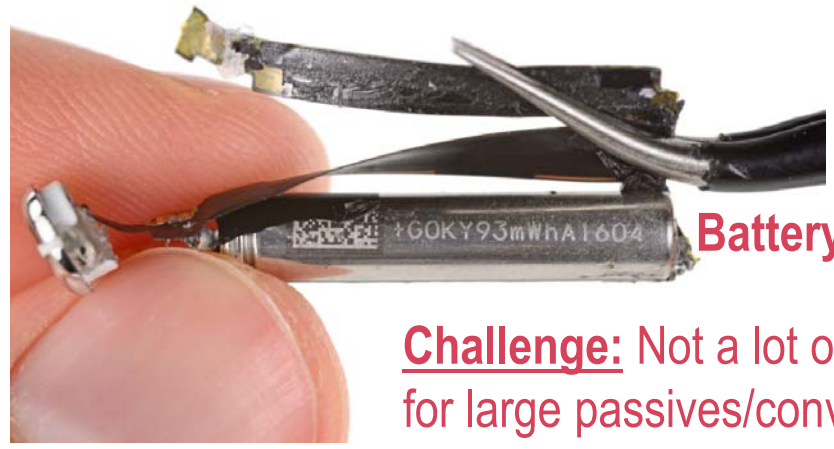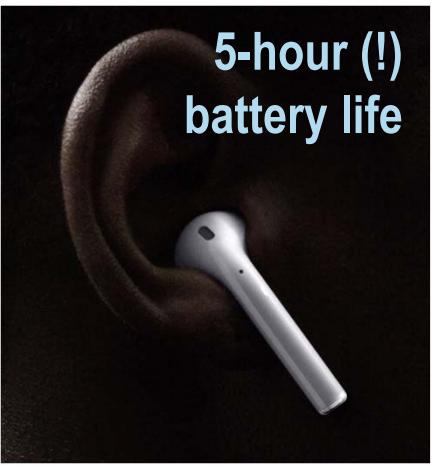

Battery

Challenge: Not a lot of room for large passives/converters

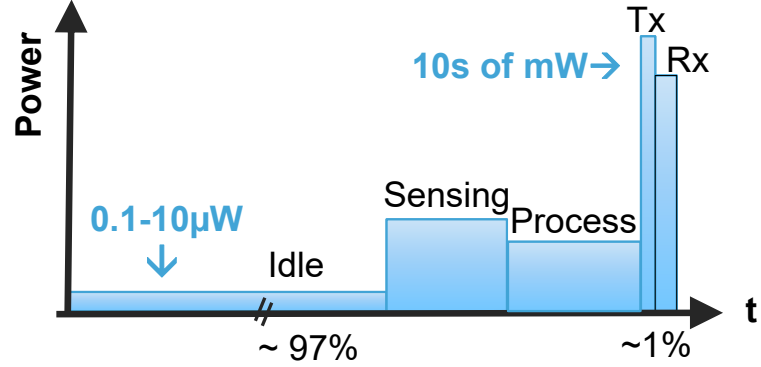Challenge: Require high efficiency over 1,000,000x dynamic range




Research goal: Simultaneously increase efficiency and power density over a wide dynamic range




Powering IoT and Wearables in Scaled-CMOS

Conventional

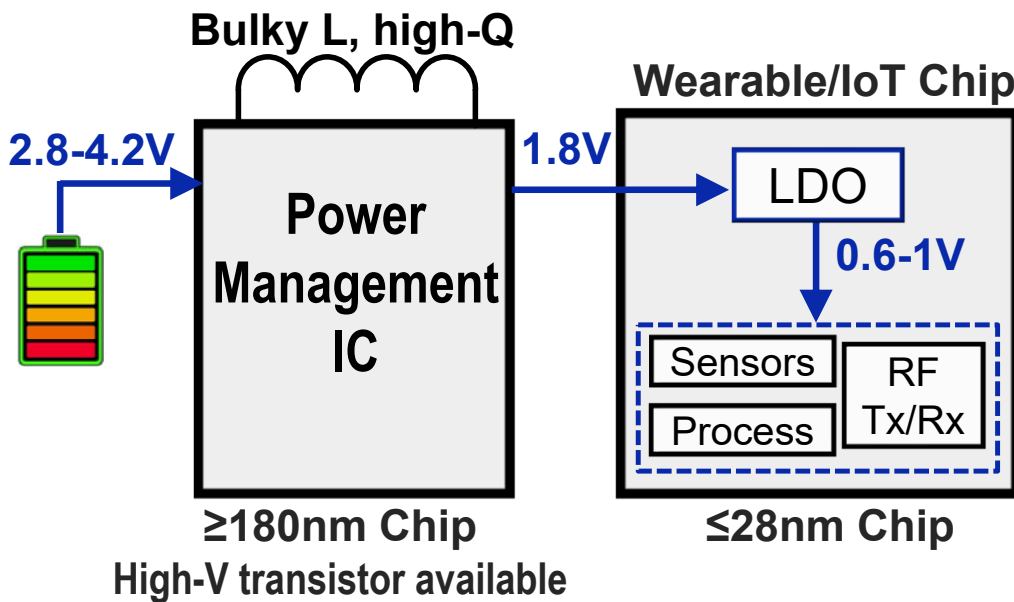

Goal

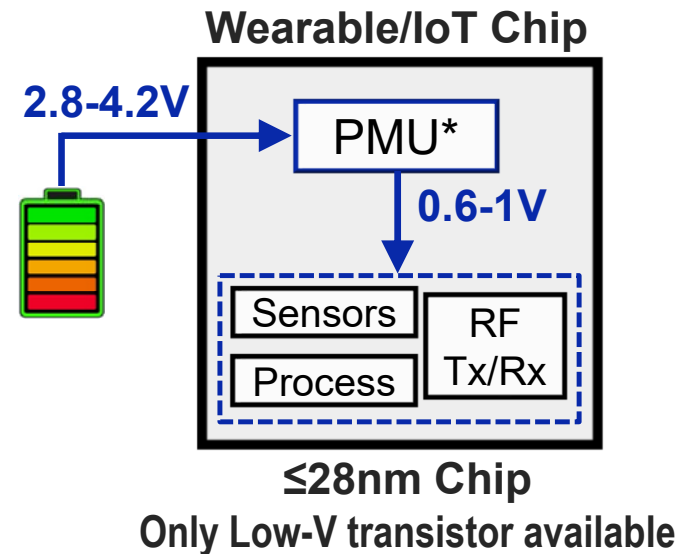

PMU*: Power Management Unit with or without off-chip inductor



Li-ion Fully-Integrated PMU Challenges in 28nm FDSOI

Scaled-CMOS Challenges

Only Low-V transistors available

Transistors stacking required

- High switching & conduction losses
- Complex power-hungry drivers
- Many level shifters

Poor efficiency

Only Low-V capacitors available

Capacitors stacking required


Large area

Low power density

Poor quality on-chip passives


- Large ESR, parasitic cap
- Low density

Poor efficiency
Low power density

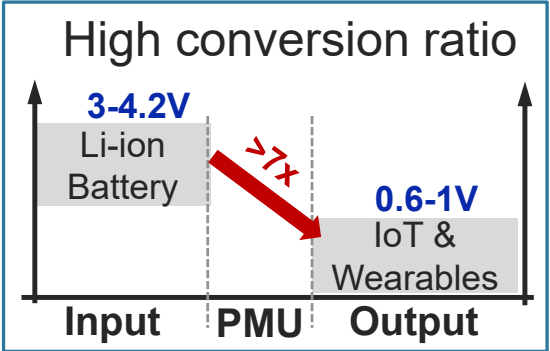




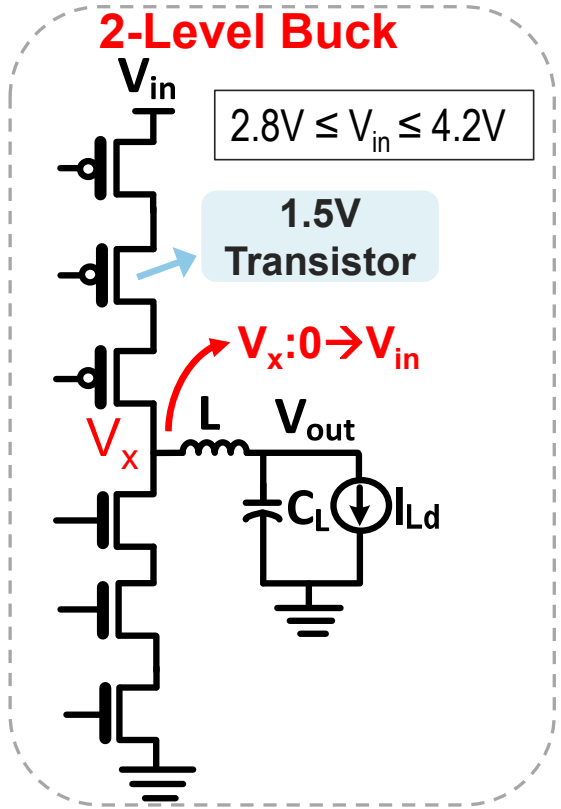
Towards Fully-Integrated Li-ion PMU in Scaled CMOS



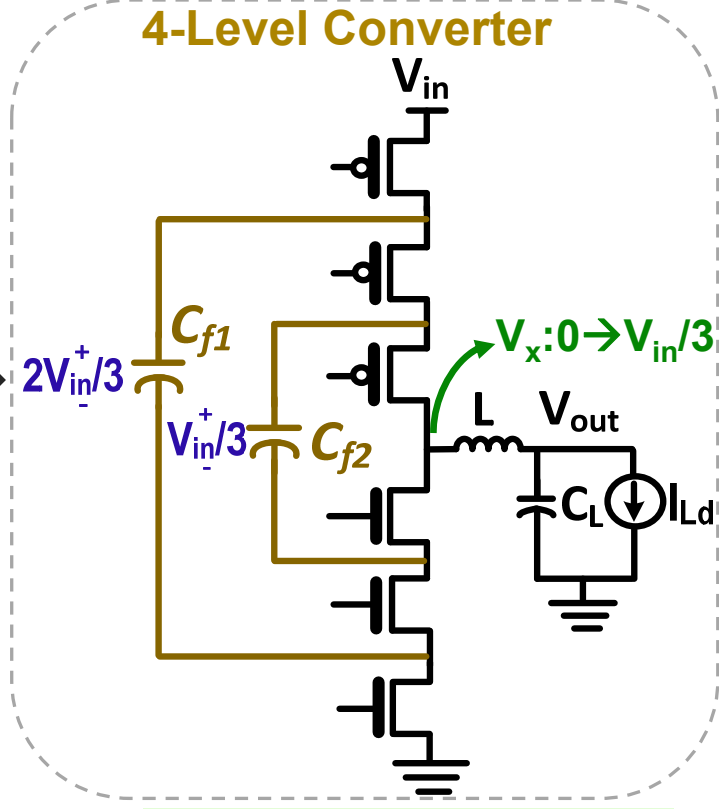Small on-chip L, large ESR
 -High Switching & conduction losses
 -Poor efficiency



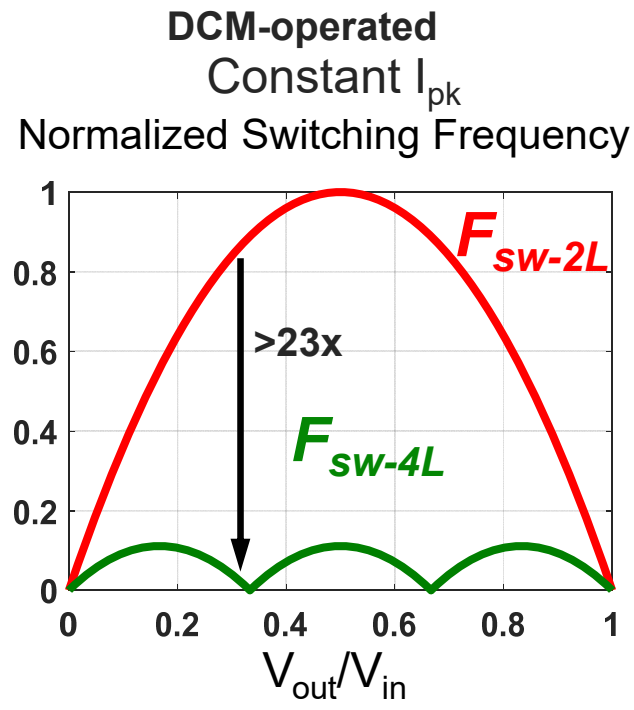Reduced swing at Vx
 F_{sw} reduced by $> 23x$
 & efficiency by up to 33%




$$\frac{F_{sw-4L}}{F_{sw-2L}} = \frac{1/3 - V_{out}/V_{in}}{1 - V_{out}/V_{in}}$$




Conventional 4-Level Converter Area Penalty

Conventional 4-Level

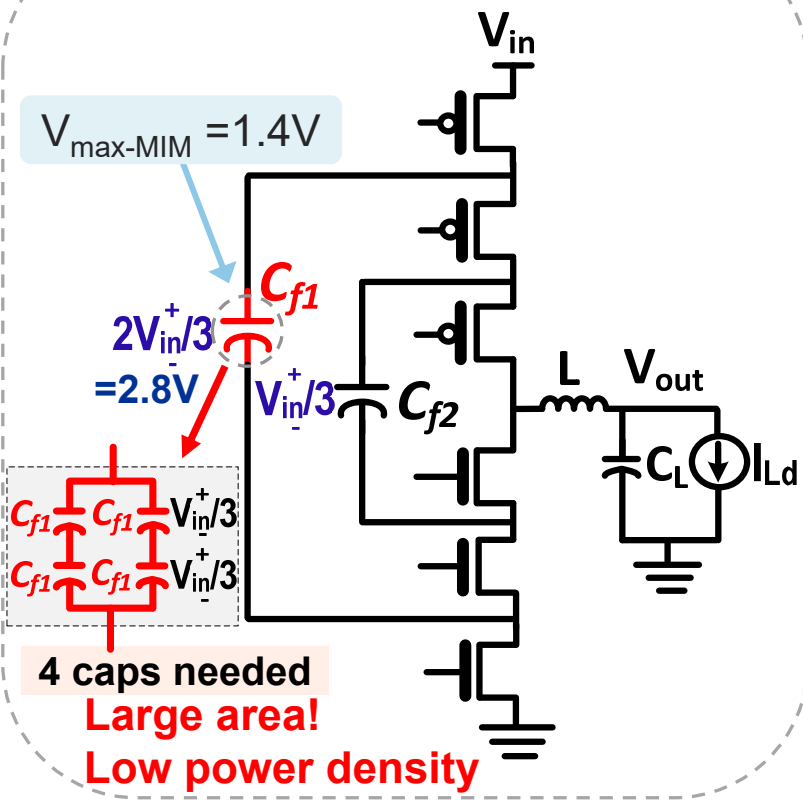

Reducing cap area by 4x



Proposed Modified 4-Level

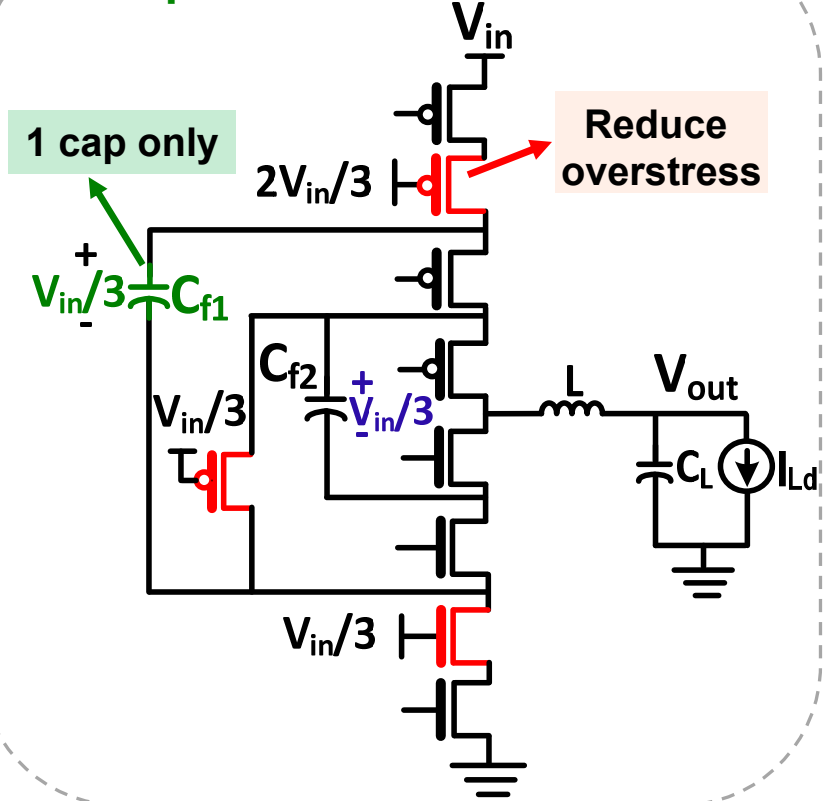



Changing the switching states of flying caps reduces the cap voltage stress



Driver Architecture

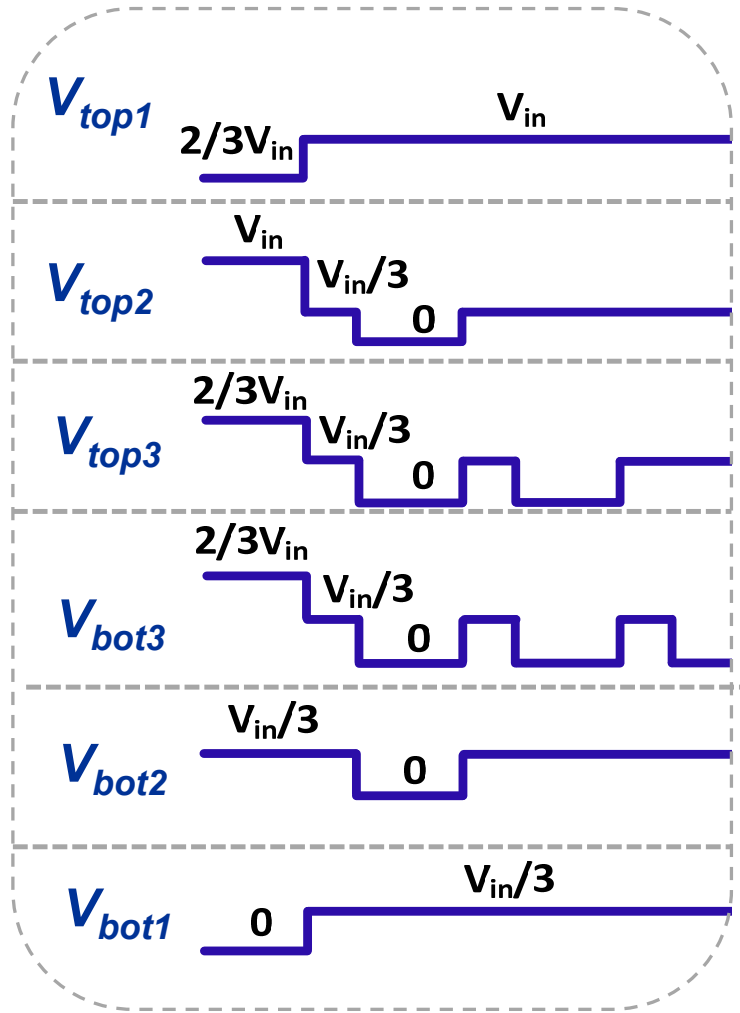
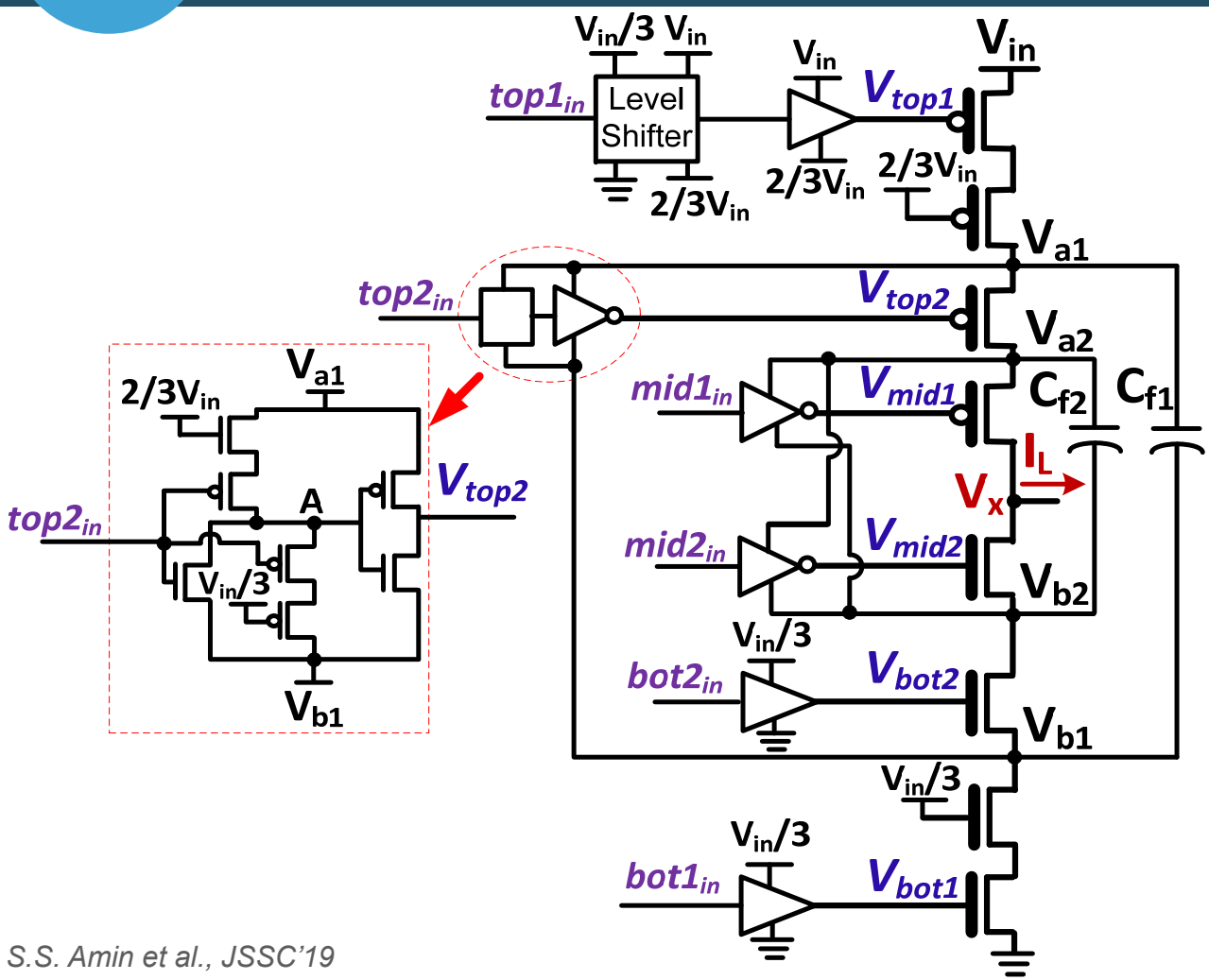


Measurement Results

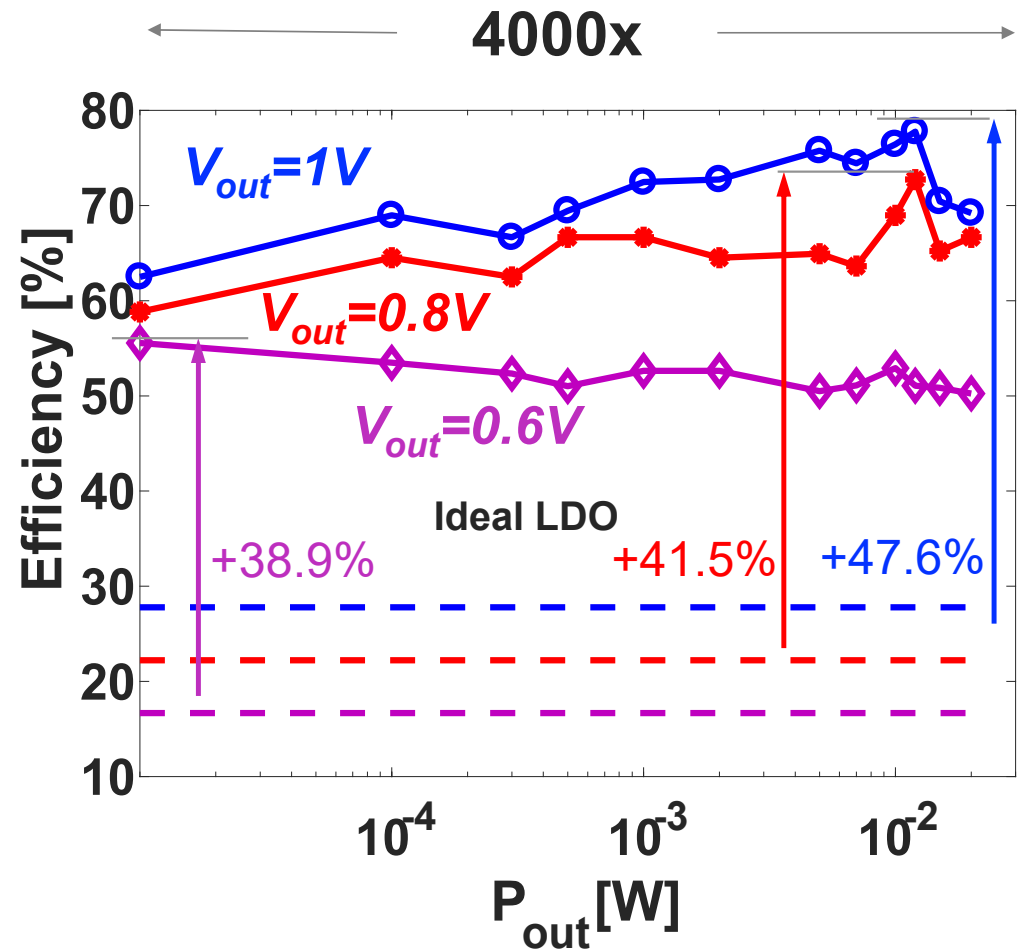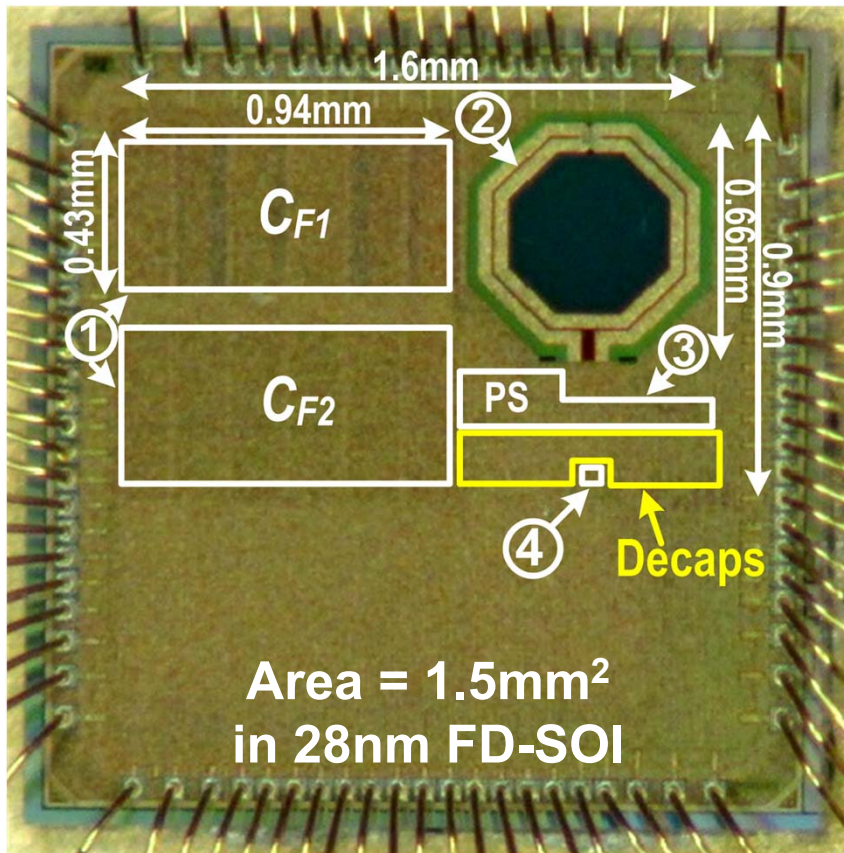




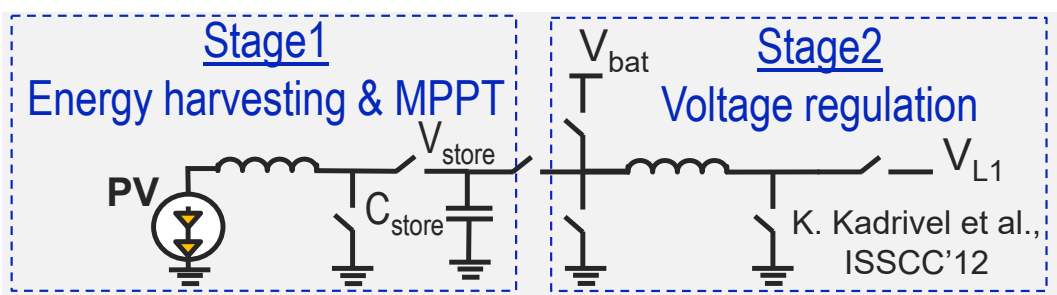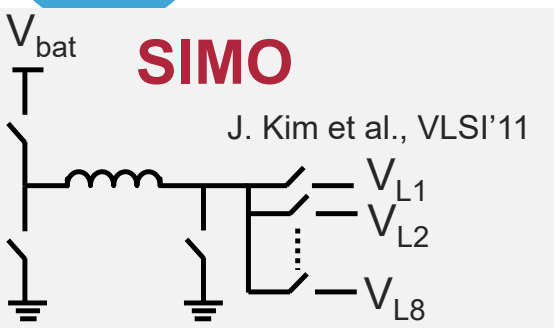
Towards Small Form-Factor Single-Inductor Converters



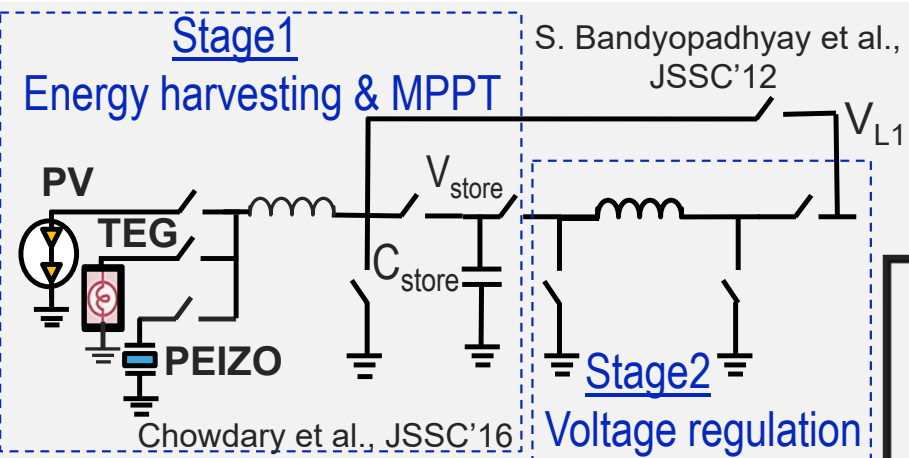
- Single input
- Single output
- Cascaded losses



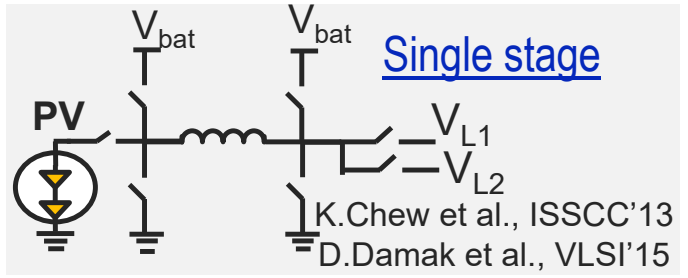- + Multiple inputs
- Cascaded losses
- Single output




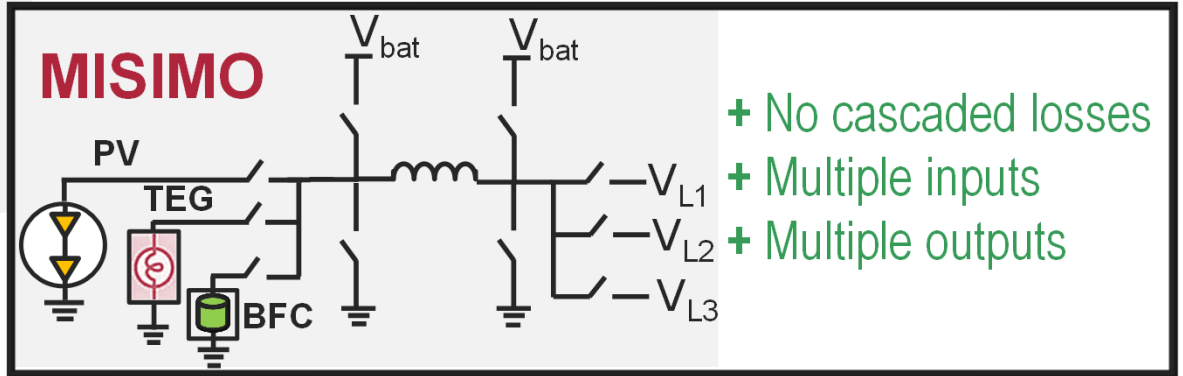
- + No cascaded losses
- + Multiple outputs
- Single input



- + No cascaded losses
- + Multiple inputs
- + Multiple outputs





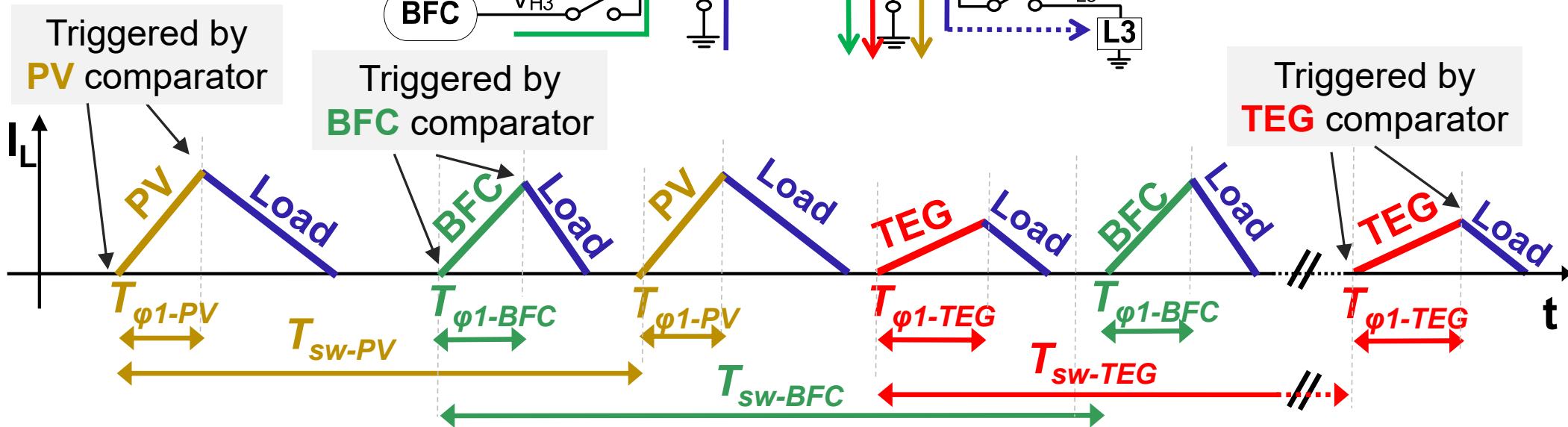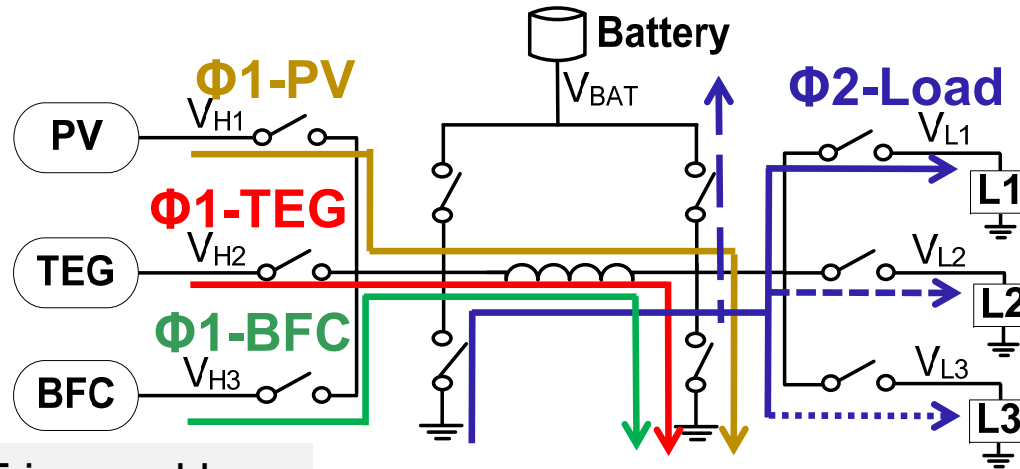Time-Shared Inductor for Multi-Input Harvesting






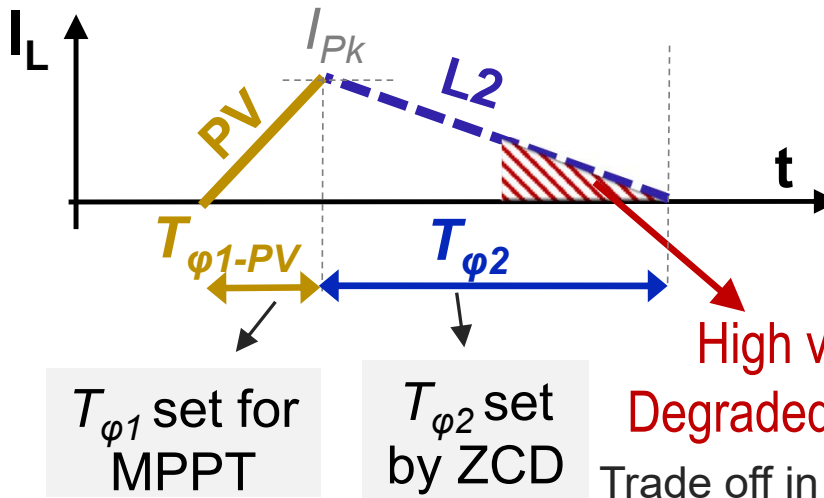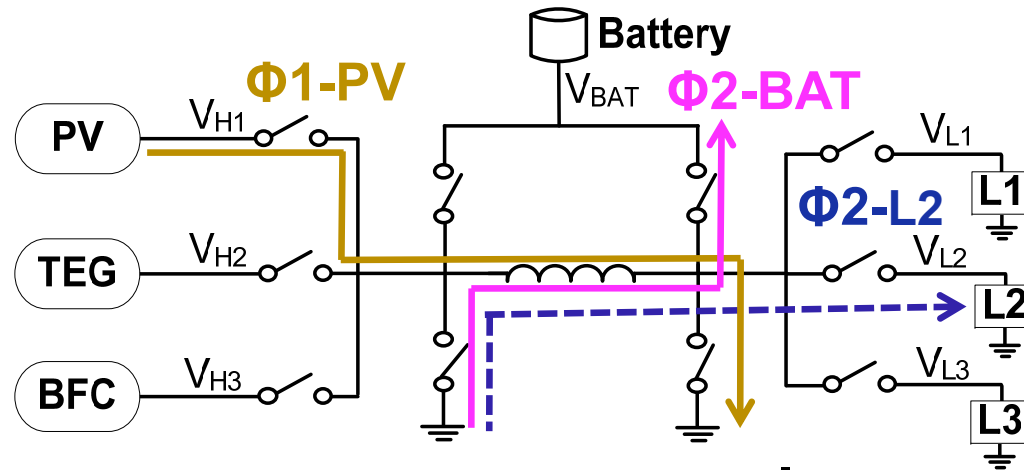Challenge: decoupling MPPT and Load Regulation



Proposed


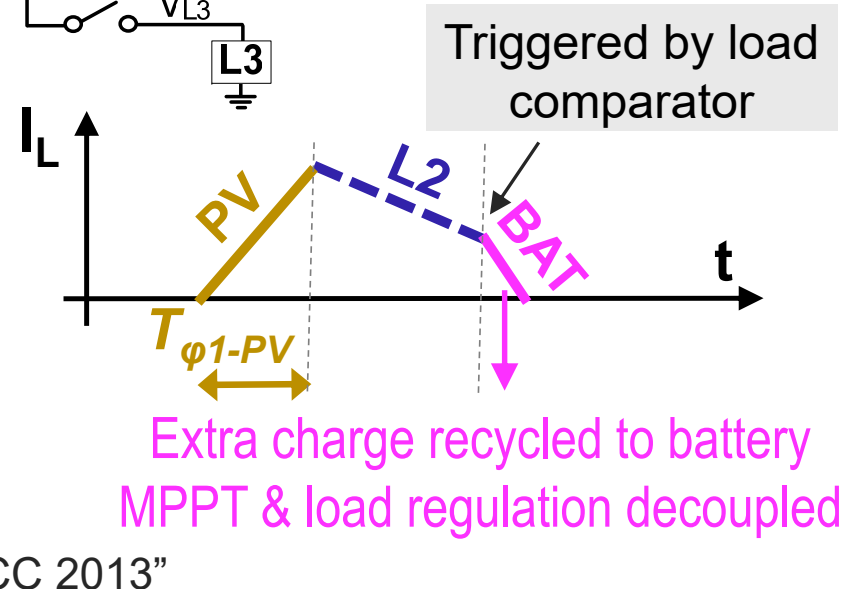


High voltage ripple
 Degraded load regulation
 Trade off in "K. Chew et al., ISSCC 2013"




MISIMO Event Driven Controller

MISIMO Triggers

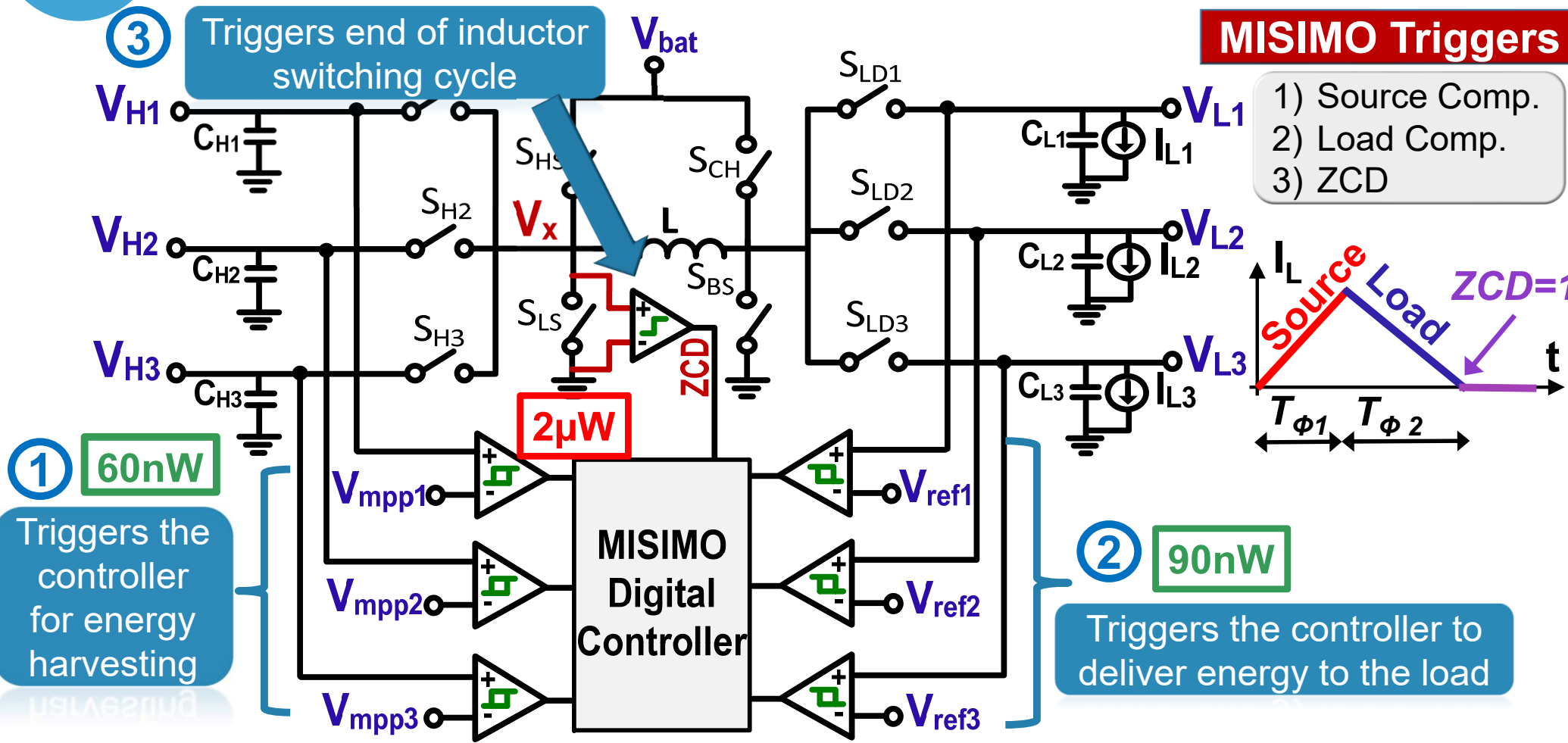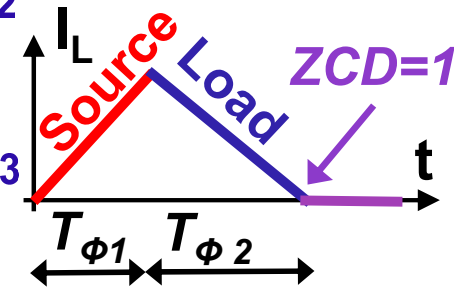- 1) Source Comp.
- 2) Load Comp.
- 3) ZCD






MISIMO Measurement Results

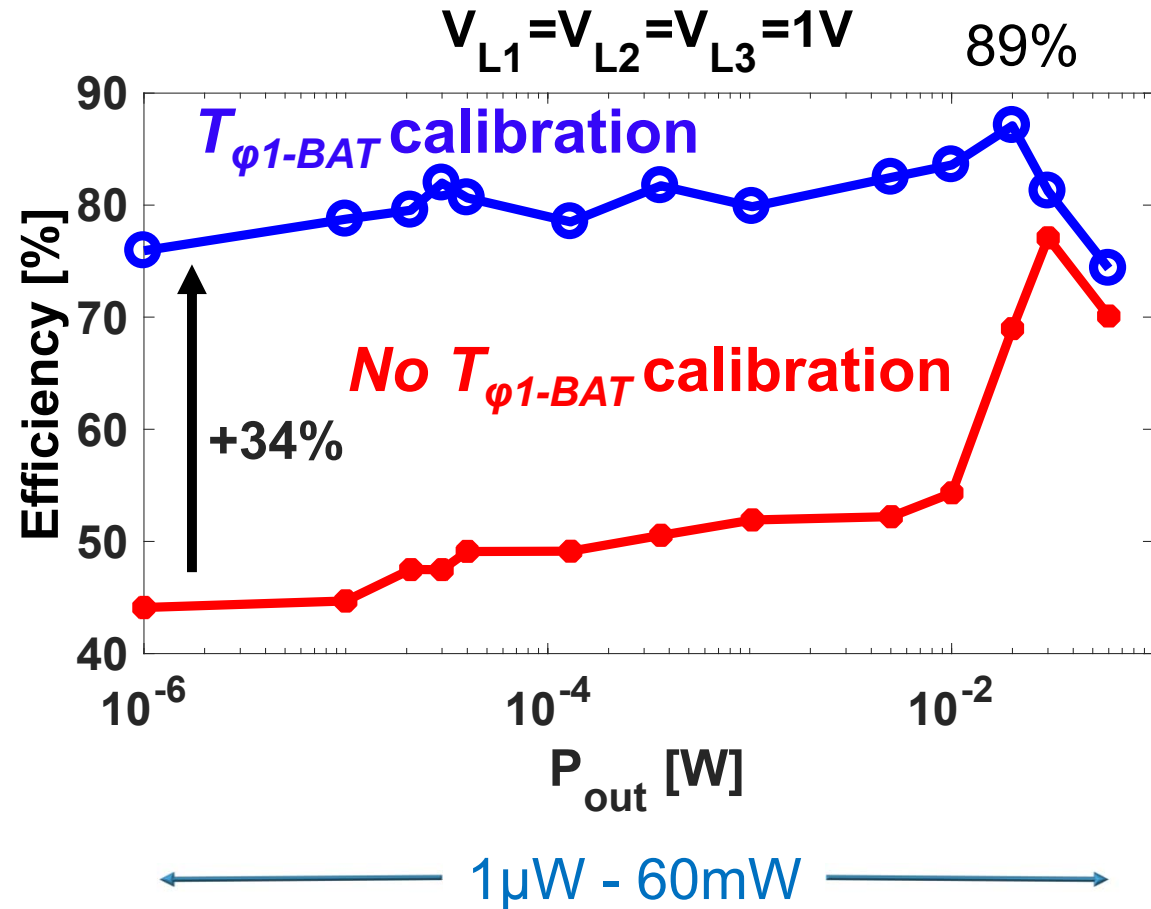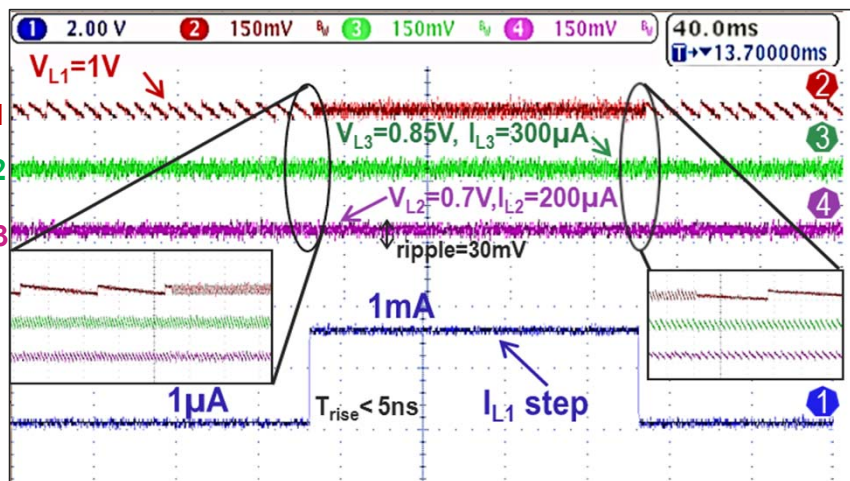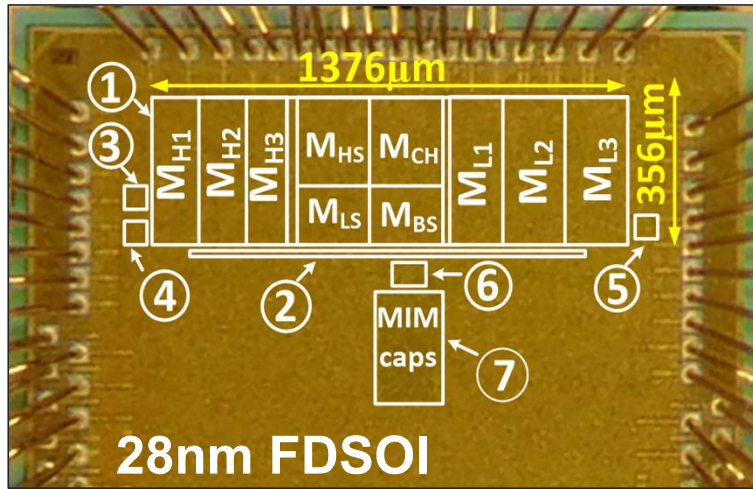

Hybrid SIMO

H-SIMO: Hybrid SIMO

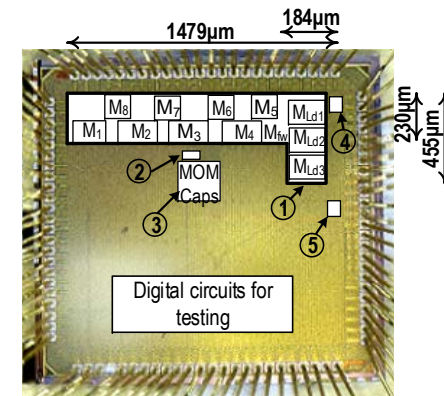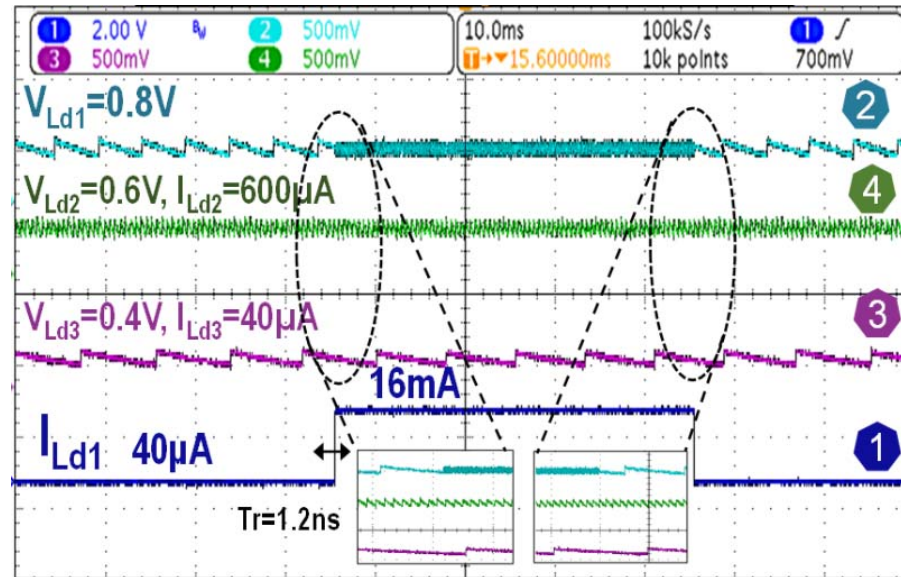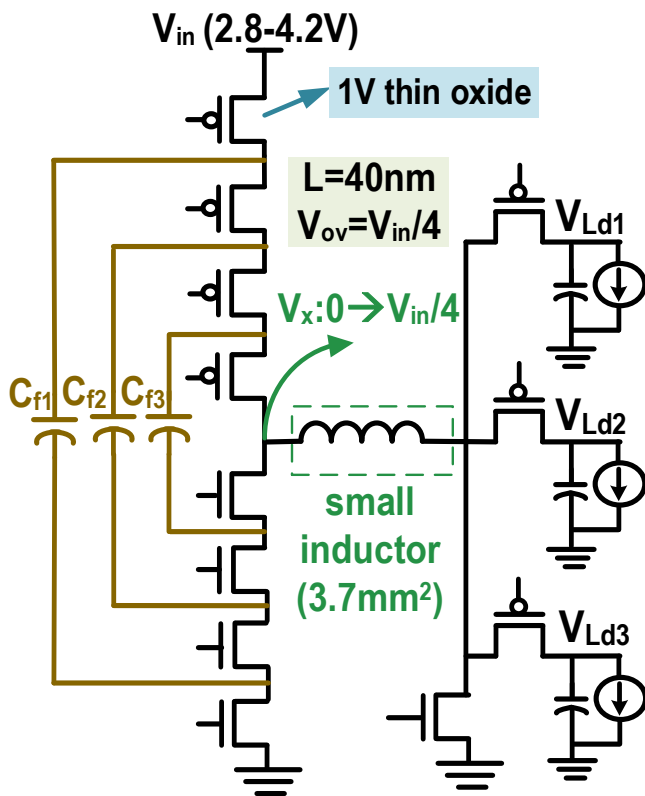


- Li-ion compatible in 28nm FDSOI
- Simultaneously regulates 3 loads w/ one inductor
- Peak efficiency = 91.4%
- 4,000x dynamic range w/ >70% efficiency



Power Management Research Focus Areas

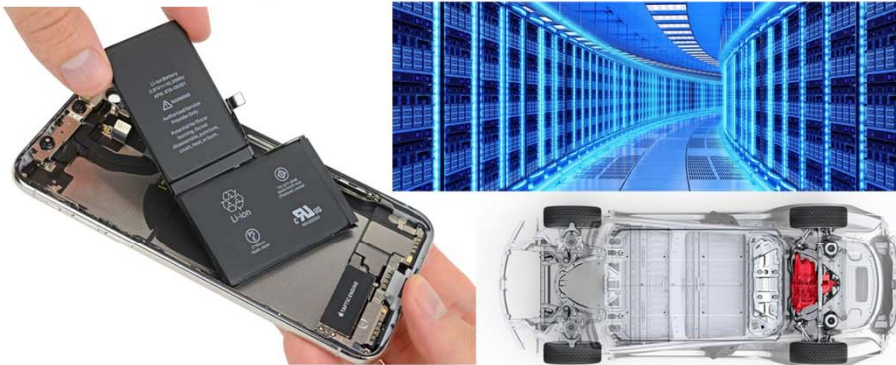
High Power Density Hybrid Converters:
Mobile phones, data centers, automotive



RF Power Amplifiers
5G, Wi-Fi 6, Long Range IoT



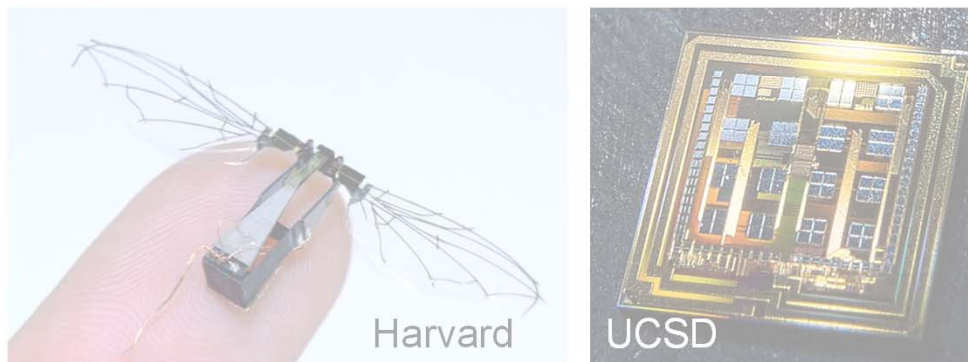Integrated High-Voltage Conversion
Microrobotics, Neural Implants





Wide Dynamic Current Range Converters
IoT, Wearables





Inductor-first conversion

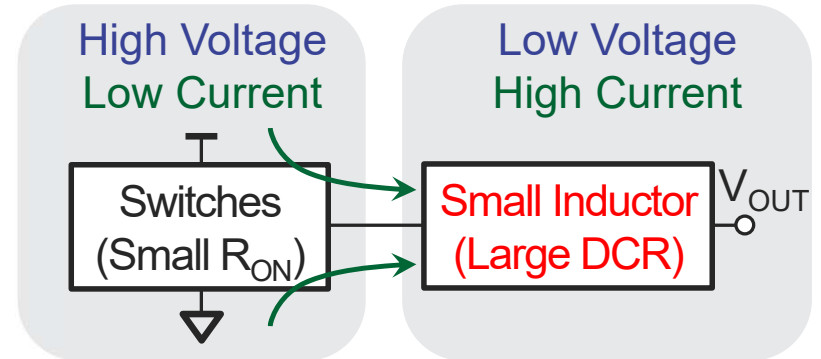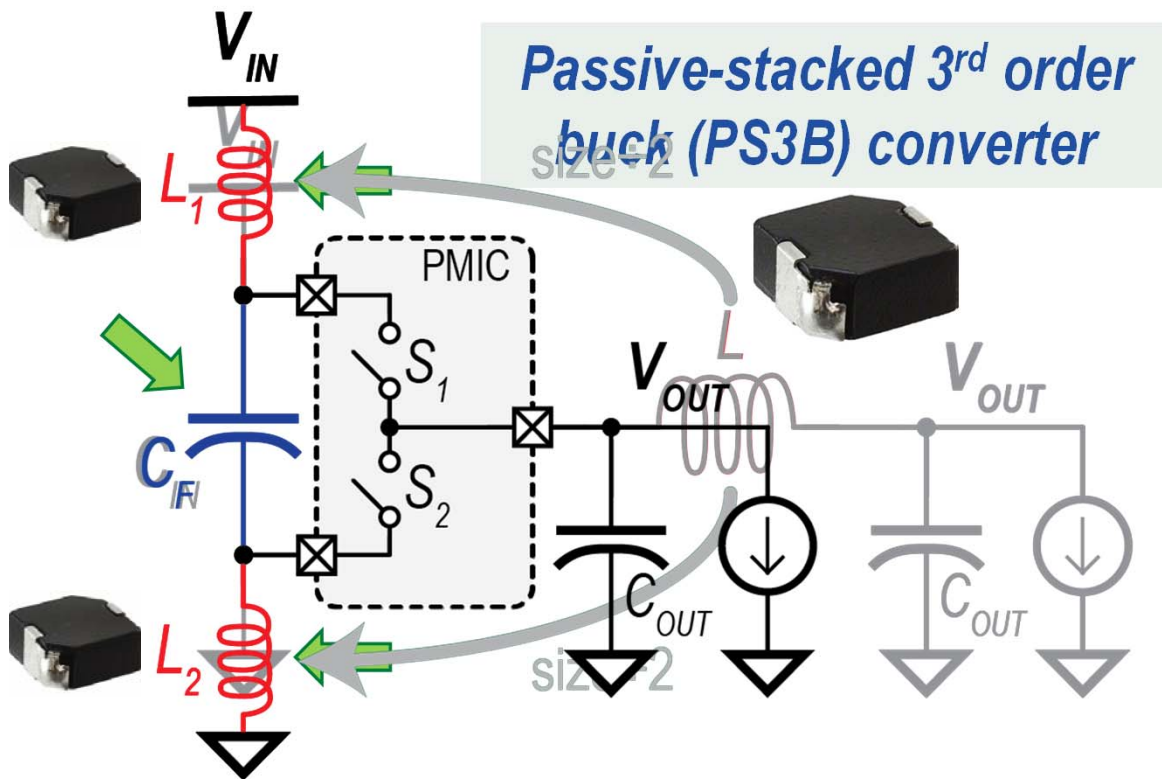

Split into two half-sized inductors and stack at input


The input capacitor is now flying

All passives are stacked at input

Inductors are placed at the low-current side of the converter


PS3B Measurement Results

Top-side

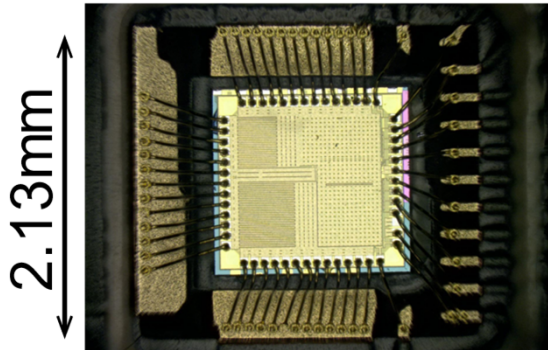


2.33mm

Bottom-side

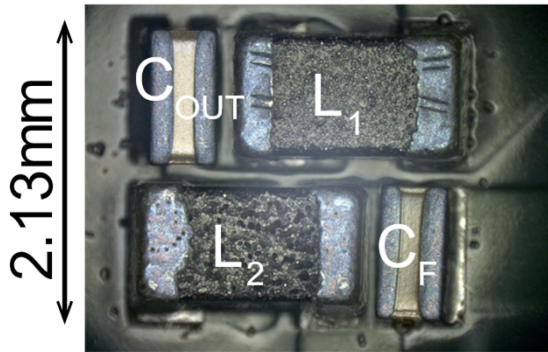


2.33mm

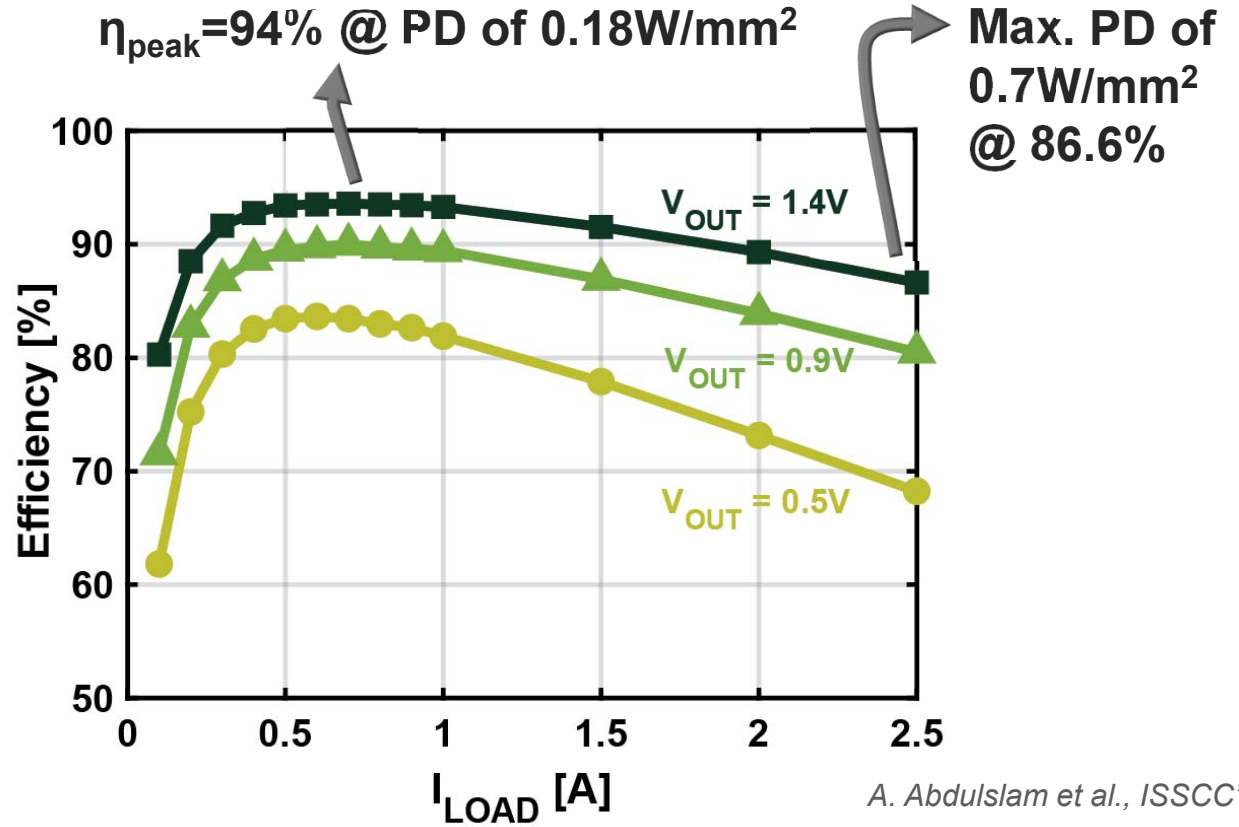


Benefits: reduced EMI and input noise, area-efficient stacked-passives, smaller inductors volume

Li-ion-compatible SMML Converter




- ❖ A symmetric modified multilevel ladder (SMML) converter:
 - Consists of two sides each with 2 capacitors and 6 switches.
- ❖ Features:
 - ✓ **Decreased conduction losses** due to inherent phase interleaving.
 - ✓ **Minimum blocking voltage** on all switches/capacitors.
 - ✓ **No need for voltage balancing modules** flying capacitors are naturally stable.
 - ✓ **All necessary supplies are generated internally** to power drivers and level shifters.

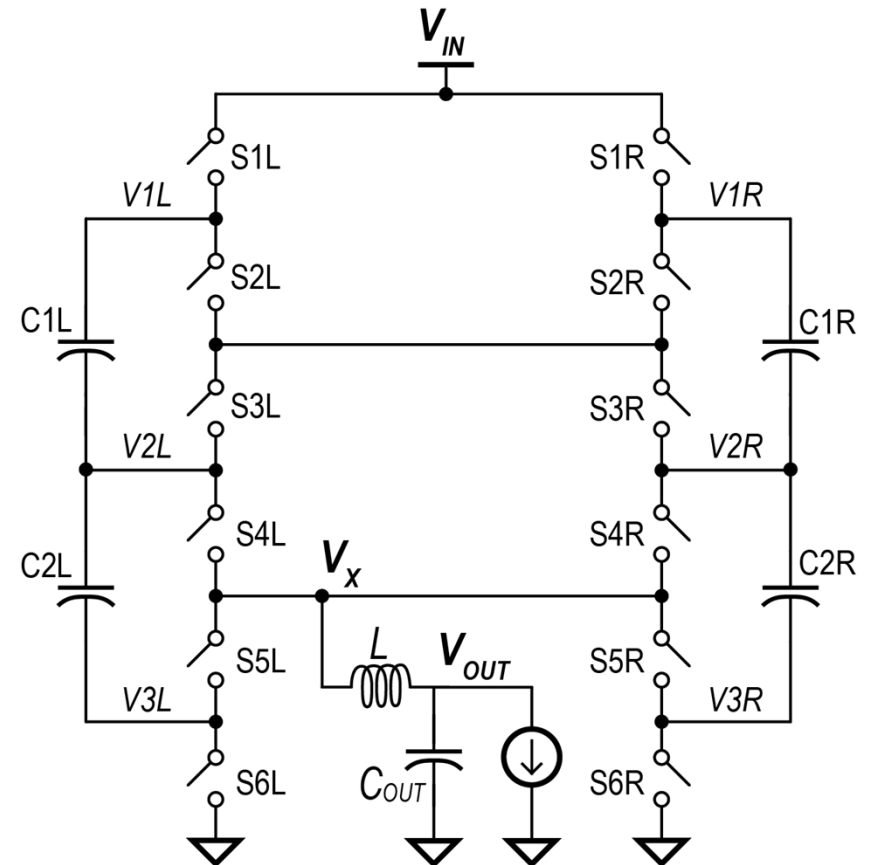

SMML Measurement Results

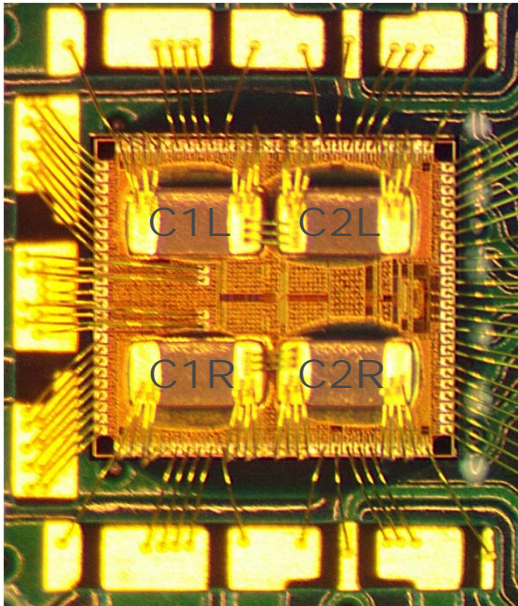

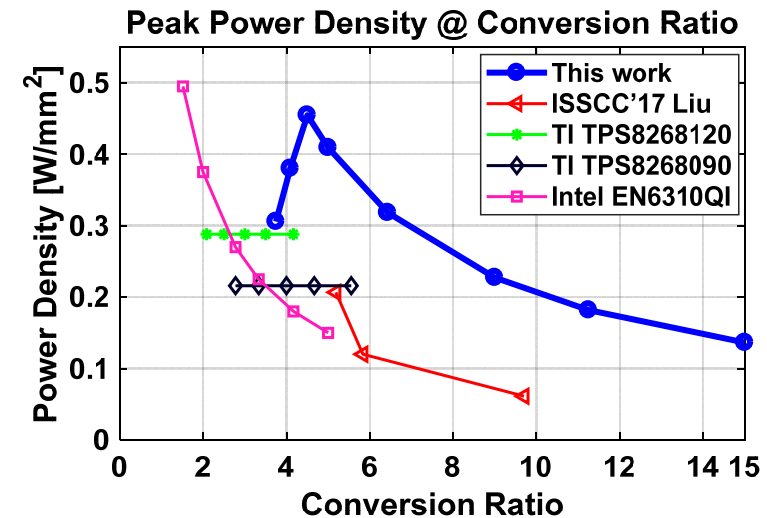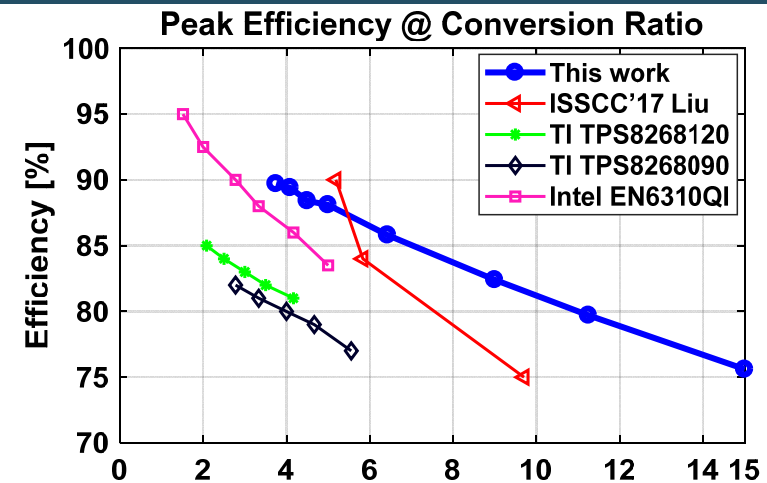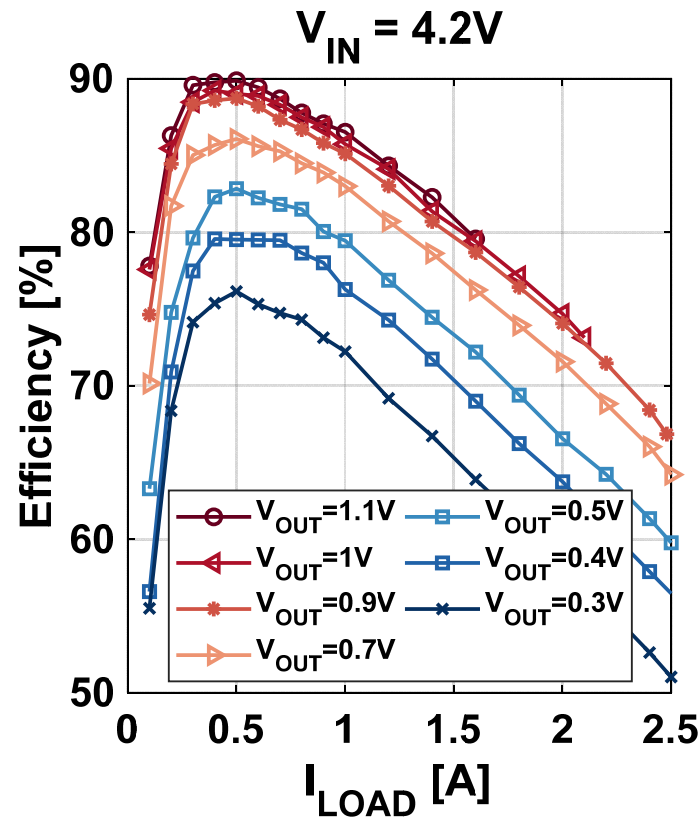The inductor and the output capacitor are mounted under the chip




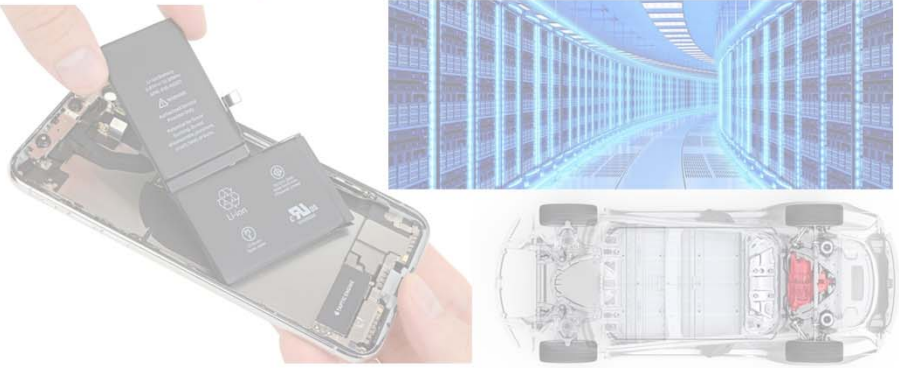A. Abdulslam et al., JSSC'20



Power Management Research Focus Areas


High Power Density Hybrid Converters:
Mobile phones, data centers, automotive



RF Power Amplifiers
5G, Wi-Fi 6, Long Range IoT



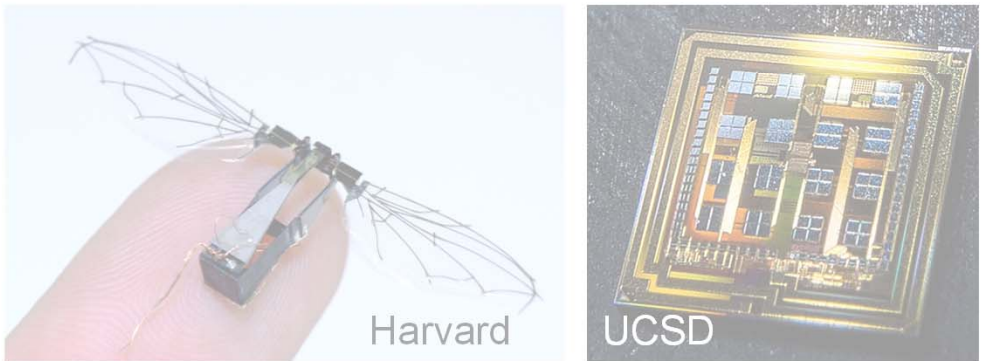
Integrated High-Voltage Conversion
Microrobotics, Neural Implants



Wide Dynamic Current Range Converters
IoT, Wearables



CMOS Power Amplifier Voltage Challenge

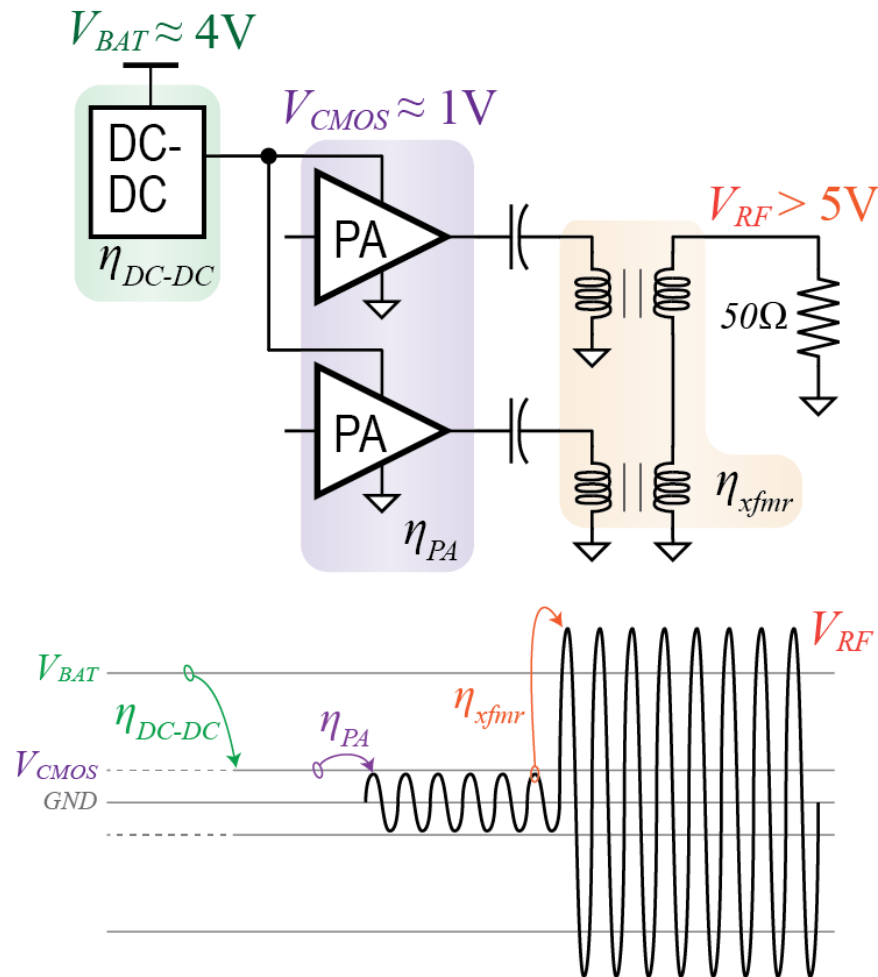

Idea: utilize many efficient $\sim 1V$ class-D PAs and combine power with transformers

Problem: three voltage conversion stages leads to cascaded losses:

$$\eta_{tot} = \eta_{DC-DC} \eta_{PA} \eta_{xfmr} < 30\%$$


Why do we go down, then back up in voltage?
There must be a better way!

Partial Solution: PA Stacking

Stack entire class-D PAs for current re-use:

~100% efficient *implicit* DC-DC conversion

(each PA sees only $V_{BAT}/2$)

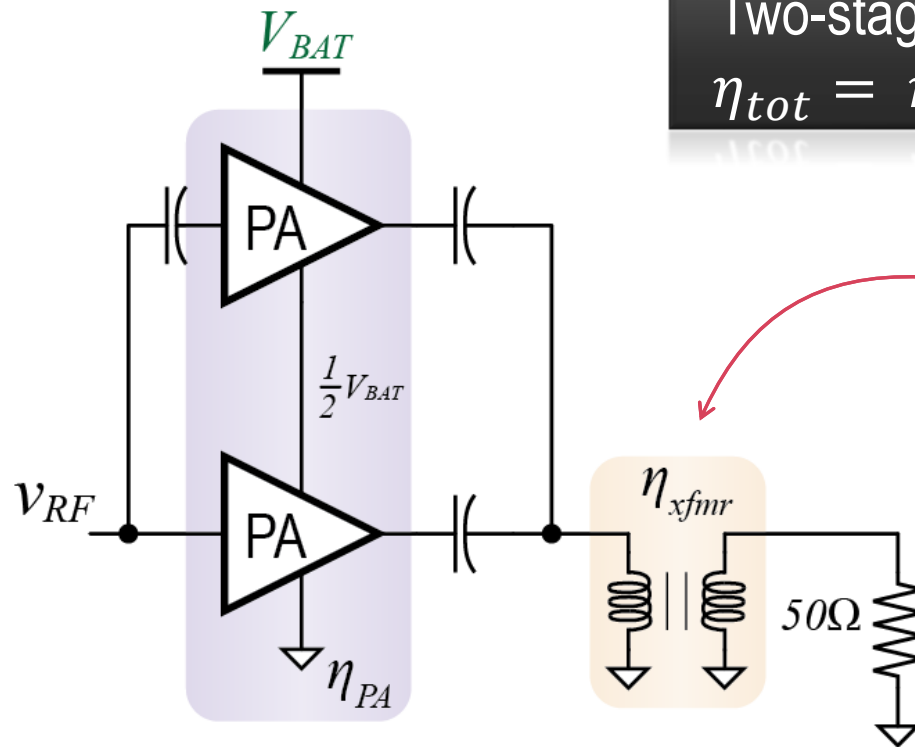


Two-stage cascade:

$$\eta_{tot} = \eta_{PA} \eta_{xfmr}$$

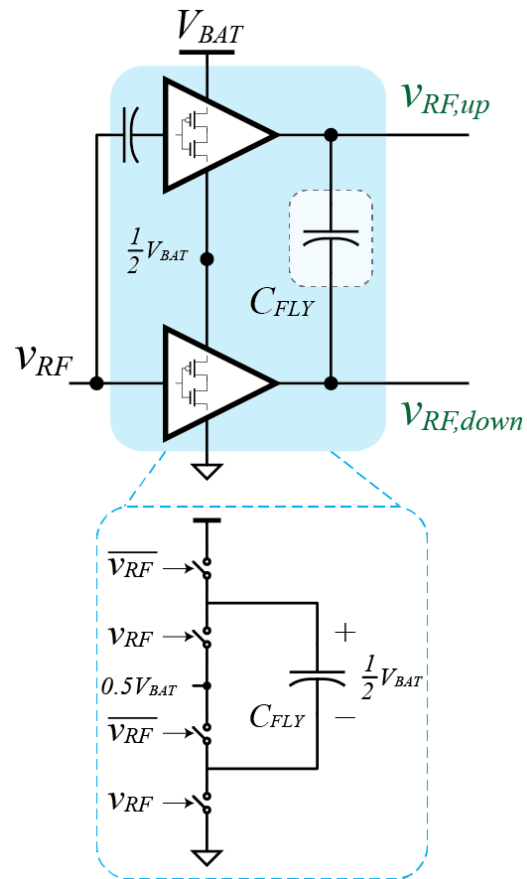
Problem: still require lossy transformer to achieve high output power in scaled CMOS

Solid-State RF Impedance Transformation

Idea: generate large RF voltages directly from a battery using ~1V devices by stacking PAs, then flying subsequent PAs between the rails of the prior stages in a *House-of-Cards* Topology




Animation
not seen in print


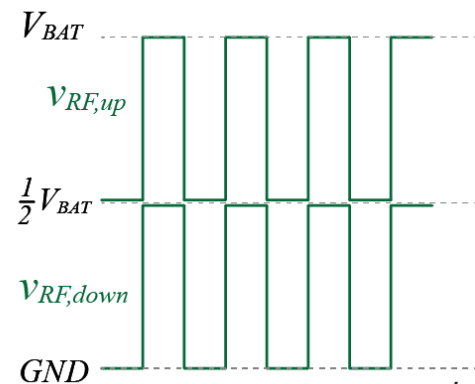


Solid-State RF Impedance Transformation

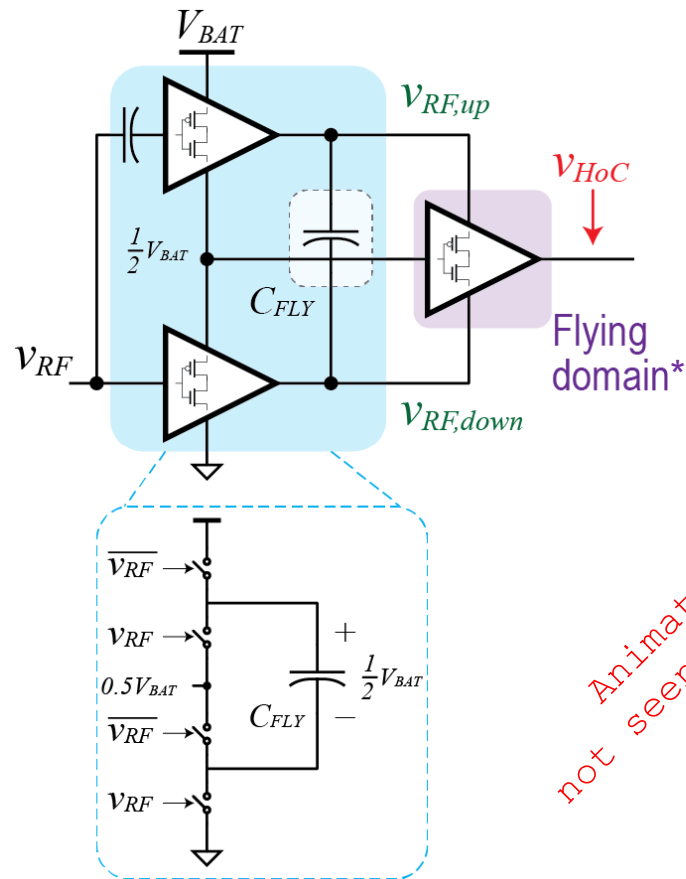Idea: generate large RF voltages directly from a battery using ~1V devices by stacking PAs, then flying subsequent PAs between the rails of the prior stages in a *House-of-Cards* Topology






Animation
not seen in print

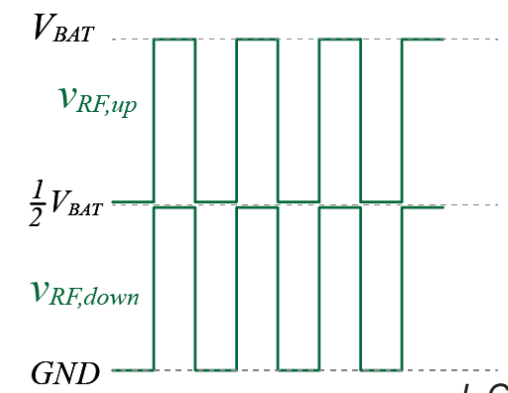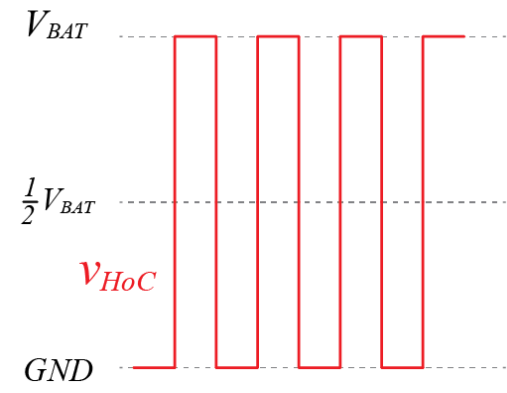


*For more information, see Salem et al., ISSCC'16

Solid-State RF Impedance Transformation

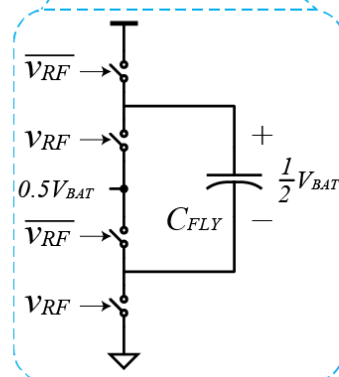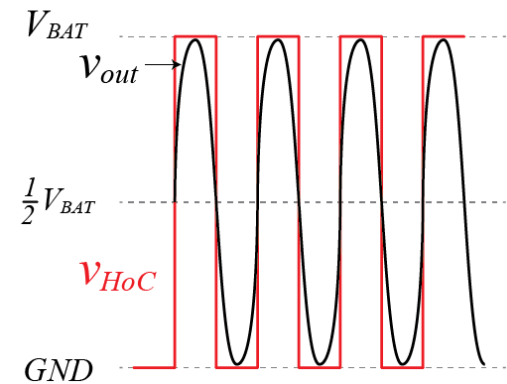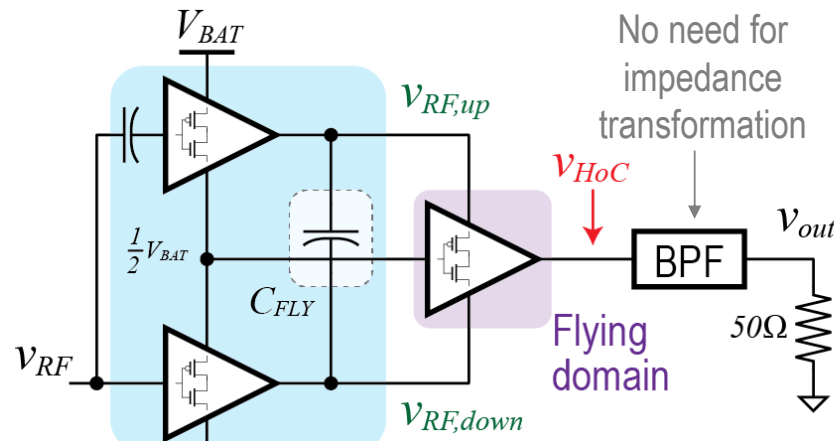Idea: generate large RF voltages directly from a battery using ~1V devices by stacking PAs, then flying subsequent PAs between the rails of the prior stages in a *House-of-Cards* Topology




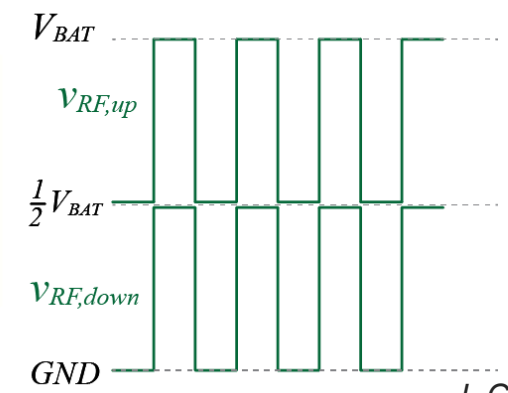High power RF waveform synthesized directly from V_{BAT} using low-voltage transistors




*For more information, see Salem et al., ISSCC'16


House-of-Cards (HoC) Schematic

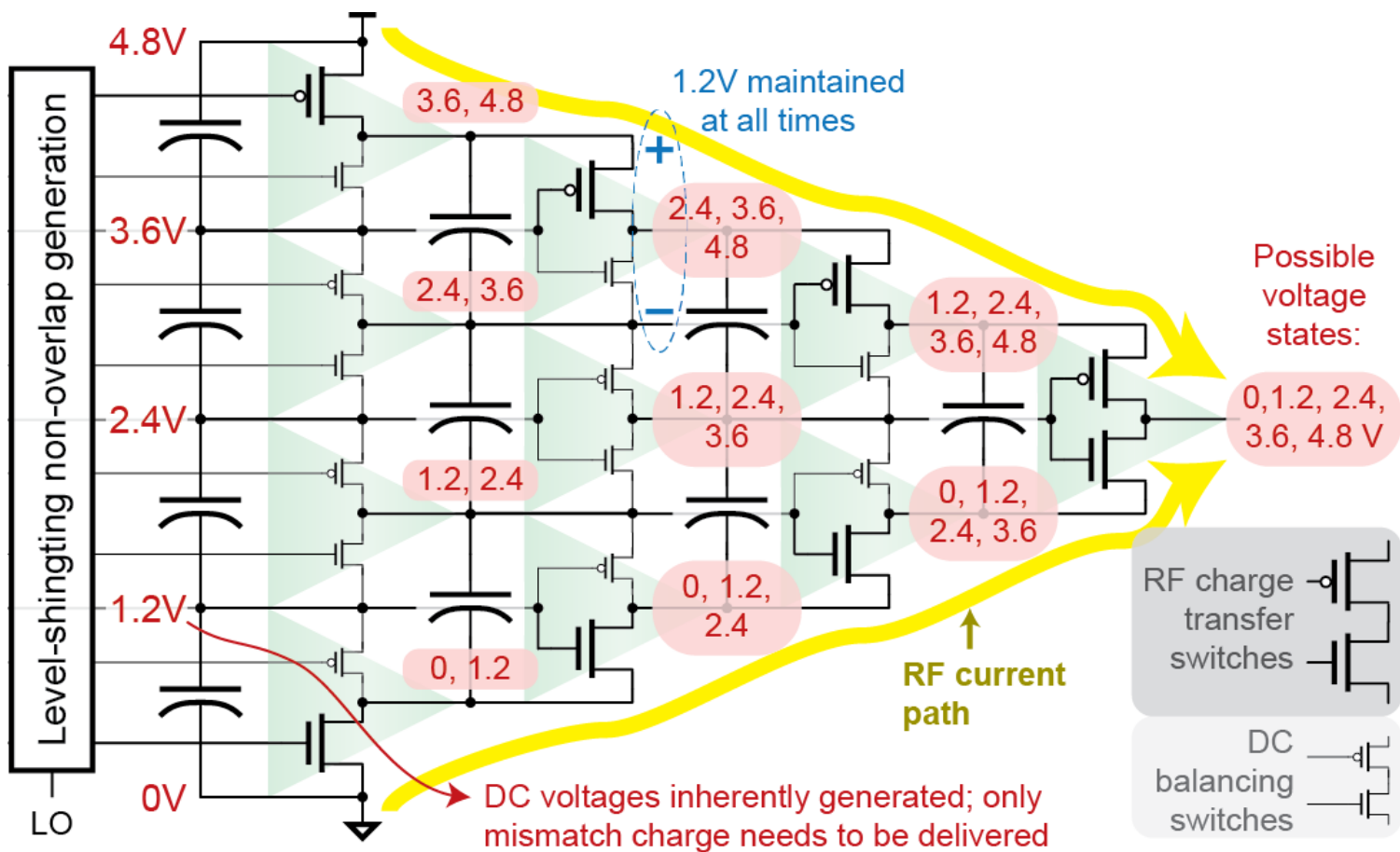

Measurement results: PAE

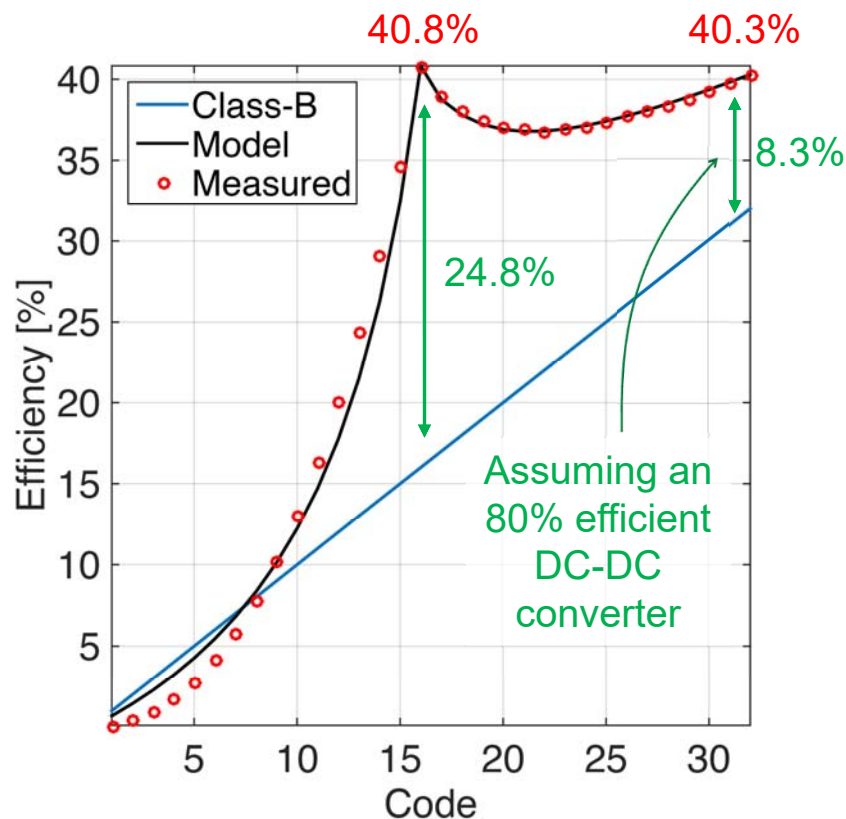

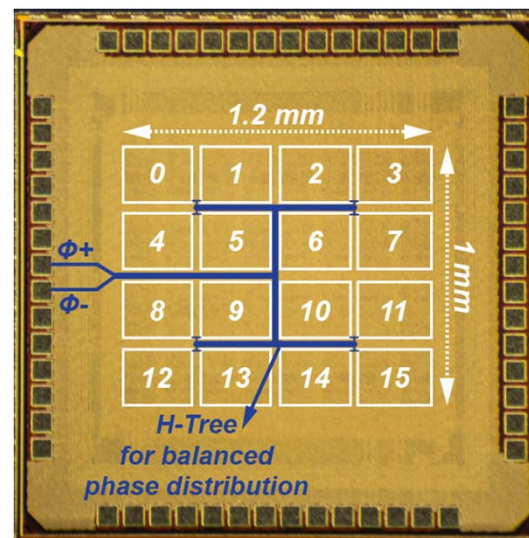65nm LP
 1.2V transistors
 Direct 4.8V Li-ion battery connection



>40% battery-to-RF power-added efficiency at both peak power (23dBm) and at 6dB backoff



Acknowledgements

