

Hybrid-Switched-Capacitor-Resonant DC-DC Converter for LED Driver Application

Chengrui Le

Oct. 2014



Outline

- Introduction
 - Motivation and challenges for better LED drivers
- Solutions
 - Take advantage of capacitors, new architecture combining L & C, capacitive isolation, integration, chip-stackable and expandable module
- The Hybrid-Switched-Capacitor-Resonant converter
- IC implementation
- Measurement results
- Integration with thin film Metacapacitors
- Conclusions

Building Better LED Drivers

- **Solid state lighting:** efficient, environmental friendly, and affordable
- **LED drivers:** Current regulation, power factor correction, galvanic isolation, dimming


- **Goals:**

✓ **Efficiency**

✓ **Cost**

✓ **Size**

✓ **Life**

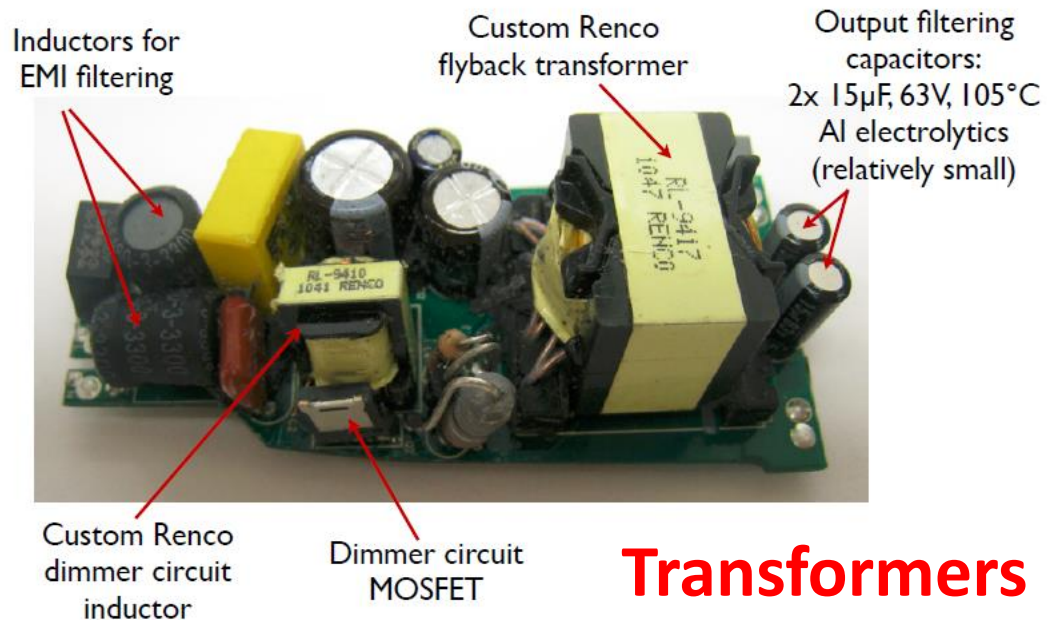

Transformers

Electrolytic Caps

Solutions

1. Architecture with lower V-A product

- Fundamental elements: Switches & Passives

- Switches:

larger I	R_{ON}	↓	} Larger device
larger V	V_{max}	↑	


- Passives: to pass larger I or Charge with lower loss to stand larger V } Larger device
Higher cost

2. Better passive components

- Higher energy density, lower cost, longer life, integration, high frequency performance...

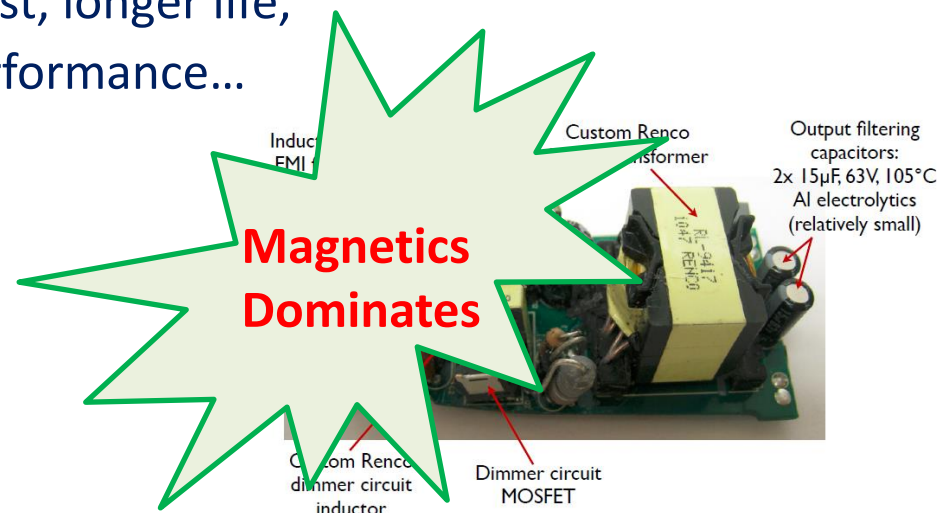3. L- C resonance


- Parasitic cancellation
- Lossless power regulation
- Isolation



Take Advantage of Capacitors


- Switched-capacitor (SC) topology:
 - Lower V-A rating for both individual and over all components. [Seeman, M.D., COMPEL 2010]
 - Multilevel architecture: modular design & reconfiguration.
- High energy density capacitors:
 - high frequency, low loss, printable thin-film Metacapacitors.
- Multilevel output L-C resonant network
 - Zero Voltage Switching (ZVS).
 - Lossless current regulation.
 - Energy merging and magnetic reuse.
 - Capacitive galvanic isolation.

Self-assembling
Nanoparticle dielectrics

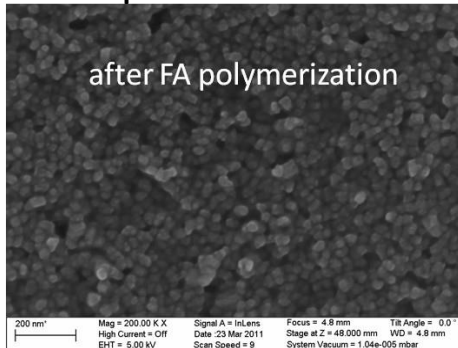


O' Brien (CUNY)

Scalable capacitor
printing technologies

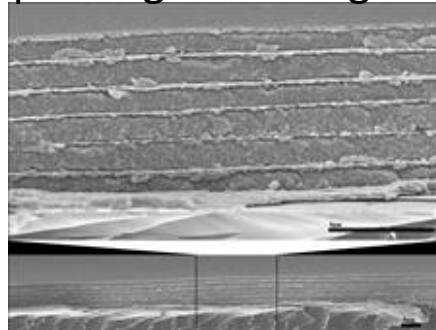


Steingart (Princeton)
Leland (CUNY)

Analog power circuits
And IC design

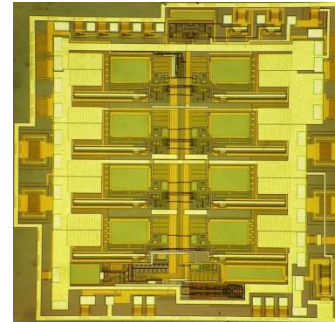


Kinget, Sanders
Columbia, Berkeley

Novel device
Integration

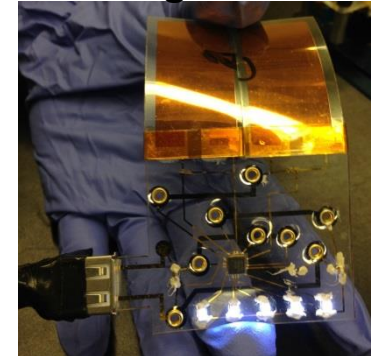



Kymissis (Columbia)

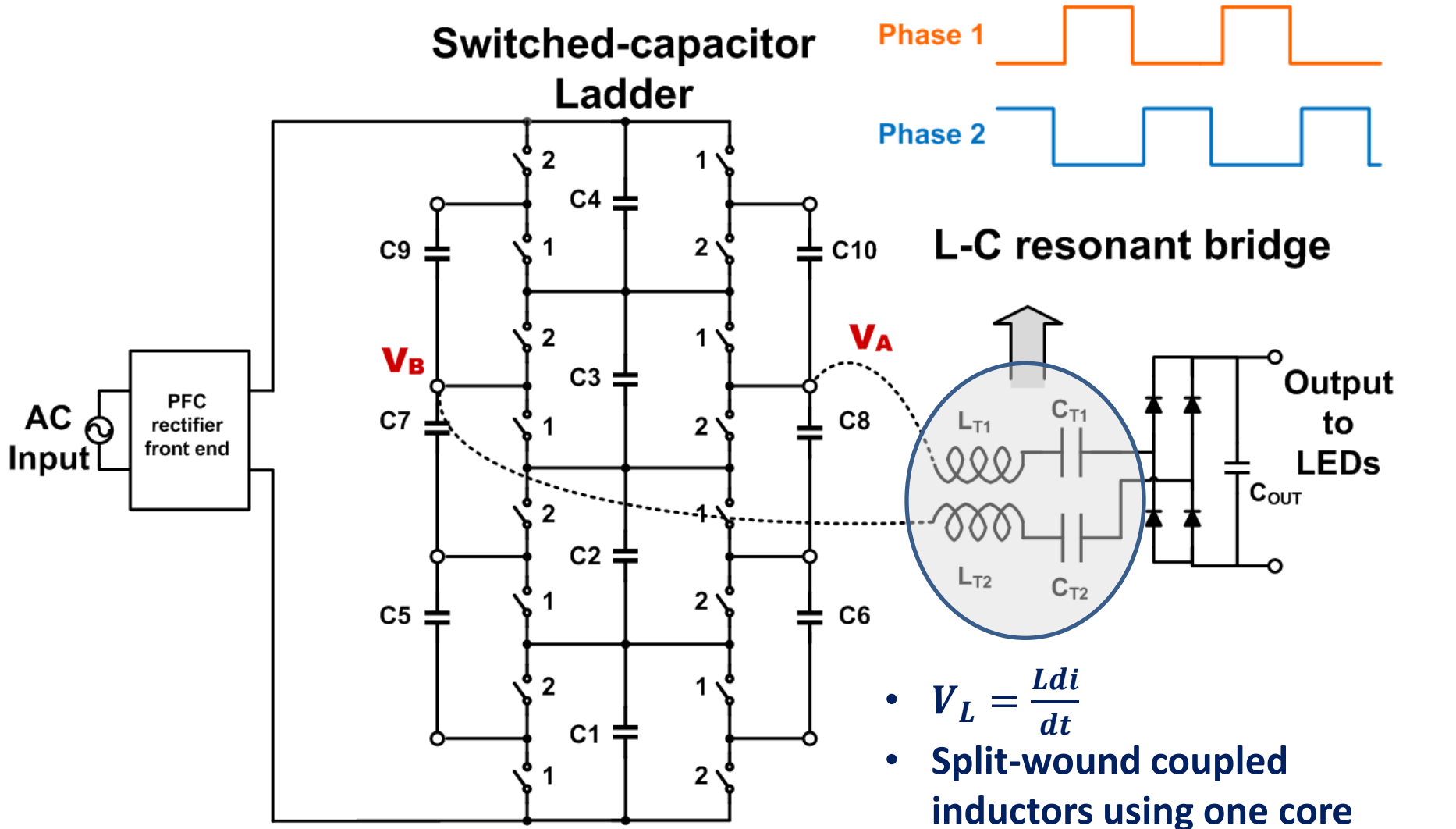Hybrid-switched-capacitor-resonant LED driver




Hybrid-switched-capacitor-resonant LED driver

Switched-capacitor Ladder

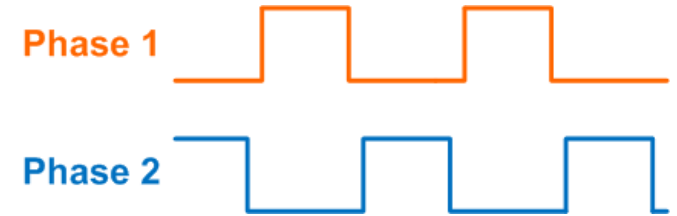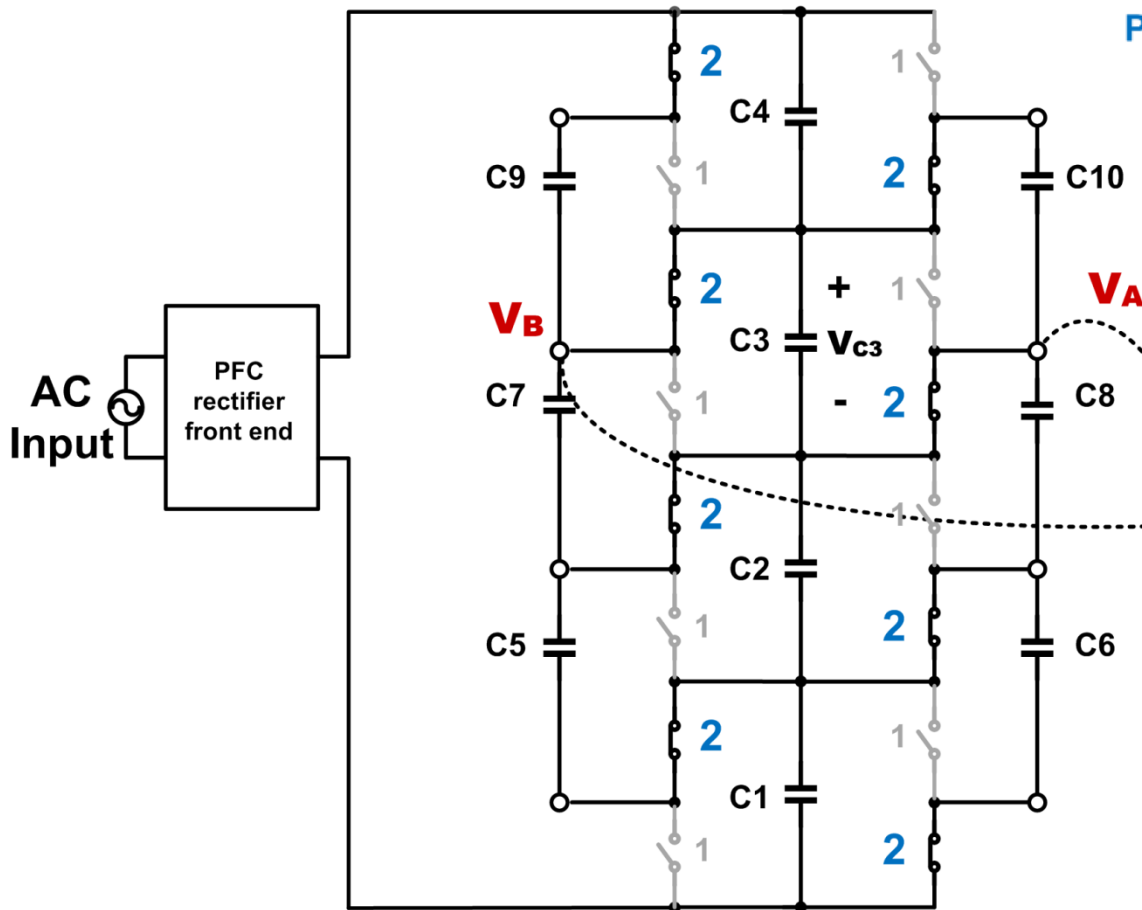





L-C resonant bridge

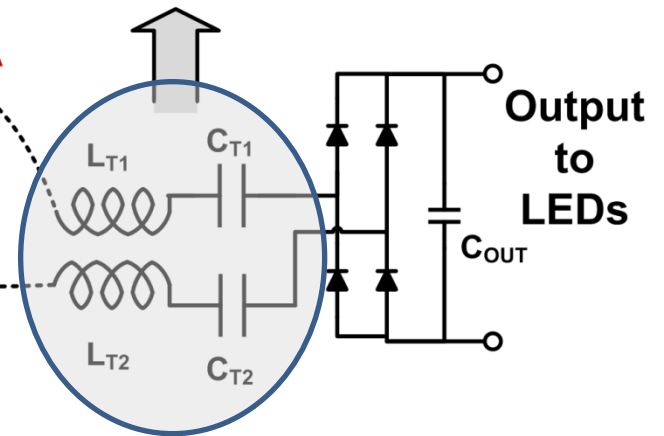

Two Phases of Operation and Output Current Regulation


Phase 1

Phase 2

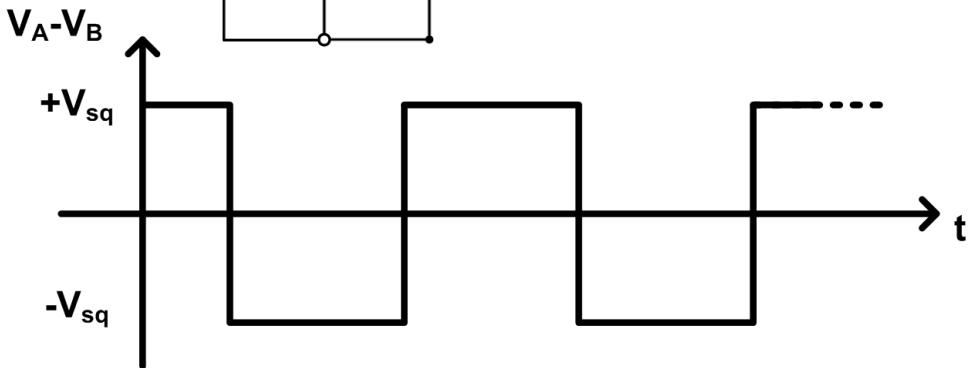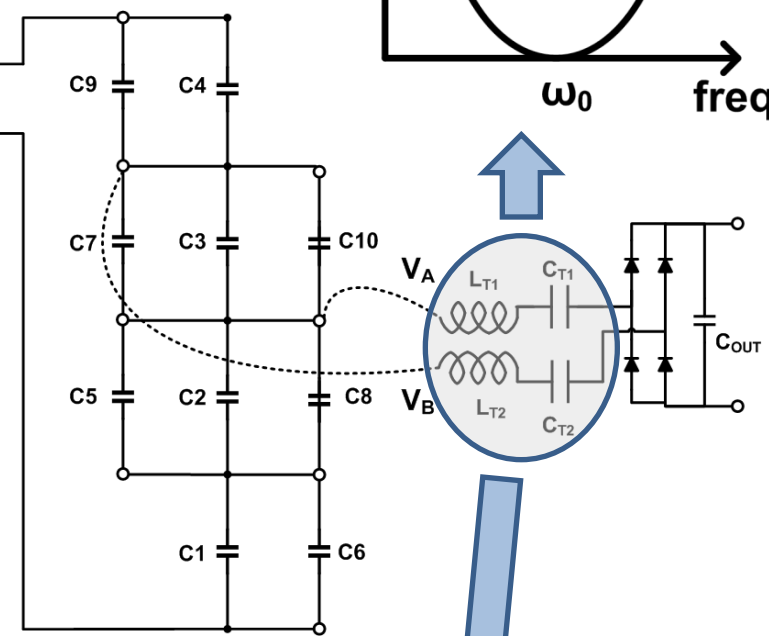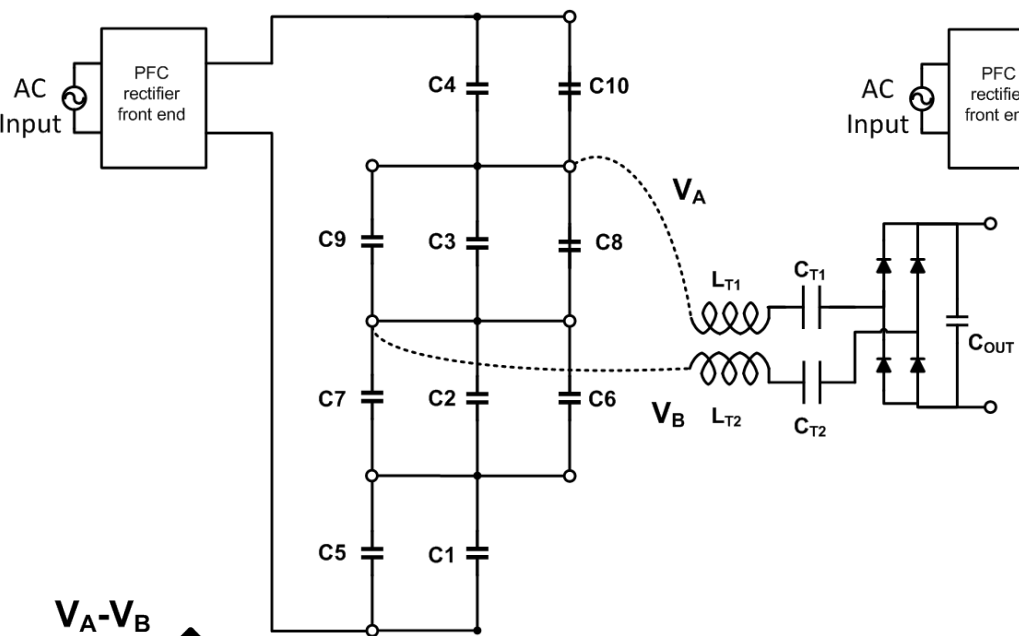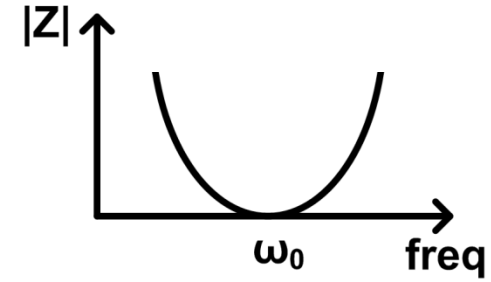

- Galvanic isolation
- Lossless regulation
- Zero voltage switching

Efficiency Analysis

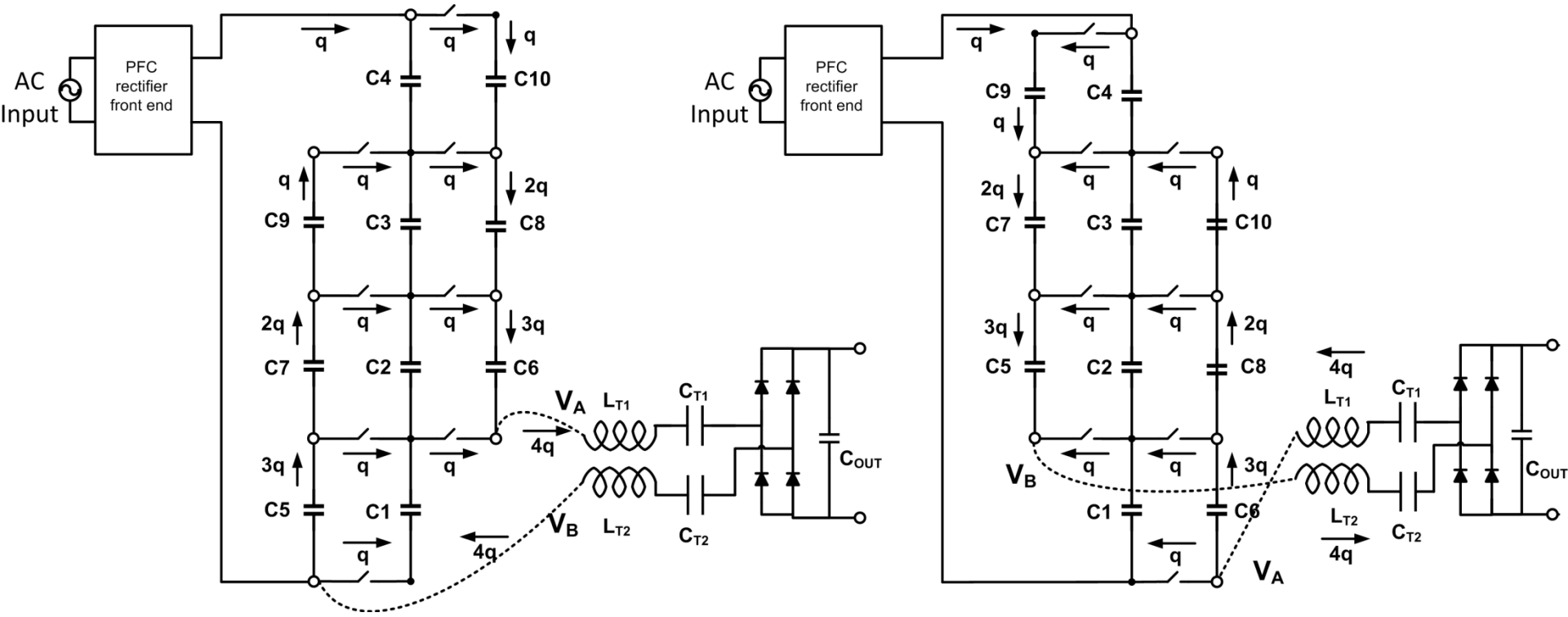

SSL and FSL charge multiplier vectors:



$$a_c = \left[\frac{3}{8}, \frac{3}{8}, \frac{2}{8}, \frac{2}{8}, \frac{1}{8}, \frac{1}{8} \right],$$

$$a_r = \left[\frac{1}{8}, \frac{1}{8}, \frac{1}{8}, \frac{1}{8}, \frac{1}{8}, \frac{1}{8}, \frac{1}{8}, \frac{1}{8} \right].$$


$$R_{SSL} = \frac{1}{C_{fly} f_{sw}} \sum_{i=1}^{n-1} 2 \left(\frac{i}{2n} \right)^2 = \frac{(n-1)(2n-1)}{12n} \frac{1}{C_{fly} f_{sw}} = \frac{7}{16} \frac{1}{C_{fly} f_{sw}},$$

$$R_{FSL} = 2 \sum_{i=1}^{2n} R_i \left(\frac{1}{2n} \right)^2 = \frac{R_{on}}{n} = \frac{R_{on}}{4},$$

Architecture of the DC-DC Converter IC

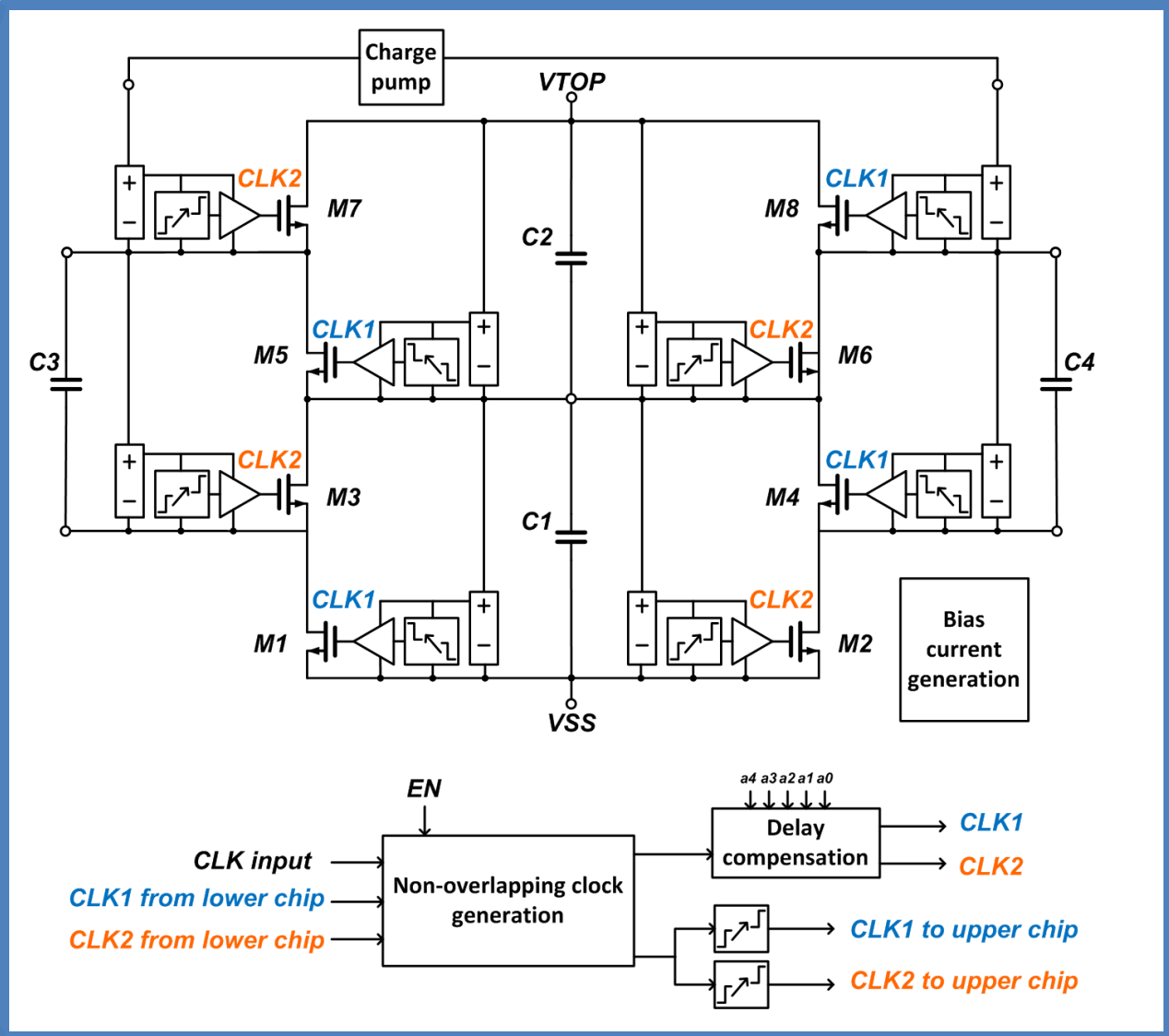
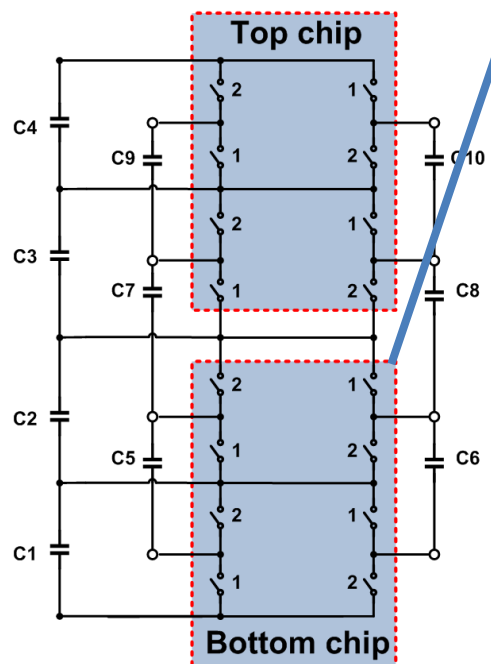


Gate-driving Circuits

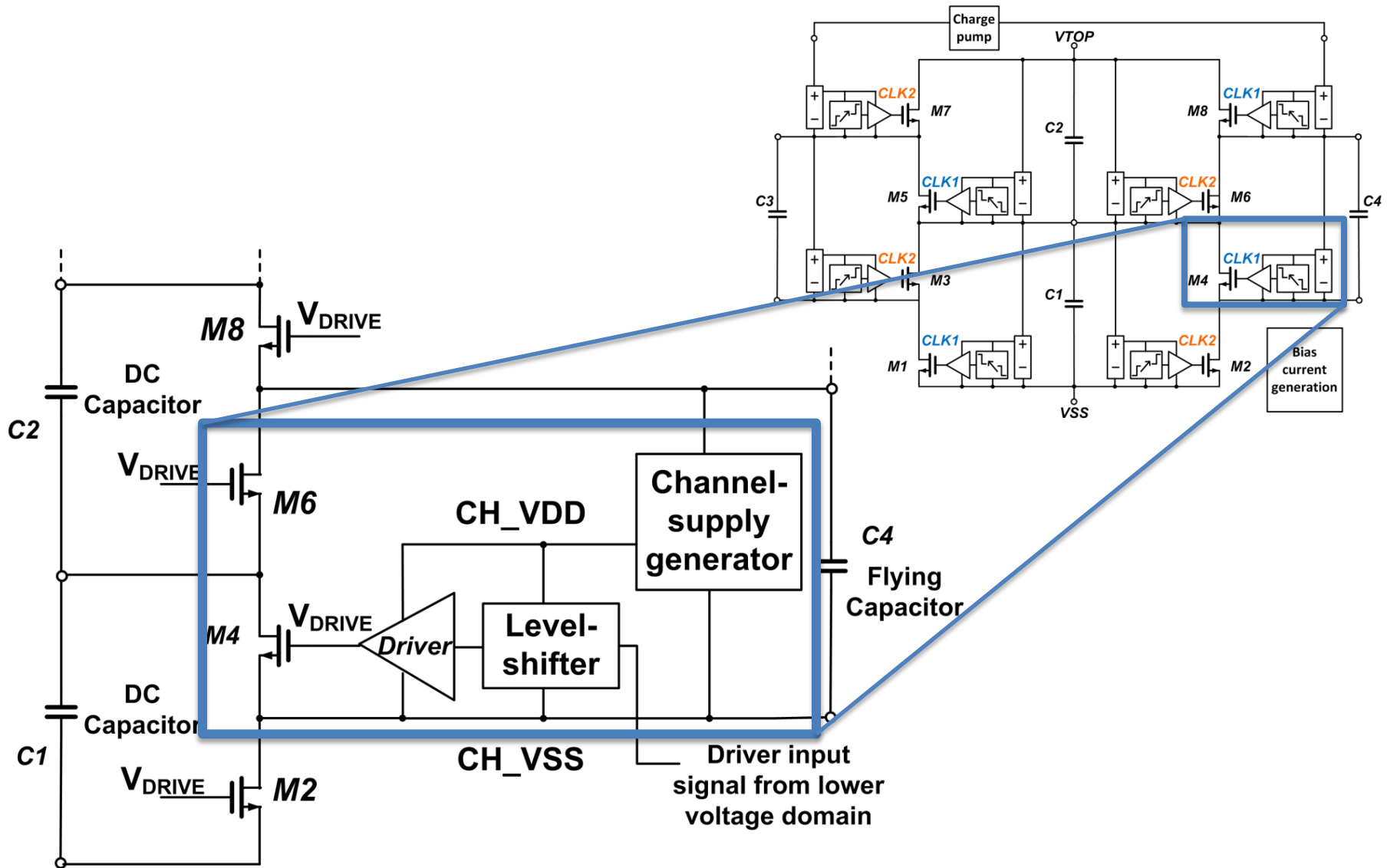

Level-shifting Circuit



Ch_VDD to Ch_VSS

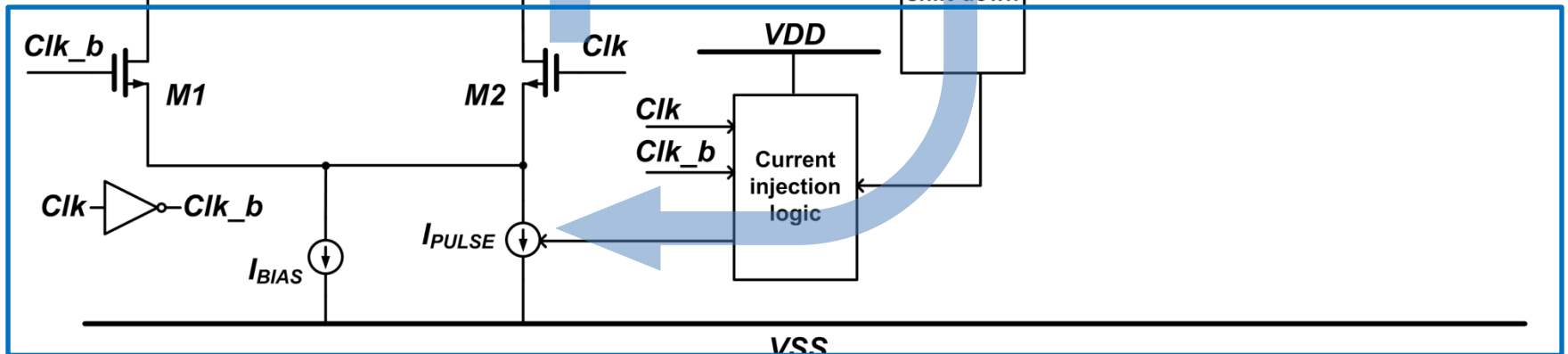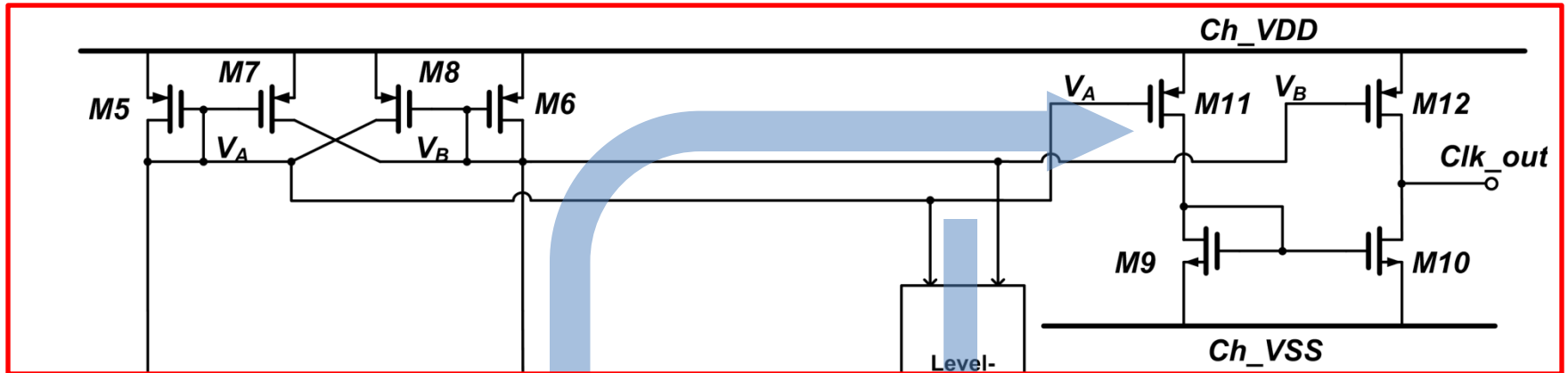

VDD to VSS

Delay Cancellation Strategy

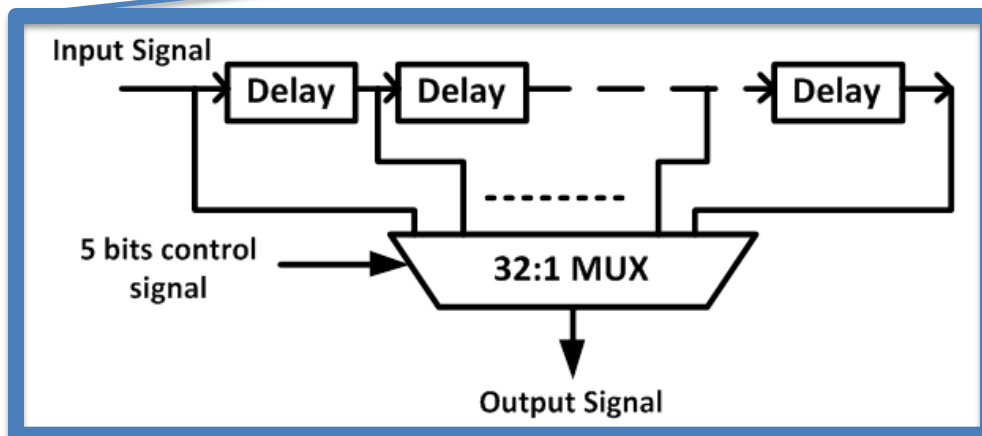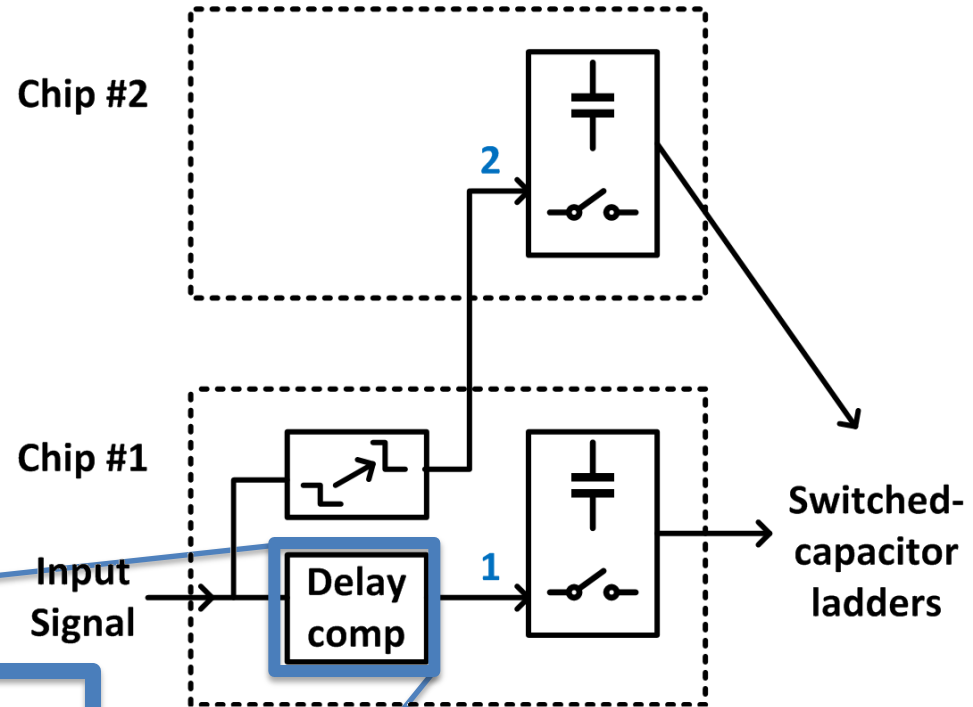- The 5V clock signal is level-shifted to the top chip
- To compensate, the clock signal for the bottom chip must be delayed



Test Board for a 170V Input 17W LED Driver

DC input up to 200V

Second chip sits at 85V DC


Clock input

DC output to the LEDs




Capacitive power transfer & galvanic isolation, 3kV rated

First chip sits at GND

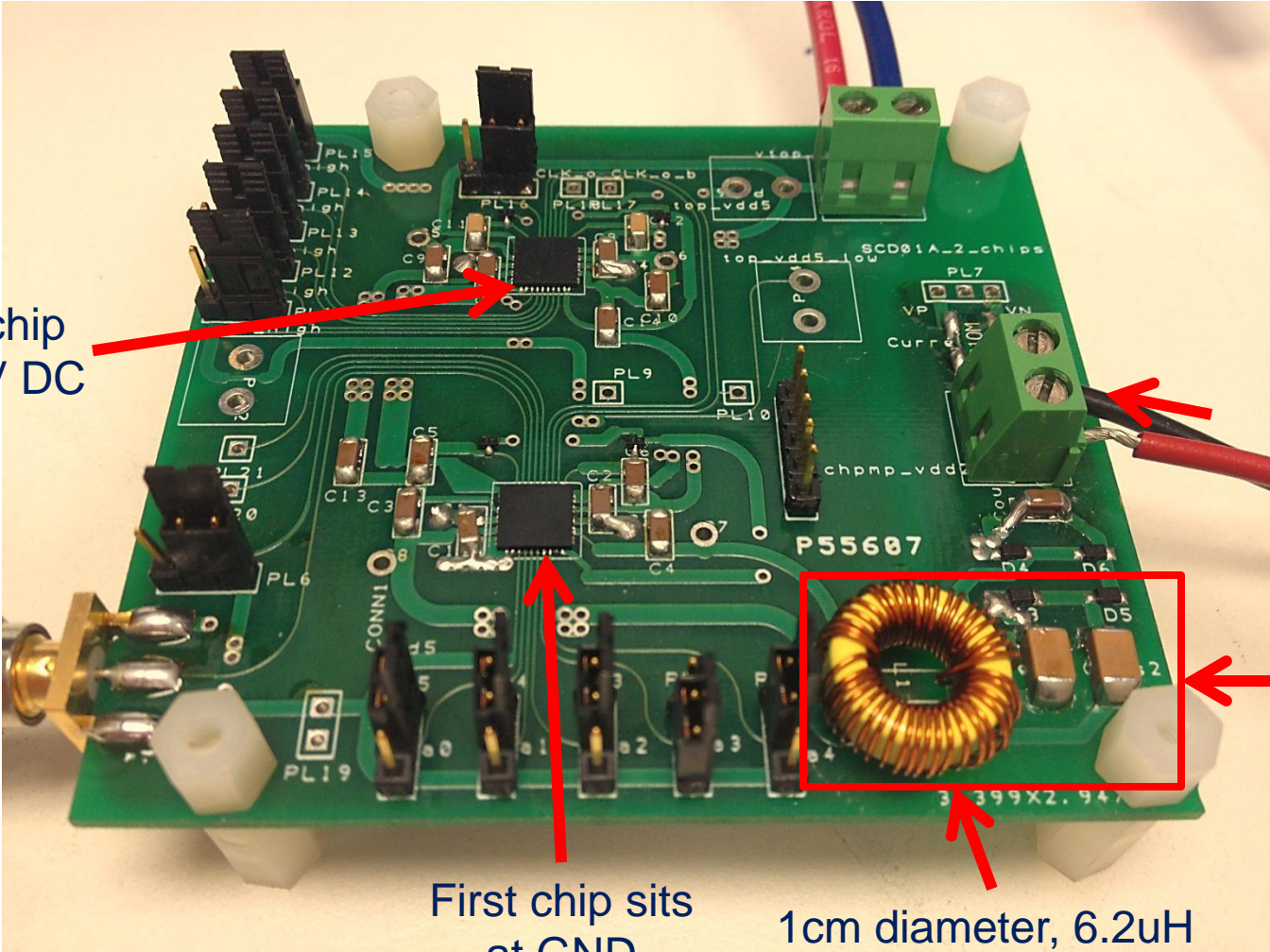1cm diameter, 6.2uH Split winding inductors








Possible Compact Layout of PCBs

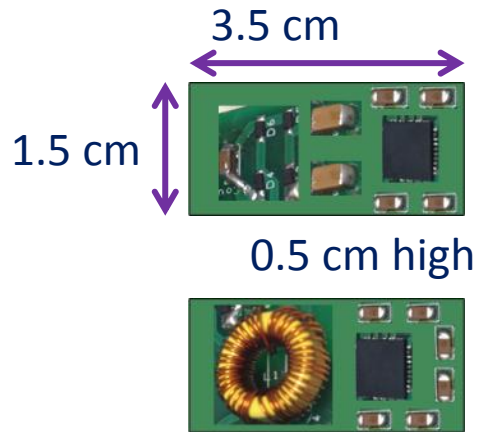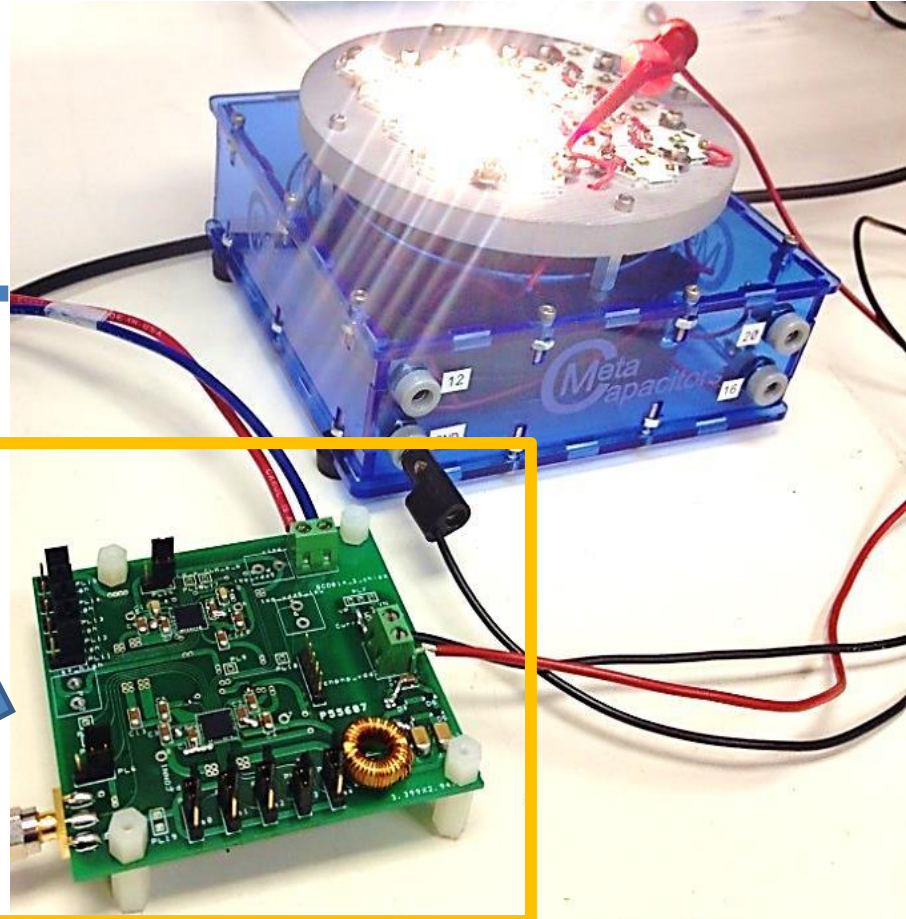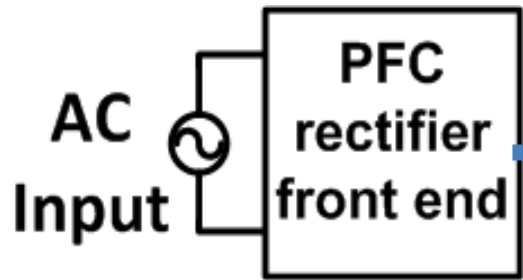


137.5 W/inch³

Current Regulation versus V_{in}

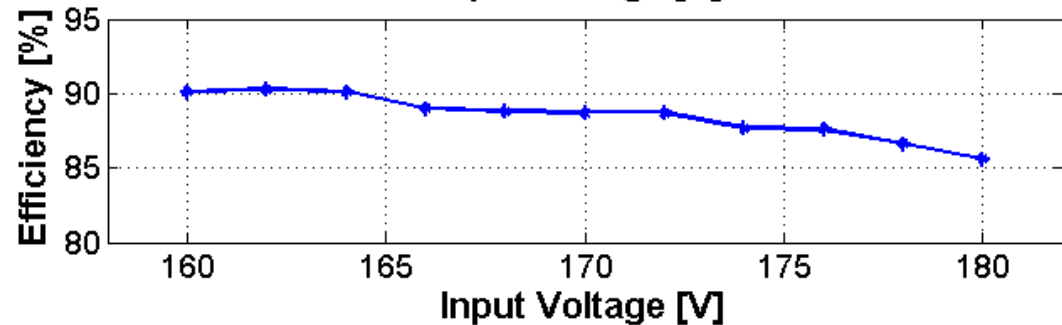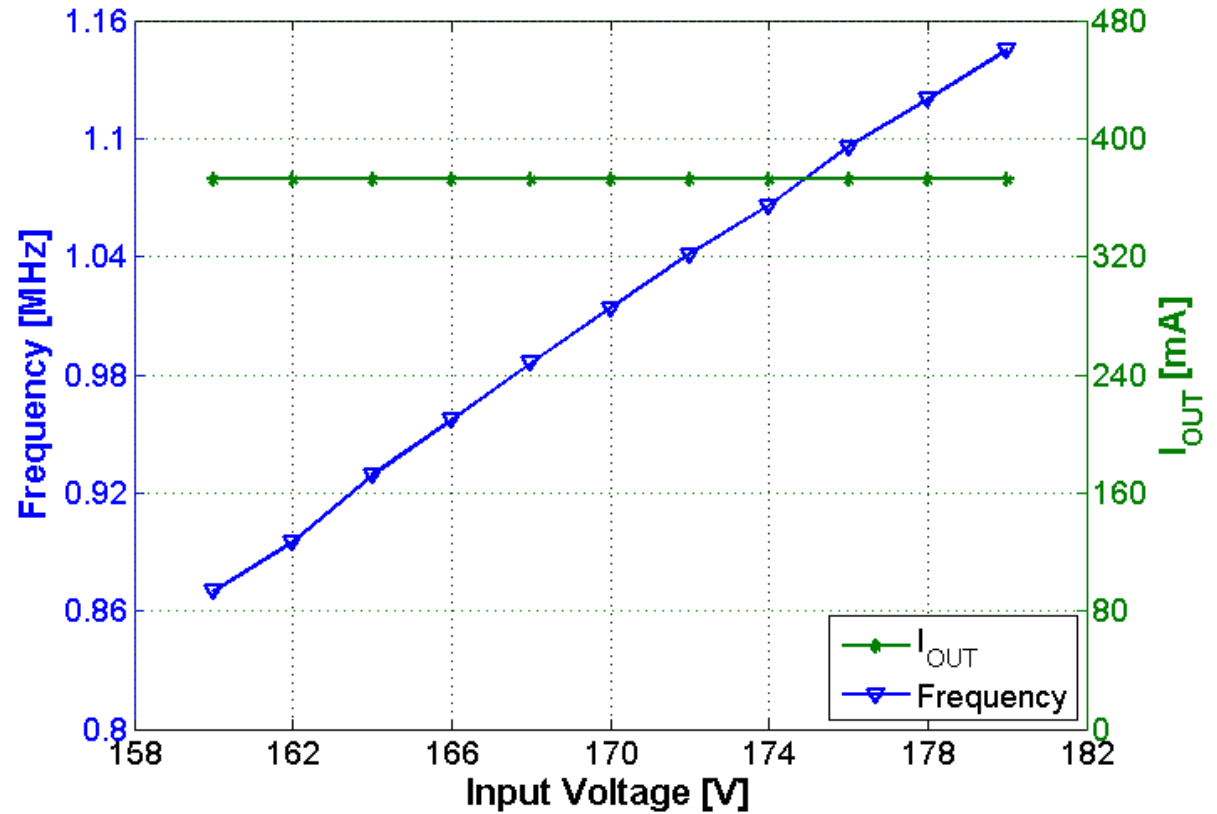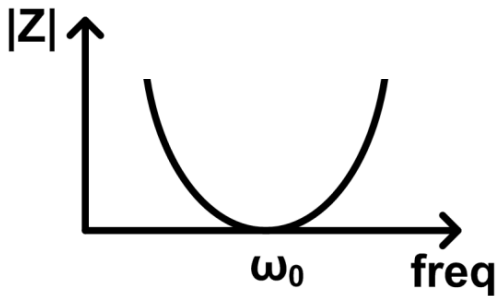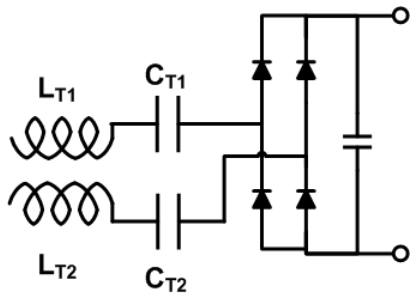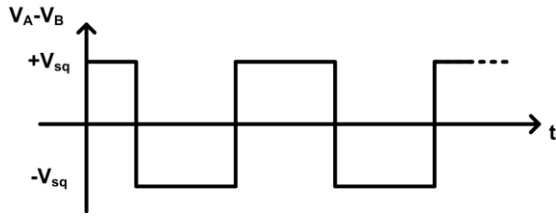



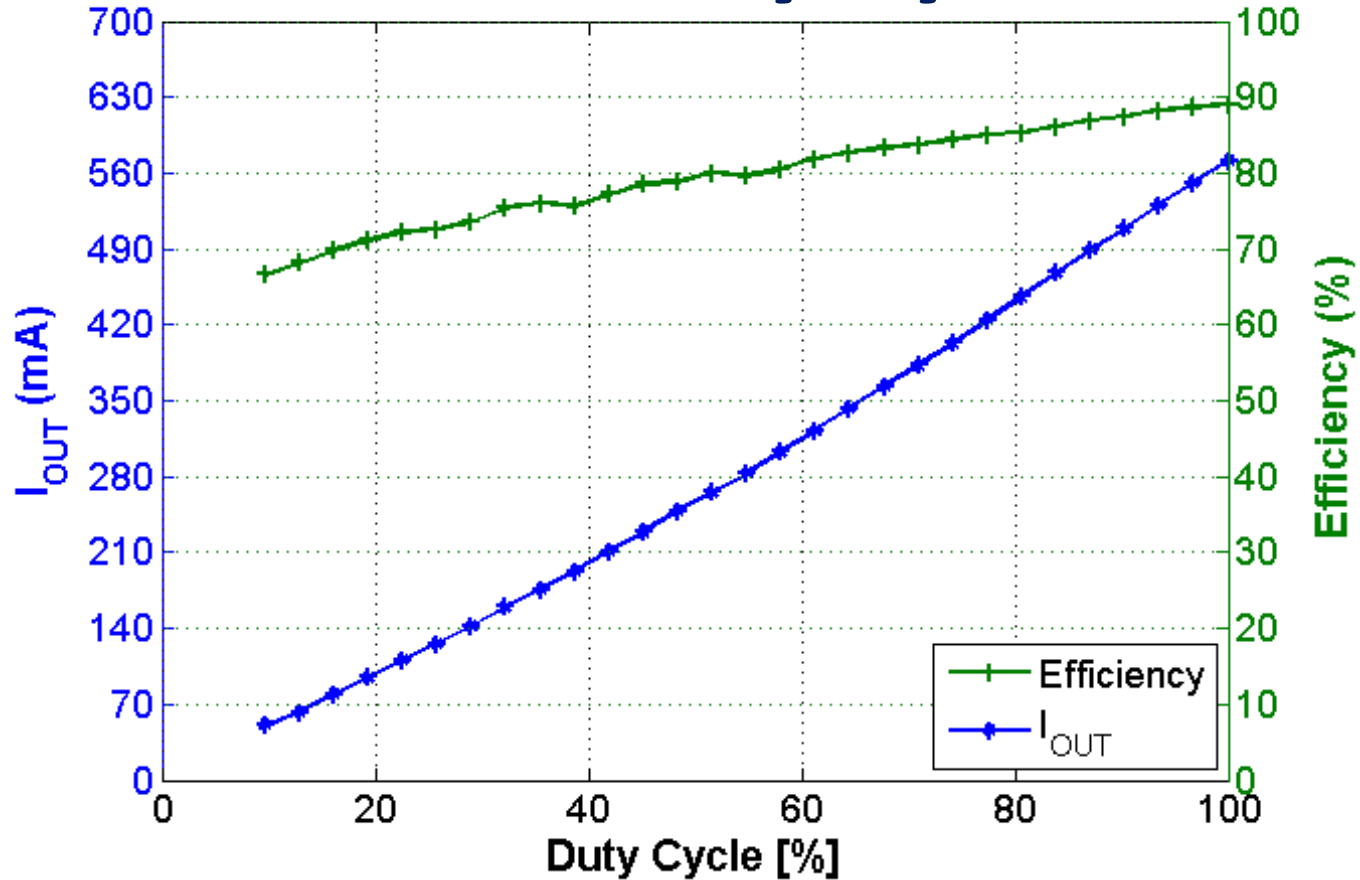
Current Regulation and Efficiency versus Duty Cycle



PMW clock
dimming control



First Integration with Metacapacitors

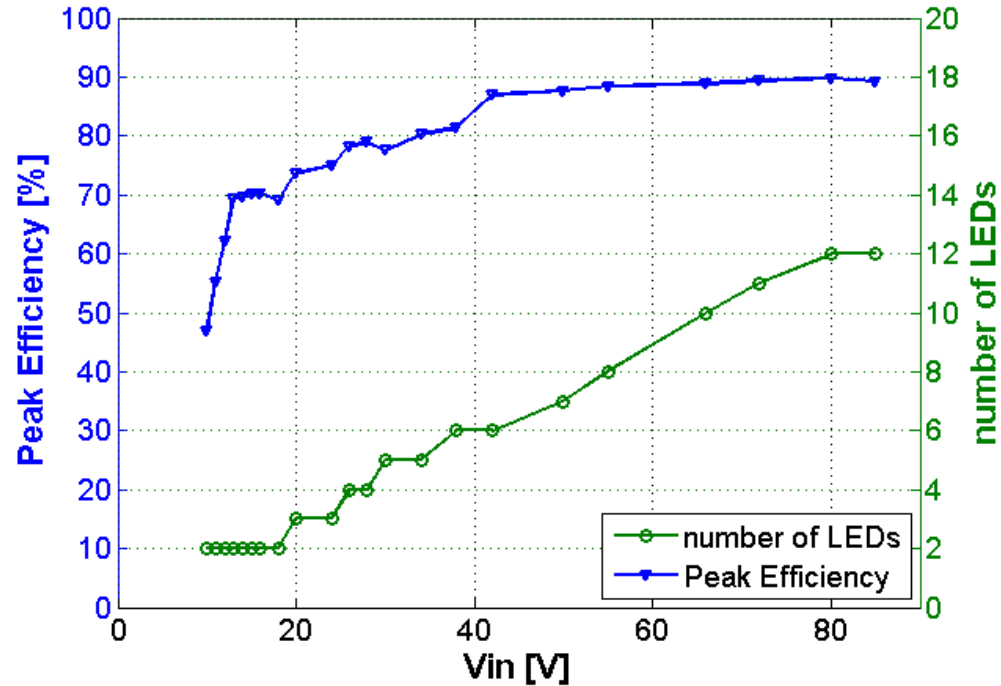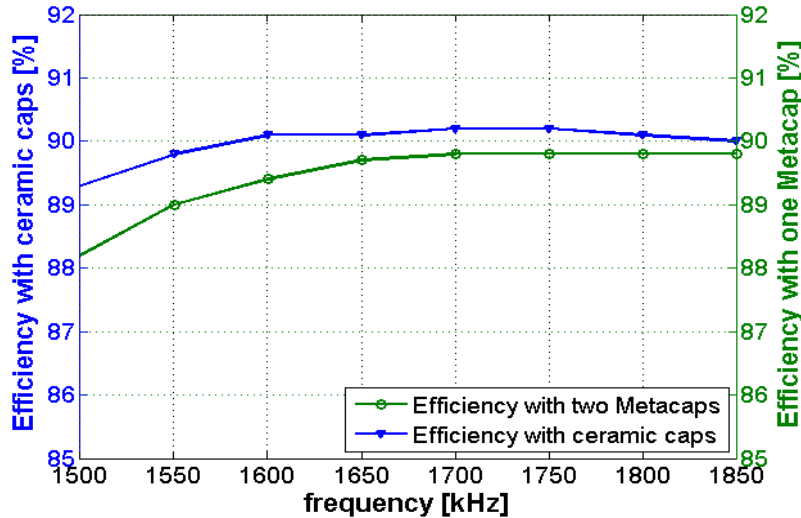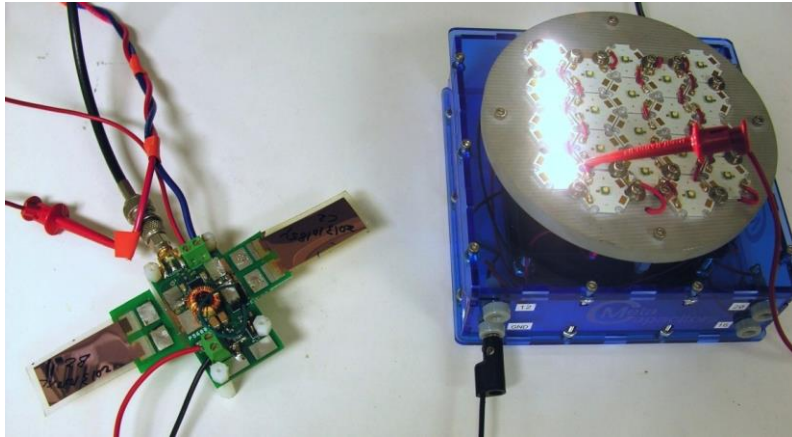

- ESR of the connector and the printed thin film could be a problem
- The capacitance of the printed Metacap is slightly smaller

Summary

- Presents a chip-stackable Switched-Capacitor (SC) DC-DC converter IC for a **hybrid-SC-resonant (HSCR) LED driver**.
- Combines the advantages of **high energy density capacitors**, the **SC converter** and the **series-resonant converter**, achieving an optimized use of reactive elements.
- Developed a **Chip-stackable integrated SC module**. The converter can be reconfigured and extended to handle different input voltage levels with relatively constant efficiency.
- The HSCR converter offers near lossless regulation, galvanic isolation and dimming function with small size reactive components.
- One of the highest power SC converters compared to the current state of the art .

Acknowledgement



Prof. Steve O'Brien
Chemistry
CCNY



Prof. Seth Sanders
Electrical engineering
UC Berkeley



Prof. Ioannis (John) Kymissis
Electrical engineering
Columbia University



Prof. Peter Kinget
Electrical engineering
Columbia University



Prof. Dan Steingart
Mechanical engineering
Princeton University



Dr. Eli Leland
Chemical engineering
CCNY

- The author would like to thank Daniel Gerber for his contribution in this project.
- The authors would like to thank Texas Instruments for silicon fabrication donation.
- Financial support was provided by the DOE under the ARPA-E ADEPT program, contract Metacapacitors DE-AR0000114.

Thank you!




Questions?

Metacapacitors™

Printable nanoparticle dielectric for high frequency capacitors





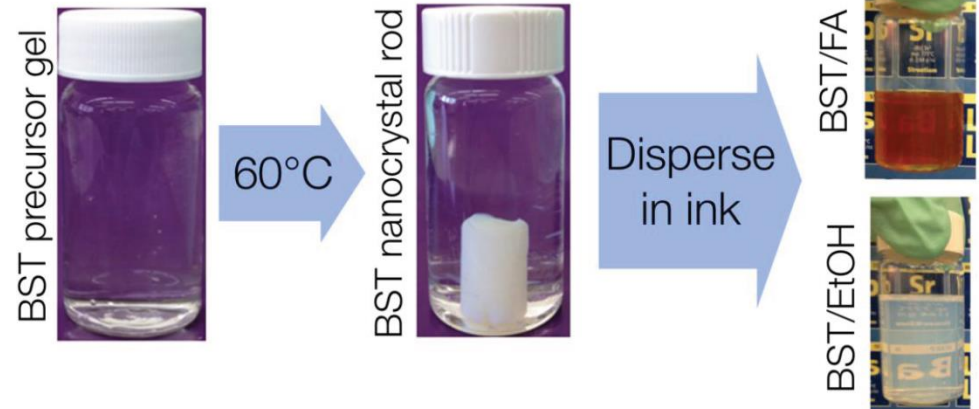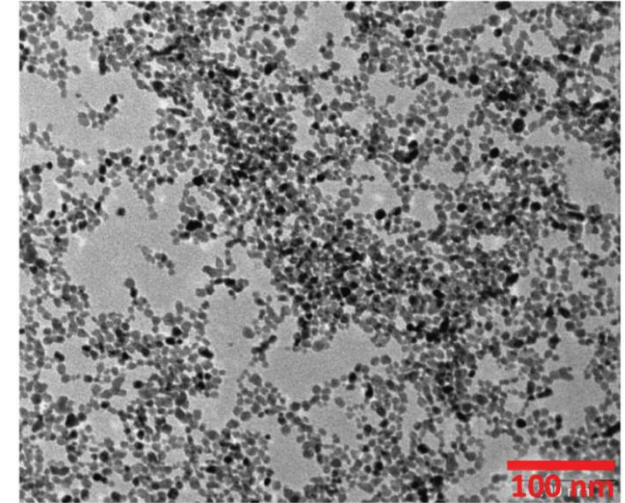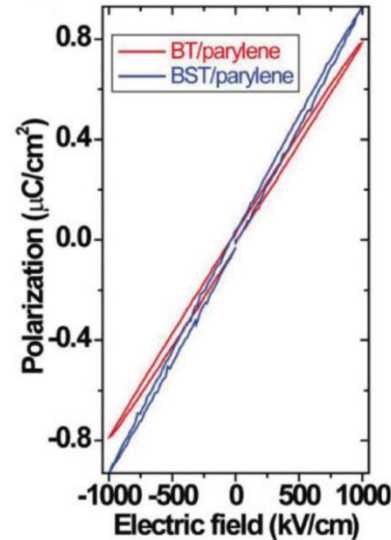- High frequency performance with low loss—single crystal nanoparticles exhibit no ferroelectric hysteresis
- Nanoparticle dielectric inks are readily printable and are compatible with spin coat deposition
- Synthesized below 100°C, No HTCC/LTCC required
- BaTiO₃ and (Ba, Sr)TiO₃ nanoparticles, size controllable from 5-100 nm
- No rare earth materials



Metacapacitors™

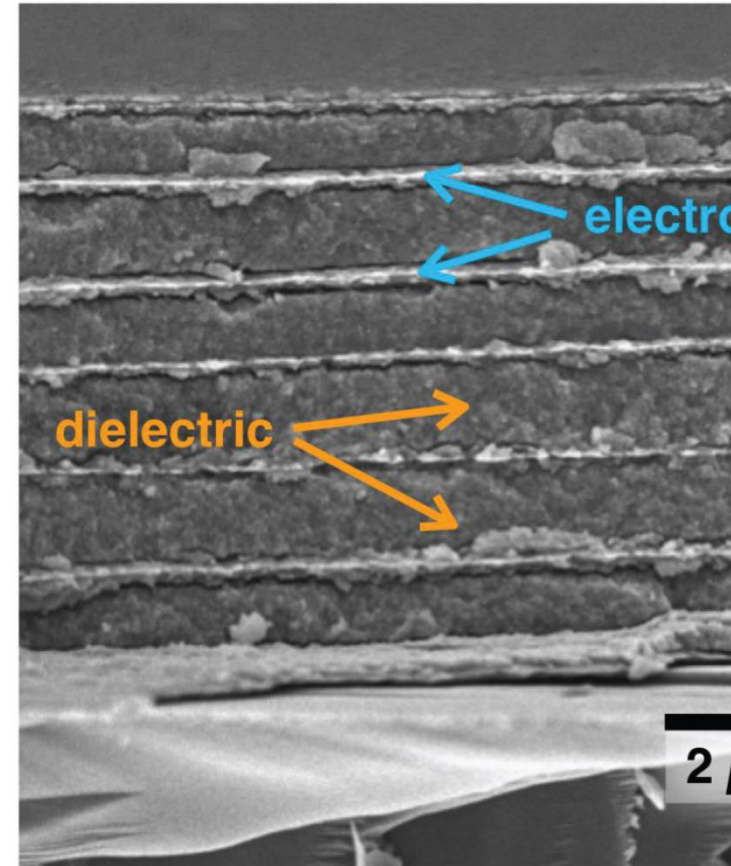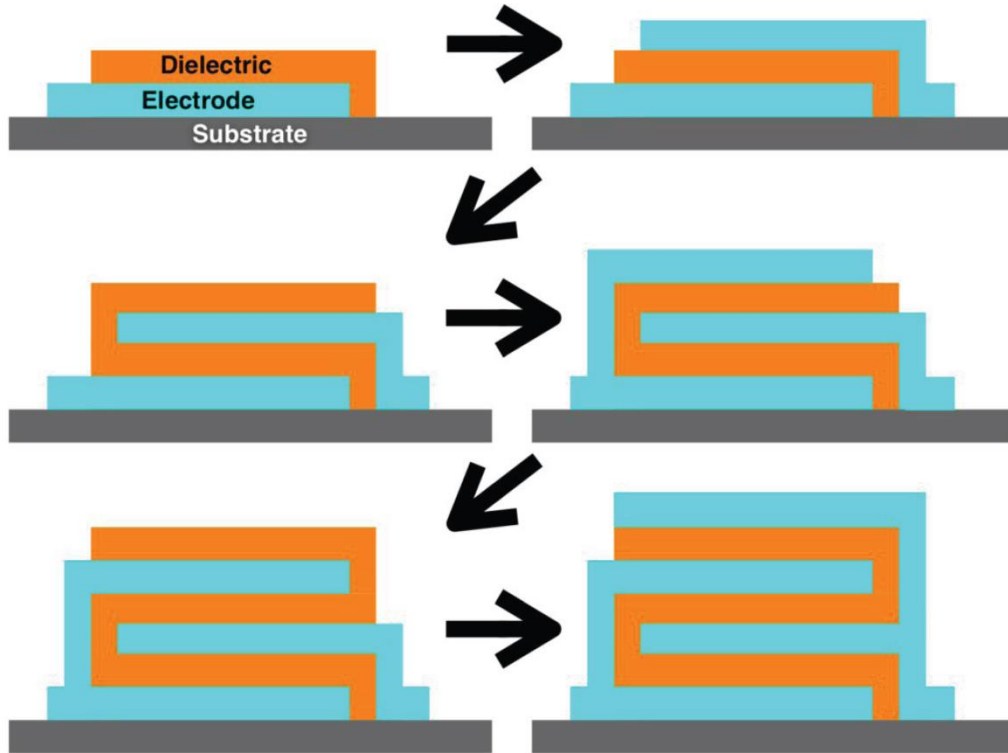Printed multilayer capacitors for power conversion



- Purely additive, roll-to-roll compatible spray-coat or gravure deposition
- All processing below 200 °C

Metacapacitors™

Printed multilayer capacitors high-frequency performance



Wide-area spray-printed multilayer capacitor

